


Problem 1. Solution

$$\begin{aligned}
 f &= x \cdot (y' (w' z)')' + wxz + w' = \\
 &= x(y + w' z) + wxz + w' = \\
 &= xy + xw' z + wxz + w' = \\
 &= xy + w'(xz + 1) + wxz = \\
 &= xy + w' + wxz = \\
 &= xy + w' + xz \quad (\text{since } a' + ab = a' + b)
 \end{aligned}$$

$$\begin{aligned}
 g &= wx(y \oplus z \oplus yz) \oplus w \oplus 1 = \\
 &= wx(y + z) \oplus w \oplus 1 \quad \leftarrow (\text{since } a \oplus b \oplus ab = \\
 &= w(x(y + z) \oplus 1) \oplus 1 = \\
 &= (w(x(y + z)))' \oplus 1 = \\
 &= w' + x(y + z) = \\
 &= w' + xy + xz
 \end{aligned}$$



$$\begin{aligned}
 &= a(1 \oplus b) \oplus b = ab' \oplus b = \\
 &= (ab')'b + ab'b' = \\
 &= (a' + b)b + ab' = \\
 &= a'b + b + ab' = b + ab' = \\
 &= a + b) \\
 &(\text{since } a \oplus 1 = a')
 \end{aligned}$$

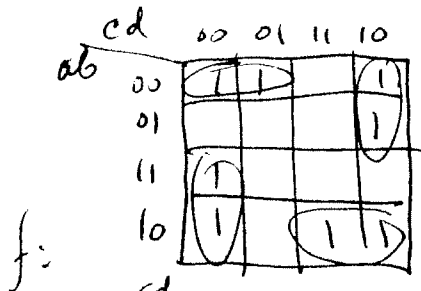(a) $f = \sum m(0, 1, 2, 6, 8, 10, 11, 12)$
 $g = \sum m(0, 1, 2, 6, 7, 8, 10, 11, 12, 13)$




SOP: $f = a'b'c' + a'cd' + ab'c + ac'd'$

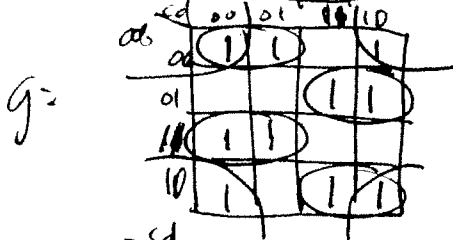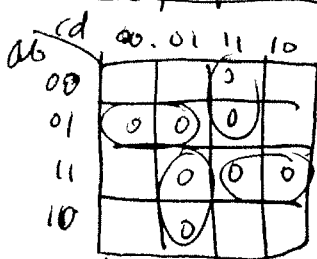POS: $f = (a+c'+d')(a+b'+c)(a'+c+d')(a'+b'+c')$




SOP: $g = b'd' + a'b'c' + a'bc + abc' + ab'c$

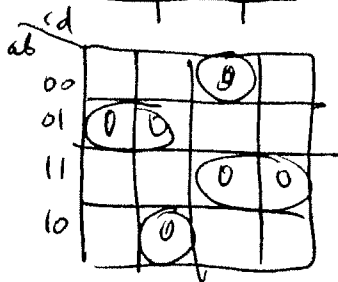POS: $g = (a+b'+c)(a'+b'+c') \times (a+b+c'+d')(a'+b+c+d')$




(b) NAND: $f = a'(b'c' + cd') + a(b'c + c'd') =$
 $= a'((b'c')'(cd')')' + a((b'c)'(c'd')')' =$
 $= \left[\underbrace{\underbrace{a' \left(\underbrace{(b'c')'}_1 \underbrace{(cd')'}_2 \right)'}_3}_{4} \cdot \underbrace{\underbrace{a \left(\underbrace{(b'c)'}_5 \underbrace{(c'd')'}_6 \right)'}_7}_8 \right]'$

ENEL 352
F 2005

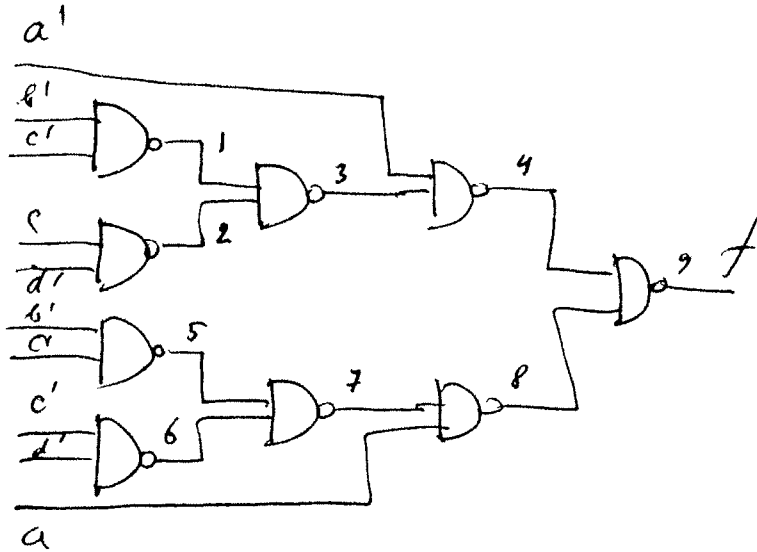


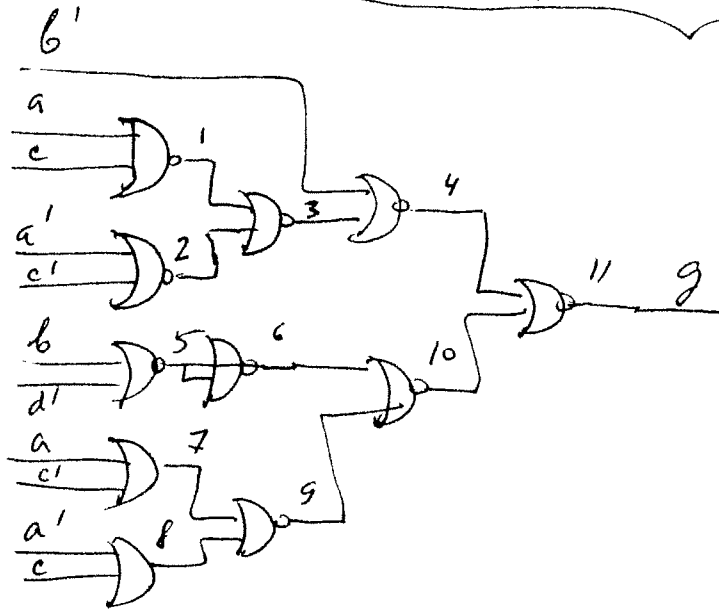(c) NOR:
$$g = (b' + (a+c)(a'+c'))((b+d') + (a+c')(a'+c)) =$$


$$= \left[\underbrace{\left(b' + \underbrace{\underbrace{(a+c)'}_{1} + \underbrace{(a'+c')'}_{2} \right)' }_{3} \right]' + \left(\underbrace{(b+d')''}_{5,6} + \underbrace{\left(\underbrace{(a+c)'}_{7} + \underbrace{(a'+c')'}_{8} \right)' }_{9} \right)' \right]'_{10} = g_{11}$$




(d) Joint minimization of f and g :

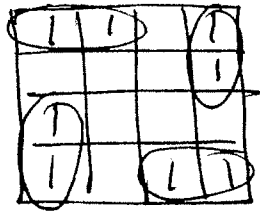


$$f = ab'c + ac'd' + a'b'e' + a'cd'$$

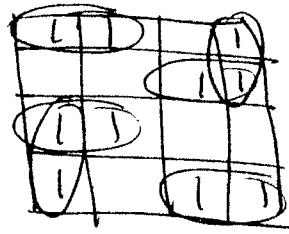

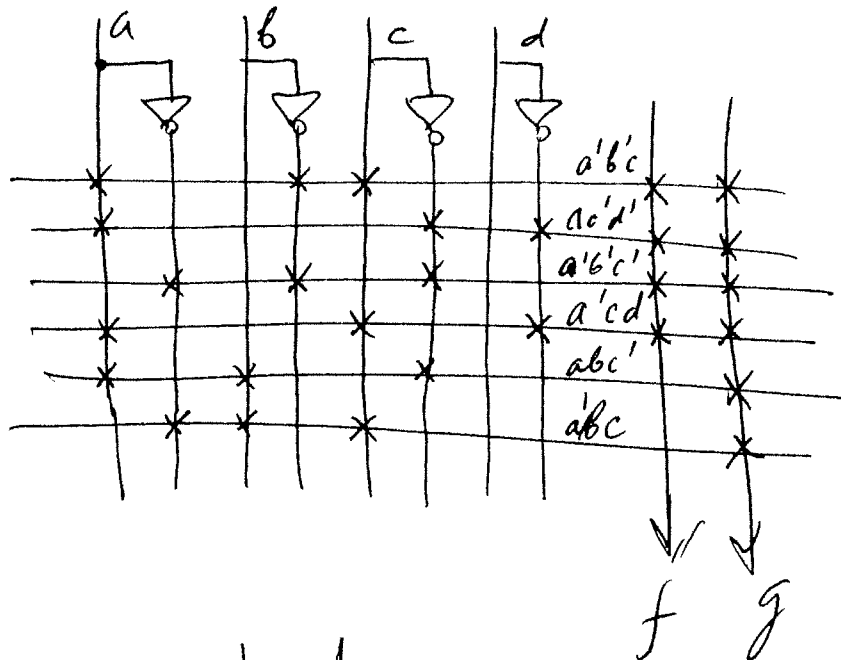
$$g = a'b'c' + ab'c + a'cd' + ac'd' + abc' + a'bc$$



(e) ROM

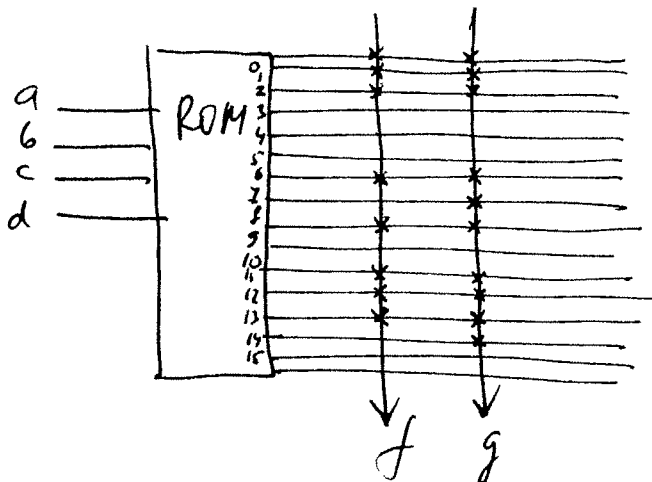

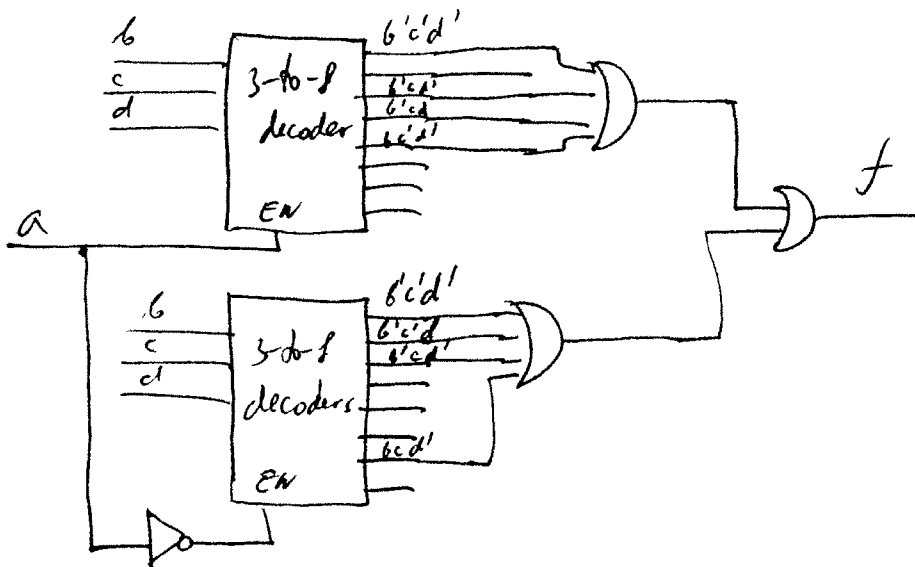
$$\begin{aligned}
 (f) \quad f &= ab'c + ac'd' + a'b'c' + a'cd' = \\
 &= a(b'c + c'd') + a'(b'c' + cd') = \\
 &= a(b'cd' + b'cd + b'c'd' + bc'd') + a'(b'c'd' + b'c'd + b'cd' + bcd')
 \end{aligned}$$



(g)

| a | b | cd | g |
|---|---|----|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 |

$(cd)' = c'd$
 c
 $(c'd)' = cd'$
 c'

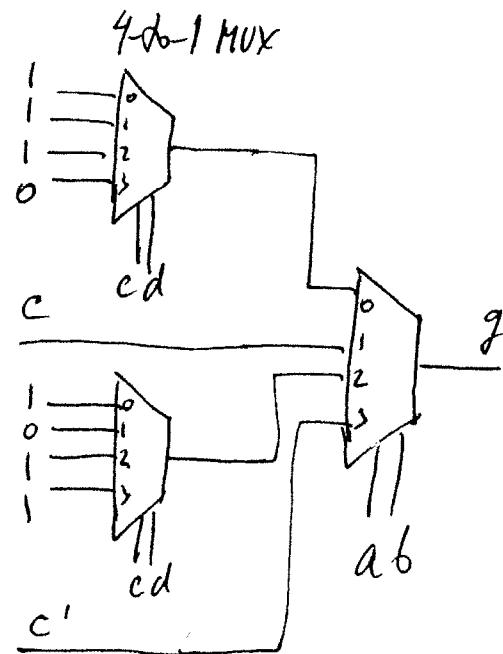


Problem 3. Solution

(a) STATE-TABLE: derived from $T_0 = 1, T_1 = Q_0', T_2 = Q_0' Q_1'$

| Q_2 | Q_1 | Q_0 | Q_2^* | Q_1^* | Q_0^* | T_2 | T_1 | T_0 |
|-------|-------|-------|---------|---------|---------|-------|-------|-------|
| 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |


Note:
 $Q_2^* = Q_2 \oplus T_2$
 $Q_1^* = Q_1 \oplus T_1$
 $Q_0^* = Q_0 \oplus T_0$

State diagram:

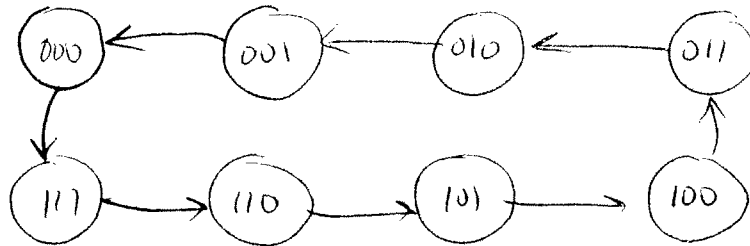


The counter counts down!

(b) For D flip-flops; $Q_2^* = D_2, Q_1^* = D_1, Q_0^* = D_0,$
 $D_2 = Q_2' Q_1' Q_0' + Q_2 Q_0 + Q_2 Q_1, D_1 = Q_1' Q_0' + Q_1 Q_0, D_0 = Q_0'$

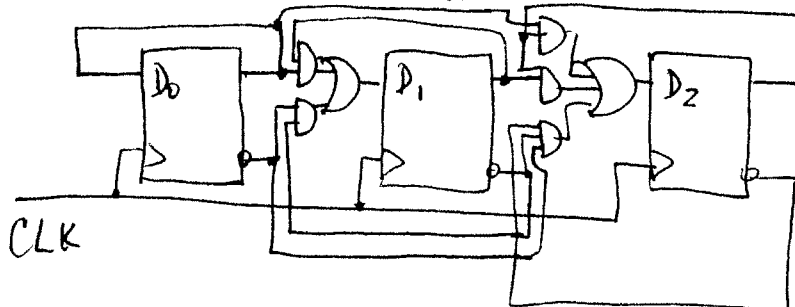

Problem 4

(a)

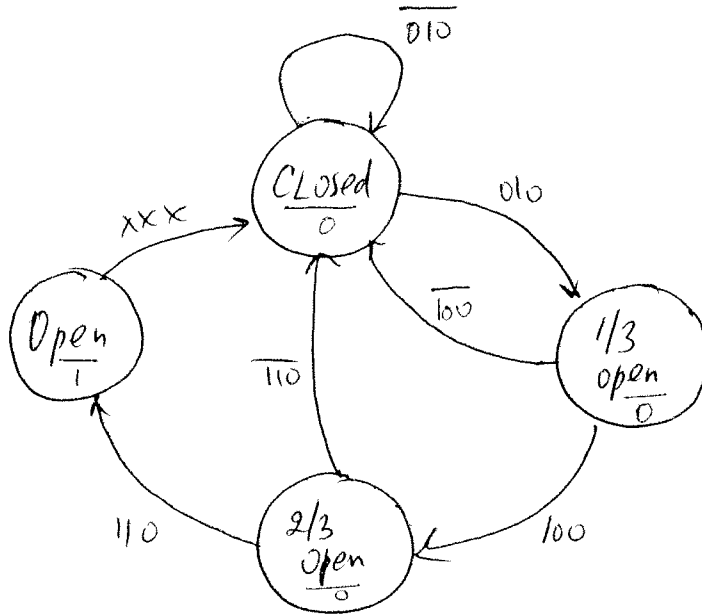

(b) STATES:

CLOSED = 00
1/3 OPEN = 01
2/3 OPEN = 10
OPEN = 11

STATE TABLE


| CURR. STATE | | INPUTS | | | NEXT STATE | | OUT |
|-------------|---|--------|---|---|------------|----|-----|
| A | B | W | X | Y | A* | B* | Z |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| | | x | x | x | 0 | 0 | |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| | | x | x | x | 0 | 0 | |
| 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| | | x | x | x | 0 | 0 | |
| 1 | 1 | x | x | x | 0 | 0 | 1 |

$$A^* = A'BWX'Y' + AB'WXY' = YW(A'BX' + AB'X)$$

$$B^* = A'B'W'XY' + AB'WXY' = B'XY'(A'W' + AW)$$

$$Z = AB$$

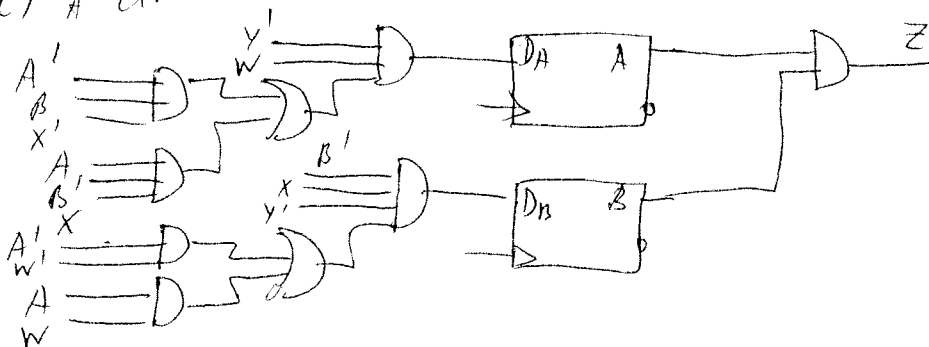(c) A circuit with 2 FLIP-FLOPS is needed; $D_A = A^*$, $D_B = B^*$



(d) using JK FFs.

| A | B | W | X | Y | A* | B* | J _A | K _A | J _B | K _B | Z |
|---|---|---|---|---|----|----|----------------|----------------|----------------|----------------|---|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | x | 1 | x | 0 |
| | | x | x | x | 0 | 0 | 0 | x | 0 | x | |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | x | x | 1 | 0 |
| | | x | x | x | 0 | 0 | 0 | x | x | 1 | |
| 1 | 0 | 1 | 1 | 0 | 1 | 1 | x | 0 | 1 | x | 0 |
| | | x | x | x | 0 | 0 | x | 1 | 0 | x | |
| 1 | 1 | x | x | x | 0 | 0 | x | 1 | x | 1 | 1 |

Use the table for JK

| Q | Q* | J | K |
|---|----|---|---|
| 0 | 0 | 0 | x |
| 0 | 1 | 1 | x |
| 1 | 0 | x | 1 |
| 1 | 1 | x | 0 |

FROM table:

$$J_A = A'BWx'y + A = BWx'y + A$$

$$K_A = (A' + AB'WXY) = (A' + B'WXY)'$$

$$J_B = A'B'W'XY' + AB'WXY = B'XY'(A'W' + AW) =$$

$$K_B = 1$$

$$= B'XY'(A \oplus W)$$

$$Z = AB$$

