

Name: \_\_\_\_\_

Lecture Section: \_\_\_\_\_

**L01** – N. Bartley 11:00-11:50

**L02** – S. Norman, 12:00-12:50



DEPARTMENT OF ELECTRICAL  
AND COMPUTER ENGINEERING

ENEL 353 - Digital Circuits

## Midterm Examination

Wednesday, October 30, 2013

---

### Instructions:

- Time allowed is 90 minutes.
  - In order to minimize distraction to your fellow students, you may not leave during the last 10 minutes of the examination.
  - The examination is closed-book.
  - Non-programmable calculators are permitted.
  - The maximum number of marks is 50, as indicated; the midterm examination counts 20% toward the final grade.
  - Please use a pen or heavy pencil to ensure legibility.
  - Please answer questions in the spaces provided; if space is insufficient, please use the back of the pages.
  - Please show your work; where appropriate, marks will be awarded for proper and well-reasoned explanations.
-

UCID: \_\_\_\_\_

## 1. [12 marks total.]

(a) [2 marks.] Use repeated division to convert  $329_{10}$  to hexadecimal representation.

(b) [2 marks.] Convert  $275_8$  to decimal representation. Show your work.

(c) [2 marks.] Convert  $A7B_{16}$  to octal representation. Show your work.

(d) [3 marks.] The 5-bit unsigned binary representation of  $25_{10}$  is  $11001_2$ . Use this information to determine the following two bit patterns.


6-bit two's complement  
representation of  $-25_{10}$ :

8-bit sign/magnitude  
representation of  $-25_{10}$ :

(e) [3 marks.] For each of the three additions below, answer YES or NO regarding unsigned and signed overflow, and briefly give a reason for each YES answer and for each NO answer. Marks will only be given if reasons are correct.

<i>carries:</i> 1 11110000 a: 10011001 b: 01111000 <hr/> <i>sum:</i> 00010001	unsigned overflow?  signed overflow?
<i>carries:</i> 1 00000000 a: 10100000 b: 11000000 <hr/> <i>sum:</i> 01100000	unsigned overflow?  signed overflow?
<i>carries:</i> 0 11110010 a: 01101101 b: 01011001 <hr/> <i>sum:</i> 11000110	unsigned overflow?  signed overflow?


 
2. [5 marks.] Consider the circuit below.



Let  $G = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$ . By *algebraic manipulation*, prove or disprove that  $F = G$ . (Do not use a truth table or a K-map.)

3. [8 marks total.]

(a) [3 marks.]

  


Check the box belonging to the correct statement:

- Contention is possible in circuit (i) but not in circuit (ii).
- Contention is possible in circuit (ii) but not in circuit (i).
- Contention is possible in both circuits.
- Contention is not possible in either circuit.

For full credit you must give a correct explanation for your answer in the space below.

 (b) [3 marks.] Use bubble-pushing and/or algebra to find a sum-of-products expression for  $Y$ . If you use bubble-pushing, draw your equivalent circuit to the right of the given circuit.



(c) [2 marks.] Suppose that  $\bar{A}C + BD + A\bar{B}\bar{D}$  is a minimal sum-of-products expression for some logic function  $F$ . Use that information and some algebra to find a minimal product-of-sums expression for  $\bar{F}$ .

4. [11 marks total.]

- (a) [8 marks.] Consider the function  $F$  given in the truth table below. Use the blank K-maps to derive *all* minimum SOP and POS expressions for  $F$ . Indicate all essential prime implicants for  $F$  or  $\bar{F}$  in your maps. You may add more maps if you need them.

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	X
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	X
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	X
1	1	0	0	0
1	1	0	1	0
1	1	1	0	X
1	1	1	1	1

	$AB$	00	01	11	10
$CD$	00				
	01				
	11				
	10				

	$AB$	00	01	11	10
$CD$	00				
	01				
	11				
	10				

	$AB$	00	01	11	10
$CD$	00				
	01				
	11				
	10				


- (b) [3 marks.] Sketch a two-level NOR-NOR circuit for a minimal POS expression from part (a). If you found more than one minimal POS expression in part (a), state which one you have chosen to implement. Assume that inputs  $A$ ,  $B$ ,  $C$  and  $D$  are available in true and complementary forms. There is no restriction on the number of inputs on each NOR gate.

5. [9 marks total.]


- (a) [3 marks.] Draw a schematic to show how the function given in the truth table can be implemented with a 4:1 multiplexer, *one* inverter, and no other components. Show any intermediate work you had to do to design the circuit.

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

 - (b) [3 marks.] Show how the function  $Y = A(B \oplus C)D$  can be implemented using a 2:4 decoder with an enable input, *one* AND gate, *one* OR gate, and no other components. Express your answer by adding gates and wires to the schematic below.



 - (c) [3 marks.] Consider the following circuit and information about  $t_{pd}$  (propagation delay) and  $t_{cd}$  (contamination delay) for NAND and NOR gates.



gate	$t_{pd}$	$t_{cd}$
NAND	33 ps	27 ps
NOR	40 ps	34 ps

Determine the overall  $t_{pd}$  and  $t_{cd}$  for the circuit. Briefly explain how you got your answers.

6. [5 marks.] Consider the following 5-variable K-map for  $F(A, B, C, D, E)$ . Use the K-map to find a minimal SOP expression for  $F$ .

	<i>BC</i>			
<i>DE</i>	00	01	11	10
00				1
01	1	1		1
11	1	1	1	1
10				

$A = 0$

	<i>BC</i>			
<i>DE</i>	00	01	11	10
00			1	1
01	1			1
11	1		1	1
10			1	

$A = 1$

Name (printed):

U of Calgary ID number:

Section (L01 is 11:00–11:50 with N. Bartley,  
L02 is 12:00–12:50 with S. Norman):

Problem	Mark
1	/ 12
2	/ 5
3	/ 8
4	/ 11
5	/ 9
6	/ 5
TOTAL	/ 50