

## Component One

Name: \_\_\_\_\_

Lecture Section: \_\_\_\_\_

L01 — N. Bartley

L02 — S. Norman

1. [Total of 11 marks.] In parts (a), (b) and (c) you must show your work carefully to get credit.

- (a) [3 marks.] Use repeated division to convert  $5095_{10}$  to hexadecimal representation.

division	quotient	remainder
$5095 \div 16$	318	7
$318 \div 16$	19	$14 = E_{16}$
$19 \div 16$	1	3
$1 \div 16$	0	1

Answer:  $13E7_{16}$ 

- (b) [2 marks.] Find the octal representation of  $E5BC_{16}$ .

E	5	B	C	
0 0 1 1 1 0	0 1 0 1	1 1 0 1	1 1 1 0 0	
1	6	2	6	7 4

Answer:  $162674_8$

- (c) [2 marks.] What is the decimal representation of the 8-bit two's complement number  $11101011_2$ ?

Let  $X$  be the number, and let's do two's complement negation to find  $-X$ .

$$-X = 00010100_2 + 1 = 00010101_2 = 16 + 4 + 1 = 21_{10}$$

Answer:  $-21$ 

- (d) [2 marks.] Complete the following 6-bit integer addition. Show all of the carry bits involved regardless of whether they are 0's or 1's.

$$\begin{array}{r}
 1\ 1\ 0\ 0\ 1\ 0\ 0 \\
 1\ 1\ 0\ 0\ 1\ 1 \\
 +\ 0\ 1\ 1\ 0\ 1\ 0 \\
 \hline
 0\ 0\ 1\ 1\ 0\ 1
 \end{array}$$

- (e) [1 marks.] If all the integers in part (d) are interpreted as two's complement, is there overflow in the addition? Give a reason for your answer.


No. Reason: Addition of two's complement numbers with opposite signs never results in overflow. Alternate reason: The carry out of the most-significant-bit (MSB) column matches the carry in to the MSB column.

- (f) [1 marks.] If all the integers in part (d) are interpreted as unsigned, is there overflow in the addition? Give a reason for your answer.

Yes. Reason: The carry out from the MSB column is 1. Alternate reason: The sum  $001101$  is smaller than either of the numbers being added,  $110011$  and  $011010$ .

2. [4 marks.] The table below gives voltage parameters for Advanced Ultra-Low-Voltage CMOS logic gates operating with  $V_{DD}$  equal to 2.50 V. For each of nodes n1, n2, n3 and Y in the circuit below, either state the range of possible output voltages or give a reason why a range cannot be determined.

parameter	voltage
$V_{IH}$	1.70 V
$V_{IL}$	0.70 V
$V_{OH}$	1.80 V
$V_{OL}$	0.60 V

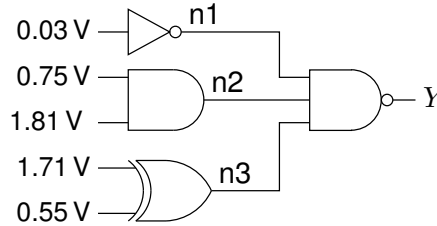

node	voltage range
n1	from 1.80 V to 2.50 V
n2	unknown, because input 0.75 V is in the “forbidden zone”
n3	from 1.80 V to 2.50 V
Y	unknown, because voltage at n2 is unknown

3. [Total of 4 marks.]

- (a) [3 marks.] Find a canonical product-of-sums expression for the function given by the truth table.

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Method: AND together the false maxterms for all the rows in which  $Y = 0$ .

Answer:

$$(A + B + C + D)(A + \bar{B} + \bar{C} + D)(\bar{A} + B + \bar{C} + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D})$$

Answer using maxterm numbers:

$$M_0 M_6 M_{10} M_{15}, \text{ or } \Pi(0, 6, 10, 15)$$

- (b) [1 mark.] How many products would there be in a canonical sum-of-products expression for the function? (You do *not* have to list all the products.)

Answer: 12. Reason:  $Y = 1$  in 12 rows of the truth table.

### Component Two

Name: \_\_\_\_\_

Lecture Section: \_\_\_\_\_

L01 — N. Bartley

L02 — S. Norman

4. [Total of 8 marks.]

- (a) [4 marks.] Use algebraic manipulation to simplify  $Y$  in the following expression to a minimal SOP form having three product terms and five literals. (You may check your work with a truth table or a K-map, but you must not include any truth table or K-map work as part of your answer.)

$$Y = A \oplus B \oplus C + (\overline{A \oplus B})\overline{C}$$

$$Y = \underbrace{(A\overline{B} + \overline{A}B)}_{\overline{A \oplus B}} \overline{C} + (\overline{A\overline{B} + \overline{A}B})C + (\overline{A\overline{B} + \overline{A}B})\overline{C}$$

$$\underbrace{[(A\overline{B} + \overline{A}B) + (\overline{A\overline{B} + \overline{A}B})]}_{\overline{A \oplus B} + \overline{\overline{A \oplus B}} = 1} \overline{C} = \overline{C}$$


$$\overline{A \oplus B} = AB + \overline{A}\overline{B}$$

$$Y = \overline{C} + (\overline{A\overline{B} + \overline{A}B})C$$

$$Y = \overline{C} + AB + \overline{A}\overline{B}$$

Note that there are many ways to solve this!

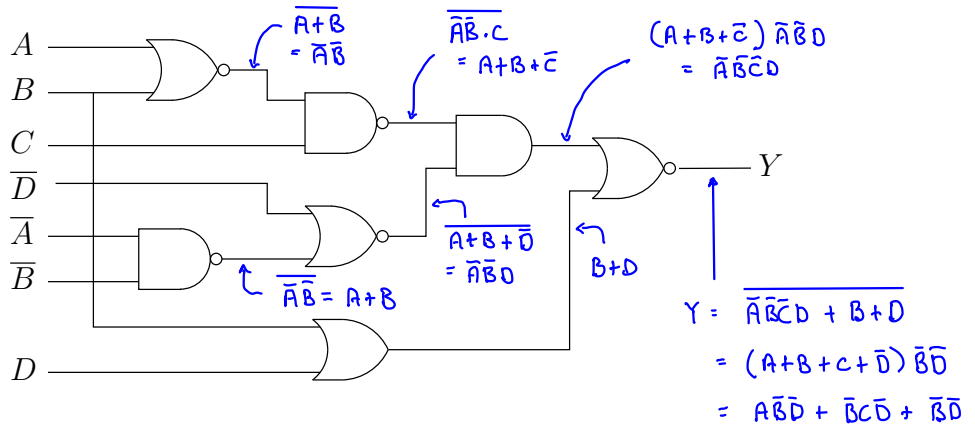- (b) [4 marks.] Consider the schematic below. Use “bubble-pushing” and/or Boolean algebra to find an SOP expression for the function  $Y$ .



Optional steps!  $Y = (A+C+1)\overline{B}\overline{D}$   
 $Y = \overline{B}\overline{D}$

5. [Total of 10 marks.]

(a) [5 marks.] Consider the function

$$Y(A, B, C, D) = \sum(0, 1, 2, 5, 7, 9) + X(A, B, C, D),$$

where  $X(A, B, C, D) = \sum(6, 8, 11, 13, 14, 15)$  are don't-cares. Derive *all* possible minimal SOP expressions for  $Y$ .

$Y = \bar{A}\bar{B}\bar{D} + \bar{C}D + \begin{Bmatrix} BC \\ BD \end{Bmatrix}$ 
 or
  $Y = \bar{B}\bar{C} + BD + \begin{Bmatrix} \bar{A}\bar{B}\bar{D} \\ \bar{A}\bar{C}D \end{Bmatrix}$

Four solutions.

(b) [5 marks.] Derive *all* possible minimal POS expressions for  $Y$  in part (a). Indicate all distinguished 1-cells and essential prime implicants.

$\bar{Y}$  map.

$\bar{Y} = \bar{B}C D + \bar{B}D + \begin{Bmatrix} AC \\ A\bar{D} \end{Bmatrix}$

DeMorgan's theorem

$$\begin{aligned}
 Y &= \overline{\bar{B}C D + \bar{B}D + \begin{Bmatrix} AC \\ A\bar{D} \end{Bmatrix}} \\
 &= (\overline{\bar{B}C D})(\overline{\bar{B}D}) \begin{Bmatrix} \overline{AC} \\ \overline{A\bar{D}} \end{Bmatrix} \\
 &= (B + \bar{C} + \bar{D})(\bar{B} + D) \begin{Bmatrix} (\bar{A} + C) \\ (\bar{A} + D) \end{Bmatrix}
 \end{aligned}$$

### Component Three

Name: \_\_\_\_\_

Lecture Section: \_\_\_\_\_

**L01** — N. Bartley


**L02** — S. Norman

6. [5 marks.]

The truth table for function  $F(A, B, C, D, E)$  can be described as follows:

- output is 1 in rows 1, 2, 3, 9, 11, 13, 15, 16, 17, 18, 19
- output is 0 in rows 0, 4, 5, 6, 7, 8, 10, 12, 14, 20, 21, 22, 23
- output is don't-care in rows 24–31

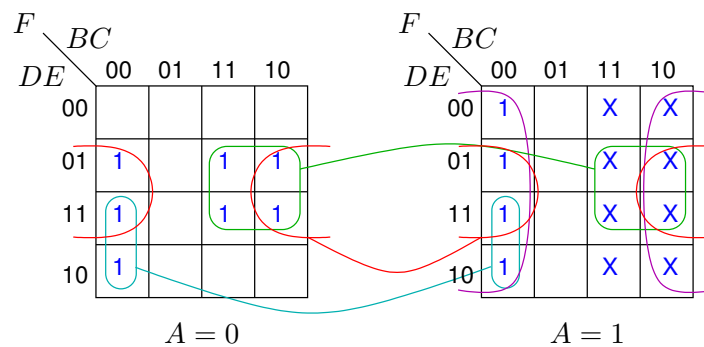Fill in the following 5-variable K-map, and then use it to find a minimal SOP expression for  $F$ . If there is more than one such expression, you only need to give one of them.




In this particular map, every prime implicant is an essential prime implicant, so there is a unique minimal SOP expression:

$$F = BE + A\bar{C} + \bar{C}E + \bar{B}\bar{C}D$$

7. [Total of 4 marks.]

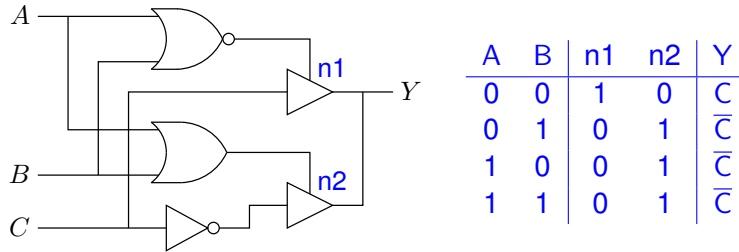- (a) [2 marks.] Either give an SOP expression for  $Y$  as a function of  $A$ ,  $B$  and  $C$ , or explain why it is not possible to do so.




A	B	n1	n2	Y
0	0	1	0	C
0	1	0	1	$\bar{C}$
1	0	0	1	$\bar{C}$
1	1	0	1	$\bar{C}$

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

(There are other valid SOP expressions, including  $Y = \bar{A}\bar{B}C + A\bar{C} + B\bar{C}$  and a few others.)

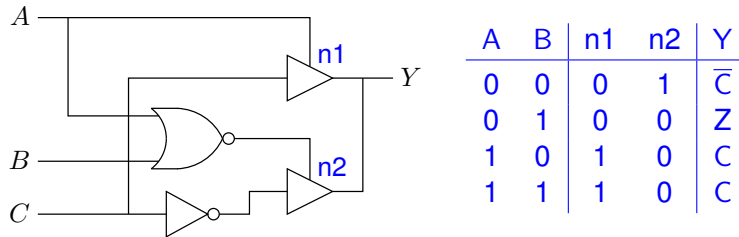- (b) [2 marks.] Either give an SOP expression for  $Y$  as a function of  $A$ ,  $B$  and  $C$ , or explain why it is not possible to do so.




A	B	n1	n2	Y
0	0	0	1	$\bar{C}$
0	1	0	0	Z
1	0	1	0	C
1	1	1	0	C

It is not possible to give an SOP expression, because Boolean algebra can't describe a circuit that can have a Z output.

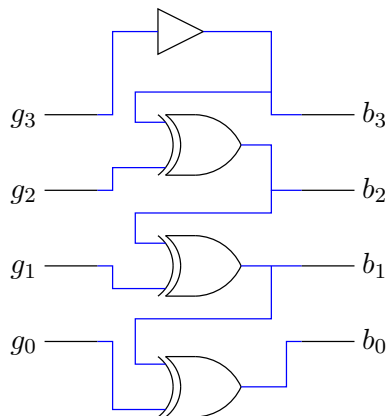8. [3 marks.] Add wires but no more gates to make a 4-bit Gray code to unsigned binary converter circuit.  $g_3g_2g_1g_0$  is the Gray code and  $b_3b_2b_1b_0$  is the unsigned binary number. You must use all four of the given gates.

To help with readability, please use horizontal and vertical lines only when drawing wires.




Explanation: Here is the layout for conversion between 4-bit Gray and binary codes ...

$g_3$	$g_2$	$g_1$	$g_0$
0	$b_3$	$b_2$	$b_1$
			$b_0$

Clearly  $b_3 = g_3$ . Then each remaining  $b_i$  is the same as  $b_{i+1}$  if  $g_i$  is 0, and the opposite if  $g_i$  is 1. In other words, each remaining  $b_i$  is equal to  $b_{i+1} \oplus g_i$ .

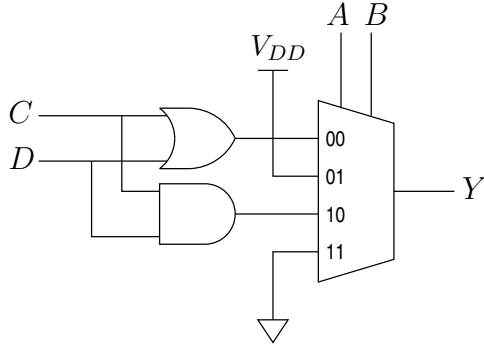9. [4 marks.]

Consider the multiplexer circuit below in which  $A$  is the most-significant select bit. Derive a SOP expression for  $Y(A, B, C, D)$ .



There are *many* different SOP expressions for  $Y$ . A few of them are found below. Only one correct SOP expression was needed for full credit.


**Solution 1.** Make a function table:

A	B	Y
0	0	$C + D$
0	1	1
1	0	$CD$
1	1	0

By inspection,  $Y = \bar{A}\bar{B}(C + D) + \bar{A}B + A\bar{B}CD = \bar{A}\bar{B}C + \bar{A}\bar{B}D + \bar{A}B + A\bar{B}CD$ .

**Solutions 2a and 2b.** These both start with a full truth table:

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

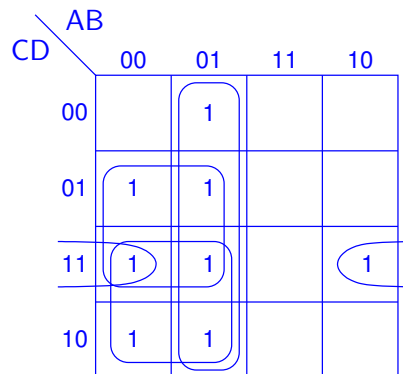

**2a.** Canonical SOP:  $\Sigma(1, 2, 3, 4, 5, 6, 7, 11)$ .

**2b.** Minimal SOP from K-map:  $\bar{A}B + \bar{A}C + \bar{A}D + \bar{B}CD$ .