

Name: Solutions ID: _____

1. [10 marks total.]

- (a) [6 marks.] Represent the following numbers using 7-bit 2's-complement format and perform the addition. Indicate in each case if an overflow occurs, and why. Convert your answer to signed decimal notation.

i. $48_{10} + 23_{10}$

$48 = 32 + 16, \text{ so } 48_{10} = 0110000_2$

$23 = 16 + 4 + 2 + 1 \text{ so } 23_{10} = 0010111_2$

different!
so overflow

$$\begin{array}{r} 0110000 \\ 0010111 \\ \hline 1000111 \end{array}$$

also negative, so overflow

$$1000111 \rightarrow 0111000$$

$$\begin{array}{r} 0111000 \\ + 0111001 \\ \hline 0111001 \end{array} \quad (57)$$

result = -57

ii. $14_{10} + (-33_{10})$

$14_{10} = 8 + 4 + 2 = 0001110_2$

$33_{10} = 32 + 1 = 0100001_2 \rightarrow 1011110$

same!
so no overflow

$$\begin{array}{r} 0001110 \\ 1011111 \\ \hline 1101101 \end{array} \rightarrow \begin{array}{r} 0010010 \\ + 0010011 \\ \hline 0010011 \end{array} \quad (19)$$

result = -19

- (b) [2 marks.] Represent each of the following numbers in 7-bit sign-magnitude and 2's-complement binary formats.

i. 33_8

$33_8 = 0011011_2$

same in both representations

ii. $(-3E)_{16}$

$3E_{16} = 0111110_2$

Sign-magnitude = 1111110

two's-complement = $\begin{array}{r} 1000001 \\ + 1000010 \\ \hline 1000010 \end{array}$

(c) [2 marks]. Add the decimal numbers 96 and 87 using BCD arithmetic.


$$\begin{array}{r}
 96 = \quad 1001 \ 0110 \\
 \quad \quad 1000 \ 0111 \\
 \hline
 1 \ 0001 \ 1101 \quad \leftarrow \text{correction} \\
 \quad \quad \quad \quad 0110 \\
 \hline
 1 \ 0010 \ 0011 \\
 \leftarrow \text{correction} \quad \quad \quad \quad 0110 \\
 \hline
 1 \ 1000 \ 0011 \quad \leftarrow 183_{BCD}
 \end{array}$$

2. [8 marks total (4 marks each).] Perform algebraic manipulation for each of the following tasks:


(a) Expand the function $f = a + b + c'$ to its canonical form.

$$\begin{aligned}
 f &= a(b+b')(c+c') + b(a+a')(c+c') + c'(a+a')(b+b') \\
 &= (ab+ab')(c+c') + (ab+a'b)(c+c') + (ac'+a'c')(b+b') \\
 &= \underline{abc} + \underline{abc'} + \underline{ab'c} + \underline{ab'c'} + \underline{abc} + \underline{abc'} + \underline{a'bc} + \underline{a'bc'} \\
 &\quad + \underline{abc'} + \underline{abc'} + \underline{a'bc'} + \underline{a'bc'} \quad \text{(duplicated terms)} \\
 &= abc + abc' + ab'c + ab'c' + a'bc + a'bc' + a'b'c' \\
 &\quad m_7 \quad m_6 \quad m_5 \quad m_4 \quad m_3 \quad m_2 \quad m_0
 \end{aligned}$$

 (b) Prove or disprove algebraically that the following circuits are functionally equal:


 
$$\begin{aligned}
 f &= x' \oplus y \\
 &= x'y' + xy
 \end{aligned}$$



$$\begin{aligned}
 g &= (x+y)' + xy \\
 &= x'y' + xy
 \end{aligned}$$

same!

3. [6 marks total.] Karnaugh maps are given identically for a function $F(a, b, c, d)$ in parts (a) and (b) below:

(a) [3 marks.] Find a minimal SOP algebraic expression using this map.

- If there is more than one minimal sum, give any *one* of them.
- Give the "cost" associated with this function (give the number of gate-inputs as well as the number of gates, assuming any number of inputs is allowed on each gate).

		cd			
ab		00	01	11	10
	00	1	1	0	1
	01	1	1	1	0
	11	0	1	1	0
	10	0	0	1	1

SOP: multiple correct answers

One of them is

$$F = a'c' + bd + ab'c + b'cd'$$

This corresponds to 14 gate inputs and 5 gates

(b) [3 marks.] Similarly, find any *one* minimal POS expression using this map, and give the "cost" associated with this function.

		cd			
ab		00	01	11	10
	00	1	1	0	1
	01	1	1	1	0
	11	0	1	1	0
	10	0	0	1	1

POS: also multiple correct answers

$$F' = ac'd + ab'c' + bcd' + a'b'cd$$

$$\text{so } F = (a'+c+d')(a'+b+c)(b'+c+d)(a+b+c+d')$$


This corresponds to 17 gate inputs and 5 gates

Note: When drawing circuits in the questions below, you may assume that the inputs are available in both complemented and uncomplemented form.


4. [18 marks total.] Consider a two-bit magnitude comparator circuit such as the one designed in Lab #2. It has two two-bit inputs $A = a_1a_0$ and $B = b_1b_0$ (where a_1 and b_1 are the most-significant bits). The output f should be $f = 1$ when $A \neq B$; otherwise $f = 0$.

- (a) [4 marks.] Find a minimal SOP expression for f . Draw the logic diagram of an AND-OR circuit implementation of f using only 2-input gates. Use whatever answer you obtain here to answer parts (b)-(d) below.


a_1	a_0	b_1	b_0	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 

 
$$f = a_0 b_0' + a_1 b_1' + a_0' b_0 + a_1' b_1$$



 
- (b) [4 marks.] Using algebraic transformations and/or circuit manipulation, implement the circuit you drew in part (a) using 2-input NAND gates only (inverters are not available).



 - (c) [4 marks.] Implement the logic function f using 2-to-4 decoders. You may use any additional AND, OR, and NOT gates as necessary. Each decoder has an ENABLE input.



 - (d) [6 marks.] Implement the logic function f using two 4-to-1 multiplexers and one 2-to-1 multiplexer. You may use any additional AND, OR, and NOT gates as necessary.



$a_1 a_0 b_1 b_0$	f	
0000	0	$f = b_0$ $a_1 = 0, a_0 b_1 = 00$
0001	1	
0010	1	$f = 1$ $a_1 = 0, a_0 b_1 = 01$
0011	1	
0100	1	$f = b'_0$
0101	0	
0110	1	$f = 1$
0111	1	
1000	1	$f = 1$
1001	0	
1010	1	$f = b_0$
1011	1	
1100	1	$f = 1$
1101	1	
1110	1	$f = b'_0$
1111	0	

etc.

5. [8 marks.] Design a circuit with four inputs x_3, x_2, x_1, x_0 (x_3 is the MSB) and two outputs f_1 and f_2 that implements a BCD code detector. The function f_1 should be $f_1 = 1$ if the BCD code is 1, 3, 5 or 7; otherwise $f_1 = 0$. The function f_2 should be $f_2 = 1$ if the code is 0, 5, 6, 7 or 8; otherwise $f_2 = 0$.

Give minimal SOP expressions for each output suitable for the simplest-possible multiple-output circuit implementation. Use don't-cares for the invalid BCD codes. Carefully indicate shared product terms (if any) that can be used. (It is not necessary to draw the circuit.)

x_3	x_2	x_1	x_0	f_1	f_2
0	0	0	0	0	1
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	0	0
1	0	1	0	X	X
1	0	1	1	X	X
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X

f_1

f_2

$$f_1 = x_3' x_0$$

$$f_2 = x_2' x_1' x_0' + x_2 x_0 + x_2 x_1$$