

Mon Dec 2

Tutorial problems tomorrow

- synchronous system timing
- memory arrays

Lectures this week


Mon - slide set 10

Wed - Finish slide set 10, exam review

Fri - more exam review

Set 10, Slide 37

 Let's first do an example with one NMOS transistor connected to a wire - the wire will play the role of a bitline in the ROM circuit.



- current can flow through R

- voltage drop across R close to  $V_{DD}$

- voltage at n1 close to ground

- buffer output is logic 0

In the  $4 \times 3$  array, if wordline 2 is ON and the other three wordlines are OFF ...

Bitline 2 is HIGH - no transistor is pulling it down.

Bitline 1 is LOW - the NMOS transistor has much lower effective resistance than  $R$ , so the voltage drop across  $R$  is close to  $V_{DD}$ .

Bitline 0 is LOW for the same reason that Bitline 1 is LOW.

<u>Array contents</u>	<u>Address</u>	<u>Data</u>
	11	010
	10	100
	01	110
	00	011

ENEL 353  
Dec 2 2019  
2 of 2