

ENEL 353 Section 02 Lecture

Wed Dec 4 2019

page 1 of 4

- today - finish yesterday's tutorial
- shift registers (not an exam topic)
 - PLAs (also not an exam topic)
 - exam review


Friday - more exam review

Quiz 4

- about 80 papers have been marked
- about 40 papers have not yet been marked - they will be available Friday

Exercise 5 from yesterday's tutorial

state transition diagram

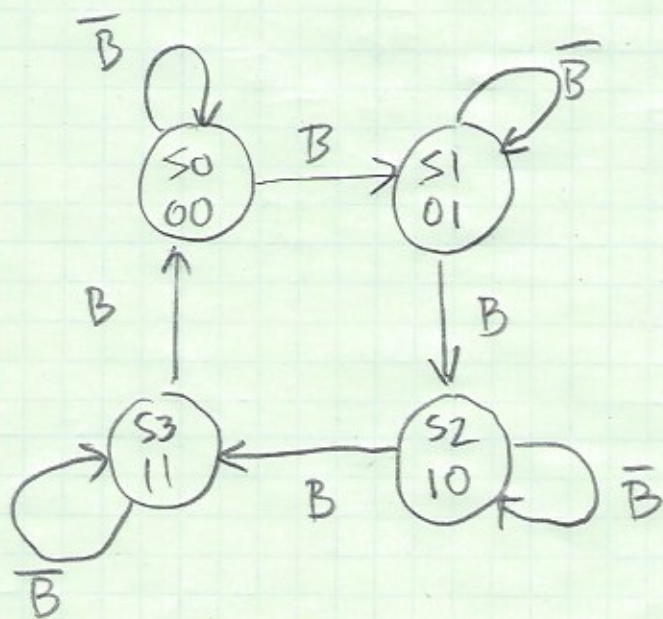

The output is the state, so the encoding must be

S0	00
S1	01
S2	10
S3	11

state transition table


Y_1	Y_0	B	Y_1'	Y_0'
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

ENEL 353


Dec 4 2019

Z of 4

3:8 decoder

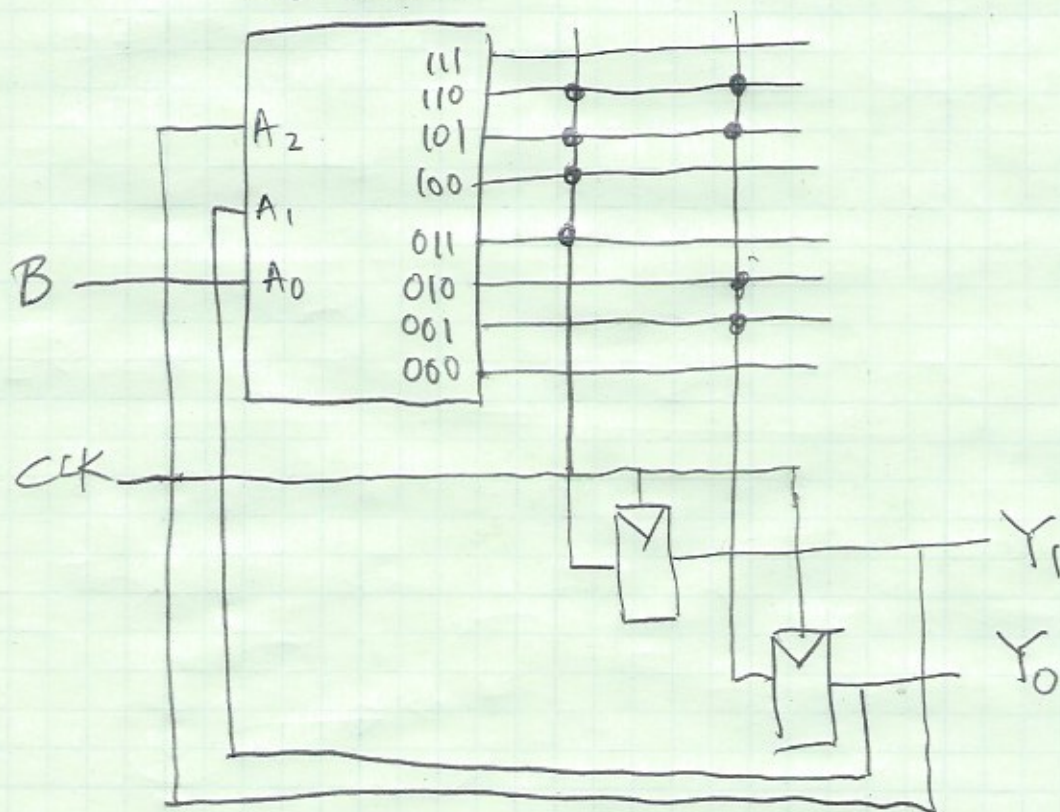

Set 10, Slide 12

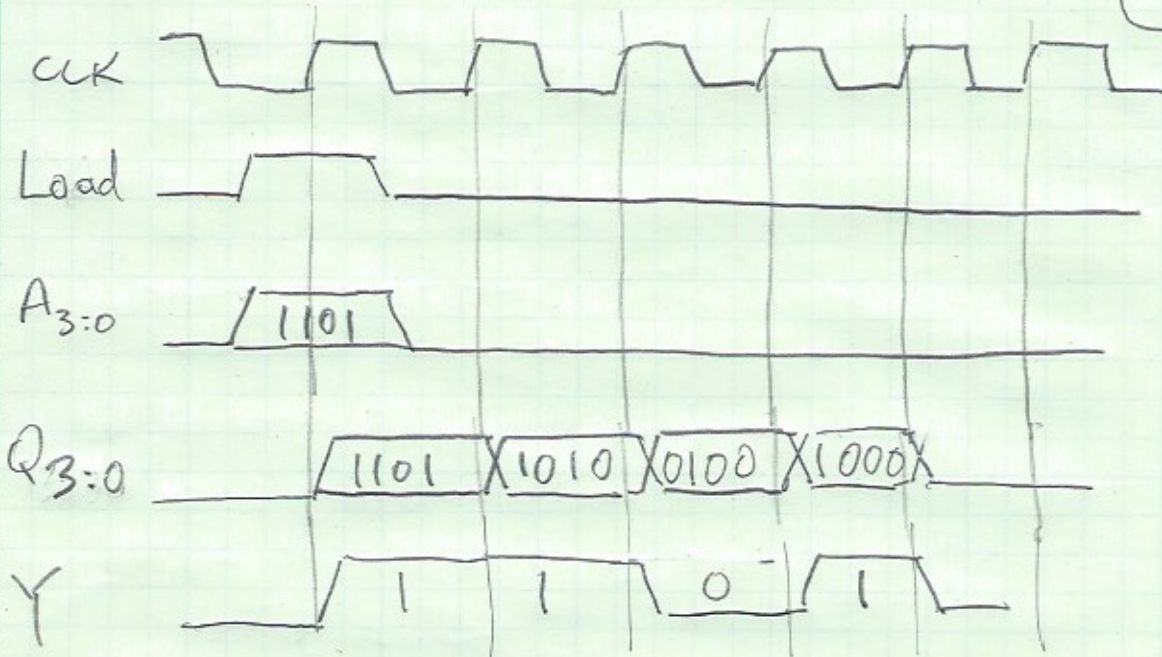

Slide 13

Companion circuit? A counter - for example the counter could count down from 7 down to 0.

Slide 14 For the circuit to work correctly, A must go $1 \rightarrow 0$ or $0 \rightarrow 1$ no more than once per clock cycle. Transitions on A must not happen in the DFF setup/hold. aperture around rising clock edges.

A special circuit called a "clock recovery circuit" can inspect a signal like A, and produce an appropriate CLK signal.

Exam Review Problem - Sequence detection

ENEL 353
Dec 4 2019
4 of 4

Part a.

<u>state</u>	<u>description</u>
S0	from reset, or looking for 1st 1 in 11011
S1	got first 1 in 11011
S2	" 2nd 1 in 11011
S3	got middle 0 in 11011
S4	got 3rd 1 in 11011
S5	got 4th 1 in 11011
S6	unused
S7	unused

