

ENEL 353 Section 02 Lecture

Wed Nov 6 2019

page 1 of 4


Midterm return - Fri Nov 8

Section B03 Lab 3 reports are due Wed Nov 20.

Set 8, Slide 27

Please do the reading!

Slide 34

 

Slide 36

state encoding

<u>state</u>	<u>S₁</u>	<u>S₀</u>
S ₀	0	0
S ₁	0	1
S ₂	1	0



state transition table
(with state encodings plugged in)

<u>state</u>		<u>next state</u>	
<u>S₁</u>	<u>S₀</u>	<u>S₁'</u>	<u>S₀'</u>
0	0	0	1
0	1	1	0
1	0	0	0
1	1	X	X

← don't-care outputs

next-state equations

ENEZ 353
Nov 6 2019
2 of 4

  


output logic

S ₁	S ₀	Y
0	0	1
0	1	0
1	0	0
1	1	X

$Y = \bar{S}_1 \bar{S}_0 = \text{NOR}(S_1, S_0)$

Schematic

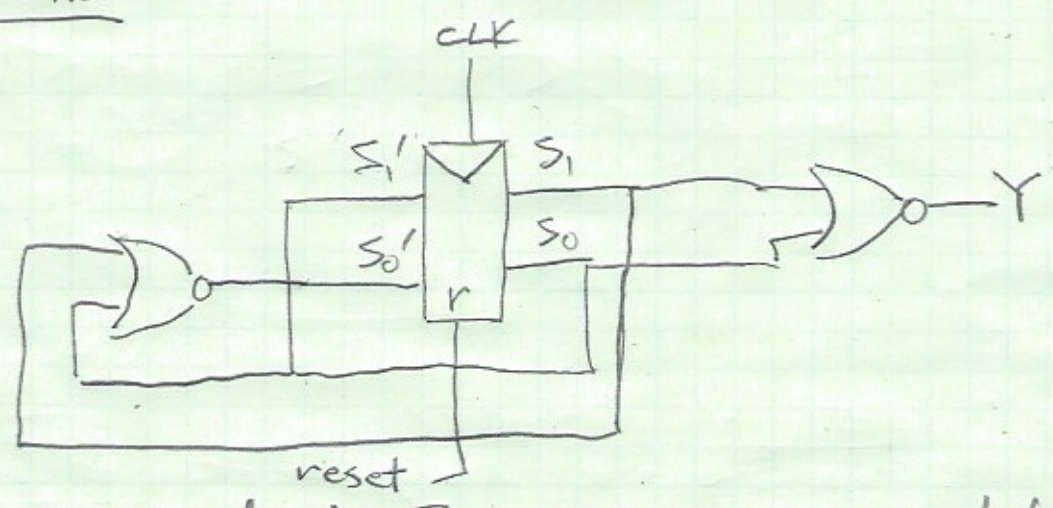

Slide 37 Divide-by-3 counter using one-hot state encoding.

<u>state</u>	<u>S₂</u>	<u>S₁</u>	<u>S₀</u>
S0	0	0	1
S1	0	1	0
S2	1	0	0

Remark: There are 5 unused state encodings
000, 011, 101, 110, 111

state transition table, with state encodings

current state			next state		
S_2	S_1	S_0	S_2'	S_1'	S_0'
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	0	0	1
[unused states]			x	x	x

ENEZ 353
Nov 6 2019
3 of 4

next state equations, for the rows that matter


$$S_2' = S_1, \quad S_1' = S_0, \quad S_0' = S_2$$

No logic gates needed! Just wires!

Output logic $Y = S_0$

Reset logic for 1-hot encoding

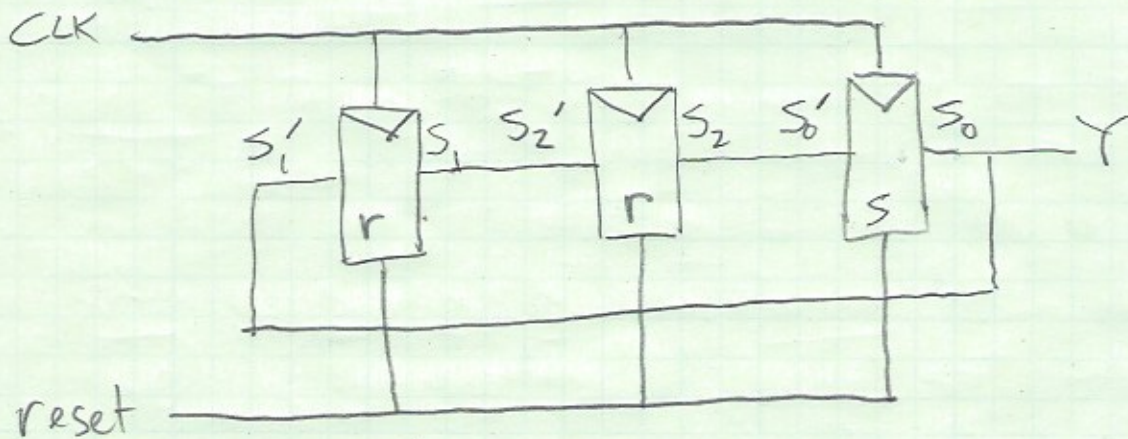On reset, the FSM should go to S_0 , encoded as 001. To make this work, use two resettable DFFs and one settable DFF.



Remark: The structure of this circuit is an example of what is called a shift register.

Slide 41

A: No. Makes a $1 \rightarrow 0$ transition near
in time to the rising clock edge at t_3 .

B: Yes

C: Two transitions between t_2 and t_3

D: Yes

Slide 42

(a) Moore. Output depends only on current state.

(b) Mealy. Output depends on current state
and current input.

Slide 43

Moore: Input was 0 at most recent rising edge
of CLK, was 1 at the 3 previous rising
edges of CLK.

Mealy: Input was 1 at the 3 most recent
rising edges of CLK, current input is 0.