

Remark
Transitions could be labelled with 0 or 1 instead of \bar{A} or A.

ENEL 353
Nov 8 2019
2 of 4

Slide 45 - Mealy FSM


States

S0: from reset, looking for first 1

S1: looking for 2nd 1

S2: looking for 3rd 1

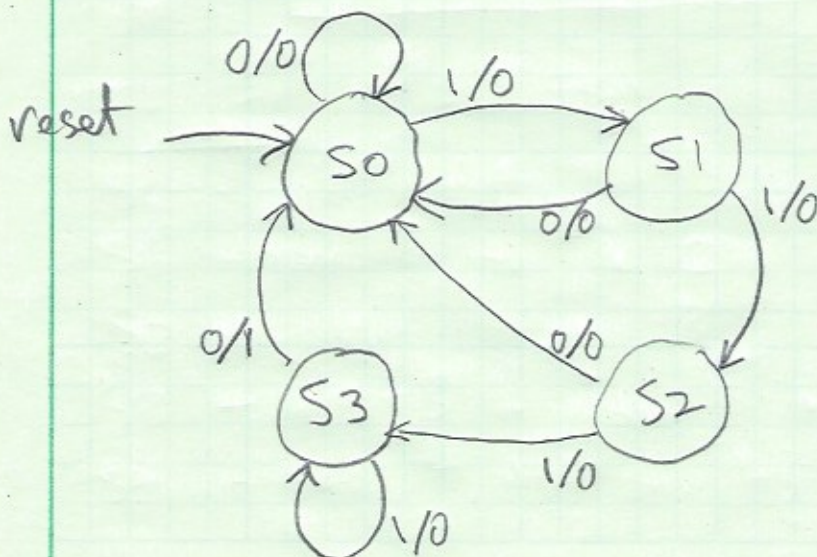S3: got 3 or more 1's - make $Y=1$ if $A=0$,
 $Y=0$ if $A=1$



arc labelling

input / output

General remarks: In Moore FSM diagrams, output should be indicated within states. That can't be done in Mealy FSM diagrams, because output depends on current input as well as current state — in Mealy diagrams, it's convenient to indicate output on transition arcs.

Slide 46



unsigned binary encoding

| state | S_1 | S_0 |
|-------|-------|-------|
| S_0 | 0 | 0 |
| S_1 | 0 | 1 |
| S_2 | 1 | 0 |
| S_3 | 1 | 1 |

Combined state and output table

| current state | | input A | next state | | output Y |
|---------------|-------|--------------|------------|--------|---------------|
| S_1 | S_0 | | S_1' | S_0' | |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 |

Equations

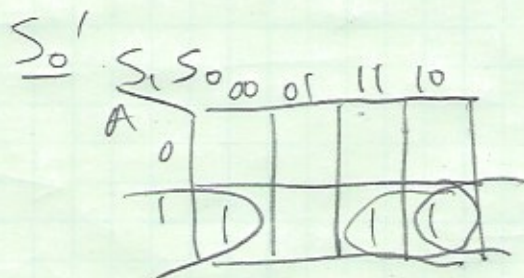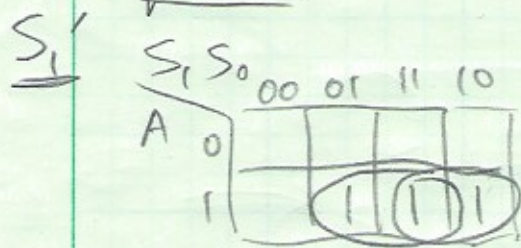

Output
(by inspection)


$$Y = S_1 S_0 \bar{A}$$

$$S_1' = S_0 A + S_1 \bar{A}$$

$$S_0' = \bar{S}_0 A + S_1 \bar{A}$$

↑ shared product ↓

ENEL 353
Nov 8 2019
3 of 4

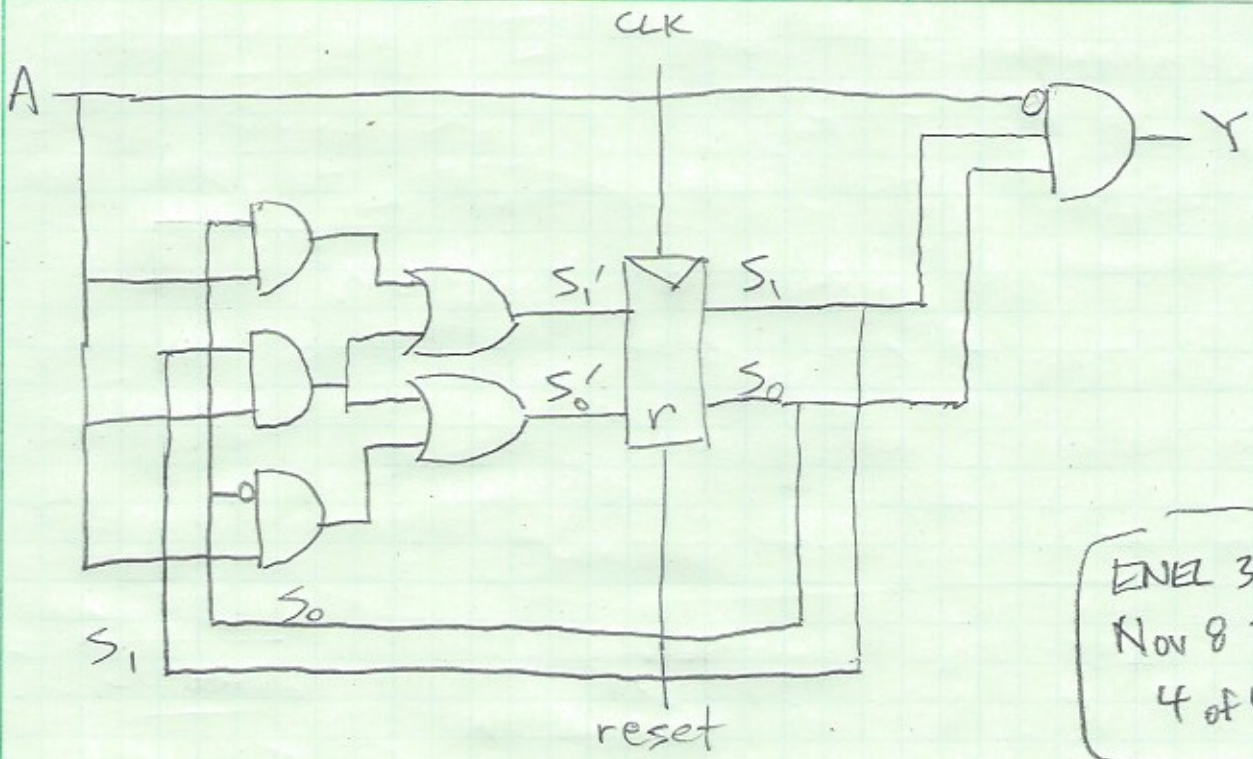

ENEL 353
 Nov 8 2019
 4 of 4