

ENEZ 353 Section W2 Lecture

page 1 of 3

Fri Nov 29 2019

- Quizzes 1, 2, 3 and Midterm are available for pick up.
- Lab marking corrections will be done by early next week.

Set 10, Slide 18

$$\underline{N=16}$$

There are  $2^{16} = 65,536$  rows. The depth is 65,536.

$$\underline{M=8}$$

There are 8 columns. The width (word size) is 8.

$$\begin{aligned} \text{Number of stored bits} &= 2^{16} \times 2^3 \\ &= 524,288 \end{aligned}$$

Slide 22

ROM is combinational. The Data output is a function of the current address only.

RAM is sequential. During a read, the Data output depends on the current Address input, and also depends on writes that occurred in the past.

Some RAM circuits are synchronous and others are asynchronous.

Slide 25

is

CORRECTION: ... ~~ix~~ stored ...

ENEL 353

Nov 29 2019


2 of 3

Number of wordlines =  $2^8 = 256$

Number of bitlines = 9

Slide 26 The "perfectly suited" element is a decoder. It receives an N-bit input, and turns on ONE of  $2^N$  output wires.

Slide 29 IMPORTANT: Dots in this style of diagram do NOT represent simple connections of wires.

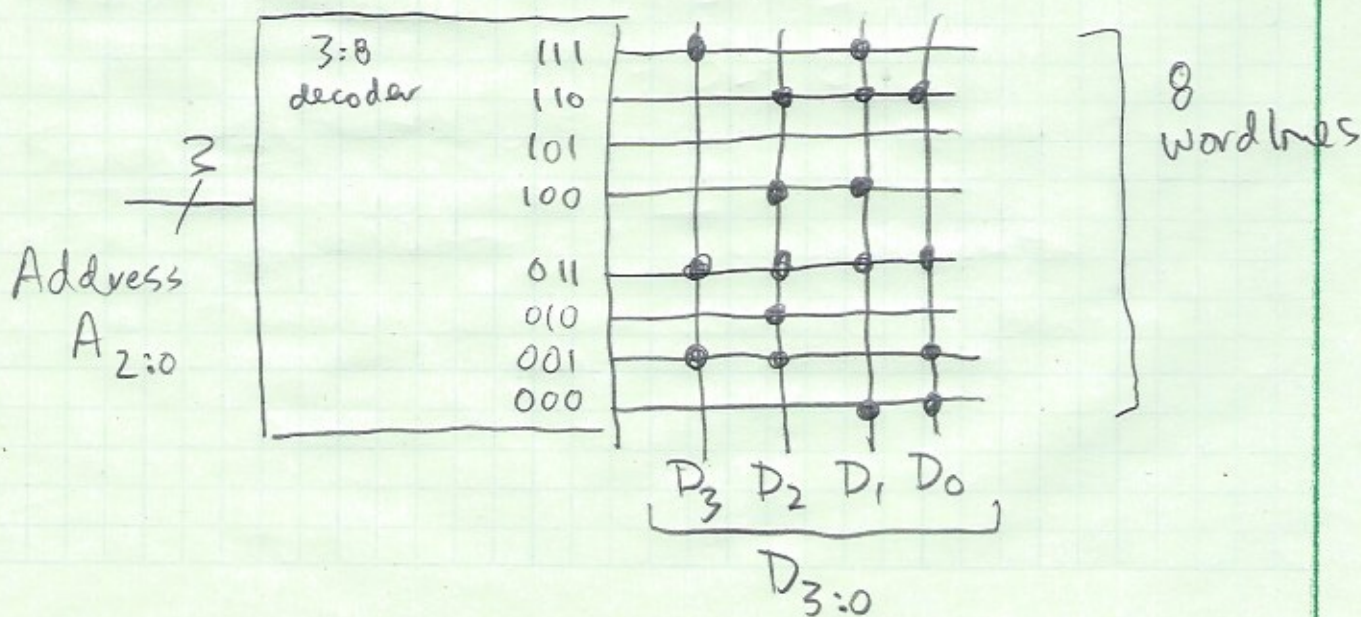

Slide 31

Example 1 2 input bits, 3 output bits

⇒ array  $2^2 \times 3$

function

minterm numbers (binary)

$$F = A \oplus B = \bar{A}B + A\bar{B}$$

01, 10

$$G = \overline{A \oplus B} = \bar{A}\bar{B} + AB$$


00, 11

$$H = \bar{A} + \bar{B}$$

$$= \bar{A}(\bar{B} + B) + \bar{B}(\bar{A} + A)$$

$$= \bar{A}\bar{B} + \bar{A}B + \bar{A}B + A\bar{B} \quad 00, 01, 10$$

ENEL 353  
Nov 29 2019  
3 of 3

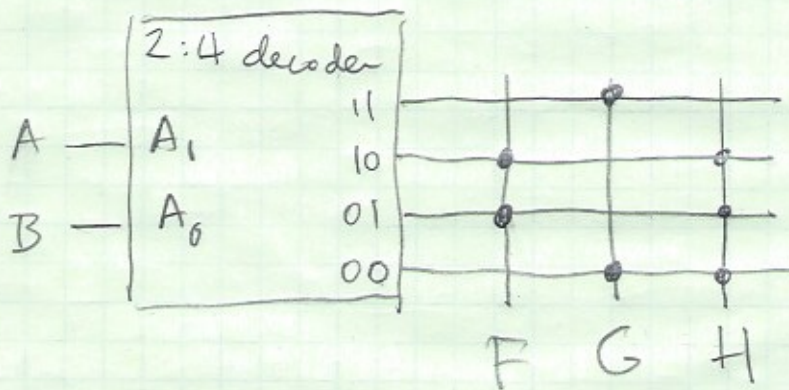

Example 2 3 input bits, 4 output bits

⇒ array size is  $2^3 \times 4$

A	B	C	E	F	G	H
0	0	0	0	0	0	1
0	0	1	0	0	0	1
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	0	1
1	0	1	0	1	1	1
1	1	0	1	0	1	1
1	1	1	0	0	1	1

