

ENEL 353 Section 02 Lecture

Wed Oct 2 2019

page 1 of 4


Quiz #2 Tue Oct 8

- topics listed on ENEL 353 Home Page
- Problem Set 2 has been posted

Set 4, Slide 22


2-input AND
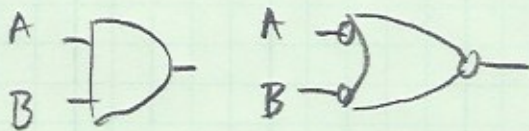
$$AB = \overline{\overline{AB}} = \overline{(\overline{A} + \overline{B})}$$




3-input OR
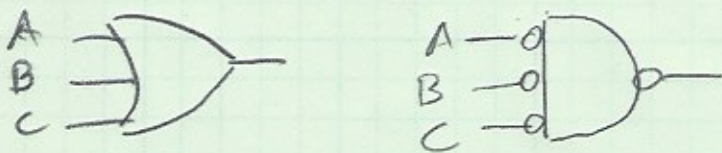
$$A+B+C = \overline{\overline{A+B+C}} = \overline{\overline{A} \overline{B} \overline{C}}$$




For the given example ...

Push a bubble starting at output Y

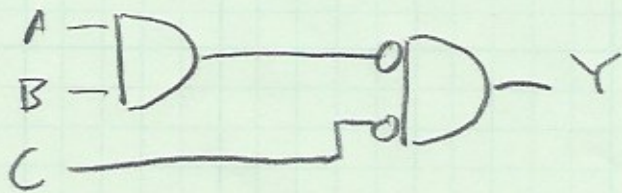


Bubble-push on the AND gate ...

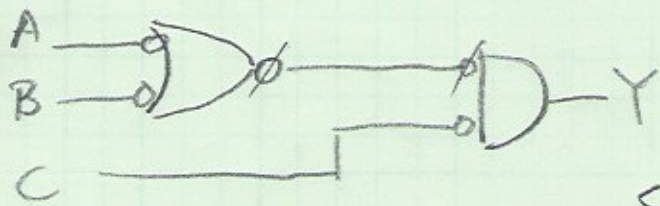

$$\text{So } Y = (\overline{A+B})\overline{C}$$

Slide 28

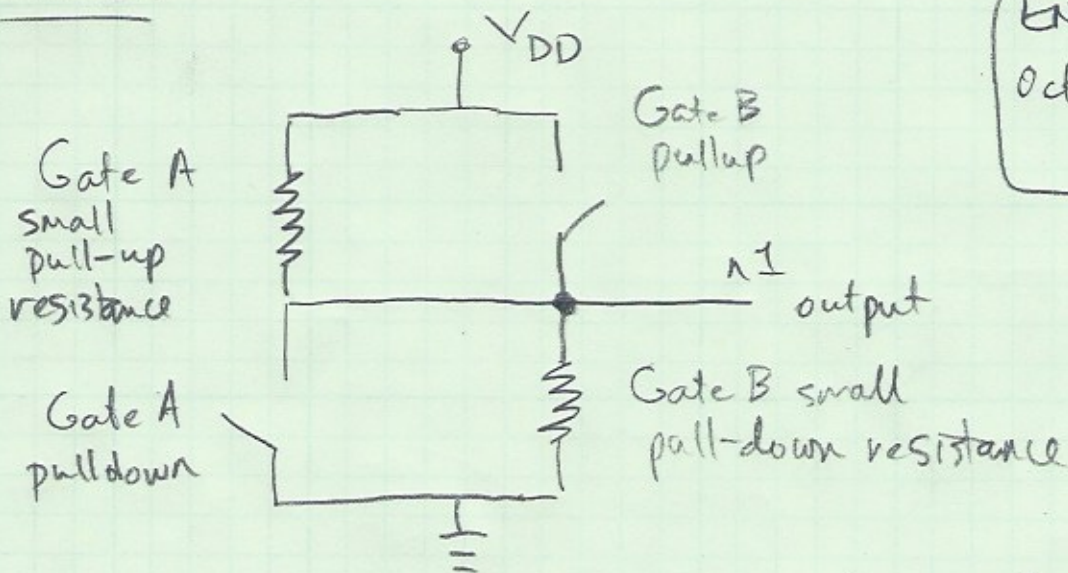

ENEL 353
Oct 2 2019
2 of 4

The voltage at $n1$ depends on the relative strength of the Gate A pull-up and the Gate B pull-down. V_{n1} is probably in the "forbidden zone." This situation is called contention or fighting.

Another problem: There is a low-resistance path from V_{DD} to ground - lots of current, so wasted power, possible circuit destruction.

Slide 32

The output node is isolated from both V_{DD} and GND. It is said to be floating or in a high-impedance state. Circuits use Z as a symbol for this state

ENEL 353

Oct 2 2019

3 of 4

Slide 33

Let's add a column to the table

E	A	pull-up	pull-down	state at Y
0	0	OFF	OFF	Z
0	1	OFF	OFF	Z
1	0	OFF	ON	LOW - same as A
1	1	ON	OFF	HIGH - same as A

In words, if $E=0$, Y is in state Z.

IF $E=1$, Y is a copy of A.

Slide 34

At any given time, only one E_i should be 1.

Example: IF $E_2 = 1$ and $E_1 = E_3 = \dots = E_N = 0$,

then gate 2 drives the common output wire and gates 1, 3, ..., N have no effect on the common output wire.

What if all of E_1, E_2, \dots, E_n are 0?

Common output wire will be in the Z state.

What if two or more of E_1, \dots, E_n are 1?

Contention is possible.

ENEL 353

Oct 2 2019

4 of 4