

# ENEL 353 Section 02 Lecture

Mon Oct 21 2019

page 1 of 4

Midterm - evening of Mon Oct 28

- more details on course home page

Set 6, Slide 12

Select bits for 16:1 mux? 4

Select bits for 32:1 mux? 5

Select bits for  $N:1$  mux?  $\log_2 N$  ← general formula


(But the general formula only makes sense if  $N$  is a power of two.)

Slide 14 Here the output of the AND gate is 0.

Slide 15


8:1 mux

Solution

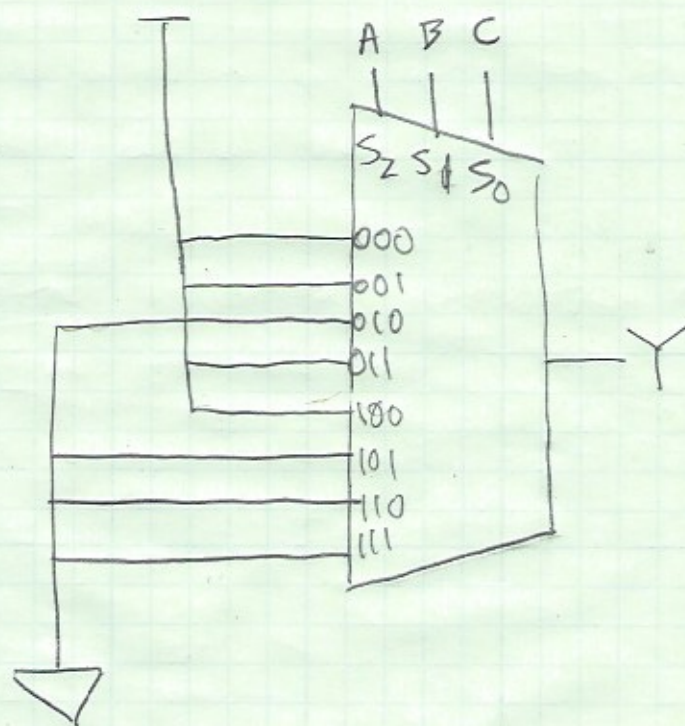

4:1 mux solution


Let's try using (A, B) as  $(S_1, S_0)$

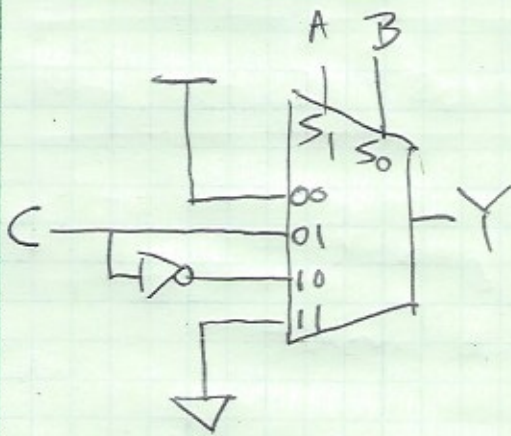

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$Y=1$  (for rows 000, 001)  
 $Y=C$  (for rows 010, 011)  
 $Y=\bar{C}$  (for rows 100, 101)  
 $Y=0$  (for rows 110, 111)

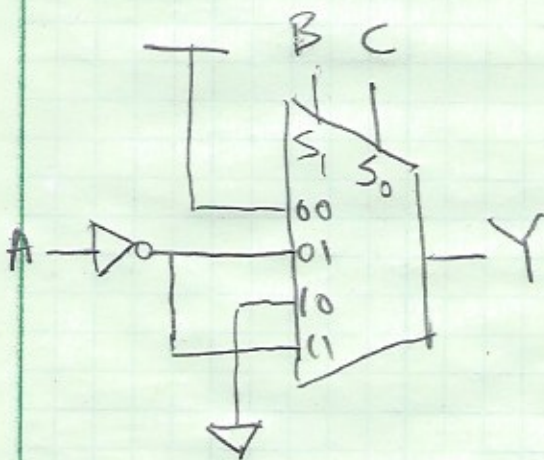4:1 mux solution, using (B, C) as  $(S_1, S_0)$




A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$Y=1$  (for rows 000, 001)  
 $Y=\bar{A}$  (for rows 010, 011)  
 $Y=0$  (for rows 100, 101)  
 $Y=\bar{A}$  (for rows 110, 111)

Slide 16

3:1 mux (two different reasonable specifications)

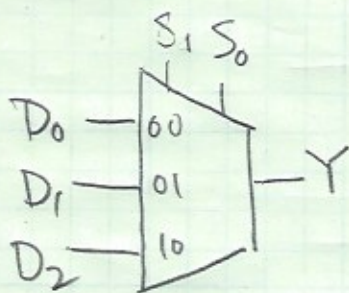

choice 1

$S_1$	$S_0$	Y
0	0	$D_0$
0	1	$D_1$
1	X	$D_2$

choice 2


$S_1$	$S_0$	Y
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	X

↑  
don't care input


↑  
don't care output

Let's go with choice 1

Implementation with two 2:1 muxes

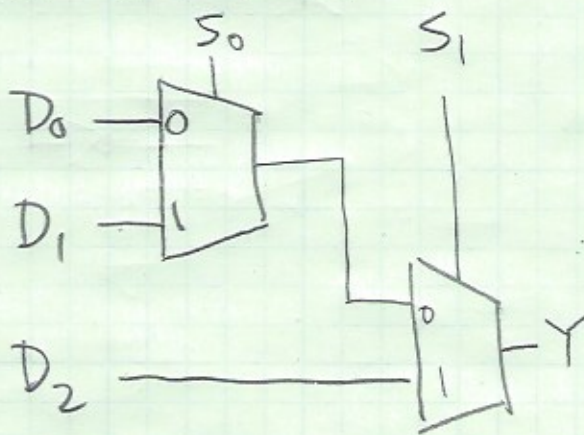

With a 4:1 mux

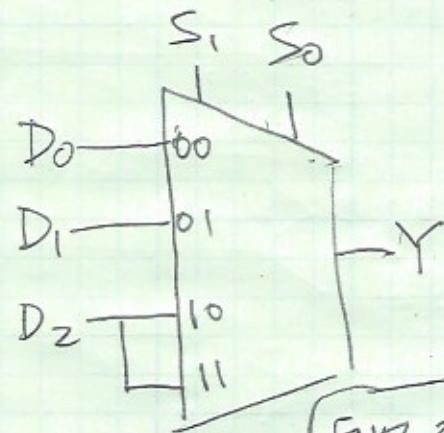

ENEL 353  
Oct 21 2019  
3 of 4


Slide 18

2:4 decoder. Let  $k$  be the number encoded by  $A_1, A_0$  in unsigned binary. Then  $Y_k = 1$  and all the other outputs are 0.

Truth table

$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


Implementation with NOT and AND gates.

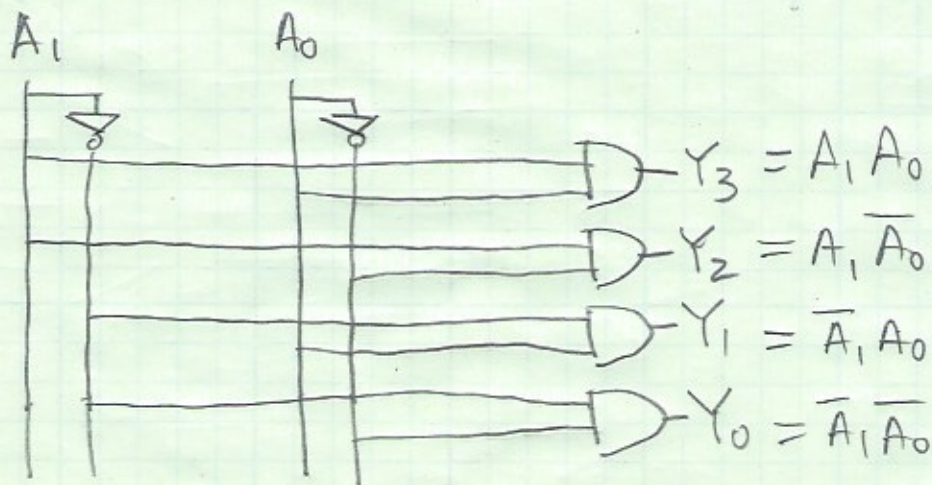

A decoder can be thought of as a "minterm generator."

Slide 19

A	B	$C_{IN}$	$C_{OUT}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

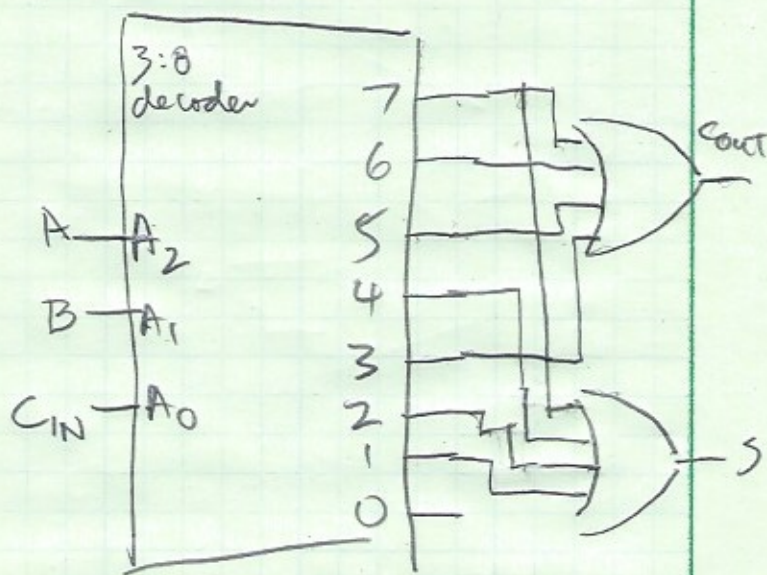

$$C_{OUT} = m_3 + m_5 + m_6 + m_7$$

$$S = m_1 + m_2 + m_4 + m_7$$

$Y_0$  output of decoder should float. It should NOT be connected to ground — that would cause high current when  $(A, B, C_{IN}) = (0, 0, 0)$

ENEL 353  
Oct 21 2019  
4 of 4