

ENEL 353 Section 02 Lecture

Wed Oct 30 2019

page 1 of 4


Quiz #3 - Tue Nov 5

Set 7, Slide 18

A D latch is said to be level-sensitive with respect to CLK - Q follows D or ignores D based on the level (LOW or HIGH) of CLK.


(We'll see soon that a D flip-flop is not level-sensitive - instead it's edge-triggered with respect to CLK.)

Slide 22

 

Slide 23

D flip-flop behaviour

 

glitches on D
between rising edges of CLK
have no effect on (Q, \bar{Q})


Slide 26

Master latch - goes opaque when the flip-flop CLK goes HIGH - that is, on a rising edge of that CLK. So the signal at NI will be the value "grabbed" when the FF CLK had a rising edge, and NI persists in that state for half a clock cycle.

Slave latch - is transparent for the first half of a cycle. So $Q_{out} = NI$ during that time. For the second half of the cycle, the latch is opaque and holds the value NI had when the FF CLK went LOW.

ENEZ 353
Oct 30 2019
2 of 4


Slide 27

 


Slide 30

t_{ccq} is clock-to-Q contamination delay, the shortest possible delay between a rising on the CLK input of a DFF and a change in the Q output of that DFF.

Q=0 just before a rising edge of CLK1

 

Q=1 just before a rising edge of CLK1

 

In both cases, the change in D is safely separated by at least $t_{ccq} + t_{cd_NOT}$ from the rising CLK edge, so changes in Q will be predictable.

Slide 32 If $f_{CLK} = 100 \times 10^3$ Hz, then

$$T_{CLK} = \frac{1}{10^5 \text{ s}^{-1}} = 10^{-5} \text{ s} = 10,000,000 \text{ ps}$$

The period of CLK1 is so long that the edges of CLK1 and CLK2 appear to be perfectly vertical and aligned.

ENEL 353
Oct 30 2019
4 of 4