

T02 Tutorial Slides for Week 5

ENEL 353: Digital Circuits — Fall 2019 Term

Steve Norman, PhD, PEng

Electrical & Computer Engineering
Schulich School of Engineering
University of Calgary


01 October, 2019

Exercise 1: Algebraic expression to truth table

Write out the truth table for $F(A, B, C) = AB + \bar{A}\bar{B} + A\bar{B}C$.

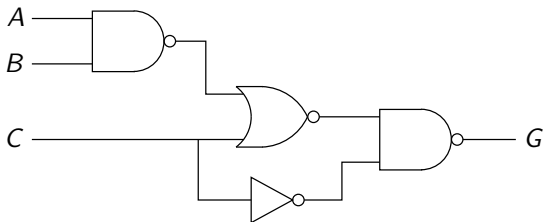Exercise 2: Circuit to truth table



Write out the truth table for $G(A, B, C)$.



Which would be a simpler description for $G(A, B, C)$:
SOP canonical form or POS canonical form?

Exercise 3: Voltage levels

Consider these two buffer designs:

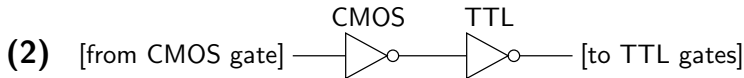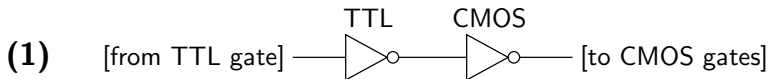

Use the table below to determine which of the buffer designs will work reliably. Assume that there is no significant additive noise on any of the wires.

Family	V_{DD}	V_{IL}	V_{IH}	V_{OL}	V_{OH}
TTL	5.0 V	0.8 V	2.0 V	0.4 V	2.4 V
CMOS	5.0 V	1.35 V	3.15 V	0.33 V	3.84 V

Exercise 4: Expressions—SOP, SOP canonical, POS, POS canonical

Suppose the input variables for a logic function are A , B and C . Which of the following expressions are in

- ▶ sum-of-products form?
- ▶ sum-of-products canonical form?
- ▶ product-of-sums form?
- ▶ product-of-sums canonical form?

1. $A + \bar{B} + C$

2. $\bar{A}\bar{B}C$

3. $AB + \bar{A}\bar{B}\bar{C}$

4. $(A+B+\bar{C})(\bar{A}+B+C)$

5. $\bar{A}BC + A\bar{B}C + AB\bar{C}$

6. $(A+B)(\bar{B}+\bar{C})$

Exercise 5: Truth table to SOP and POS canonical forms

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Write SOP and POS canonical forms for $F(A, B, C)$. Express your answers using literals, and also using minterm or maxterm numbers.

Exercise 6: Algebra practice

From Exercise 1, $F(A, B, C) = AB + \bar{A}\bar{B} + A\bar{B}C$.

Use algebra to get a canonical SOP expression for F .

Then check that the truth table from Exercise 1 leads to the same canonical SOP expression.