

T02 Tutorial Slides for Week 11

ENEL 353: Digital Circuits — Fall 2019 Term

Steve Norman, PhD, PEng

Electrical & Computer Engineering
Schulich School of Engineering
University of Calgary

19 November, 2019

Topics for today


Exercises on FSM structure.

FSM design exercises.


If time permits, an FSM analysis problem.

 Exercise 1: Moore FSMs and the clock divider

This is the general structure of a Moore FSM ...



And this is a clock divider circuit ...

 

The clock divider circuit is just about the simplest possible Moore FSM.

For the clock divider,

- ▶ What is M , the number of input bits?
- ▶ What is k , the number of state bits?
- ▶ What is N , the number of output bits?
- ▶ What is correct Boolean algebra for the next-state logic?
- ▶ What is correct Boolean algebra for the output logic?

Notes about notation for FSMs (review)

Your ENEL 353 instructors will follow notation used in the course textbook.

S_0, S_1, S_2 and so on are **names of states**. Note that the numbers are the same size as the S , on the same level.

S_0, S_1, S_2 and so on are **state bits**— Q outputs of DFFs. Note that the numbers are **subscripts**.


S'_i is the **next value** of the state bit S_i .

Many books use the $'$ operator for NOT. (For example, in those books A' means what our textbook would write as \bar{A} .)

Watch out for that!

In discussion of FSMs, some books use Q_i for the i th state bit, and Q_i^* for the next value of Q_i .


Exercise 2

 

For this Moore FSM, what are


- ▶ M , the number of inputs?
- ▶ k , the number of state bits?
- ▶ the number of possible states of the machine?
- ▶ N , the number of output bits?
- ▶ next-state equations?
- ▶ output equations?

Exercise 2, continued

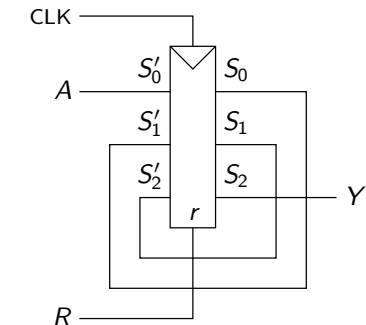

Let's add waveforms for S_0 , S_1 and S_2 to the timing diagram.

Let's assume **synchronous reset** for the three DFFs in the register.

 

Exercise 3: Simple FSM design

Design an FSM with a single output bit, such that

- ▶ on reset the output goes to 0;
- ▶ when reset is turned off, the output repeats the sequence of 0 for one clock cycle, 1 for three cycles, 0 for one cycle, 1 for three cycles, and so on.

Exercise 4: Mealy FSM design

Here's a specification for an FSM:

- ▶ inputs are CLK, reset, and a 1-bit signal called A;
- ▶ output is a 1-bit signal called Y;
- ▶ on reset, Y should go to 0 as quickly as possible;
- ▶ as soon as there have been at least two post-reset rising edges of CLK, Y should be 1 if the current value of A matches the value of A at the last two rising edges of CLK.

Why does this require a Mealy FSM? (Why can't it be Moore?)

Let's draw a state transition diagram.

Let's make a combined state transition and output table, using symbols (S_0 , S_1 , etc.) to represent the states.

For convenience, here's a repeat of the specification:


- ▶ inputs are CLK, reset, and a 1-bit signal called A;
- ▶ output is a 1-bit signal called Y;
- ▶ on reset, Y should go to 0 as quickly as possible;
- ▶ as soon as there have been at least two post-reset rising edges of CLK, Y should be 1 if the current value of A matches the value of A at the last two rising edges of CLK.

We won't continue all the way to next-state equations and a schematic, but let's think about some of the steps.

What is the minimum number of state bits? If we choose a state encoding with that number of bits, how many rows will the truth table for next-state and output logic have?

Should the state register have synchronous or asynchronous reset?

Exercise 5: Analysis of an FSM

 

Is this a Moore FSM or a Mealy FSM?

Let's draw a state transition diagram for the circuit.

Exercise 6: FSM analysis, continued

Describe in English what the circuit of Exercise 5 does. Add a timing diagram if that helps with the description.

(This is too fuzzy a question to put on a quiz or exam, but it's useful to think about.)