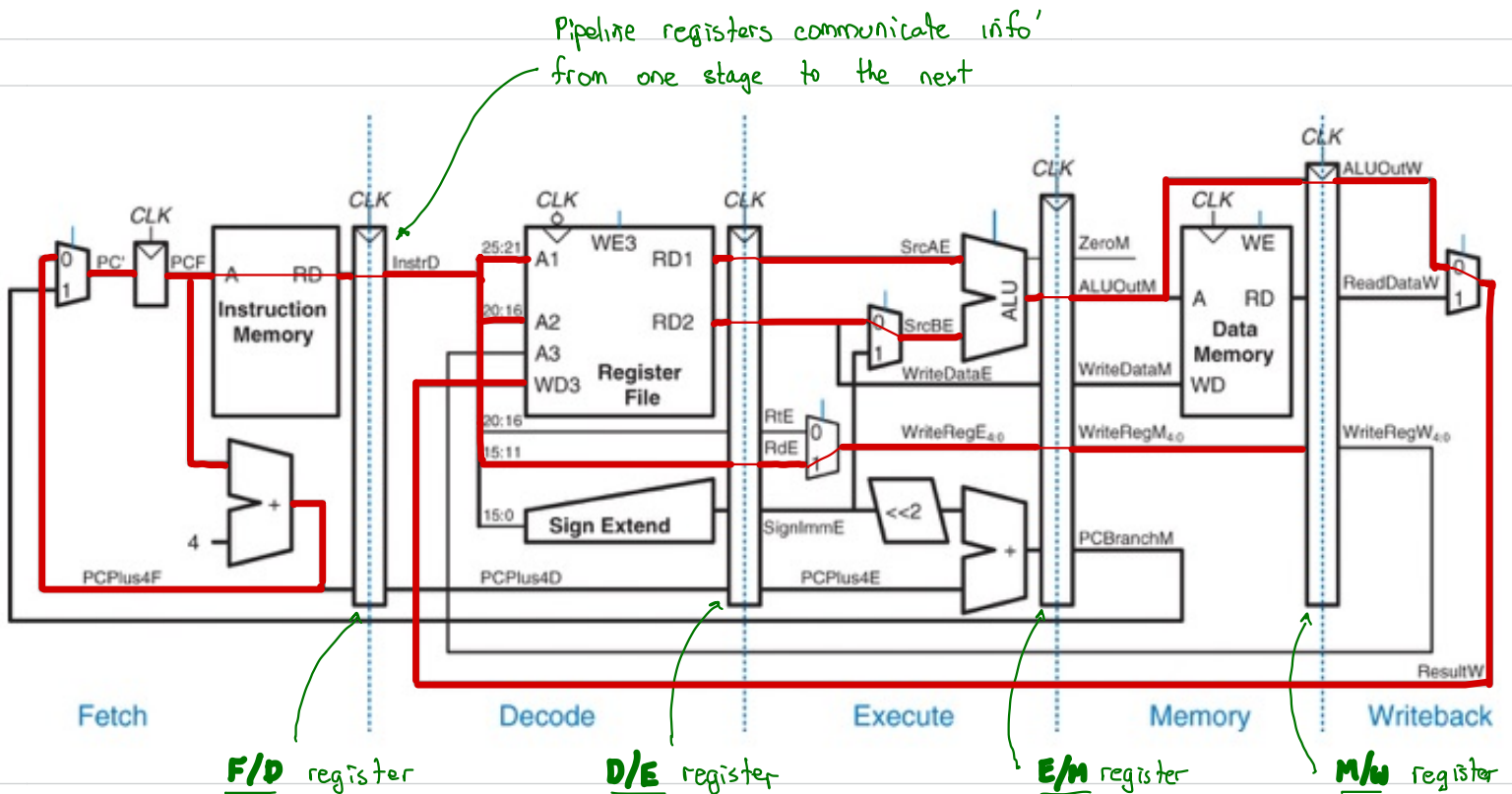


Pipeline registers (continued)

Pipelining is made possible by using more DFFs to make pipeline registers.

- more than 32 bits
- updates made on positive clock edges.

The processor now fitted with pipeline registers (Textbook Fig. 7.46)



Tracing the main datapath of an R-type instruction

Tracing an R-type instruction - details


Suppose we have

Address : 0x0040_0030 sllt \$2, \$4, \$5
 (rd) (rs) (rt)

Fetch stage

Data written to the F/D register

 - 32-bit instruction word for slt
- PC+4 (0x0040-0034) written to PCplus4F



CLOCK EDGE: Data written to the "F" side of F/D register now available on "D" side.

Decode stage

Data written to the D/E pipeline register:

Needed for R-type instructions:

- RD1 (contents of GPR \$4)
- RD2 (contents of GPR \$5)
- Instr_{15:11} 00010₂ (GPR \$2)

Not need, but still copied

- Instr_{20:16} 00101₂ (GPR \$5)
- sign-extended 32-bit constant
- PCplus4D 0x0040-0034

- this is information that might be needed for other instruction types, but not R-type.

Execute stage

Data written to the E/M stage:

Important for R-type:

- 32-bit ALUResult, and Zero
- Instr_{15:11} 00010₂ (GPR \$2), called WriteRegE

Not needed:

- PCBranch (branch destination)

Memory stage

Data written to M/W register:

- ALUOutM (ALUResult for s1t)
 - WriteRegM (OOO10₂, GPR \$2)
- } passed straight through the Memory stage

Not needed:

- Dmem's RD output

Writeback stage

Finally, after the clock edge that copies the "M" side to the "W" side:

- ResultW (= ALUResult) and WriteRegW given to R-file.
- Write to R-file occurs on the next NEGATIVE clock edge (one-half cycle after the main clock edge).

Pipeline control

Exactly the same control unit as the single-cycle machine.

Control signals are produced in the Decode stage

- appropriate signals proceed from stage to stage in step with each instruction.

E.g., for s1t:


- writeback controls are MemtoReg = 0, RegWrite = 1

- passed along through pipeline registers

D/E → E/M → M/W

writeback control bits are not used until after storing in M/W register.

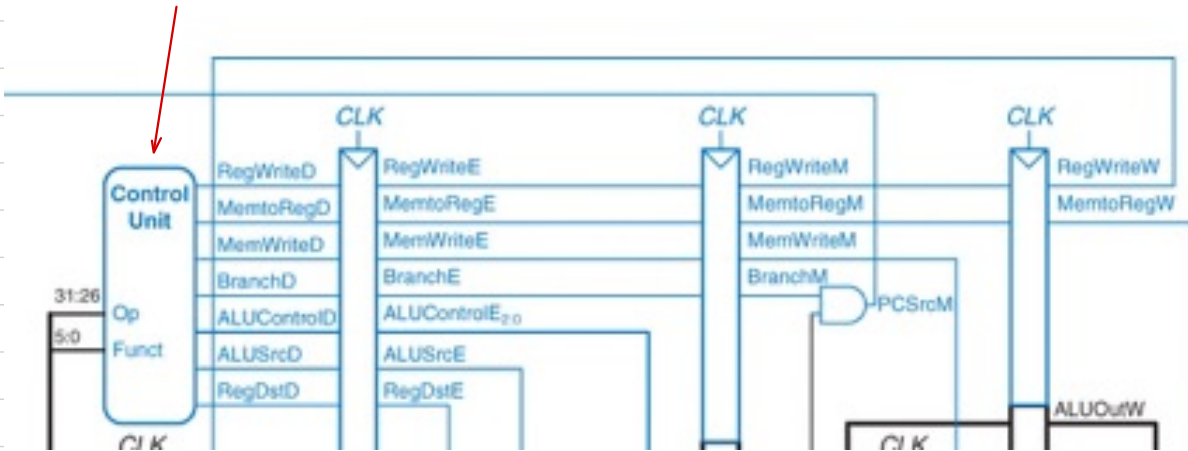Control unit identical to single cycle machine



Control signals in "lock step" with data through each pipeline stage.