

1(a) In 10's-complement, $80 \rightarrow 0080$

$$-50 \rightarrow 10000 - 50 = 9950$$

$$\begin{array}{r} \text{Add:} \\ 0080 \\ + 9950 \\ \hline 0030 \end{array} = 30_{10}$$

ignore
end carry

1(b) In 2's-complement, $80 \rightarrow 01010000$

$$-50 \rightarrow 00110010 \xrightarrow{1's} 11001101$$

$$+ \xrightarrow{1} 11001110$$

$$\begin{array}{r} \text{Add:} \\ 01010000 \\ + 11001110 \\ \hline 00011110 \end{array} = 30_{10}$$

ignore
end carry

1(c) We have $80 - (-50)$, so $80 + 50$

$$\begin{array}{r} 80 \rightarrow 01010000 \\ 50 \rightarrow 00110010 \\ \hline 10000010 \end{array}$$

Two last carries differ, so overflow has occurred

sign of sum is opposite of both augend, addend, so overflow has occurred

Result is negative, $10000010 \xrightarrow{1's} 01111101$

$$+ \xrightarrow{1} 01111110 = 126$$


Answer -126_{10} .

1(d) 8-bit sign-magnitude


$$\begin{array}{r} 80 \rightarrow 01010000 = 120_8 = 50_{16} \\ -50 \rightarrow 10110010 = 262_8 = B2_{16} \end{array}$$




2(a) $F = x_1x_2' + x_2x_3' + x_1'x_3$

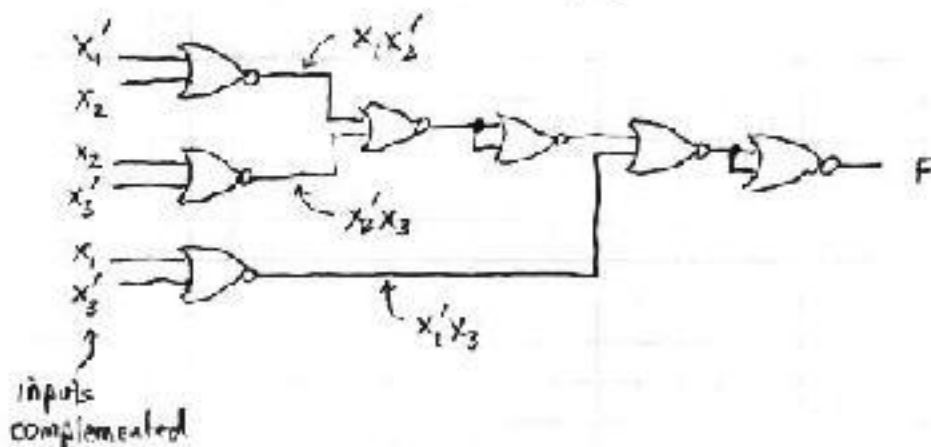


2(b) Several acceptable answers

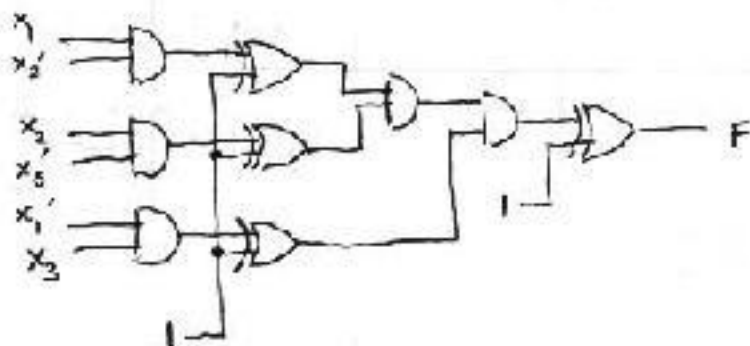

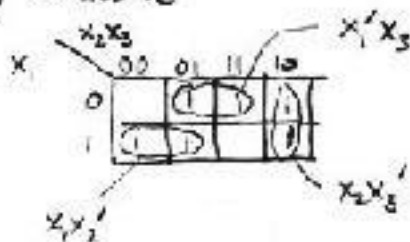More elegant solution by observing that three product terms are mutually exclusive



Then,

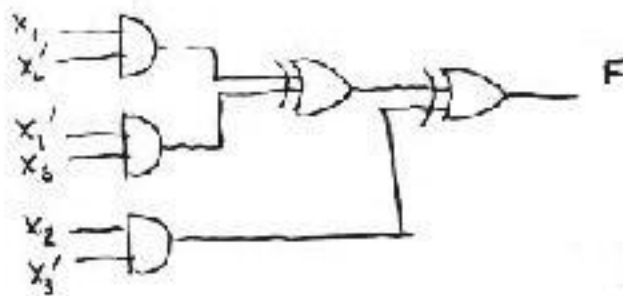

3. The truth table

a_3	a_2	a_1	a_0	g_3	g_2	g_1	g_0	C_1	C_0	V
0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	0	0	1
0	0	1	0	0	0	1	1	0	1	1
0	0	1	1	0	0	1	0	0	1	1
0	1	0	0	0	1	1	0	1	0	1
0	1	0	1	0	1	1	1	1	0	1
0	1	1	0	0	1	0	1	1	0	1
0	1	1	1	0	1	0	0	1	0	1
1	0	0	0	1	1	0	0	1	1	1
1	0	0	1	1	1	0	1	1	1	1
1	0	1	0	1	1	1	1	1	1	1
1	0	1	1	1	1	1	0	1	1	1
1	1	0	0	1	0	1	0	1	1	1
1	1	0	1	1	0	1	1	1	1	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

C_1, C_0, V are functions of a_3, a_2, a_1, a_0

$$C_1 = \sum (4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15) + d \sum (0)$$

$$C_1 = \prod (1, 2, 3) + d \prod (0)$$

$$C_0 = \sum (2, 3, 8, 9, 10, 11, 12, 13, 14, 15) + d \sum (0)$$

$$C_0 = \prod (1, 4, 5, 6, 7) + d \prod (0)$$

$$V = \sum (1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$V = \prod (0)$$

4 a

f_1

		yz			
	wx	00	01	11	10
00			1	1	
01				1	1
11	1	1		1	
10	1	1			

One of possible minimal SOP:

$$f_1 = w'x'z + w'xy + xyz + wy'$$

f_2

		yz			
	wx	00	01	11	10
00		1			1
01	1	1			
11	1	1			
10	1				1

One of possible minimal SOP:

$$f_2 = x'z' + xy' + wz'$$

OR

Minimal POS:

$$f_2 = (x+z')(y'+z')(w+x+y')$$

		yz			
	wx	00	01	11	10
00		0	0	0	
01		0	0	0	0
11			0		
10	0	0			

f_3

		yz			
	wx	00	01	11	10
00	1				1
01	1	1			
11					1
10				1	1

Minimal SOP:


$$f_3 = w'x'z' + w'xy' + wx'y + wyz'$$

OR one of possible minimal POS:

$$f_3 = (w+y)(x'+y'+z') \cdot (w+x'+y')(w+x+z')$$

		yz			
	wx	00	01	11	10
00		0	0		
01			0	0	0
11	0	0		0	
10	0	0		0	

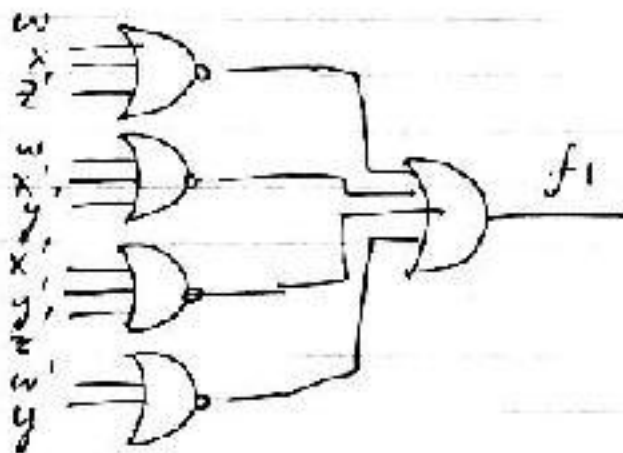
4 (b) $f_1 = w'x'z + w'xy + xyz + wy' =$
 $= \overline{w+x+z} + \overline{w+x'+y'} + \overline{x'+y'+z'} + \overline{w'+y}$




4 (c) $f_1 = w'x'z + w'xy + xyz + wy'$
 $f_2 = x'z' + xy' + w, z'$ or $f_2' = x'z + yz + w'xy$
 $f_3 = wxz' + w'xy' + wx'y + wyz'$ or
 $f_3' = wy' + xyz + w'xy + w'x'z = f_1$

w	x	y	z	f1	f2	f3
0	0	1	1	1	-	1
0	1	1	-	1	1	1
-	1	1	1	1	-	1
1	-	1	-	1	-	1
-	0	-	1	-	1	-
-	-	1	-	-	1	-

Comp. Compl.
 f_1 f_2' f_3'

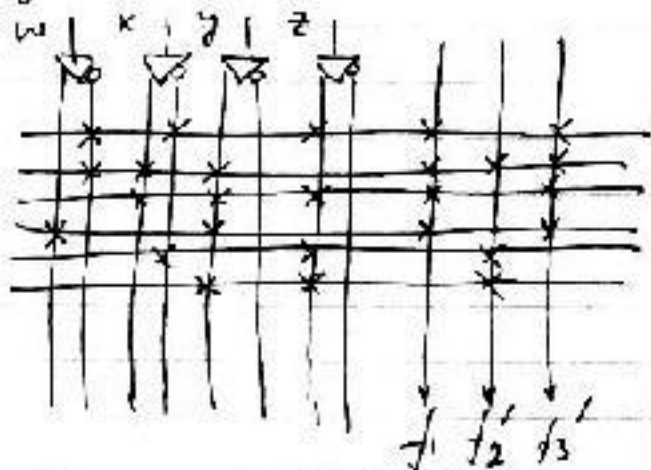


4 (d)


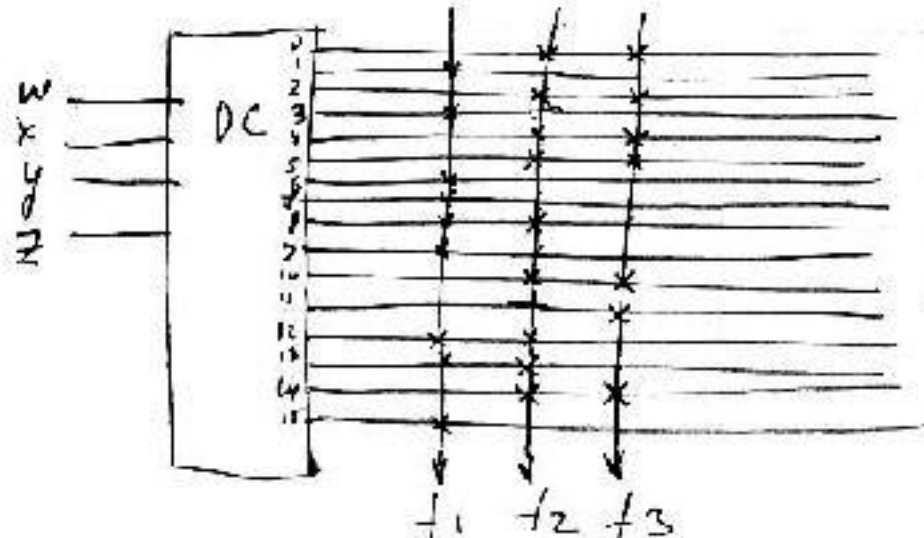


ROM is based on non minimized short hand SOP: Σ

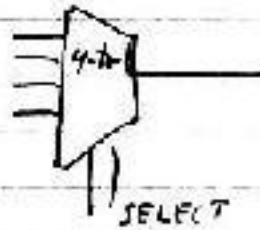4(e) 4-to-1 MUX
has 4 inputs
and 2 select
lines



W X Y Z	f_1	f_2	f_3 or $f_3 = f_1'$
00 00	0	0	0
00 01	0	0	0
00 10	0	0	0
00 11	0	0	0
01 00	0	0	1
01 01	0	0	1
01 10	0	0	1
01 11	0	0	1
10 00	1	0	0
10 01	1	0	0
10 10	1	0	0
10 11	1	0	0
11 00	1	1	0
11 01	1	1	0
11 10	1	1	0
11 11	1	1	0

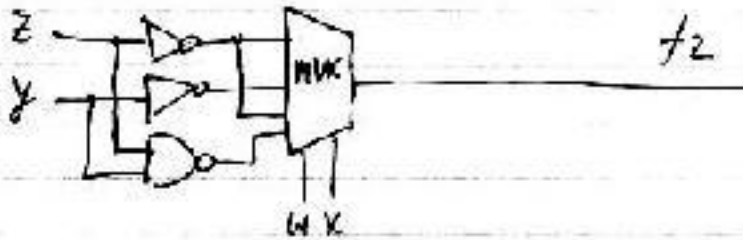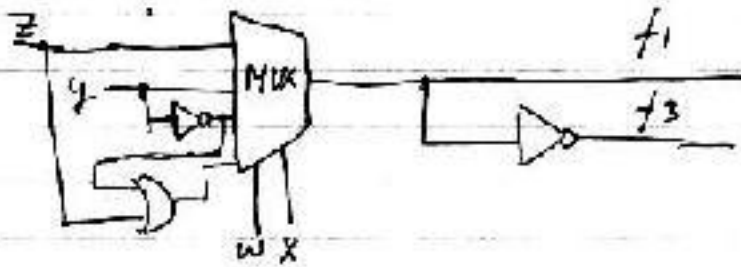

5 a) Excitation equations

$$D_1 = X(Q_1 + Q_2)$$

$$D_2 = X(Q_1 + Q_2')$$

Transition equations:

$$Q_1^+ = D_1, \quad Q_2^+ = D_2$$

Output equation:

$$Z = Q_1' + X(Q_1 + Q_2')$$

To redesign, use:

Q	Q ⁺	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present state		inp.	Next state out			J ₁	K ₁	J ₂	K ₂
Q ₁	Q ₂	X	Q ₁ ⁺	Q ₂ ⁺	Z				
0	0	0	0	0	1	0	X	0	X
0	0	1	0	1	1	0	X	1	X
0	1	0	0	0	1	0	X	X	1
0	1	1	0	0	1	1	X	X	1
1	0	0	0	0	0	X	1	0	X
1	0	1	0	0	0	X	X	0	1
1	1	0	1	1	0	X	1	X	1
1	1	1	1	1	0	X	0	X	0

J₁:

Q ₁	Q ₂	X	00	01	11	10
0	0	0			1	
0	1	0	X	X	X	X

$$J_1 = Q_2 X$$

K₁:

Q ₁	Q ₂	X	00	01	11	10
0	0	0	X	X	X	X
0	1	0	1			1

$$K_1 = X'$$

J₂:

Q ₁	Q ₂	X	00	01	11	10
0	0	0	1	X	X	
0	1	0	1	X	X	

$$J_2 = X$$

K₂:

Q ₁	Q ₂	X	00	01	11	10
0	0	0	X	X	1	1
0	1	0	X	X	0	1

$$K_2 = Q_1' + X'$$


$$= \overline{Q_1 X}$$

Z:


Q ₁	Q ₂	X	00	01	11	10
0	0	0	1	1	1	1
0	1	0	1	1	1	1

$$Z = Q_1' + X$$

Circuit on JK-FFs:

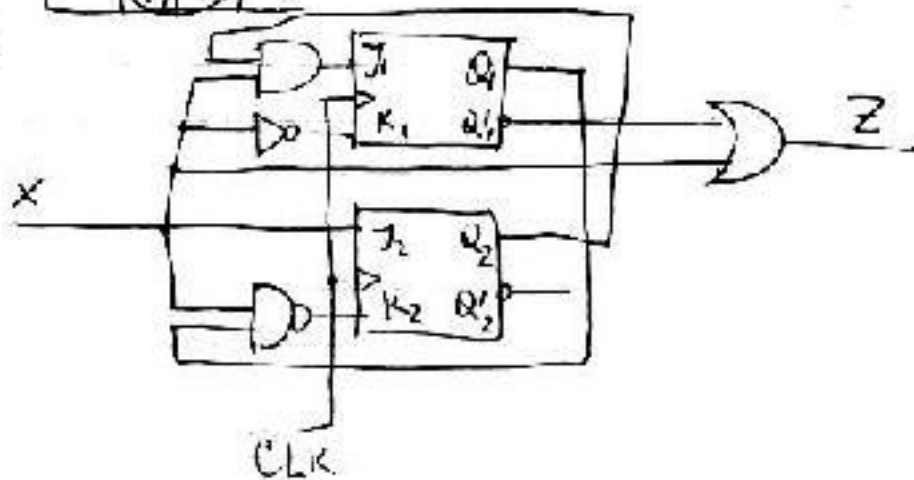

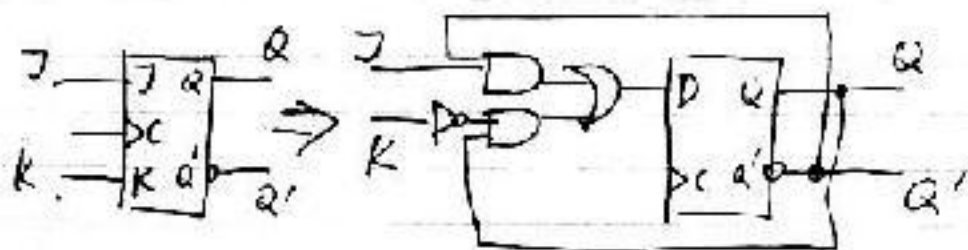5 (6) JK FFs can be replaced with D FFs connected like this:




This is because $Q^+ = JQ' + K'Q$, thus

$$Q^+ = D = JQ' + K'Q$$

for each FF.

OR JK FF can be replaced with T FF:

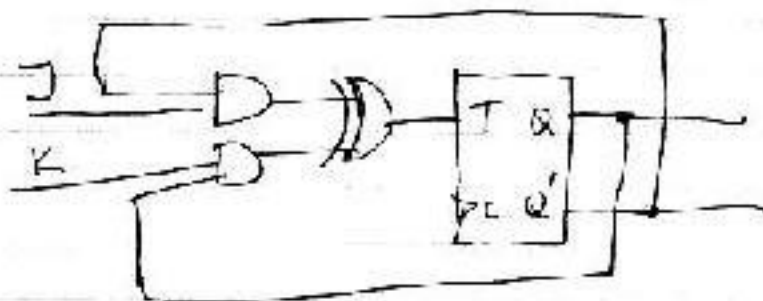

$$Q^+ = JQ' + K'Q$$

$$\text{and } Q^+ = T \oplus Q \Rightarrow$$

$$\Rightarrow T = (JQ' + K'Q) \oplus Q =$$

$$= JQ' \oplus K'Q \oplus Q =$$

$$= JQ' \oplus (K' \oplus 1)Q =$$

$$= JQ' \oplus KQ$$

The rest of the circuit must not be changed for each FF.

6. BCD down counter.

The state table :

Present state				Next state				FF inputs				
A	B	C	D	A	B	C	D	T_A	T_B	T_C	T_D	Y
0	0	0	0	1	0	0	1	1	0	0	1	1
0	0	0	1	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	1	0	0	1	1	0
0	0	1	1	0	0	1	0	0	0	0	1	0
0	1	0	0	0	0	1	1	0	1	1	1	0
0	1	0	1	0	1	0	0	0	0	0	1	0
0	1	1	0	0	1	0	1	0	0	1	1	0
0	1	1	1	0	1	1	0	0	0	0	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	1	1	0	0	0	0	0	0	1	0
				x	x	x	x	x	x	x	x	x

TFP excitation table :

	$Q(t)$	$Q(t+1)$	T
0	0	0	0
0	0	1	1
1	0	0	1
1	0	1	0

T_A - map :

		00	01	11	10
00	01	1			
11	10	x	x	x	x
					x

$T_A = 3c'd'$

T_B - map :

		00	01	11	10
00	01		1		
11	10	x	x	x	x
					x

$T_B = AD' + BC'b'$

T_C - map :

		00	01	11	10
00	01		1		1
11	10	x	x	x	x
					x

$T_C = AD' + BD' + cD'$

Y - map :

		00	01	11	10
00	01	1			
11	10	x	x	x	x
					x

$Y = A'BC'D'$

And by inspection,

$T_D = 1.$

7(e) State table:


Current state	Input	Next state	Output
A	0	B	1
A	1	E	1
B	0	D	1
B	1	C	0
C	0	E	0
C	1	A	0
D	0	C	0
D	1	E	0
E	0	B	1
E	1	E	1

equivalent states
A = E

Throw away E (or A); redraw state table

Current state	Input	Next state	Output
A	0	B	1
A	1	A	1
B	0	D	1
B	1	C	0
C	0	A	0
C	1	A	0
D	0	C	0
D	1	E	1

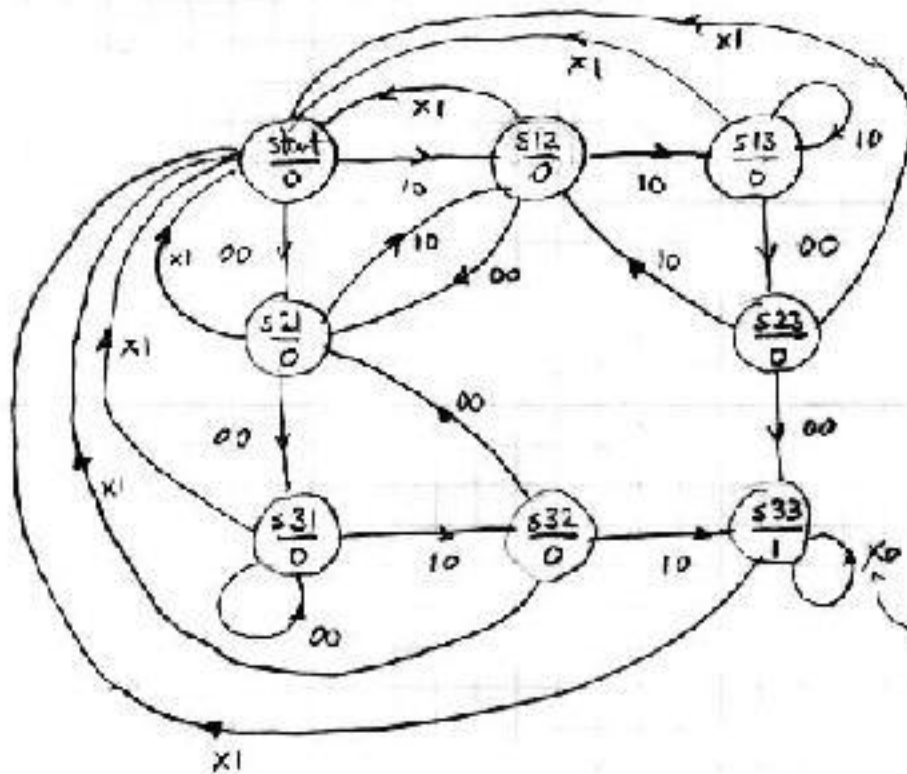7(b) Problem statement is sufficiently vague that there are many possible interpretations. Here is one possibility:



Legend: $00 \rightarrow$
 $x \rightarrow$
 $x0 \rightarrow$