

Name: _____

Lecture Section: _____

L01 – Norm Bartley, lectures in ENE 241

L02 – Steve Norman, lectures in ST 145

SCHULICH
School of Engineering



DEPARTMENT OF ELECTRICAL
AND COMPUTER ENGINEERING

ENEL 353 - Digital Circuits

Midterm Examination

Wednesday, October 29, 2014

Instructions:


- Time allowed is 90 minutes.
 - In order to minimize distraction to your fellow students, you may not leave during the last 10 minutes of the examination.
 - The examination is closed-book.
 - Non-programmable calculators are permitted.
 - The maximum number of marks is 50, as indicated; the midterm examination counts 20% toward the final grade.
 - Please use a pen or heavy pencil to ensure legibility.
 - Please answer questions in the spaces provided; if space is insufficient, please use the back of the pages.
 - Please show your work; where appropriate, marks will be awarded for proper and well-reasoned explanations.
-

UCID: _____

1. [12 marks total.]

- (a) [3 marks.] Use repeated division to convert 571_{10} to hexadecimal.
- (b) [1 mark.] What is the value of 417_8 as a decimal number?
- (c) [2 marks.] The eight-bit two's complement representation of -121_{10} is 10000111. Use this information to find the eight-bit two's complement representation of $+121_{10}$.
- (d) [2 marks.] Represent the number $+67_{10}$ in eight-bit *sign-and-magnitude* format.
- (e) [2 marks.] What is the five-bit sum generated by a five-bit adder when the inputs are 01011 and 01001, and what is the carry out of the most significant bit?
- (f) [1 mark.] If all the five-bit numbers in part (e) are interpreted as two's complement, was there overflow in the addition? Give a reason for your answer.
- (g) [1 mark.] If all the five-bit numbers in part (e) are interpreted as unsigned, was there overflow in the addition? Give a reason for your answer.

 
2. [5 marks.] Consider the circuit below.




Let $G = \bar{A}BC$. By *algebraic manipulation*, prove or disprove that $F = G$. (Do not use a truth table or a K-map.)

3. [8 marks total.]

 - (a) [3 marks.] Use “bubble-pushing” and/or algebra to find an SOP expression for the function implemented by the circuit below. Use the space beside and below the circuit to show your work.



 
- (b) [3 marks.] The circuit below is built from two tristate buffers and a NOR gate.



Is it possible to choose 0 or 1 values for the inputs that result in contention (also known as “fighting” at the output node Y)? Give a precise explanation for your answer.

Is it possible to choose 0 or 1 values for the inputs that result in Y being in the Z (floating, high-impedance)? Give a precise explanation for your answer.

 - (c) [2 marks.] The circuit below uses two tristate buffers, one with active-high enable, and one with active-low enable. What simple logic function of A and B does the circuit implement? Give a reason for your answer.



4. [11 marks total.]

- (a) [8 marks.] Consider the function Y given in the truth table below. Use the blank K-maps to derive *all* minimum SOP and POS expressions for Y . Indicate all essential prime implicants for Y or \bar{Y} in your maps. You may add more maps if you need them.

| A | B | C | D | Y |
|-----|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | X |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | X |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | X |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | X |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | X |
| 1 | 1 | 1 | 1 | 0 |

| $CD \backslash AB$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |

| $CD \backslash AB$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |

| $CD \backslash AB$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |


- (b) [3 marks.] Sketch a two-level NAND-NAND circuit for a minimal SOP expression from part (a). If there is not a unique minimal SOP expression, state which one you are implementing. Inputs are available in both true and complementary forms. Any number of inputs are allowed on each NAND gate.

5. [9 marks total.]


- (a) [3 marks.] Draw a schematic to show how the function given in the truth table can be implemented with a 4:1 multiplexer, *one* inverter, and no other components. Show any intermediate work you had to do to design the circuit.

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

 
- (b) [3 marks.] A table describing a 3:1 multiplexer is given below to the left. Add wiring to show how this function can be implemented using two inverters, three 3-input AND gates, and one 3-input OR gate.



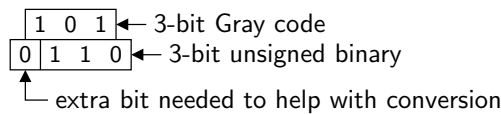- (c) [3 marks.] The diagram below is intended to serve as a reminder of how to convert between unsigned binary code and Gray code.



 Add wiring to the following schematic so that the output $Y_3Y_2Y_1Y_0$ is the four-bit Gray code corresponding to the input unsigned binary number $A_3A_2A_1A_0$. You may wire things however you like, but you may not introduce any additional logic gates.



6. [5 marks.] Use the following 5-variable K-map for $F(A, B, C, D, E)$, and find any minimal SOP expression for F .

| | | | | | |
|-----------|--|-----------|----|----|----|
| | | <i>BC</i> | | | |
| <i>DE</i> | | 00 | 01 | 11 | 10 |
| 00 | | 1 | 1 | 1 | 1 |
| 01 | | | 1 | 1 | |
| 11 | | | | 1 | |
| 10 | | 1 | | | 1 |

$A = 0$

| | | | | | |
|-----------|--|-----------|----|----|----|
| | | <i>BC</i> | | | |
| <i>DE</i> | | 00 | 01 | 11 | 10 |
| 00 | | | | | |
| 01 | | | 1 | 1 | |
| 11 | | | | 1 | |
| 10 | | 1 | | 1 | |

$A = 1$

Name (printed):

U of Calgary ID number:

Section (L01 is in ENE 241 with Norm Bartley,
L02 is in ST 145 with Steve Norman):

| Problem | Mark |
|---------|------|
| 1 | / 12 |
| 2 | / 5 |
| 3 | / 8 |
| 4 | / 11 |
| 5 | / 9 |
| 6 | / 5 |
| TOTAL | / 50 |