

Name: SOLUTION, ID: _____

1. [8 marks (2 marks each).] Consider the following 8-bit binary codes stored in a register in your computer's CPU:

- (i) 0001 0101
(ii) 1001 0111

- (a) Assuming these codes are in sign-magnitude format, give their values in decimal.

$$0001\ 0101 = \pm 001\ 0101 = + (2^4 + 2^2 + 2^0) = +21$$

$$1001\ 0111 = \mp 001\ 0111 = - (2^4 + 2^2 + 2^1 + 2^0) = -23$$

- (b) Assuming these are unsigned binary codes, convert them to unsigned octal numbers.

$$\underbrace{0001\ 0101}_2 = 25_8$$

$$\underbrace{1001\ 0111}_2 = 227_8$$

- (c) Assuming these are unsigned binary codes, convert them to unsigned decimal numbers.

$$0001\ 0101 = 2^4 + 2^2 + 2^0 = 21$$

$$1001\ 0111 = 2^7 + 2^4 + 2^2 + 2^1 + 2^0 = 128 + 16 + 4 + 2 + 1 = 151$$

- (d) For your answers to part (c), find the four-digit 10's-complement of each.

$$0001\ 0101 \Rightarrow 10^4 - 21 = 9979_{10's}$$

$$1001\ 0111 \Rightarrow 10^4 - 151 = 9849_{10's}$$

2. [4 marks.] Assume that the binary codes given in Problem 1 are now in 8-bit 2's-complement binary format. Perform 8-bit binary addition of these numbers, and express your answer in decimal. Explain whether or not overflow occurs.

$$\begin{array}{r}
 + \quad 0001 \ 0101 = 21 \\
 \quad 1001 \ 0111 = -105 \\
 \hline
 1010 \ 1100 = -84
 \end{array}$$

$$\begin{array}{r}
 1001 \ 0111_{2's} \\
 + \quad 0110 \ 1000 \\
 \hline
 0110 \ 1001 = 105 \\
 \downarrow \\
 1001 \ 0111 \Rightarrow -105
 \end{array}$$

$$\begin{array}{r}
 1010 \ 1100_{2's} \\
 + \quad 0101 \ 0011 \\
 \hline
 0101 \ 0100 = 84 \\
 \downarrow \\
 1010 \ 1100 = -84
 \end{array}$$

3. [4 marks.] Assume that the binary codes given in Problem 1 are now in BCD format. Perform BCD addition of these numbers.

$$\begin{array}{r}
 + \quad 0001 \ 0101 = 15_{BCD} \\
 \quad 1001 \ 0111 = 97_{BCD} \\
 \hline
 1010 \ 1100 \Rightarrow \text{NOT A BCD} \Rightarrow \text{must add } +6 \text{ for correction} \\
 + \text{ correct } \quad 0110 \ 0110 \\
 \hline
 10001 \ 0010 = 112_{BCD}
 \end{array}$$

4. [18 marks total.] A Boolean function F of four variables x_1, x_2, x_3 and x_4 , is given by the Karnaugh map:

	x_3x_4			
$x_1x_2 \setminus$	00	01	11	10
00	1	1	0	1
01	1	0	0	0
11	0	0	0	0
10	1	0	1	1

- (a) [2 marks.] Find a minimal SOP algebraic expression using this map.

	x_3x_4			
$x_1x_2 \setminus$	00	01	11	10
00	1	1	0	1
01	1	0	0	0
11	0	0	0	0
10	1	0	1	1

$$\text{SOP} = x_2' x_4' + x_1' x_3' x_4' + x_1' x_2' x_3' + x_1 x_2' x_3$$

- (b) [2 marks.] Find a minimal POS expression using this map.

	x_3x_4			
$x_1x_2 \setminus$	00	01	11	10
00	1	1	0	1
01	1	0	0	0
11	0	0	0	0
10	1	0	1	1


$$\text{POS} = (x_2' + x_4')(x_2' + x_3')$$

$$= (x_1' + x_2')(x_1 + x_3' + x_4')(x_1' + x_3 + x_4')$$

- (c) [2 marks.] Draw the logic diagram of an OR-AND-INVERT circuit implementation. OR and AND gates with three or more inputs are allowed. Inverters are available. (Note: for this and all remaining parts of this problem, you may assume that the variables and their complements are available to your circuit.)


SOLUTION 1:

$$x_2' x_4' + x_1' x_3' x_4' + x_1' x_2' x_3' + x_1 x_2' x_3 = [(x_2 + x_4)(x_1 + x_3 + x_4) \cdot (x_1 + x_2 + x_3)(x_1' + x_2 + x_3')]'$$

 


SOLUTION 2:
 
$$(x_2' + x_4')(x_2' + x_3')(x_1' + x_2') \cdot (x_1 + x_3' + x_4')(x_1' + x_3 + x_4')$$



- (d) [4 marks.] Using logic-symbol transformations and circuit manipulation, implement whatever circuit you give in part (c) using 2-input NAND gates only. Inverters are *not* available.

one of possible solutions:

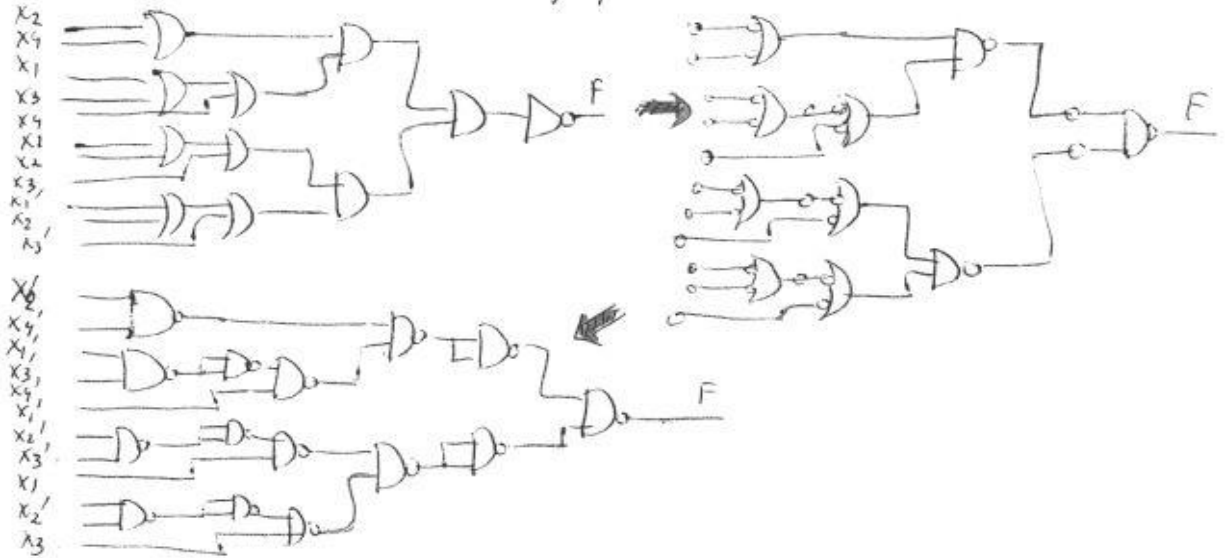


- (e) [5 marks.] Implement the logic function F using a 4-to-1 multiplexer. You may use any AND, OR, and NOT gates as necessary. (Hint: you may use either truth table decomposition or Shannon's expansion theorem.)


X_1	X_2	X_3	X_4	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

We've chosen X_1, X_2 as select inputs
 
$$\begin{aligned}
 F &= X_2' X_4' + X_1' X_3' X_4' + X_1' X_2' X_3' \\
 &+ X_1 X_2' X_3 = X_1' X_2' f_{X_1=0, X_2=0} + X_1 X_2' f_{X_1=1, X_2=0} \\
 &+ X_1 X_2' f_{X_1=1, X_2=1} = X_1' X_2' (X_4' + X_3' X_4' + X_3') + X_1 X_2' (X_3' X_4') + \\
 &+ X_1 X_2' (X_4' + X_3) + X_1 X_2 (0)
 \end{aligned}$$



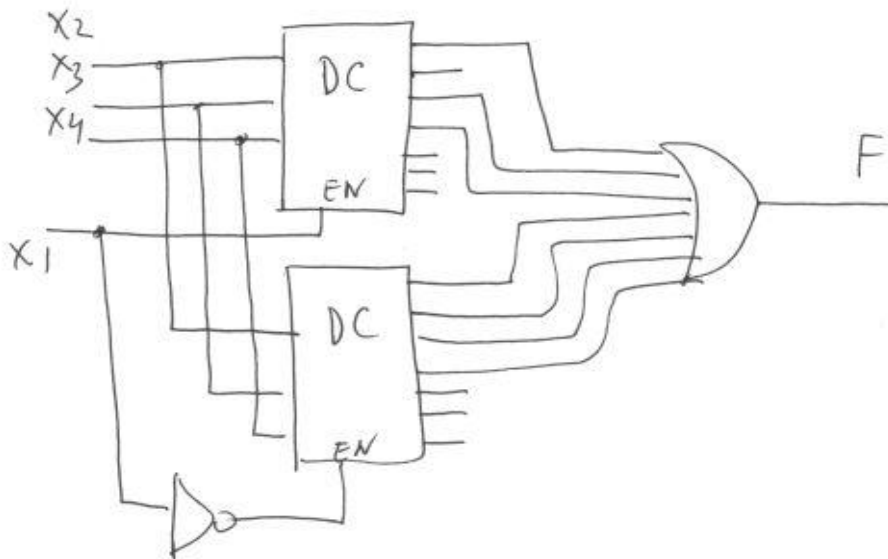- (f) [3 marks.] Implement the logic function F using 1-to-8 decoders. You may use any AND, OR, and NOT gates as necessary.



5. [6 marks.] Design a circuit with four inputs x_1, x_2, x_3, x_4 and a single output F . The output should be $F = 1$ in either of the following cases:

- $x_1 = 0$ and we have an *odd* function of x_2, x_3, x_4 ;
- $x_2 = 1$ and we have an *even* function of x_1, x_3, x_4 .

The only logic gates available are AND and XOR gates. They may have three or more inputs. Inverters are *not* available.

x_1	x_2	x_3	x_4	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	x
1	0	0	1	x
1	0	1	0	x
1	0	1	1	x
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$x_2 \oplus x_3 \oplus x_4$
 $(x_1 \oplus x_3 \oplus x_4)'$

x_1, x_2	x_3, x_4	00	01	11	10
00	0	1	0	1	
01	1	0	1	0	
11	0	1	0	1	
10	x	x	x	x	

↓

0	1	0	1
1	0	1	0
0	1	0	1
1	0	1	0

$F = x_1 \oplus x_2 \oplus x_3 \oplus x_4$

