

Question 1

(a) (i) $-64_{10} + 43_{10}$.

In 7 bits, $64_{10} = 1000000_2$. Applying 2's-complement

$$1000000 \rightarrow \begin{array}{r} 011111 \\ + \underline{\quad 1} \\ 1000000 \end{array}$$

[Note this is the same as $+64$, thanks to the asymmetry of 2's-complement representation]

And $+43_{10} = 32 + 8 + 2 + 1 = 0101011_2$

$$\text{Add: } \begin{array}{r} 1000000 \\ + 0101011 \\ \hline 1101011 \end{array} \rightarrow \text{Negative number, so find magnitude}$$

$$1101011 \rightarrow \begin{array}{r} 0010100 \\ + \underline{\quad 1} \\ 0010101 = 21 \end{array}$$

Therefore, answer = -21_{10} . Overflow not possible.

(ii) $29_{10} + 43_{10}$

From above, $43_{10} = 0101011_2$

And $29_{10} = 16 + 8 + 4 + 1 = 0011101_2$

$$\text{Add: } \begin{array}{r} \boxed{01}1111 \\ 0101011 \\ + 0011101 \\ \hline 1001000 \end{array} \quad \text{indicates overflow!}$$

Answer negative, so determine magnitude

$$1001000 \rightarrow \begin{array}{r} 0110111 \\ + \underline{\quad 1} \\ 011000 = 56_{10} \end{array}$$

Therefore, answer = -56_{10} (with overflow)

(b) Can't directly add numbers in sign-magnitude when either or both numbers are negative.

Must convert 110110_2 to 6-bit 2's complement

$$\begin{array}{r} 110110 \\ \hline \uparrow \\ \text{negative} \end{array} \quad 22_{10}$$

Convert +22:

$$\begin{array}{r} 010110 \\ + \quad 1 \\ \hline 101001 \\ + \quad 1 \\ \hline 101010 \end{array}$$

$$\begin{array}{r} \text{Add:} \quad 0111 \\ 01010 \\ 001110 \\ \hline 111000 \end{array}$$

Answer is negative,
so find magnitude

$$\begin{array}{r} 111000 \\ \rightarrow \quad 000111 \\ + \quad 1 \\ \hline 001000 \end{array}$$

Convert back to sign-magnitude

$$-001000 \rightarrow 101000_2$$

(c) $89_{10} + 84_{10}$ in BCD:

$$89_{10} = 1000 \ 1001$$

$$84_{10} = 1000 \ 0100$$


$$\begin{array}{r} 10000 \ 1101 \\ \hline \quad \quad 0110 \end{array} \rightarrow \text{not valid BCD}$$

$$\text{Also invalid BCD} \rightarrow \begin{array}{r} 10001 \ 0011 \\ \hline \quad \quad 0110 \end{array}$$

$$10111 \ 0011 \Rightarrow 173_{10}$$

Question (2)

(a) For the circuit on the left,

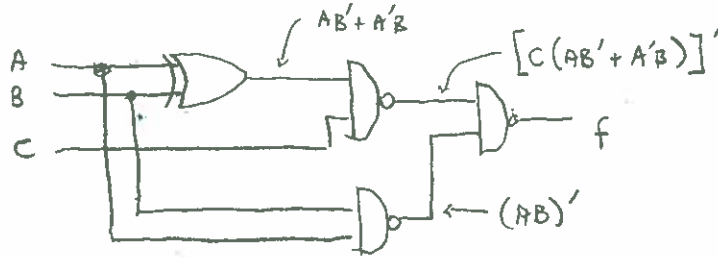

We have $f = [[AB'C + A'BC]' \cdot (AB)']'$

DeMorgan's theorem $f = AB'C + A'BC + AB$ $\leftarrow AB(C+C')$

$$f = AB'C + A'BC + ABC' + ABC$$

$$f = AC + BC + AB$$

For the circuit on the right,


$$g = [(AB)' \cdot (AC)' \cdot (BC)']'$$

$$= AB + AC + BC$$

SAME!

Bonus: This is the carry bit for a 1-bit full adder.


(b) With $g = AB + AC + BC$

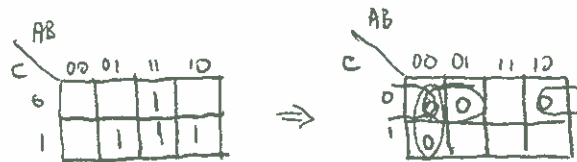

$$g' = A'B' + A'C' + B'C'$$

$$g = [A'B' + A'C' + B'C']'$$

$$= [(A+B)' + (A+C)' + (B+C)']'$$

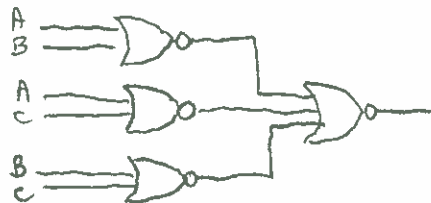

Question 3

(a)

		ab			
	cd	00	01	11	10
00		0	1	1	X
01		X	X	0	X
11		X	0	0	1
10		0	0	1	1

$$f' = bc' + ac + bd$$

$$\text{so } f = (b+c)(a+c')(b'+d')$$

		ab			
	cd	00	01	11	10
00		0			X
01		X	X	0	X
11		X	0	0	
10		0	0		

$$f' = a'b' + ac' + bd$$

$$\text{so } f = (a+b)(a+c')(b'+d')$$

(b)

		ab			
	cd	00	01	11	10
00			1	1	X
01		X	X		X
11		X			1
10				1	1

$$f = ab' + ad' + bc'd'$$

		ab			
	cd	00	01	11	10
00			1	1	X
01		X	X		X
11		X			1
10				1	1

$$f = b'd + ad' + bc'd'$$


		ab			
	cd	00	01	11	10
00			1	1	X
01		X	X		X
11		X			1
10				1	1

$$f = ab' + ad' + a'bc'$$


		ab			
	cd	00	01	11	10
00			1	1	X
01		X	X		X
11		X			1
10				1	1

$$f = b'd + ad' + a'bc'$$


(c) Let's choose $f = ab' + ad' + bc'd'$

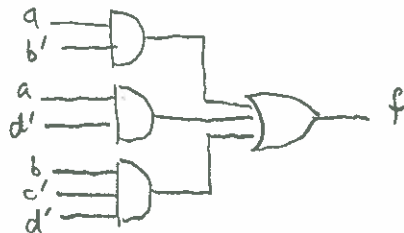

Using 2-input NOR gates

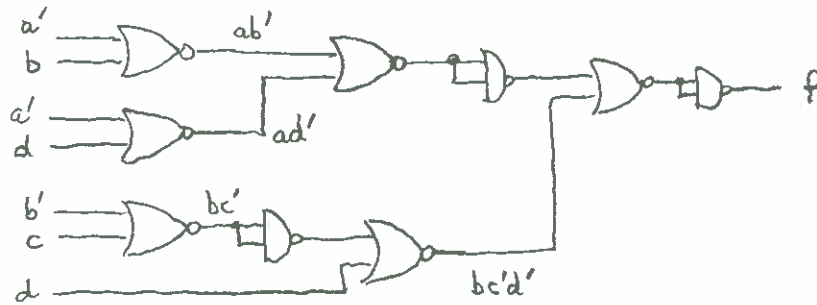


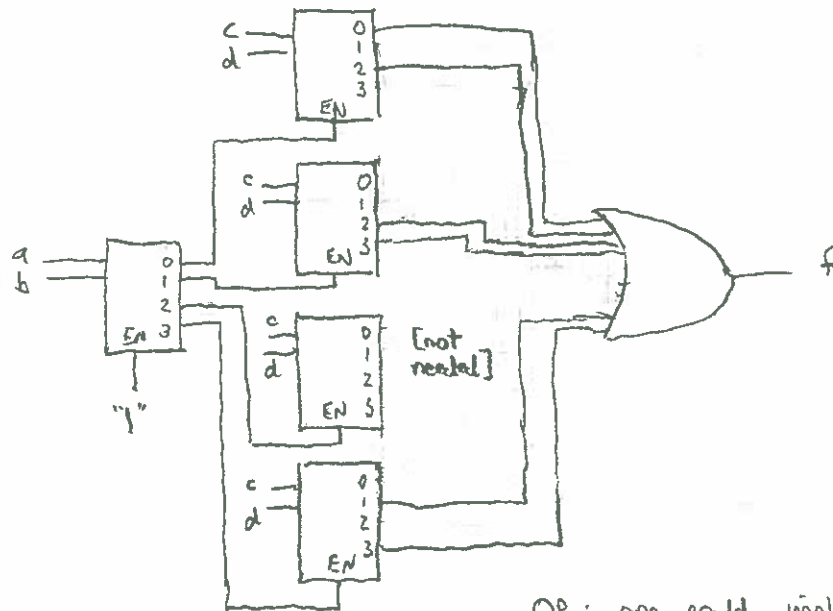(d) Decoder implementation; need $f' = \sum m(0, 2, 6, 7, 13, 15)$



OR: one could implement f and use a NOR gate.

(e) Using the don't-cares,

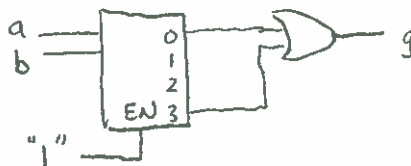

Question 4

		ab			
cd		00	01	11	10
00		1	1	1	1
01					
11				1	
10		1			1

$$F = ad' + \underbrace{bc' + ab'c' + a'b'cd'}_{\text{shared terms}} + \underline{abcd}$$

		ab			
cd		00	01	11	10
00					1
01		1			
11		1		1	
10		1			

$$G = b'd + \underline{a'b'cd'} + \underline{abcd} + \underline{ab'c'}$$

		ab			
cd		00	01	11	10
00		1	1	1	1
01		1	1	1	1
11				1	
10		1			

$$H = c'd + \underline{bc'} + \underline{a'b'cd'} + \underline{abcd}$$

Total number of shared products: 4
 Total number of non-shared products: 3
 Number of OR gates: 3

→ Total number of gates = 10 with 32 inputs