

UNIVERSITY OF CALGARY

FACULTY OF ENGINEERING

ENGG 325 - Electric Circuits and Systems

Final Examination

Tuesday, December 16, 2003

Time: 12:00 - 3:00 PM

L01 (Vijay Devabhaktuni): ENA 201

L02 (Norm Bartley): ENE 241, ENE 243

Instructions:

- Time allowed is 3 hours.
 - The examination is closed-book. One 8.5x11-inch formula sheet may be used in the examination.
 - Calculators are permitted.
 - The maximum number of marks is 100, as indicated. The final examination counts toward 50% of the final grade. Please attempt all questions.
 - Please use a pen or heavy pencil to ensure legibility.
 - If you use more than one examination booklet, please make sure that your name and ID number are on each.
 - Where appropriate, marks will be awarded for proper and well-reasoned explanations.
-

1. Using the method of your choice, determine the power in the current source.

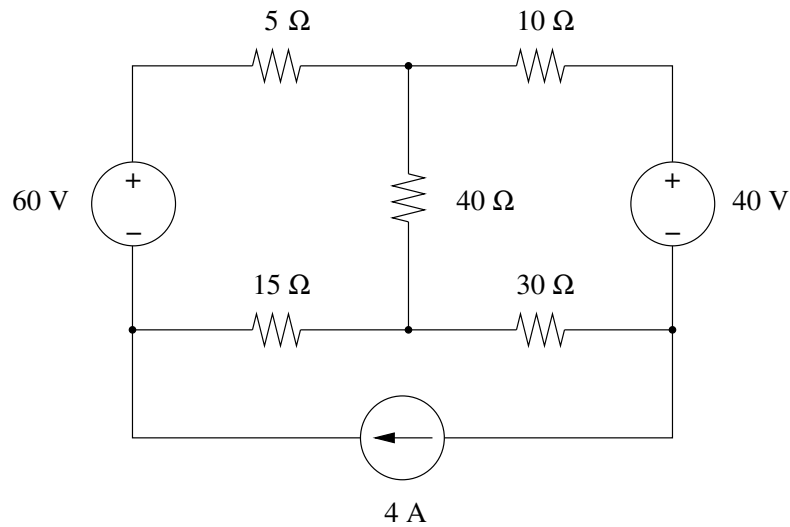


Fig. P1. Find the power in the current source

[14 marks.]

2. Using the principle of superposition, analyze the circuit given in Fig. P2.
- Determine the phasor current I_0 . [15 marks.]
 - Assuming that the frequency of operation is 100 Hz, determine the inductor and capacitor values. [3 marks.]

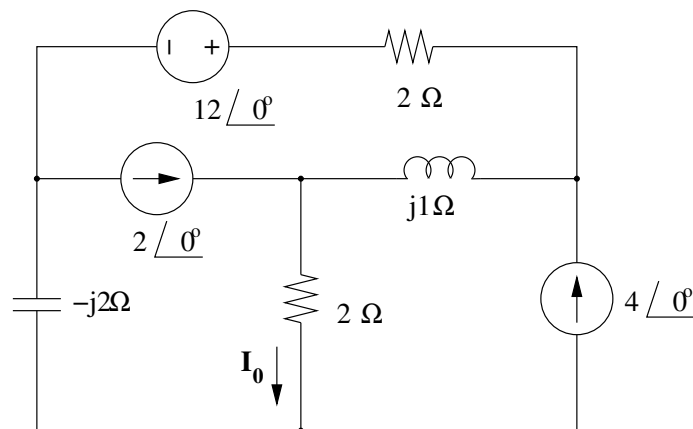


Fig. P2. Analyze using superposition

[18 marks total.]

3. For the resistor-inductor circuit shown in Fig. P3, assume that the switch has been open for a long time, allowing the circuit to reach DC steady-state. The switch is then closed at time $t = 0$.

- (a) Determine and sketch $i_L(t)$ through the inductor as shown for $t \geq 0$. [12 marks.]
- (b) Determine $v(t)$ for $t \geq 0$. [4 marks.]
- (c) Determine the energy in the inductor as $t \rightarrow \infty$. [2 marks.]

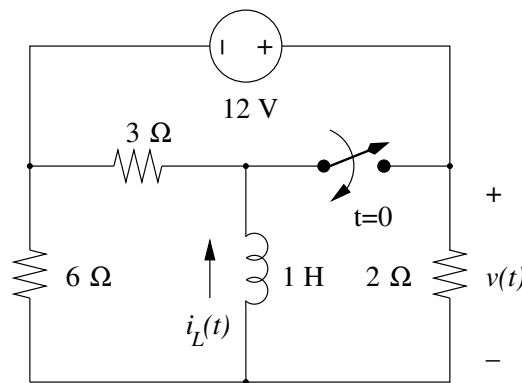


Fig. P3. A first-order RL circuit

[18 marks total.]

4. A shunt-connected 5-hp DC motor is rated for operation at $V_T = 200V$, $I_L = 23.3A$, and $n_m = 1200$ rpm. Furthermore, $I_F = 1.5A$ and $R_A = 0.4\Omega$. Assume that the motor is operating under these rated conditions.

- (a) Draw the equivalent circuit.
- (b) Determine the electrical input power.
- (c) Determine the power lost in the field circuit.
- (d) Determine the power lost in the armature resistance.
- (e) Determine the rotational (mechanical) losses.
- (f) Determine the output torque delivered to the load.
- (g) Determine the efficiency.

[18 marks.]

5. Consider the diode circuit in Fig. P5, and assume the following for the three diodes:

- D_1 is *ideal* and is in the “ON” state.
- D_2 is a *piecewise-linear model* in which $V_{D2} = 0.75V$ and $R_{D2} = 0\Omega$.
- D_3 is a *piecewise-linear model* in which $V_{D3} = 0.75V$ and $R_{D3} = 250\Omega$.

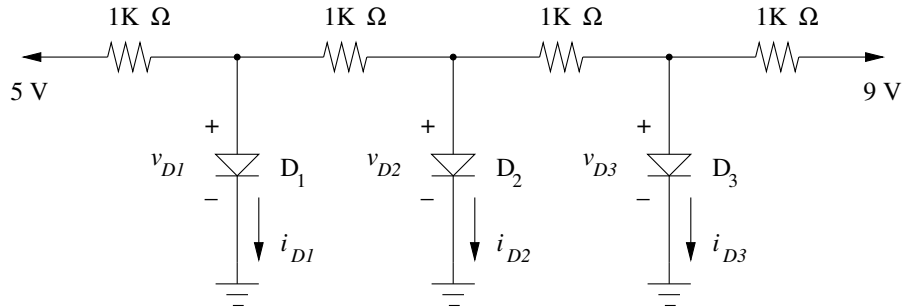


Fig. P5. Determine diode voltages and currents

Determine all of the diode voltages v_{D1} , v_{D2} , v_{D3} , and currents i_{D1} , i_{D2} , i_{D3} .

[16 marks.]

6. The op amps in Fig. P6 are ideal. Determine v_o .

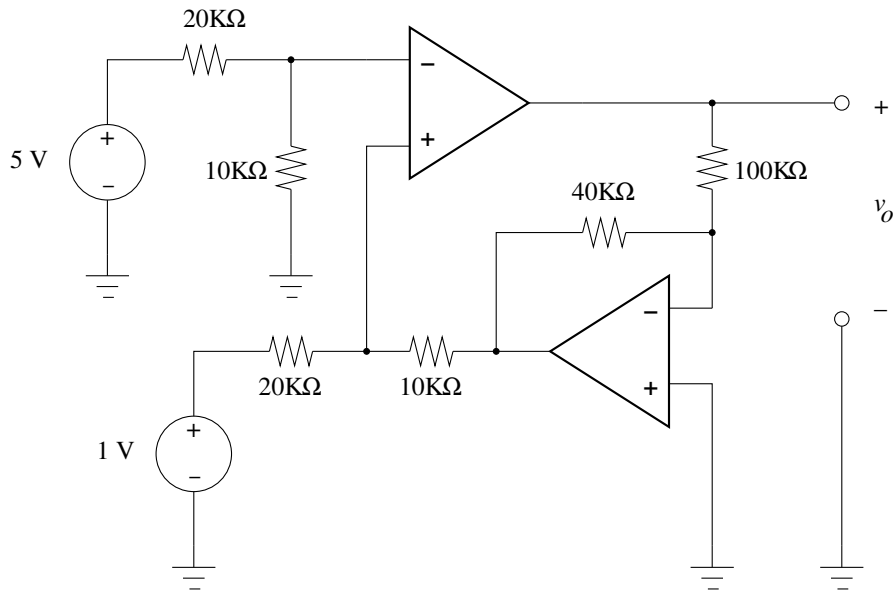


Fig. P6. Determine v_o

[16 marks.]