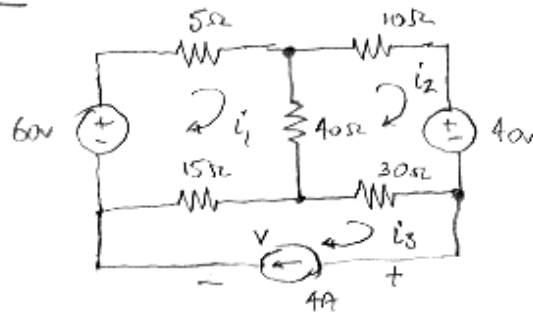


Question 1

Mech-current method looks easiest.

$$\text{Loop 1: } -60 + 5i_1 + 40(i_1 - i_2) + 15(i_1 - i_3) = 0$$

But $i_3 = 4A$, so this becomes

$$\begin{aligned} -60 + 5i_1 + 40i_1 - 40i_2 + 15i_1 - 60 &= 0 \\ 60i_1 - 40i_2 &= 120 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{Loop 2: } 40 + 30(i_2 - i_3) + 40(i_2 - i_1) + 10i_2 &= 0 \\ 40 + 30i_2 - 120 + 40i_2 - 40i_1 + 10i_2 &= 0 \\ -40i_1 + 80i_2 &= 80 \end{aligned} \quad (2)$$

Add 2x equation (1) to (2)

$$\begin{aligned} 120i_1 - 80i_2 &= 240 \\ -40i_1 + 80i_2 &= 80 \end{aligned}$$

$$80i_1 = 320 \quad \therefore i_1 = 4A$$


$$\begin{aligned} \text{And from (2), } -40(4) + 80i_2 &= 80 \\ 80i_2 &= 240 \quad \therefore i_2 = 3A \end{aligned}$$

Now do KVL around loop 3 to solve for voltage across current source:

$$\begin{aligned} V + 15(i_3 - i_1) + 30(i_3 - i_2) &= 0 \\ V + 15(4 - 4) + 30(4 - 3) &= 0 \\ \therefore V &= -30 \end{aligned}$$

With voltage and current directions as shown,

$$\begin{aligned} p = Vi_3 &= -30 \times 4 \\ &= -120 \text{ W (delivering)} \end{aligned}$$

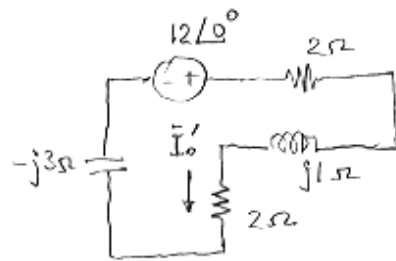
Question 2(a) Let's consider the voltage source acting alone

All elements in series, so

$$I_o' = \frac{12\angle 0^\circ}{2 + j1 + 2 - j3}$$

$$= \frac{12}{4 - j2} = \frac{6}{2 - j}$$


$$\text{Therefore, } \bar{I}_o' = \frac{6}{2 - j} \times \frac{2 + j}{2 + j} = \frac{12 + j6}{5}$$

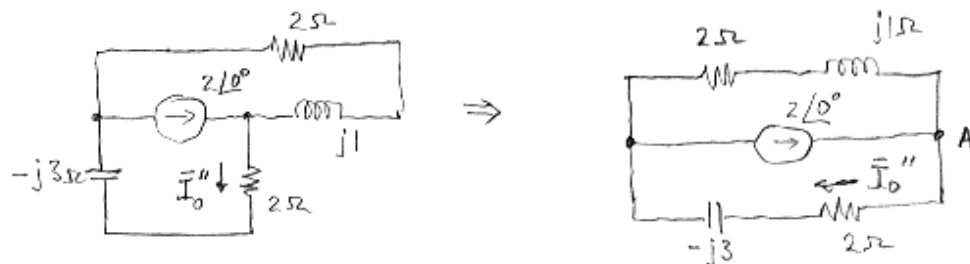Next consider the 2∠0° source acting alone

We have a current divider at node A

$$\bar{I}_o'' = \frac{2 + j1}{2 + j1 + 2 - j3} \times 2 = \frac{4 + j2}{4 - j2} = \frac{2 + j}{2 - j} \times \frac{2 + j}{2 + j}$$

$$= \frac{3 + j4}{5}$$

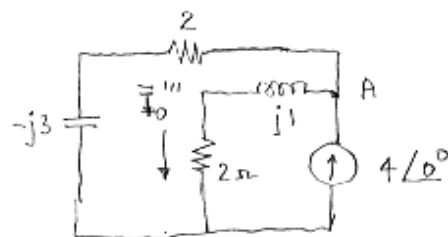Finally, consider the 4∠0° current source acting alone

Once again, we have a current divider at node A

$$I_o''' = \frac{2 - j3}{2 + j1 + 2 - j3} \times 4$$

$$= \frac{8 - j12}{4 - j2}$$

$$\bar{I}_0''' = \frac{4-j6}{2-j} \times \frac{2+j}{2-j} = \frac{14-j8}{5}$$

$$\begin{aligned} \text{Finally, } \bar{I}_0 &= \bar{I}_0' + \bar{I}_0'' + \bar{I}_0''' \\ &= \frac{12+j6 + 3+j4 + 14-j8}{5} \end{aligned}$$

$$\bar{I}_0 = \frac{29-j2}{5} = 5.814 \angle -3.95^\circ$$

(b) We have $Z_L = j\omega L$ and $Z_C = \frac{1}{j\omega C}$, where $\omega = 2\pi f$ and $f = 100 \text{ Hz}$

$$Z_L = j1\Omega = j \times 2\pi \times 100 \times L$$


$$\therefore L = \frac{1}{200\pi} = 1.59 \text{ mH}$$

$$Z_C = -j3\Omega = \frac{-j}{2\pi \times 100 \times C}$$

$$\therefore C = \frac{1}{600\pi} = 531 \mu\text{F}$$

Question 3

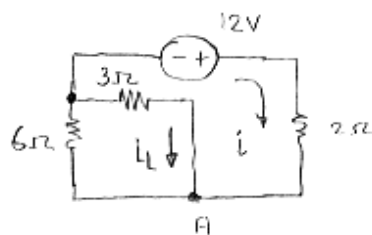(a) At $t=0^-$, circuit is in DC steady-state. First job is to find $i_L(0^-)$



Total current i :

$$\begin{aligned} R_{\text{tot}} &= 6//3 + 2 \\ &= 2 + 2 \\ &= 4\Omega \end{aligned}$$



$$\text{so } i = \frac{12}{4} = 3 \text{ A}$$

Current divides at node A:

$$i_L = \frac{-6}{6+3} \times i = -2 \text{ A}$$

Thus, $I_0 = -2 \text{ A}$, and $i_L(0^-) = i_L(0) = i_L(0^+) = -2 \text{ A}$

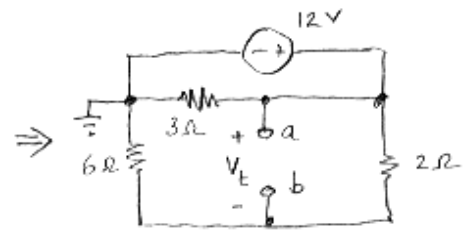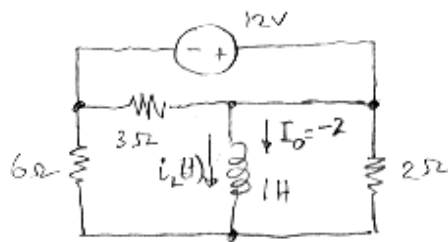Close switch at $t=0$ and the circuit becomes



Remove inductor and determine the Thevenin equivalent of nodes a and b.

First find V_t . At node a, $V_a = 12\text{v}$

$$\text{Node b: } \frac{V_b - 12}{2} + \frac{V_b}{6} = 0$$


$$3V_b - 36 + V_b = 0$$

$$4V_b = 36 \quad \therefore V_b = 9.$$

And we have $V_t = V_{ab} = V_a - V_b = 12 - 9$


$$V_t = 3\text{v}.$$

Next find R_t .

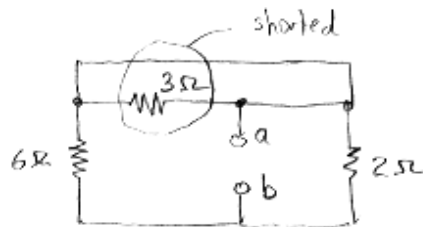

$$R_t = 2 // 6 = 1.5\Omega$$


Finally, for $t \geq 0$,

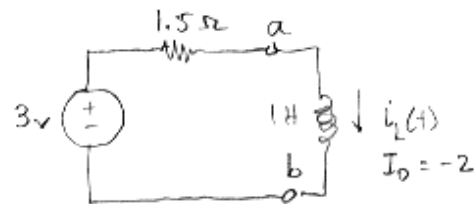

From our earlier analysis $I_L(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t(R/L)}$

giving $I_L(t) = \frac{3}{1.5} + \left(-2 - \frac{3}{1.5} \right) e^{-t(1.5)}$

$$= 2 - 4e^{-1.5t}$$

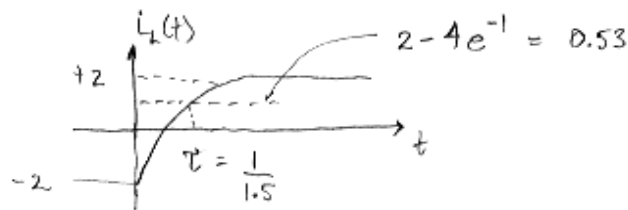

Alternative solution using Hambley's method:


- Find I_0 as before
- Find R_t as before

Assume a solution for $i_L(t)$

$$i_L(t) = K_1 + K_2 e^{-t(R_t/L)}$$

Determine K_1 and K_2 using the DC steady-state solutions at $t = 0^-$ and $t \rightarrow \infty$.

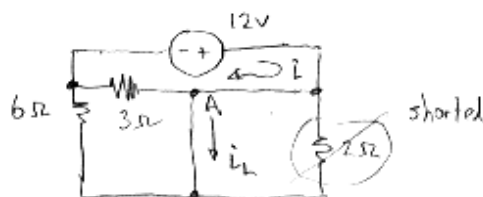The DC steady-state solution at $t \rightarrow \infty$:



$$R_{tot} = 6 \parallel 3 = 2 \Omega$$

$$\text{and } i = \frac{12}{2 \Omega} = 6 \text{ A}$$

We have a current divider at node A: $i_L = \frac{3}{3+6} \times 6 = 2 \text{ A}$.

Now set up simultaneous equations:

$$\text{At } t = 0^-, \quad K + K_2 e^{-1.5t} = K_1 + K_2 = -2$$

$$\text{At } t \rightarrow \infty, \quad K + K_2 e^{-1.5t} = K_1 = 2$$

Hence, $K_2 = -4$ and $i_L(t) = 2 - 4e^{-1.5t}$

(b) with the switch closed, $v(t)$ is the voltage across the inductor (in parallel)


$$\begin{aligned} \text{Thus, } v(t) &= L \frac{di_L(t)}{dt} \\ &= 1 \times \frac{d}{dt} [2 - 4e^{-1.5t}] = 6e^{-1.5t} \end{aligned}$$

(c) Energy $w = \frac{1}{2} L i^2(t)$. As $t \rightarrow \infty$,

$$w = \frac{1}{2} \times 1 \times 2^2 = 2 \text{ J}$$

Question 4

(a) Equivalent circuit

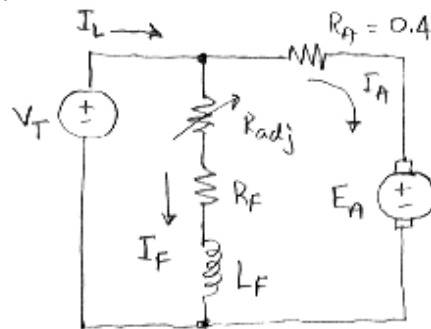

(b) Electrical input power $P_{in} = V_T I_L$
 $= 200 \times 23.3$
 $= 4660 \text{ W}$

(c) Power lost in field circuit $P_F = I_F V_T$
 $= 1.5 \times 200$
 $= 300 \text{ W}$

(d) Power lost in armature circuit $P_A = I_A^2 R_A$

where $I_A = I_L - I_F = 23.3 - 1.5 = 21.8 \text{ A}$

so $P_A = (21.8)^2 \times 0.4 = 191 \text{ W}$

(e) Rotational losses:

Motor is operating at rated speed and power. Power output (delivered to the load) is

$$P_{out} = 5 \text{ HP} \times 746$$

$$= 3730 \text{ W}$$

Rotational losses are then $P_{rot} = P_{in} - P_F - P_A - P_{out}$
 $= 440 \text{ W}$


(f) Output torque delivered to the load

$$T_{rot} = \frac{P_{out}}{\omega_m} = \frac{3730}{2\pi \times 1200} = 0.495 \text{ N-m}$$

(g) Efficiency: $\eta = \frac{P_{out}}{P_{in}} = \frac{3730}{4660} \times 100\% = 80\%$

Question 5

Using the diode models as given,

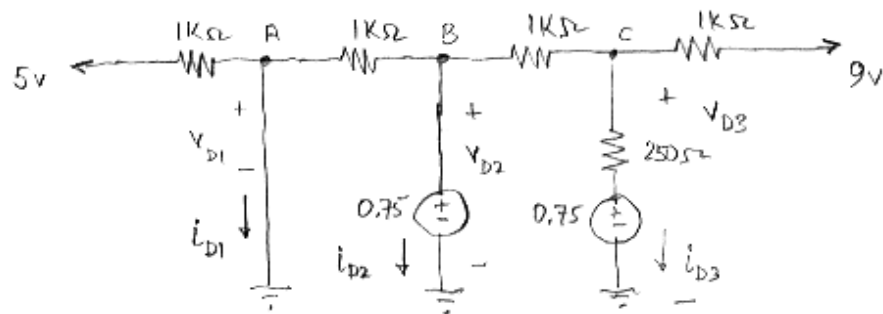

Clearly, $V_A = 0$ and $V_B = 0.75$ in this circuit. At node A, we may write

$$\frac{V_A - 5}{1000} + \frac{V_A - 0.75}{1000} + i_{D1} = 0$$

or $-5 - 0.75 + 1000 i_{D1} = 0$

$$\therefore i_{D1} = \frac{5.75}{1000} = 5.75 \text{ mA}$$

and $V_{D1} = 0$.

We know V_B , so let us now find V_C .

$$\frac{V_C - 9}{1000} + \frac{V_C - 0.75}{250} + \frac{V_C - V_B}{1000} = 0$$

$$V_C - 9 + 4V_C - 3 + V_C - 0.75 = 0$$

$$6V_C = 12.75$$

$$\therefore V_C = 2.125 \text{ V} = V_{D3}$$

We have $i_{D3} = \frac{V_C - 0.75}{250} = \frac{1.375}{250} = 5.5 \text{ mA}$

Finally, at node B

$$\frac{V_B - V_A}{1000} + i_{D2} + \frac{V_B - V_C}{1000} = 0$$


$$0.75 + 1000 i_{D2} + (0.75 - 2.125) = 0$$

$$1000 i_{D2} = 0.625$$

$$\therefore i_{D2} = 0.625 \text{ mA}$$

and $V_{D2} = 0.75 \text{ V}$

Question 6

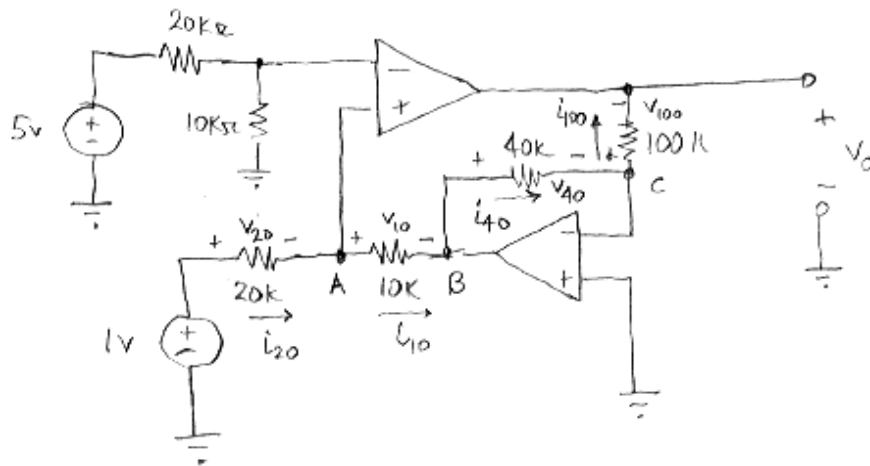

Start by observing the effects of the summing-point constraints. Notice that $V_C = 0$ and that V_A is held at

$$V_A = \frac{10K}{10K + 20K} \times 5 = \frac{5}{3} \text{ V}$$

by virtue of the voltage divider at top left. As labelled, we may determine the currents and voltages as follows:

- $i_{20} = \frac{1 - V_A}{20K} = -\frac{1}{30} \text{ mA}$ and $V_{20} = 1 - V_A = -\frac{2}{3} \text{ V}$
- $i_{10} = i_{20}$ (thanks to infinite op-amp input resistance)

$$\text{Therefore, } V_{10} = i_{10}(10K) = -\frac{1}{30K} \times 10K = -\frac{1}{3} \text{ V}$$

We may sum voltage at node A with V_{10} to obtain the voltage at node B

$$\begin{aligned} V_B &= V_A - V_{10} \\ &= \frac{5}{3} - \left(-\frac{1}{3}\right) = 2 \text{ V} \end{aligned}$$

This, in turn, determines i_{40} : $V_{40} = V_B - V_C = 2 \text{ V}$

$$\text{So } i_{40} = \frac{2}{40K} = 0.05 \text{ mA}$$

Thanks to the infinite input resistance to the op-amp at node C,

$$i_{100} = i_{40} = 0.05 \text{ mA}$$

Finally, we may determine $V_{100} = i_{100} (100k)$
 $= 5v.$

Since node C is held at ground, $V_o = -V_{100}$
 $= -5v$

KVL check: from the bottom of the 1 volt source and
around to V_o and back through ground.

$$-1 + V_{20} + V_{10} + V_{40} + V_{100} + V_o = 0$$

$$-1 - 2/3 - 1/3 + 2 + 5 - 5 = 0$$

checks!