

#1

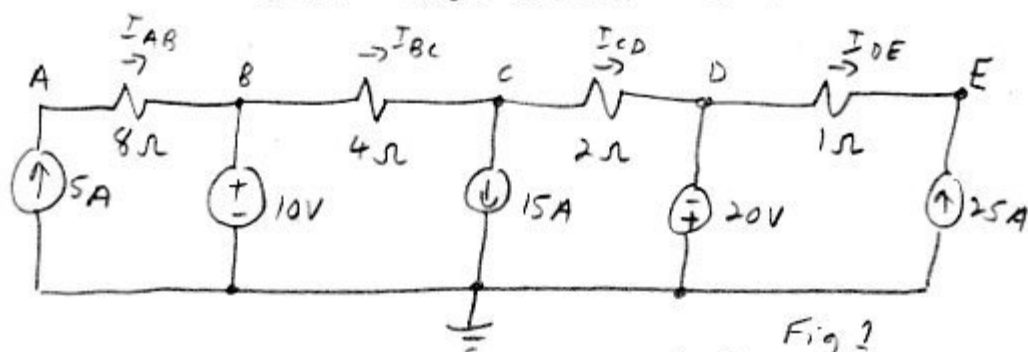


Fig 1

Note: problems may be slightly different from actual exam


- (a) Use the node voltage methodⁿ and Ohm's Law to find V_A, V_B, V_C, V_D, V_E .
- (b) Use the mesh current method to find $I_{AB}, I_{BC}, I_{CD}, I_{DE}$.
- (c) Find the power dissipated in each resistor.
- (d) From part (c) what can you conclude about the sources?

Soln (a) $V_A = V_B + IR = 10V + 5 \times 8 = \underline{50V}$, $V_B = \underline{10V}$ (given)

Node c: $\frac{V_C - 10}{4} + 15 + \frac{V_C - (-20)}{2} = 0 \Rightarrow V_C = \underline{-30V}$

$V_D = \underline{-20V}$ (given), $V_E = V_D + I_{ED}R = -20V + 25 \times 1 = \underline{5V}$

(b)

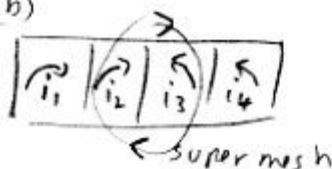

$i_1 = \underline{5A}$ (given) (1)

super: $-10 + 4i_2 - 2i_3 - 20 = 0$

$4i_2 - 2i_3 = 30$ (2)

inside super constraint: $i_2 + i_3 = 15A \Rightarrow i_3 = 15 - i_2$ (3)

plug (3) \rightarrow (2): $4i_2 - 30 + 2i_2 = 30 \Rightarrow i_2 = \frac{60}{6} = \underline{10A}$ (4)

plug (4) \rightarrow (3): $i_3 = 15 - 10 = \underline{5A}$ (5), $i_4 = 25A$ (given) (6)

\therefore From (1): $I_{AB} = \underline{5A}$ (4): $I_{BC} = \underline{10A}$ (5): $I_{CD} = \underline{-5A}$ (6): $I_{DE} = \underline{-25A}$

check: $\frac{V_A - V_B}{8} = \frac{50 - 10}{8} = 5A$, $\frac{V_B - V_C}{4} = \frac{10 - (-30)}{4} = 10A$, $\frac{V_C - V_D}{2} = \frac{-30 - (-20)}{2} = -5A$, $\frac{V_D - V_E}{1} = \frac{-20 - 5}{1} = -25A$

(c) $P_8 = I^2 R = 5^2 \times 8 = \underline{200W}$ $P_4 = 10^2 \times 4 = \underline{400W}$ $P_2 = 5^2 \times 2 = \underline{50W}$, $P_1 = 25^2 \times 1 = \underline{625W}$


(d) $|\sum P_{\text{sources}}| = \sum P_R = 1275W$ is the total or net power generated by the combined five sources.

1#2

(a) Find R_x in circuit of Fig 2 to balance the bridge (ie $\bar{V}_{ab} = 0$).

(b) For R_x found in part (a), find $v_b(t)$.

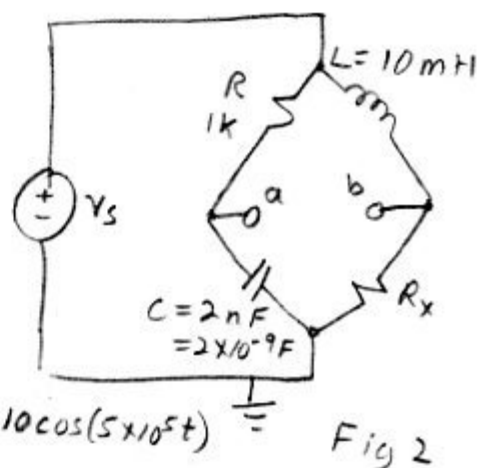(c) For R_x found in part (a), find power loss in L, C, R_x .



$$\text{Soln (a) volt div: } \bar{V}_a = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \bar{V}_s = \frac{1}{1 + j\omega RC} \bar{V}_s \quad (1)$$


$$\text{volt div: } \bar{V}_b = \frac{R_x}{R_x + j\omega L} \bar{V}_s = \frac{1}{1 + \frac{j\omega L}{R_x}} \bar{V}_s \quad (2)$$

$$\bar{V}_a = \bar{V}_b \Rightarrow (1) = (2) \Rightarrow \omega RC = \frac{\omega L}{R_x} \Rightarrow R_x = \frac{L}{RC} = \frac{10 \times 10^{-3}}{10^3 \times 2 \times 10^{-9}} = \underline{\underline{5 \text{ k}\Omega}}$$

$$(b) \text{ From (2) } \bar{V}_b = \frac{1}{1 + j \frac{5 \times 10^3 \times 10 \times 10^{-3}}{5000}} \bar{V}_s = \frac{1}{1 + j} \bar{V}_s$$

$$= 10 \angle 0^\circ / \sqrt{2} \angle 45^\circ = \frac{10}{\sqrt{2}} \angle -45^\circ$$
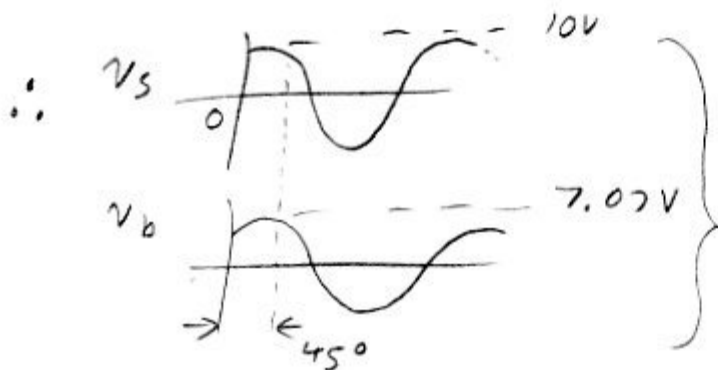
$$\therefore v_b(t) = \underline{\underline{7.07 \cos(5 \times 10^4 t - 45^\circ)}}$$



not required

(c) L, C only store/release energy temporarily: $P_{avg} = 0$.

$$P_x = I_{rms}^2 R_x = \left(\frac{7.07 \text{ V}}{\sqrt{2} \times 5 \text{ k}\Omega} \right)^2 \times 5 \text{ k}\Omega = (1 \text{ mA}_{rms})^2 \times 5 \text{ k}\Omega = \underline{\underline{5 \text{ mW}}}$$

$$\text{or } P_x = V_x^2 / R_x = (5 \text{ V})^2 / 5 \text{ k}\Omega = \underline{\underline{5 \text{ mW}}} \checkmark$$


#3

In Fig 3 switch open long time, prior to $t=0$.

- (a) sketch $i_L(t)$ for all t .
 (b) Find change in inductor energy between $t=0$ and $t \rightarrow \infty$.
 Does inductor energy increase or decrease?


(c) Sketch $i_{R1}(t)$ for all t .

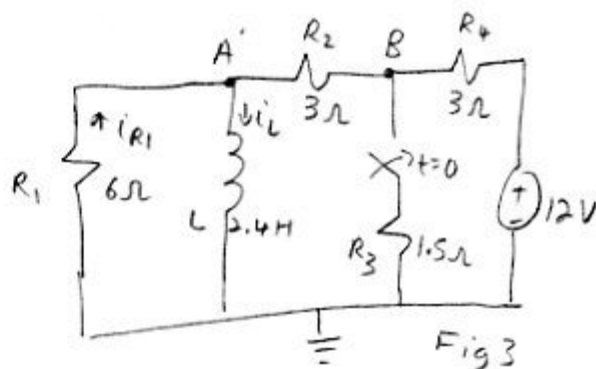- (d) Find change in $R1$ energy between $t=0$ and $t \rightarrow \infty$, where does this energy go?




Hints ans < 15

(a) Step 1

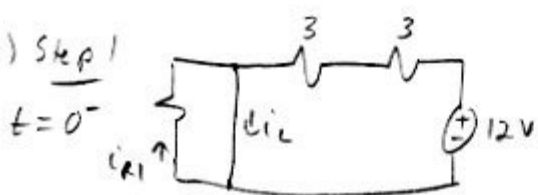

$$i_L(0^-) = \frac{12}{6\Omega} = \underline{2A} \quad i_{R1}(0^-) = \underline{0}$$

Step 2

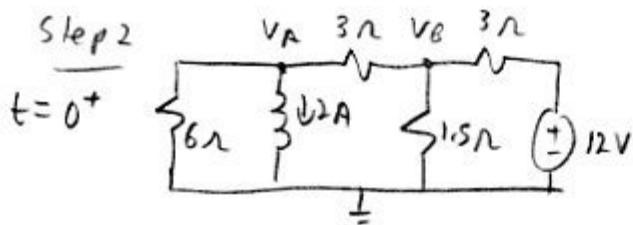

$$i_L(0^+) = i_L(0^-) = \underline{2A}$$

$$\text{Node A: } \frac{V_A}{6} + 2 + \frac{V_A - V_B}{3} = 0$$

$$6x: \quad 3V_A - 2V_B = -12 \quad (1)$$


$$\text{Node B: } \frac{V_B - V_A}{3} + \frac{V_B}{1.5} + \frac{V_B - 12}{3} = 0$$

$$3x: \quad -V_A + 4V_B = 12 \quad (2)$$

$$(1) \times 2: \quad 6V_A - 4V_B = -24 \quad (3)$$

$$(2) + (3): \quad 5V_A = -12 \Rightarrow V_A = -2.4V$$

$$\therefore i_{R1}(0^+) = \frac{-V_A}{R} = \frac{2.4}{6} = \underline{0.4A}$$

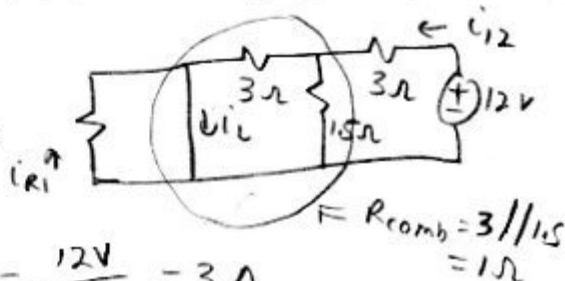Step 3
 $t \rightarrow \infty$ 

$$i_{R2} = \frac{12V}{(3+1)\Omega} = 3A$$

$$\text{Current Div: } i_L(\infty) = 3A \times \frac{1.5}{4.5} = \underline{1A}$$

$$i_{R1}(\infty) = \underline{0}$$


Step 4

Req




$$R_{eq} = [(3//1.5) + 3] // 6 = 4//6 = \underline{2.4\Omega}$$
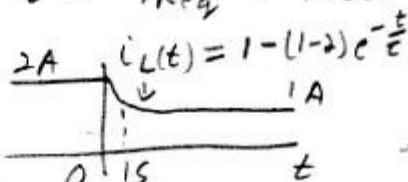
$$\therefore \tau = L/R_{eq} = 1 \text{ sec.}$$



$$\begin{aligned} \Delta W &= \Delta \left(\frac{1}{2} L I^2 \right) \\ &= \frac{1}{2} \times 2.4H (1^2 - 2^2) \\ &= 1.25 - 4.85 \\ &= -3.6 \text{ J} \end{aligned}$$

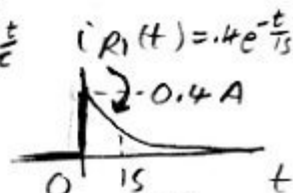\therefore inductor energy decreases by 3.6 Joules.



$$\begin{aligned} \Delta W &= \int P dt \\ &= \int_0^{\infty} I^2 R dt \\ &= \int_0^{\infty} (0.4e^{-t})^2 R dt \\ &= 0.4^2 \times 6\Omega \left[-\frac{e^{-2t}}{2} \right]_0^{\infty} \\ &= 0.4^2 \times 6 \times \frac{1}{2} \\ &= 0.48 \text{ J} \end{aligned}$$

Heat in $R1$.



#4

For circuit of Fig 4,
 (a) find v_o if S_1 and S_2 are closed,

(b) find v_o if S_1 and S_2 are open,

(c) find v_o if S_1 is open and S_2 is closed,

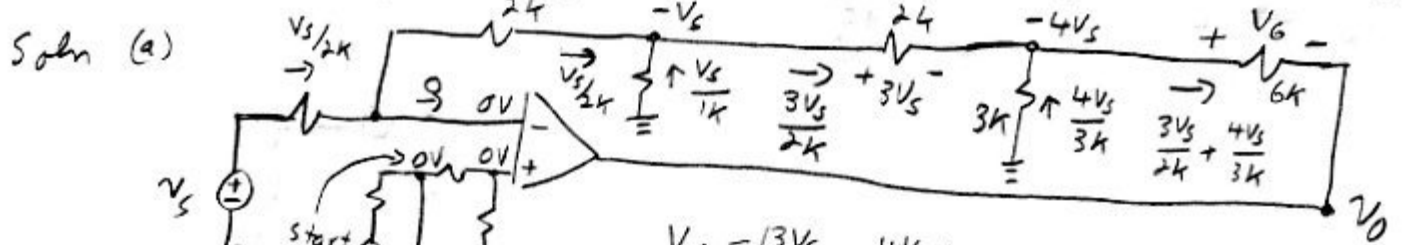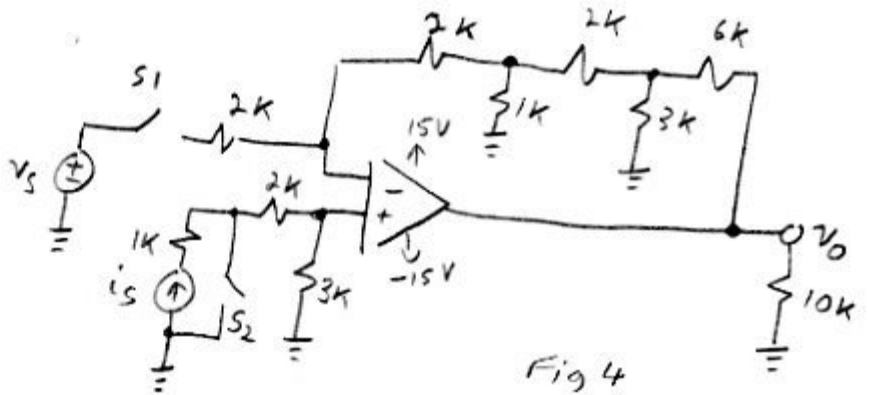(d) For part (a), roughly sketch $v_o(t)$ if $v_s(t) = 2 \sin(\omega t) V$.




$$v_6 = \left(\frac{3v_s}{2k} + \frac{4v_s}{3k} \right) \times 6k = 9v_s + 8v_s = 17v_s$$

$$v_o = -4v_s - v_6 = -4v_s - 17v_s = \underline{\underline{-21v_s}}$$

ie this circuit has gain of -21 for v_s and gain of zero for i_s .

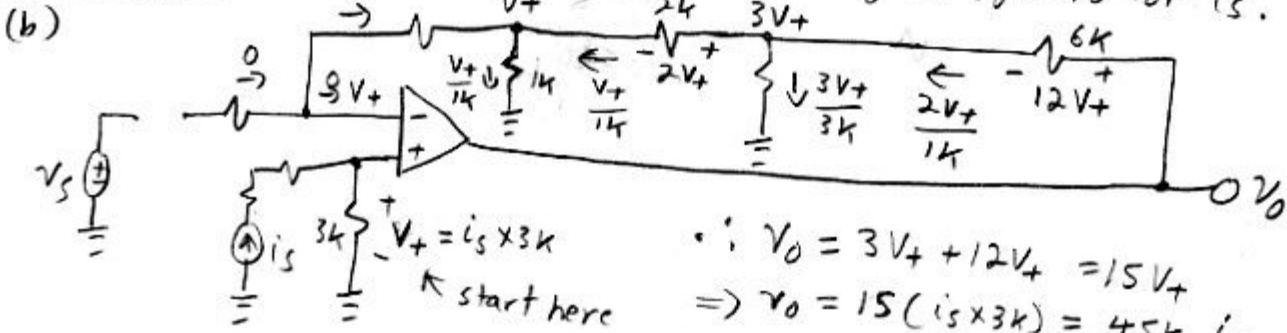Note: For parts (a) and (b) Node Method also works



$$v_+ = i_s \times 3k$$


$$\therefore v_o = 3v_+ + 12v_+ = 15v_+$$

$$\Rightarrow v_o = 15(i_s \times 3k) = \underline{\underline{45k i_s}}$$

ie this circuit has gain = zero for v_s and gain $45k \frac{V}{A}$ for i_s .

(c) In this case all resistors have zero current, $\therefore v_o = \underline{\underline{0V}}$
 Except for 1k in series with i_s ,

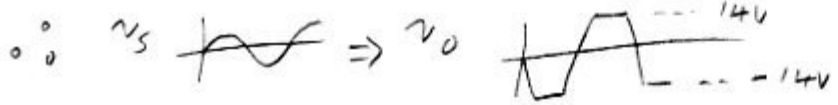
(d) For gain = -21 $\Rightarrow v_o(t) = -41 \sin(\omega t) V$, but Op-Amp $\pm 15V$ power supply will limit out voltage max $\approx 14V$.



Aside: S_1 closed, S_2 open
 Superposition does not work since in (b) S_1 can't zero v_s .

#5

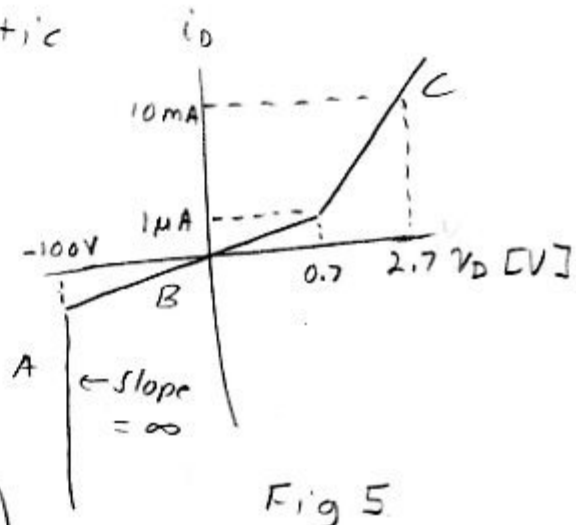(a) For the diode characteristic shown in Fig 5, find the diode equivalent circuit corresponding to each line segment (label i_D and v_D in each equivalent circuit).
 Note $1\mu A = 10^{-6} A$.



- (b) i) Find I_1 and I_2 in Fig 5-1.
 ii) " " " " " " 5-2.
 iii) " " " " " " 5-3. } All diodes characterized as in part (a).
 Hint in each case at least one current is order μA .

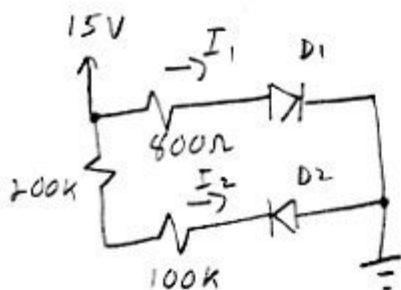


Fig 5-1

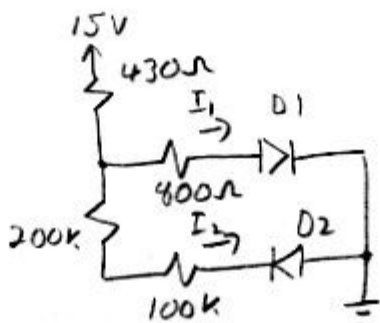


Fig 5-2

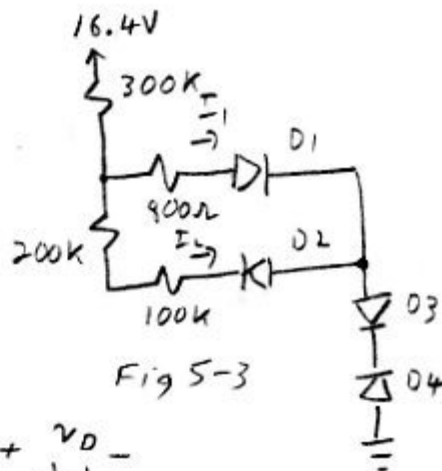


Fig 5-3

Soln (a) (A) $\begin{matrix} + v_D - \\ \rightarrow i_D \end{matrix} \Rightarrow \begin{matrix} + v_D - \\ \ominus \oplus \\ \rightarrow 100V \\ i_D \end{matrix} \Leftrightarrow \begin{matrix} + v_D - \\ | | | \\ \rightarrow -100V + \\ i_D \end{matrix} \quad R_{eqA} = 0$

(B) $R_{eqB} = \frac{\Delta V}{\Delta I} = \frac{0.7V}{1\mu A} = 700k\Omega \Rightarrow \begin{matrix} + v_D - \\ \rightarrow 700k \\ i_D \end{matrix}$

(C) $R_{eqC} = \frac{\Delta V}{\Delta I} = \frac{2V}{10\mu A - 1\mu A} = 200\Omega \quad V_{on} \approx 0.7V \Rightarrow \begin{matrix} + v_D - \\ | | | \\ \rightarrow 200\Omega + 0.7V \\ i_D \end{matrix}$

- (b) i) $D1$ on $D2$ off $I_1 = \frac{15V - 0.7V}{800 + 200} = 14.3 \mu A$ $I_2 = \frac{15V}{(100 + 200 + 700)k} = 15 \mu A$
 ii) $D1$ on $D2$ off $I_2 \ll I_1 \Rightarrow I_1 = \frac{15V - 0.7V}{800 + 200 + 430} = 10 \mu A$ $I_2 = \frac{10.7V}{1000k} = 10.7 \mu A$
 iii) $D1, D3$ on $D2, D4$ off $I_{300k} = \frac{16.4V - (0.7 + 0.7)V}{300k + 700k} = 15 \mu A$
 $I_2 \approx \frac{0.7V}{(200 + 100 + 700)k} = 0.7 \mu A$ (more exact: $0.715 \mu A$) $I_1 = 15 \mu A - 0.7 \mu A = 14.3 \mu A$

#6 (a) A shunt connected (ie field winding and armature are connected in parallel) DC machine is observed to have the following operating conditions,

Shaft Power: $P_{dev} = 30 \text{ HP}$ (recall $1 \text{ HP} = 746 \text{ W}$)

Friction Power: $P_{rot} = 0$

Terminal Voltage: $V_T = V_A = V_F = 230 \text{ V}$

Armature Current: $I_A = 100 \text{ A}$

Field Current: $I_F = 5 \text{ A}$

Shaft speed: $n = 4500 \text{ rpm}$

Is the machine operating as a motor or generator? Explain.

(b) Find i) Arm R, R_A ^{Hint: use Power} ii) Arm EMF, E_A iii) Shaft torque, T_{dev} ^{Efficiency} iv) η .

(c) Same machine is now operated having $V_T = 230 \text{ V}$, $n = 4687 \text{ rpm}$.

Is operation as a motor or generator? ^{Hint: opposite of (a).} Explain.

(d) Find i) E_A , ii) I_A , iii) T_{dev} iv) η and explain change in η compared to (b).

Soln (a) $V_T I_A = 230 \times 100 = 23000 \text{ W} > P_{dev} = 30 \times 746 = 22380 \text{ W} \therefore$ motor

(b) $I_A^2 R_A = 100^2 R_A = 23000 - 22380 = 620 \text{ W} \Rightarrow R_A = 0.062 \Omega$

$E_A = V_T - I_A R_A = 230 - 100 \times 0.062 = 223.8 \text{ V} \leftarrow$ or $E_A I_A = P_{dev}$

$P_{dev} = 22380 = T_{dev} \omega = T_{dev} \times \frac{2\pi}{60} (4500) = T_{dev} (471.24 \frac{\text{rad}}{\text{s}}) \Rightarrow T_{dev} = 47.5 \text{ Nm}$

$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{dev} - P_{rot}}{P_{Arm} + P_{field}} = \frac{22380 \text{ W}}{23000 + 230 \times 5} = \frac{22380}{23000 + 1150} = 92.67 \%$

(c) $E_A = k\phi\omega \Rightarrow E_{A_{new}} = E_{A_{old}} \times \frac{n_{new}}{n_{old}} = 223.8 \times \frac{4687}{4500} = 233.1 \text{ V} \leftarrow > V_T$

(d) $E_A = 233.1 \text{ V}$, $I_A = \frac{233.1 - 230}{0.062 \Omega} = \frac{3.1 \text{ V}}{0.062 \Omega} = 50 \text{ A} \leftarrow$

$P_{dev} = E_A I_A = 233.1 \times 50 = 11655 \text{ W} = T_{dev} \omega = T_{dev} \times \frac{2\pi}{60} 4687 = T_{dev} \times 490.82 \frac{\text{rad}}{\text{s}}$

$\therefore 11655 \text{ W} = T_{dev} (490.82) \Rightarrow T_{dev} = 23.746 \text{ Nm}$

$\eta = \frac{P_{out}}{P_{in}} = \frac{V_T I_A - V_T I_F}{E_A I_A + P_{rot}} = \frac{230 \times 50 - 230 \times 5}{11655 + 0} = \frac{11500 - 1150}{11655} = \frac{10350}{11655} = 88.8 \%$

\therefore gen
or from power
see generator
 -50 A acceptable too.

lower η \therefore lower
power, same field
losses