

marks [10]

(a) Find all node voltages.

All mesh currents given:

- $i_1 = 1A$
- $i_2 = 2A$
- \vdots
- $i_7 = 7A$
- $i_8 = 8A$

$$\therefore V_1 = (i_1 - i_2) \times 1\Omega = (1 - 2) \times 1 = \boxed{-1V}$$

$$V_2 = (i_2 - i_3) \times 2\Omega = (2 - 3) \times 2 = \boxed{-2V}$$

$$\boxed{V_3 = -3V}$$

$$\boxed{V_4 = -4V}$$

$$\boxed{V_5 = -5V}$$

$$\boxed{V_6 = -6V}$$

$$\boxed{V_7 = -7V}$$

$$V_8 = (i_8 - i_1) \times 8\Omega = (8 - 1) \times 8 = \boxed{56V}$$

Part (a) Alternative Soln: Node Method
 Node 1: $-1A + v_1/1\Omega + 2A = 0 \Rightarrow v_1 = 1\Omega(1A - 2A) = -1V$
 Node 2: $-2A + v_2/2\Omega + 3A = 0 \Rightarrow v_2 = -2V$ etc

Part (b) Alternative Soln:
 KVL is also based on conserv. of energy
 So pick a loop eg. loop 1:
 $(V_8 - V_1) + V_1 + (0 - V_8) = 0$
 $\Rightarrow 57V + (-1V) + (-56V) = 0$ which can be interpreted as meaning: the 1A source "pumps up" elec. potential energy by 57J/C and 1Ω R "drops" 1J/C & 8Ω R drops 56J/C.

$$(b) P_{all\ resistors} = \sum i^2 R = 1^2 \times 1\Omega + 1^2 \times 2\Omega + 1^2 \times 3\Omega + 1^2 \times 4\Omega + 1^2 \times 5\Omega + 1^2 \times 6\Omega + 1^2 \times 7\Omega + 7^2 \times 8\Omega$$

$$= 1 + 2 + 3 + 4 + 5 + 6 + 7 + 392 = 420W$$

$$P_{all\ sources} = \sum v_i i = (V_8 - V_1) \times 1A + (V_1 - V_2) \times 2A + (V_2 - V_3) \times 3A + \dots + (V_7 - V_8) \times 8A$$


$$= 57 + 2 + 3 + 4 + 5 + 6 + 7 + (-7 - 56) \times 8$$

$$= 84 - 504 = -420W$$

[4]

\therefore In each second the resistors absorb a total of 420J.
 In each second the sources supply a total of 420J.
 Thus energy is conserved. ①

1#2

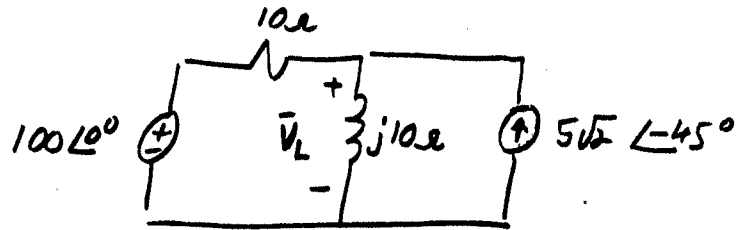
Given $f = 1000 \text{ Hz}$ 

(a) Node eqn: $\frac{\bar{V}_L - 100}{10} + \frac{\bar{V}_L}{j10} - \overbrace{5\sqrt{2} \angle -45^\circ}^{= 5-j5} = 0$ (1) [3] marks

(b) Superposition let $I_{\text{source}} = 0 \therefore I_{\text{source}}$ open circuit
 voltage division: $\bar{V}_{L1} = 100 \times \frac{j10}{10+j10} = \frac{100}{\sqrt{2}} \angle 90^\circ - 45^\circ = \frac{100}{\sqrt{2}} \angle 45^\circ$ [10]
 $= 50 + j50 \text{ V}$

let $V_{\text{source}} = 0 \therefore V_{\text{source}}$ is short $\therefore R // L$

$$Z_{\text{eq}} = 10 // j10 = \frac{10 \times j10}{10 + j10} = \frac{100j}{10\sqrt{2} \angle 45^\circ} = \frac{100}{10\sqrt{2}} \angle 90^\circ - 45^\circ = \frac{10}{\sqrt{2}} \angle 45^\circ$$

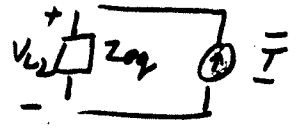$\Rightarrow \bar{V}_{L2} = \bar{I} Z_{\text{eq}}$ (Ohm's Law: )
 $= 5\sqrt{2} \angle -45^\circ \times \frac{10}{\sqrt{2}} \angle 45^\circ$
 $= 50 \text{ or } 50 \angle 0^\circ$ ← passive notation for Z_{eq}

$\therefore \bar{V}_L = \bar{V}_{L1} + \bar{V}_{L2} = 50 + j50 + 50 = 100 + j50 = 111.8 \angle 26.57^\circ \text{ V}$

$\therefore |V_L(t) = 111.8 \cos(2000\pi t + 26.6^\circ) \text{ V}|$

(c) plug soln for \bar{V}_L into (1): [3]

(1) $\times 10$: $\bar{V}_L - 100 - j\bar{V}_L - 50\sqrt{2} \angle -45^\circ = 0$

$V_L = 100 + j50$: $100 + j50 - 100 - j(100 + j50) - (50 - j50) = 0$


$j50 - j100 + 50 - 50 + j50$
 $j50 + j50 - j100 = 0 \checkmark$ ← eqn (1) is verified

(2)

1#2

Given $f = 1000 \text{ Hz}$

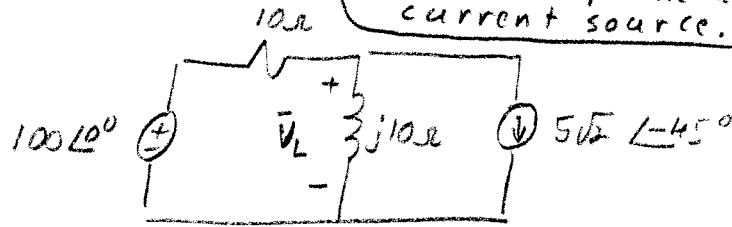For practice here is a solution if we flip the arrow of the current source.




marks

(a) Node eqn:
$$\frac{\bar{V}_L - 100}{10} + \frac{\bar{V}_L}{j10} + 5\sqrt{2} \angle -45^\circ = 0 \quad (1) \quad [3]$$

(b) Superposition let $I_{\text{source}} = 0 \therefore I_{\text{source}}$ open circuit [10]
 voltage division:
$$\bar{V}_{L1} = 100 \times \frac{j10}{10+j10} = \frac{100}{\sqrt{2}} \angle 90^\circ - 45^\circ = \frac{100}{\sqrt{2}} \angle 45^\circ = 50 + j50 \text{ V}$$

let $V_{\text{source}} = 0 \therefore V_{\text{source}}$ is short $\therefore R \parallel L$

$$Z_{\text{eq}} = 10 \parallel j10 = \frac{10 \times j10}{10 + j10} = \frac{100j}{10\sqrt{2} \angle 45^\circ} = \frac{100}{10\sqrt{2}} \angle 90^\circ - 45^\circ = \frac{10}{\sqrt{2}} \angle 45^\circ$$

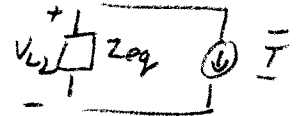$\Rightarrow \bar{V}_{L2} = -\bar{I} Z_{\text{eq}}$ (Ohm's Law: ) ← not passive notation for Z_{eq}

$$= -5\sqrt{2} \angle -45^\circ \times \frac{10}{\sqrt{2}} \angle 45^\circ = -50 \text{ or } 50 \angle 180^\circ \text{ V}$$

$\therefore \bar{V}_L = \bar{V}_{L1} + \bar{V}_{L2} = 50 + j50 - 50 = j50 \text{ V} = 50 \angle 90^\circ \text{ V}$

$\therefore |v_L(t)| = 50 \cos(2000\pi t + 90^\circ) \text{ V} \text{ or } -50 \sin \omega t \text{ V}$

(c) plug soln for \bar{V}_L in to (1):

[3]

(1) $\times 10$: $\bar{V}_L - 100 - j\bar{V}_L + 50\sqrt{2} \angle -45^\circ = 0$

$V_L = j50$: $j50 - 100 - j(j50) + 50 - j50 = 0$

~~$j50 - 100 + 50 + 50 - j50 = 0$~~ ✓

(3)


[#3] For the RC circuit shown in Fig P3, assume that the switch has been open for a long time and is then closed at time $t=0$.

[4] (a) Find V_c and i_c at $t=0^-$


[8] b) Find expressions for $V_c(t)$ and $i_c(t)$ for $t > 0$.

[4] (c) Sketch $V_c(t)$, $i_c(t)$ for all t , indicating τ , $V_c(\tau)$, $i_c(\tau)$.


16

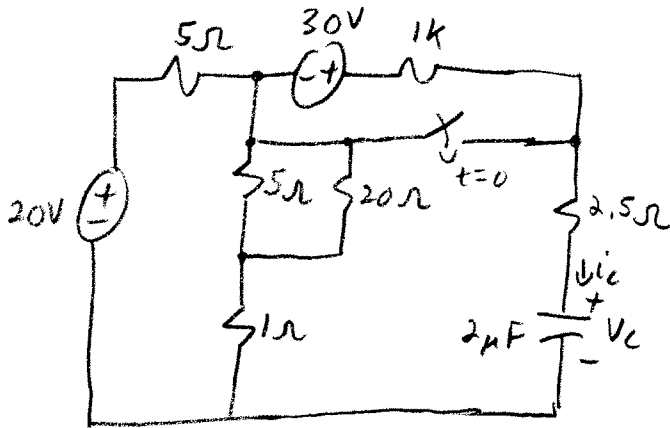

Soln: (a) Circ at $t=0^-$

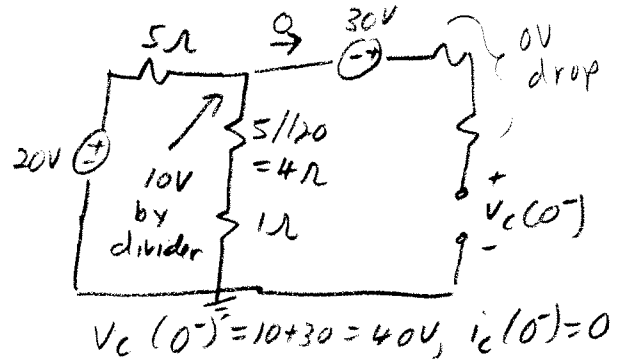


(b) Circuit at $t = \infty$

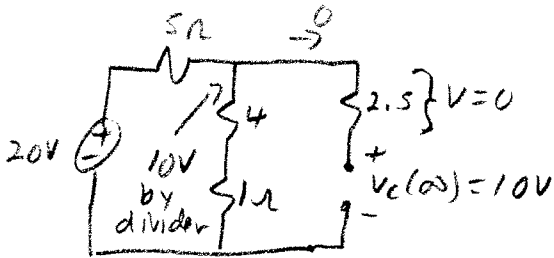

$$\begin{aligned} \therefore V_c(t) &= V_f + (V_i - V_f) e^{-t/\tau} \\ &= 10 + (40 - 10) e^{-t/\tau} \text{ V} \\ &= 10 + 30 e^{-10^5 t} \text{ V} \quad (1) \end{aligned}$$


Req: (short 20V)

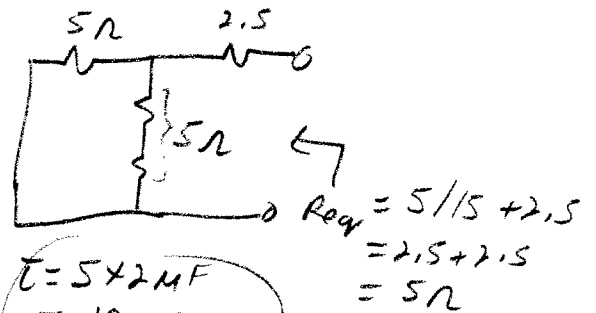

$$\begin{aligned} \therefore \tau &= 5 \times 2 \text{ MF} \\ &= 10 \text{ MS} \\ &= 1 \times 10^{-5} \text{ s} \end{aligned}$$


$$i_c(t) = C \frac{dV}{dt} = 2 \times 10^{-6} \times 30 (-10^5) e^{-10^5 t} = -6 e^{-10^5 t} \text{ A} \quad (2)$$

Alternatively: Circ at $t=0^+$

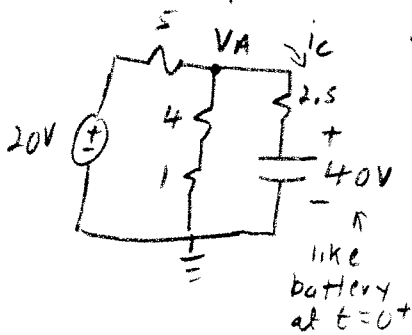

$$\begin{aligned} \frac{V_A - 20}{5} + \frac{V_A}{4+1} + \frac{V_A - 40}{2.5} &= 0 \\ \Rightarrow V_A(0^+) &= 25 \text{ V} \\ \Rightarrow I_c(0^+) &= \frac{25 - 40}{2.5} = -6 \text{ A} \\ &\text{as agrees with (2)} \end{aligned}$$


(4)

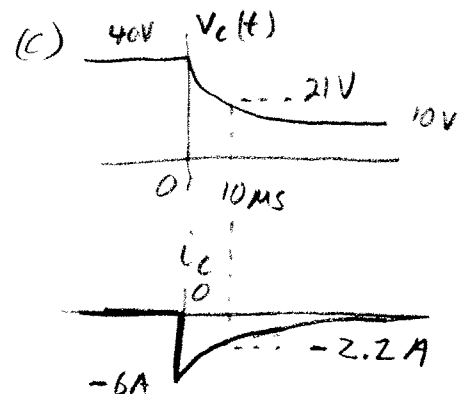


#4 The op-amps in Fig P4 are ideal.

- (a) Find V_{o1} , V_{o2} , and V_{xy} , by Node Voltage analysis or inspection, [10] and/ marks
- (b) Find the Thevenin equiv circ. left of terminals X, Y, [4]
- Hint: Since V_{o1} and V_{o2} are constant voltages, think in terms of an ideal independent voltage source at these nodes.
- (c) Find V_{xy} using the Thevenin circuit of part (b). [2]

Total 16


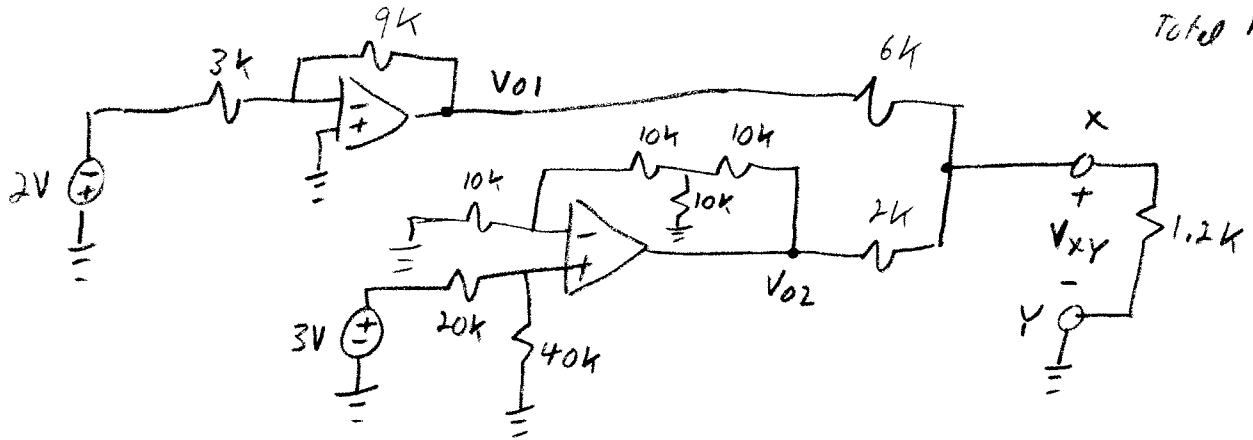


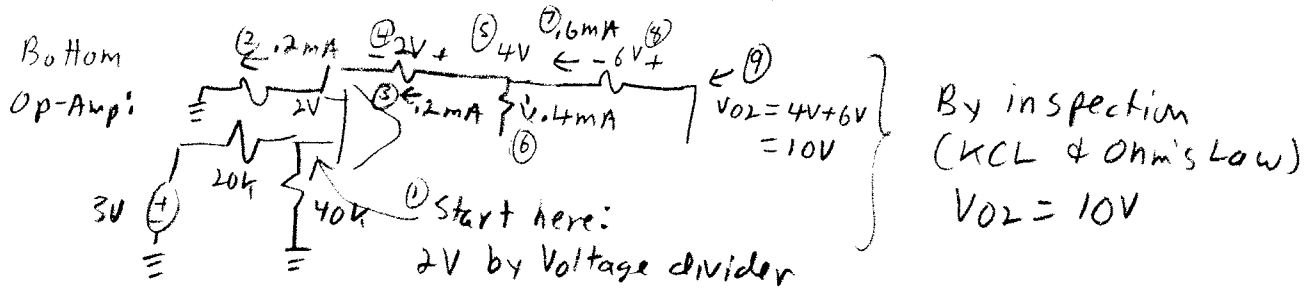Soln: TOP op Amp: $V_{o1} = -2V \times \left(-\frac{9k}{3k}\right) = -2V \times (-3) = +6V$



Node eqn at node X: $\frac{V_{xy} - V_{o1}}{6k} + \frac{V_{xy} - V_{o2}}{2k} + \frac{V_{xy}}{1.2k} = 0$

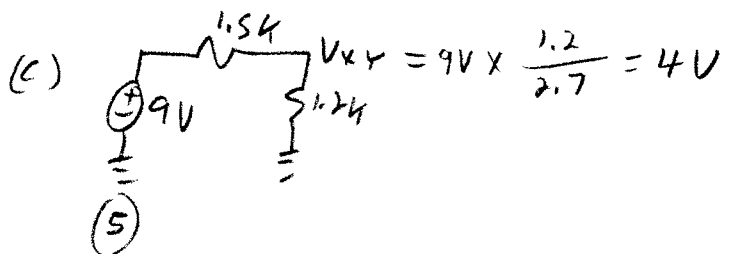
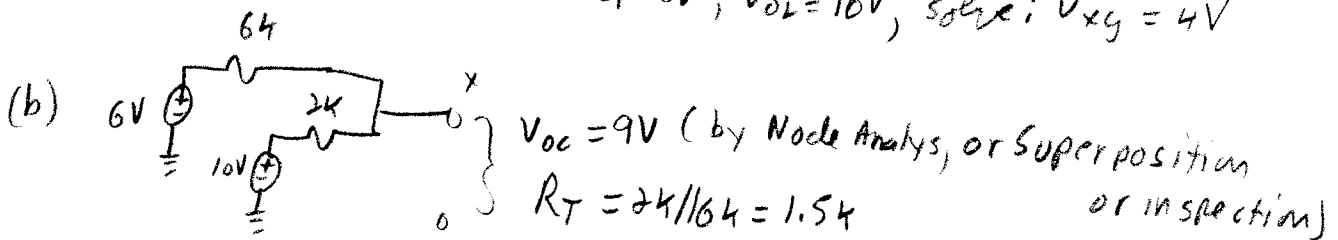
let $V_{o1} = 6V$, $V_{o2} = 10V$, solve: $V_{xy} = 4V$



(#5) Consider the diode circuit shown in Fig P5 (a).

(a) Assuming ideal diodes, find V_D and i_D for each diode. Justify your choice of the on/off state for each diode. [8]

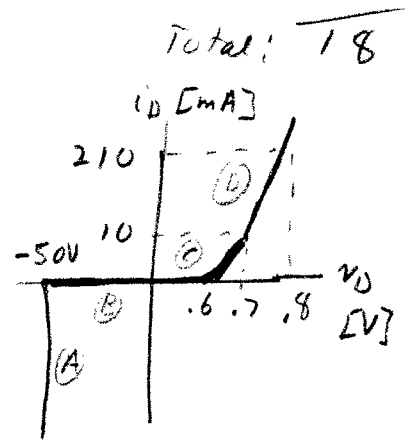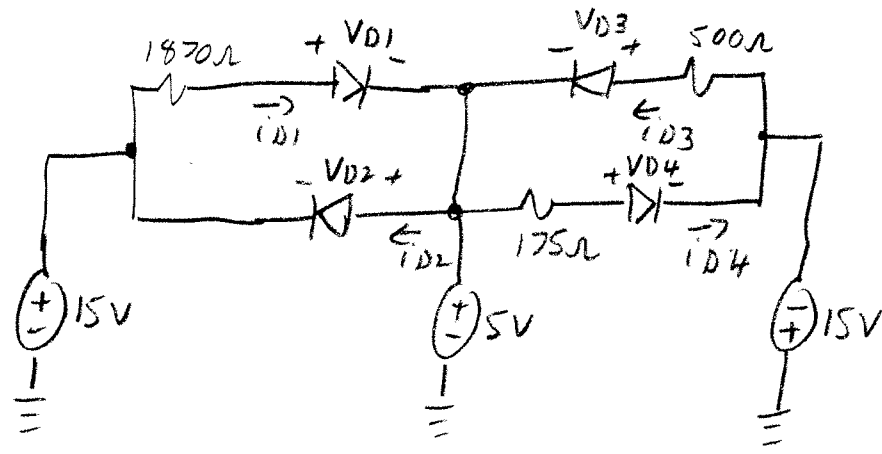
(b) Now assume each diode is characterized by the $i_D - V_D$ relationship shown in Fig. P5(b). Find V_D and i_D for each diode. [10]




Soln: Assume D1 on (15-5=10V applied to anode thru 1870Ω)
 D2 off ($V_{anode} < V_{cathode}$)
 D3 off ($V_{anode} < V_{cathode}$)
 D4 on (high $i_D > 0$ ∴ 5-(-15)=20V applied to anode by 175Ω)

∴ $i_{D1} = 10V/1870 = 5.35mA$, $V_{D1} = 0V$ ($i_{D1} > 0$ ∴ assumption correct)
 $i_{D2} = 0$, $V_{D2} = 5-15 = -10V$ $V_{D2} < 0$ " "
 $i_{D3} = 0$, $V_{D3} = -15-5V = -20V$ $V_{D3} < 0$ " "
 $i_{D4} = 20V/175 = 114.3mA$, $V_{D4} = 0V$ ($i_{D4} > 0$ " ")

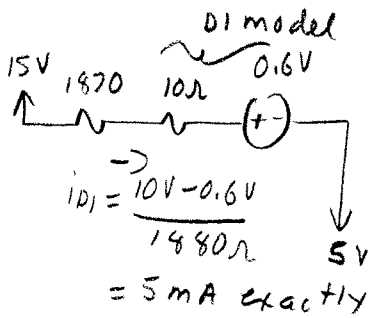(b) Expect D2, D3 still off + b1 in region (C), D4 in region (D)
 region C: $V_D = 10 i_D + 0.6V$, region D: $V_D = 0.5 i_D + 0.695V$



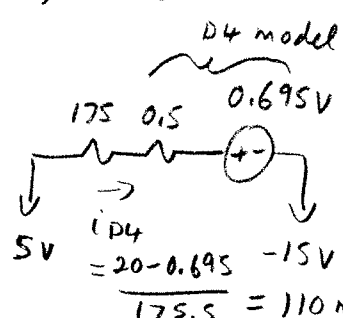$i_{D1} = \frac{10V - 0.6V}{1880\Omega} = 5mA$ exactly
 $V_{D1} = 0.6 + 5mA \times 10 = 0.65V$



$i_{D4} = \frac{20 - 0.695}{175.5} = 110mA$ exactly
 $V_{D4} = 0.695 + 110mA \times 0.5 = 0.75V$

Still have:
 $V_{D2} = -10V, i_{D2} = 0$
 $V_{D3} = -20V, i_{D3} = 0$

1#6

Given shunt DC motor having rated (full-load) conditions:

$$\begin{aligned} n &= 5000 \text{ rpm} \\ T_{out} &= 14.5 \text{ Nm} \\ V_T &= 150 \text{ V} \\ I_L &= 58.1 \text{ A} \\ R_{adj} + R_F &= 75 \Omega \\ R_A &= 0.178 \Omega \end{aligned}$$

Part (a):

- Find
- Field loss
 - Arm loss
 - EA
 - Pdev (in HP)
 - Prot loss (in HP)
 - efficiency

Part (b):

Let T_{rot} be same as part (a).
If $T_{out} = 0$
Find No-load and speed regulation.

$$(a) P_{field} = 150^2 / 75 = 150 \times I_f = 150 \times 2 = 300 \text{ W}$$

$$I_A = I_L - I_f = 58.1 \text{ A} - 2 \text{ A} = 56.1 \text{ A}$$

$$P_{arm \text{ loss}} = I_A^2 R_A = 560.2 \text{ W}$$

$$E_A = V_T - I_A R_A = 150 - 56.1 \times 0.178 = 150 - 10 \text{ V} = 140 \text{ V}$$

$$P_{dev} = E_A I_A = 140 \times 56.1 = 7854 \text{ W} = \frac{7854}{746} = 10.528 \text{ HP}$$

$$P_{out} = T_{out} \omega = 14.5 \times \frac{2\pi}{60} \times 5000 = 14.5 \times 523.6 = 7592 \text{ W} = 10.177 \text{ HP}$$

$$\therefore P_{rot} = P_{dev} - P_{out} = 262 \text{ W} = 0.35 \text{ HP} = 10.528 - 10.177$$

$$P_{in} = V_T I_L = 150 \times 58.1 = 8715 \text{ W} \Rightarrow \eta = \frac{7592}{8715} = 87.1 \%$$

$$(b) \text{ From (a): } K\phi = \frac{E_A}{\omega} = \frac{140}{523.6} = 0.2674 \text{ V-sec}$$

$$P_{rot} = T_{rot} \omega \Rightarrow 262 \text{ W} = T_{rot} \times 523.6 \Rightarrow T_{rot} = 0.5 \text{ Nm (or } T_{dev} - T_{out})$$

$$\text{Part (b): Find } n_{NoLoad}: T_{rot} = K\phi I_A (\because T_{out} = 0) \Rightarrow I_A = 1.97 \text{ A}$$

$$E_A = V_T - I_A R_A = 150 - 1.97 \times 0.178 = 149.667 \text{ V}$$

$$= K\phi \omega_{NL} \Rightarrow \omega_{NL} = 559.7 \text{ rad/s}$$

$$n_{NL} = \frac{60}{2\pi} \times \omega_{NL} = 5345 \text{ rpm}$$

$$SR = \frac{5345 - 5000}{5000} = 6.9\%$$

FYI, Note: Now have $P_{rot} = E_A I_A = 290 \text{ W}$
Real Life: windage $\uparrow \Rightarrow P_{rot} \approx 300 \text{ W}, T_{rot} \approx 0.55 \text{ Nm}$

(7)