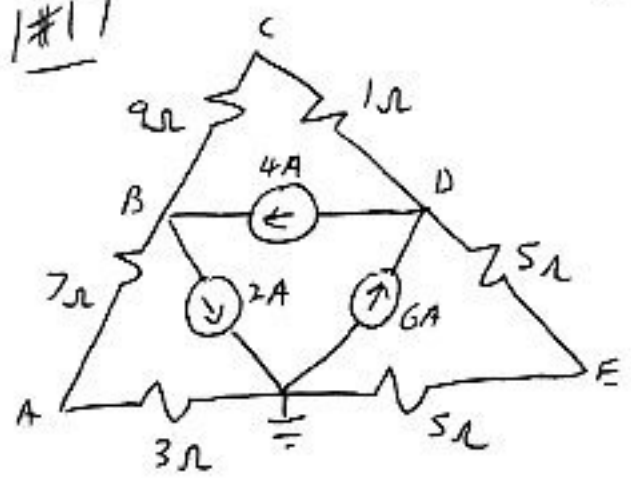


#1



Email Ed any errors or comments

We can use voltage division to find V_A, V_C, V_E after using node analysis to find V_B & V_D :

Node B:
$$\frac{V_B}{7+3} + 2A - 4A + \frac{V_B - V_D}{9+1}$$

Node D:
$$\frac{V_D}{5+5} - 6A + 4A + \frac{V_D - V_B}{9+1}$$

Pure Inspection: An alternative method is based on symmetry and noting that the current sources inject 2A at nodes B+D and $V_B = V_D$.
 $\therefore V_B = 2(7+3) = 20V$
 $= V_D$

10 x (1) $2V_B - V_D = 20$

20 x (2) $-2V_B + 4V_D = 40$

$$3V_D = 60 \Rightarrow V_D = 20V$$

$$V_B = 20V$$

$\therefore V_A = \frac{3}{7+3} \times 20 = 6V$ $V_E = \frac{5}{5+5} \times 20 = 10V$

$$V_C = V_D + \frac{1\Omega}{1+9} \times (V_B - V_D) = 20V + \frac{1}{10} \times (20 - 20) = 20V$$

(b) $P_2 = V_B \times 2A$ (passive) = $20V \times 2A = 40W$ absorbed

$P_4 = (V_D - V_B) \times 4A = 0W$

$P_6 = -V_D \times 6A$ (active) = $-20 \times 6 = -120W$ supplied

(c) $P_{source\ total} = 40W - 120W = -80W$ (supplied)

$$\sum P_R = \frac{V_B^2}{7+3} + \frac{V_D^2}{5+5} + 0$$


$$= \frac{400}{10} + \frac{400}{10} = 80W$$
 absorbed

\therefore In each second 80J is supplied by the sources and 80J is absorbed by the resistors.




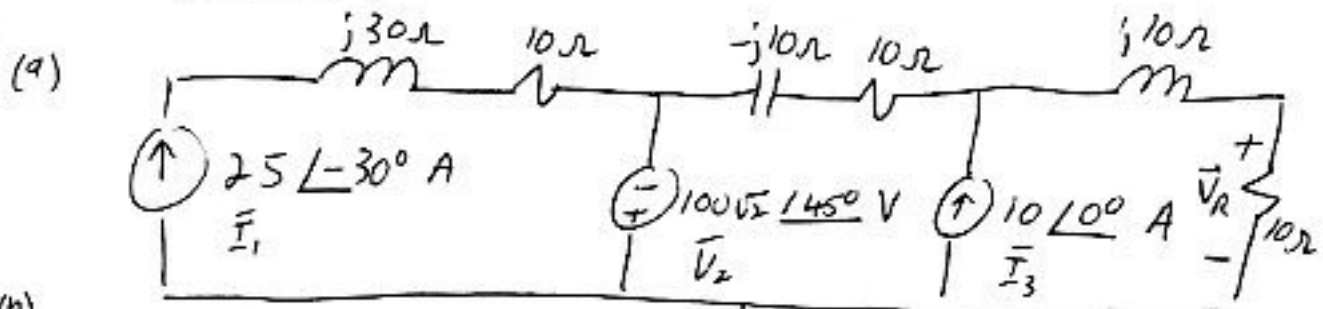
#2

$\omega = 2\pi \times 50 \text{ Hz} = 314.159 \text{ rad/s}$
 $j\omega \times 95.49 \times 10^{-3} \text{ H} = j30 \Omega$
 $j\omega \times 31.83 \times 10^{-3} \text{ H} = j10 \Omega$
 $\frac{1}{j\omega 318.3 \times 10^{-6} \text{ F}} = -j10 \Omega$

notes:
 $50 \text{ A}_{\text{eff}} \Rightarrow 75 \text{ A}_{\text{peak}}$
 $100 \text{ V}_{\text{rms}} \Rightarrow 100\sqrt{2} \text{ V}_{\text{peak}}$




(b)

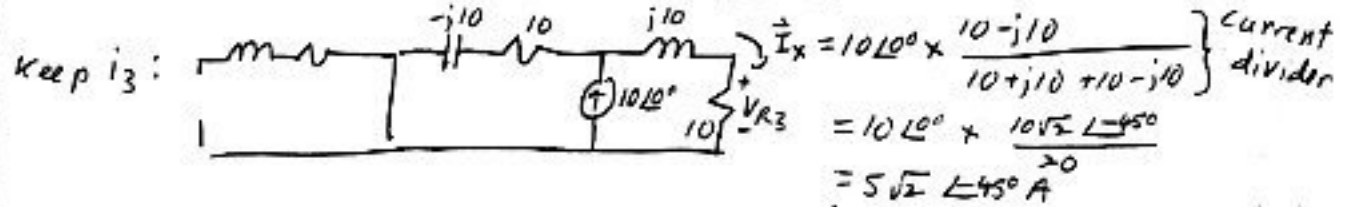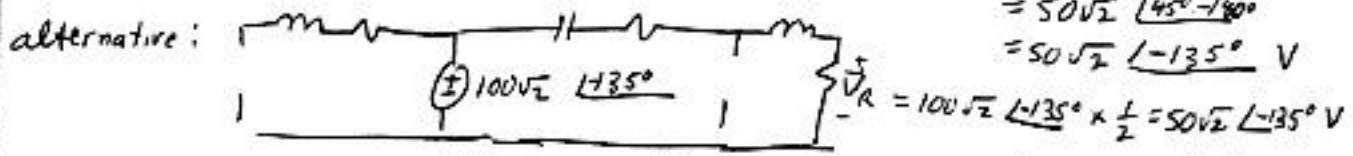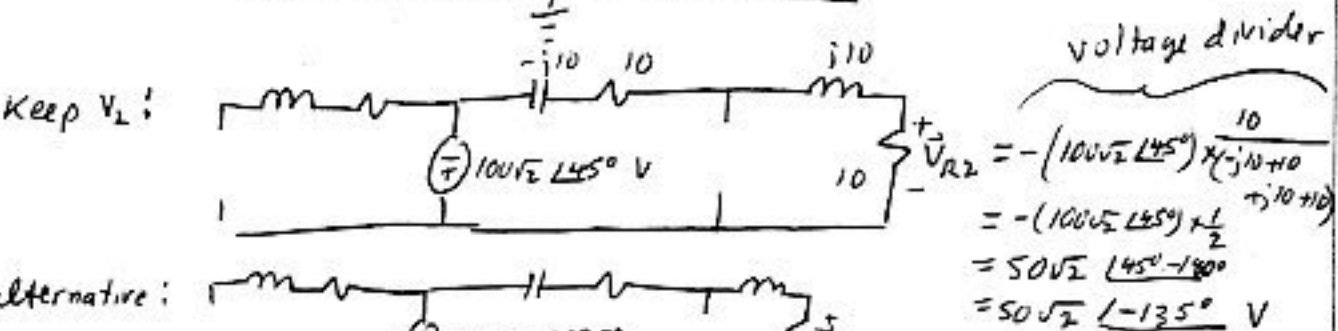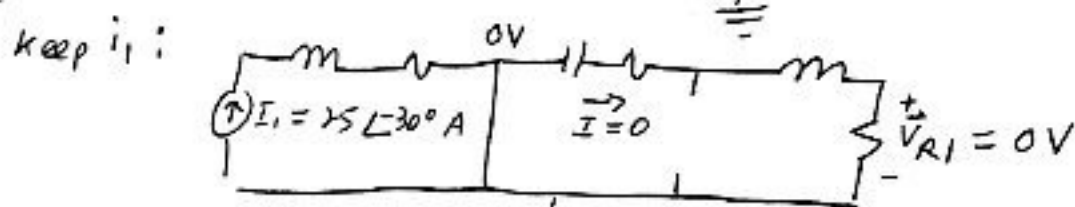


$\therefore \bar{V}_R = \bar{V}_{R1} + \bar{V}_{R2} + \bar{V}_{R3} = 50\sqrt{2} \angle -135^\circ + 50\sqrt{2} \angle -135^\circ$
 $= 100 \angle -90^\circ \text{ V}$

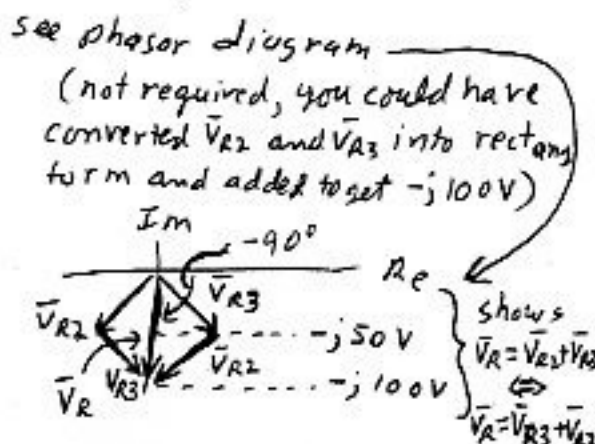
$\therefore \bar{V}_{R3} = \bar{I}_x \times 10 \Omega = 50\sqrt{2} \angle 45^\circ \text{ V}$



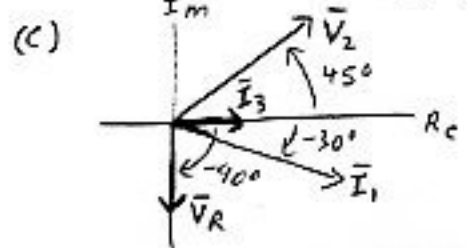$\therefore v_R(t) = 100 \cos(2\pi 50t - 90^\circ) \text{ V}$
 OR $= 100 \sin(2\pi 50t) \text{ V}$



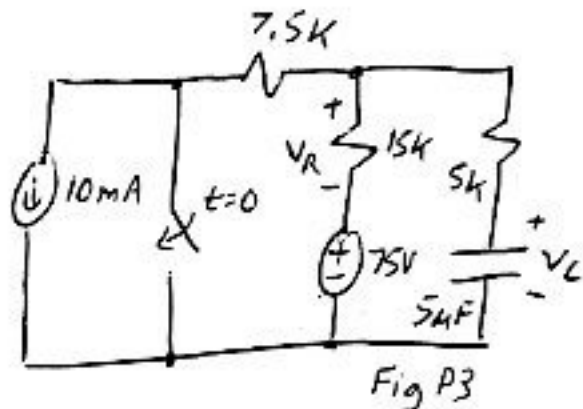
1 #3 For the resistor-capacitor circuit shown in Fig. P3, assume that the switch has been open for a long time, allowing the circuit to reach DC steady-state. The switch then closes at time $t=0$.



(a) Express $v_C(t)$ in equation form for all t , and sketch $v_C(t)$ for all t , indicating also $v_C(t=\tau)$ on the sketch.

(b) Express $v_R(t)$ in equation form ... $v_R(t=\tau)$...

Equiv Circ at $t=0^-$:

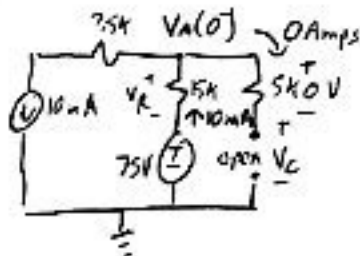

$V_R(0^-) = -(10\text{mA}) \times 15\text{k}$ (active notation)


$V_R(0^-) = -150\text{V}$

5k resistor has 0V across it

$\therefore V_C = V_A$ but $V_A = 75\text{V} + V_R = -75\text{V}$

$V_C(0^-) = -75\text{V}$ note: $V_C(0^+) = V_C(0^-)$

Equiv Circ at $t=0^+$

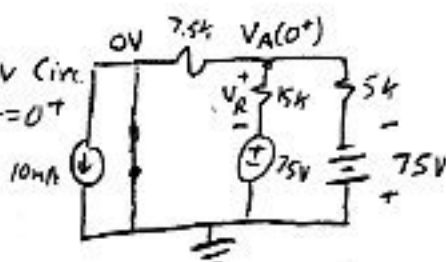


Node A: $\frac{V_A}{7.5\text{k}} + \frac{V_A - 75\text{V}}{15\text{k}} + \frac{V_A - (-75\text{V})}{5\text{k}} = 0$

$\times 15\text{k}$: $2V_A + V_A - 75\text{V} + 3V_A + 3 \times 75\text{V} = 0$

$6V_A = -150\text{V} \Rightarrow V_A(0^+) = -25\text{V}$

$\Rightarrow V_R(0^+) = V_A(0^+) - 75\text{V} = -100\text{V}$

Equiv Circ. as $t \rightarrow \infty$

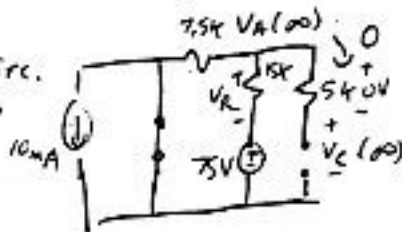


Node A: $\frac{V_A}{7.5\text{k}} + \frac{V_A - 75\text{V}}{15\text{k}} + 0 = 0$

$\times 15\text{k}$: $2V_A + V_A - 75 = 0 \Rightarrow V_A(\infty) = \frac{75}{3} = 25\text{V}$

$\Rightarrow V_C(\infty) = 25\text{V}$ and $V_R(\infty) = V_A(\infty) - 75 = -50\text{V}$

Req zero sources for $t > 0$

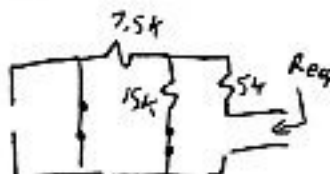



$R_{eq} = (7.5\text{k} \parallel 15\text{k}) + 5\text{k} = 5\text{k} + 5\text{k} = 10\text{k}$

$\therefore \tau = R_{eq}C = 10\text{k} \times 5\mu\text{F} = 10 \times 10^3 \times 5 \times 10^{-6} = 50\text{ms}$

V_R at	0^-	0^+	∞
	-150V	-100V	-50V

V_C at	0^-	0^+	∞
	-75V	-75V	25V

note: $1 - \frac{1}{e} = 63.2\%$

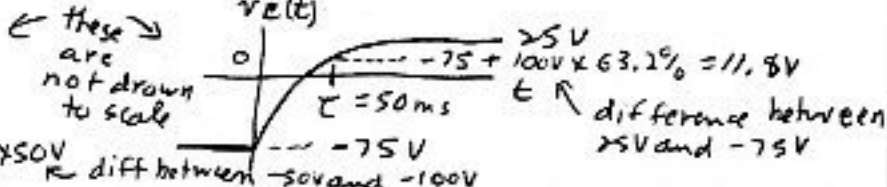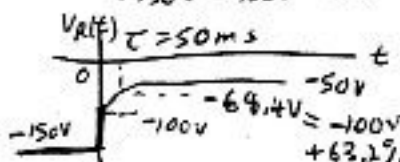

#4] The op amps shown in Figs P4a and P4b are ideal.

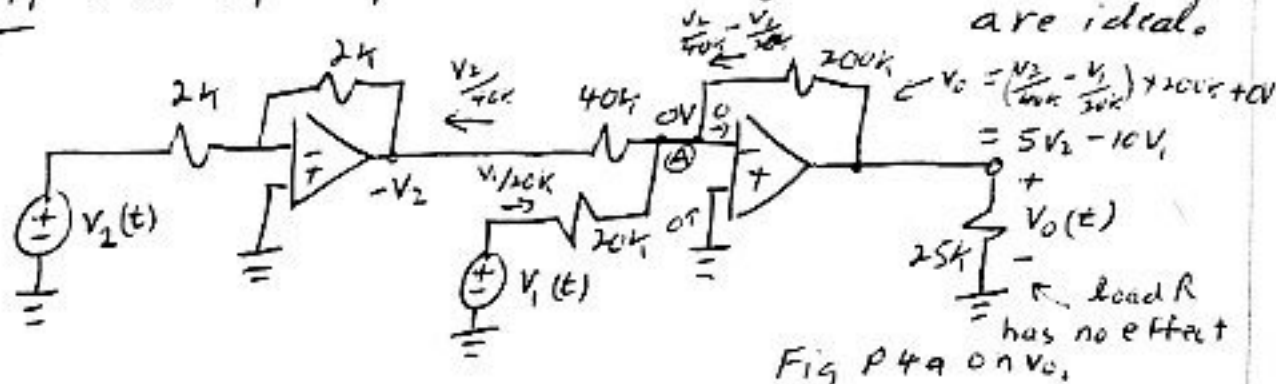


Fig P4a on V_0

(a) For the circuit of Fig P4a, find $V_0(t)$ in terms of $V_1(t)$ and $V_2(t)$. If $V_1(t) = 1 + 2 \sin(100\pi t)$ V

and $V_2(t) = 1 + 5 \sin(100\pi t)$ V sketch $V_0(t)$.

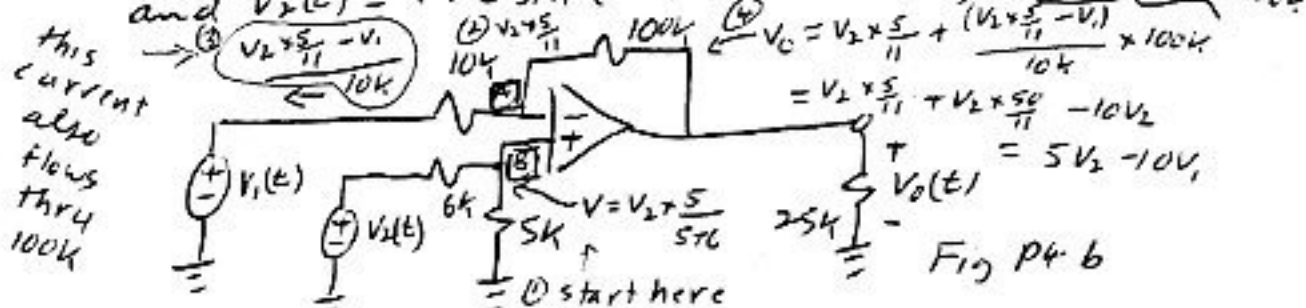


Fig P4 b

(b) For the circuit of P4b, find $V_0(t)$... sketch $V_0(t)$.
Comment.


Comment: Both circuits have same function but 4b does it with one opamp.

For $V_1 = 1 + 2 \sin 100\pi t$ V $V_2 = 1 + 5 \sin 100\pi t$ V

$$V_0 = 5 + 25 \sin 100\pi t - 10 - 20 \sin 100\pi t$$

$$= -5V + 5 \sin 100\pi t \text{ V}$$

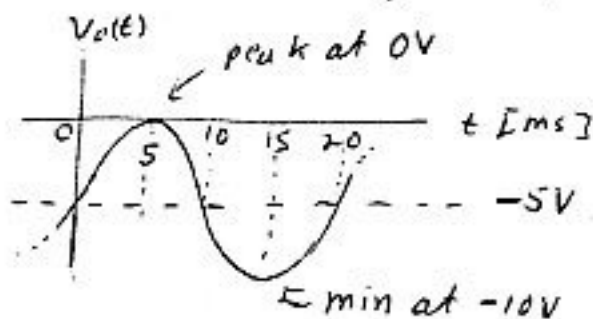This is a sin wave of 5V amplitude and a dc offset of -5V:



Note: $\omega = 100\pi \frac{\text{rad}}{\text{s}} = 2\pi f \Rightarrow f = 50\text{Hz}$
 $\Rightarrow T = \frac{1}{f} = 20\text{ms}$

Inspection Method above
(fast if you truly understand Ohm's Law + Definition of Voltage)

Node Method:

Fig P4a At Node (A):

$$0 - \frac{(-V_2)}{40k} + \frac{0 - V_1}{20k} + \frac{0 - V_0}{200k} = 0$$

$$\Rightarrow V_0 = 5V_2 - 10V_1$$

Fig P4b let $V_B = V_A$ by virtual short

Node (B): $\frac{V_A - V_2}{6k} + \frac{V_A}{5k} = 0$ (1)

Node (A): $\frac{V_A - V_1}{10k} + \frac{V_A - V_0}{100k} = 0$ (2)


From (1): $V_A = \frac{5}{11} V_2$ (3)

Substitute (3) into (2): $V_0 = 5V_2 - 10V_1$

PS Superposition works good too.

#5 (a) Ideal Diodes: Looking at the 50mA and 1.8V sources, it is reasonable that D1 + D3 are on and D2 is off. Then it makes sense that i_1 and i_3 are positive and flow together into i_4 , i_2 locks on.

Equivalent circuit:

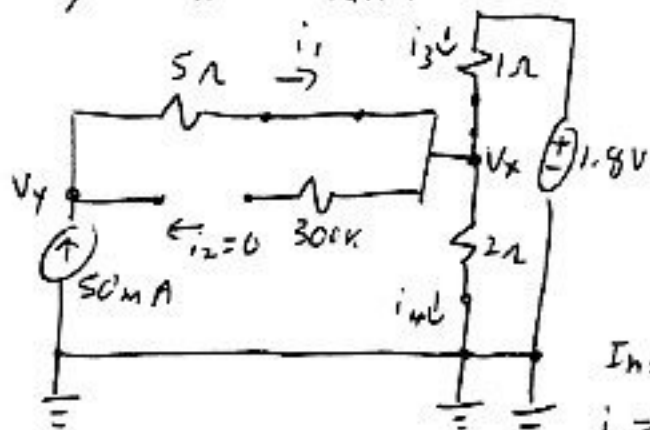

Node Eqn at terminal x:

$$-50\text{mA} + \frac{V_x - 1.8}{1\Omega} + \frac{V_x}{2\Omega} = 0$$


$$\times 2\Omega: 2V_x - 3.6V + V_x = 0.1V$$

$$V_x = \frac{3.7V}{3} = \underline{1.23V}$$

Inspection: $V_y = V_x + 50\text{mA} \times 5\Omega = \underline{1.48V}$

$$i_1 = 50\text{mA}, i_2 = 0, i_3 = \frac{1.8 - 1.23}{1\Omega} = \underline{567\text{mA}}, i_4 = i_1 + i_3 = \underline{617\text{mA}}$$

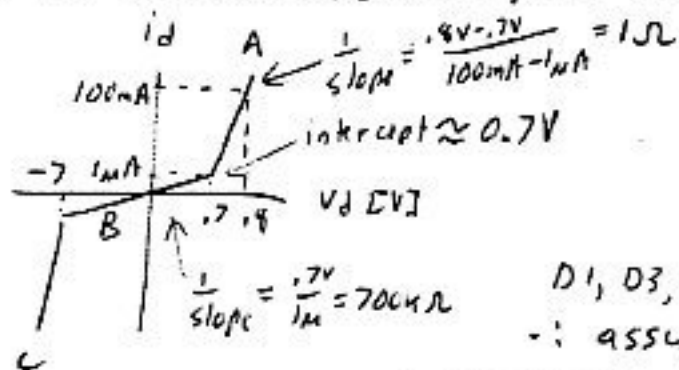(b) More realistic model with piece-wise model:




No voltages in part (a) analysis are near the breakdown voltage of -7V

∴ Assume D2 in region B

D1, D3, D4 were on in part (a)

∴ assume D1, D3, D4 in region A

Equivalent circuit:

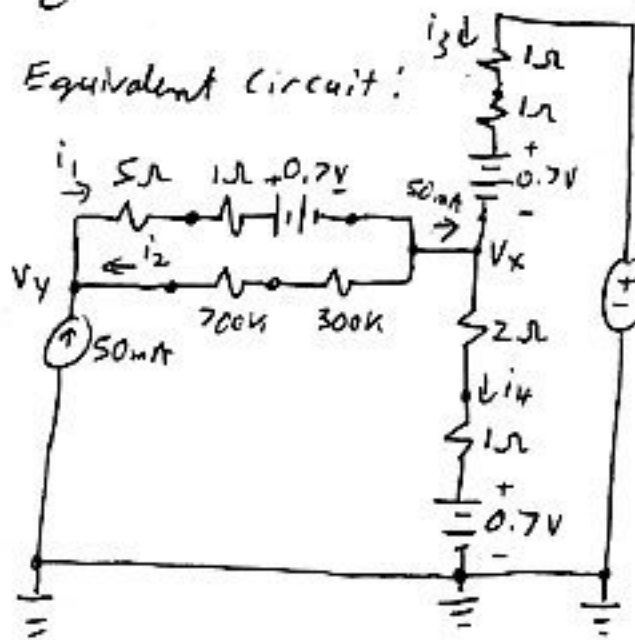

Node Eqn at terminal x:

$$-50\text{mA} + \frac{(V_x + 0.7V) - 1.8V}{1\Omega + 1\Omega} + \frac{V_x - 0.7V}{2\Omega + 1\Omega} = 0$$

$$\times 6\Omega: -3V + 3V_x - 3.3V + 2V_x - 1.4V = 0$$

$$5V_x = 5V \Rightarrow V_x = \underline{1.0V}$$

$$\therefore V_y \approx V_x + 0.7V + 50\text{mA} \times (5 + 1)\Omega = \underline{2.0V}$$


$$i_2 = \frac{V_x - V_y}{700\Omega + 300\Omega} = -1\text{mA} \Rightarrow i_1 = 50\text{mA} - 1\text{mA} \approx \underline{50\text{mA}}$$

$$i_3 = \frac{1.8V - (V_x + 0.7V)}{1 + 1\Omega} = \underline{50\text{mA}}$$

$$i_4 = \frac{V_x - 0.7V}{1\Omega + 2\Omega} = \underline{100\text{mA}} \approx i_1 + i_3 \checkmark$$

#6 (a) Given:

(a) Soln:

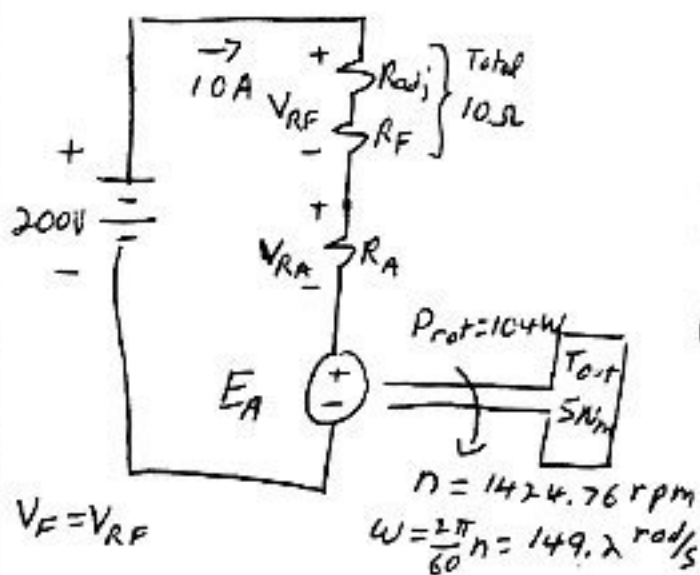

(i) $P_{out} = T_{out} \omega = 5 \times 149.2 = 746W = 1HP$

(ii) $P_{dev} = P_{rot} + P_{out} = 104 + 746 = 850W$

(iii) $E_A I_A = P_{dev}$
 $E_A \times 10A = 850W \Rightarrow E_A = 85V$

(iv) $200V = E_A + V_{RA} + V_{RF}$
 $= 85V + 10A \times R_A + 10A \times 10\Omega$
 $\Rightarrow R_A = 15V / 10A = 1.5\Omega$

(v) $E_A = k\phi \omega \Rightarrow k\phi|_a = \frac{85V}{149.2} = 0.5697 \frac{Vs}{rad}$


$T_{rot}|_a = \frac{P_{rot}}{\omega} = \frac{104}{149.2} = 0.697 Nm$

This is $k\phi$ calculation for part (a)

This is T_{rot} for part (a) and (b)

(b) Given:

(b) Soln:

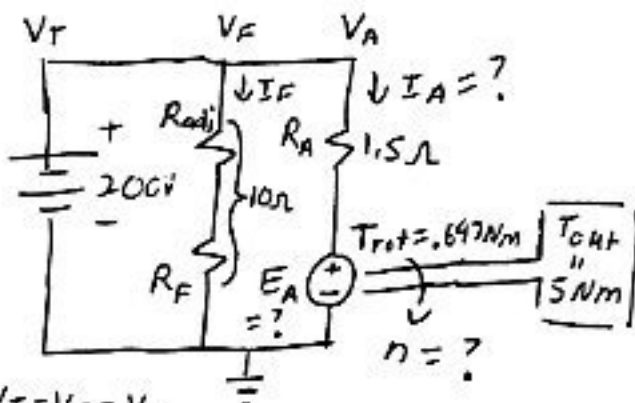

$V_T = V_F = V_A$
 $V_{RA} = I_A R_A$

(i) $I_F = \frac{200V}{10\Omega} = 20A$ (was 10A in part (a))

* (ii) $k\phi \propto I_F$
 $\therefore k\phi|_b = \frac{20A}{10A} \times k\phi|_a = 1.1394 \frac{Vs}{rad}$

(iii) $T_{dev} = k\phi I_A$
 $\Rightarrow I_A = \frac{T_{dev}}{k\phi} = \frac{5.897}{1.1394} = 5A$

(iv) $200V = E_A + I_A R_A$
 $= E_A + 5 \times 1.5$
 $\Rightarrow E_A = 200 - 7.5 = 192.5V$

** (v) $E_A = k\phi \omega \Rightarrow \omega = \frac{E_A}{k\phi} = \frac{192.5}{1.1394} = 168.95 \frac{rad}{s}$
 $n = \frac{60}{2\pi} \omega = 1613.3 rpm$

* Since we are still in the linear region of the magnetization curve, the field must have a rated voltage of at least 200V.

** In Theory if we let $R_A = 0$ then doubling $k\phi$ and doubling E_A means ω does not change $\because E_A = k\phi \omega$ } That's why n did not change much in part (b).