

Question 1

- (a) We may write equations for each of the key nodes C, D, A, B. For E and F, we can treat these as simple voltage dividers.

$$\begin{aligned} \text{Node C: } 4 - 2 + \frac{V_C}{5+15} + \frac{V_C - V_A}{5} &= 0 \\ 40 + V_C + 4V_C - 4V_A &= 0 \\ -4V_A + 5V_C &= -40 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{Node D: } 2 - 5 + \frac{V_D}{15+5} + \frac{V_D - V_B}{5} &= 0 \\ -60 + V_D + 4V_D - 4V_B &= 0 \\ -4V_B + 5V_D &= 60 \end{aligned} \quad (2)$$

Nodes A and B form a supernode.

$$\begin{aligned} \frac{V_A - V_C}{5} + \frac{V_B - V_D}{5} &= 0 \\ V_A + V_B - V_C - V_D &= 0 \end{aligned} \quad (3)$$

$$\text{and } V_A - V_B = 5$$

$$\text{or } V_A = V_B + 5 \quad (4)$$

From here, there are many ways to proceed. Let's add equations (1) and (2) with (3):

$$\begin{aligned} -4V_A - 4V_B + 5V_C + 5V_D &= 20 & (1)+(2) \\ 4V_A + 4V_B - 4V_C - 4V_D &= 0 & (3) \times 4 \end{aligned}$$

$$V_C + V_D = 20 \quad (5)$$

$$\text{Therefore, (3) becomes } V_A + V_B = 20 \quad (6)$$

Using (4), equation (6) becomes

$$\begin{aligned} V_B + 5 + V_B &= 20 \\ 2V_B &= 15 \end{aligned}$$

$$\text{so } \boxed{V_B = 7.5}$$


$$\text{and } V_A = V_B + 5, \text{ so } \boxed{V_A = 12.5}$$

Then, from (1) $V_C = \frac{-40 + 4V_A}{5} = \frac{-40 + 50}{5}$

$$V_C = 2$$

and from (5), $V_D = -20 - V_C$, so $V_D = 18$

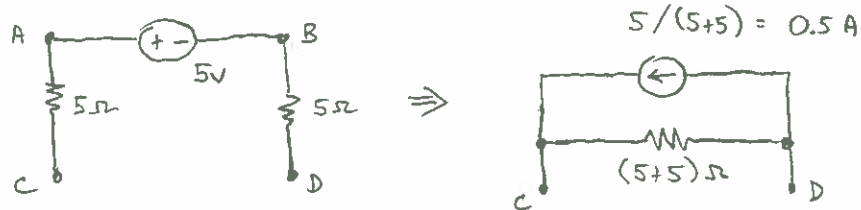An alternative solution could be to recognize that the top portion of the circuit can be redrawn using a source transformation



The equations for C and D became

Node C: $4 - 2 + \frac{V_C}{5+15} - 0.5 + \frac{V_C - V_D}{10} = 0$

$$40 + V_C - 10 + 2V_C - 2V_D = 0$$

$$3V_C - 2V_D = -30 \quad (7)$$

Node D: $2 - 5 + \frac{V_D}{15+5} + 0.5 + \frac{V_D - V_C}{10} = 0$

$$-60 + V_D + 10 + 2V_D - 2V_C = 0$$

$$3V_D - 2V_C = 50 \quad (8)$$

Solving (7) and (8)

$$\begin{array}{r} 6V_C - 4V_D = -60 \quad (7) \times 2 \\ -6V_C + 9V_D = 150 \quad (8) \times 3 \\ \hline \end{array}$$

$$5V_D = 90, \text{ so } V_D = 18$$

and $V_C = 2$.

V_A and V_B can then be found using (3) and (4)

Finally, using the voltage-divider principle,

$$V_E = \frac{15}{5+15} \times V_C = 1.5 \text{ V}$$

$$V_F = \frac{5}{5+15} \times V_D = 4.5 \text{ V}$$


(b) Power in all circuit elements

Sources:

$$P_{4A} = 4 \text{ A} \times V_C = +8 \text{ W} \quad (\text{absorb})$$

$$P_{5A} = -5 \text{ A} \times V_D = -90 \text{ W} \quad (\text{supply})$$
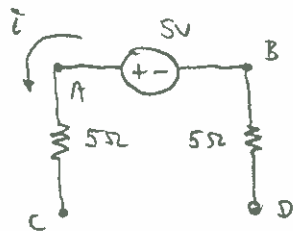
$$P_{2A} = -2 \text{ A} \times (V_C - V_D) = +32 \text{ W} \quad (\text{absorb})$$



$$i = \frac{V_A - V_C}{5} = \frac{10.5}{5} = 2.1 \text{ A}$$

$$P_{5V} = -i \times 5 = -10.5 \text{ W} \quad (\text{supply})$$

Resistors: Connected to node E:

$$P_{CE} = \frac{(V_C - V_E)^2}{5} = 0.05 \text{ W}$$

$$P_{ED} = \frac{V_E^2}{15} = 0.15 \text{ W}$$

Connected to node F:

$$P_{DF} = \frac{(V_D - V_F)^2}{15} = 12.15 \text{ W}$$

$$P_{FD} = \frac{V_F^2}{5} = 4.05 \text{ W}$$

Top portion of circuit:

$$P_{AC} = \frac{(V_A - V_C)^2}{5} = 22.05 \text{ W}$$

$$P_{BD} = \frac{(V_B - V_D)^2}{5} = 22.05 \text{ W}$$


Energy balance:

$$\frac{8 - 90 + 32 - 10.5}{\text{sources}} = -60.5 \text{ W} \quad + \quad \frac{0.05 + 0.15 + 12.15 + 4.05 + 2 \times 22.05}{\text{resistors}} = +60.5 \text{ W}$$

$$= 0 \quad (\text{good!})$$

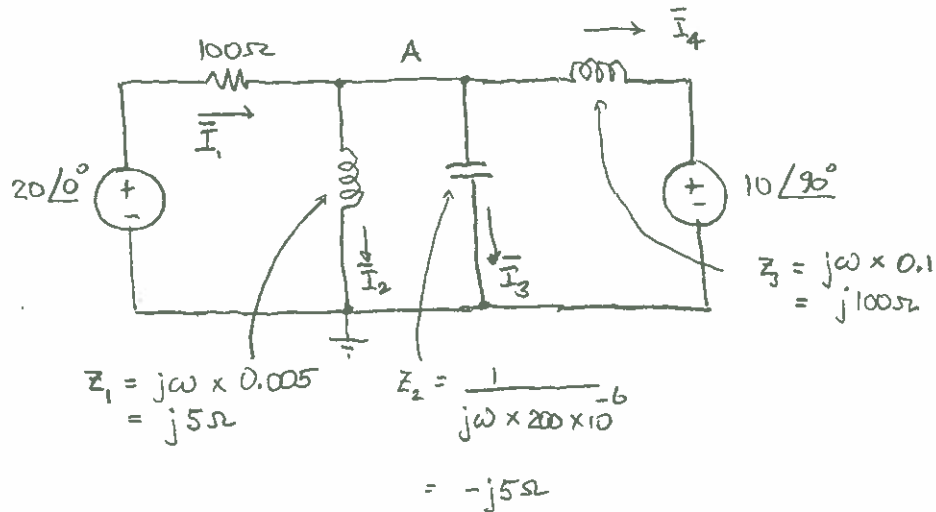Question 2

Redrawing the circuit with phasors and complex impedances



(a) One node-voltage equation at node A

$$\frac{\bar{V}_A - 20}{100} + \frac{\bar{V}_A}{j5} + \frac{\bar{V}_A}{-j5} + \frac{\bar{V}_A - 10\angle 90^\circ}{j100} = 0$$

$$\bar{V}_A - 20 + \frac{\bar{V}_A - j10}{j} = 0$$

$$j(\bar{V}_A - 20) + \bar{V}_A - j10 = 0$$

$$\bar{V}_A(1 + j) = j30$$

$$\text{Thus, } \bar{V}_A = \frac{j30}{1 + j} = \frac{j30}{1 + j} \cdot \frac{1 - j}{1 - j}$$

$$= \frac{j30 + 30}{2}$$

$$\bar{V}_A = 15 + j15$$

Phasor currents:

$$\bar{I}_1 = \frac{20 - \bar{V}_A}{100} = \frac{20 - 15 - j15}{100} = 0.05 - j0.15 = 0.158 \angle -71.57^\circ$$


$$\bar{I}_2 = \frac{\bar{V}_A}{j5} = \frac{15 + j15}{j5} = \frac{3 + j3}{j} \times \frac{-j}{-j} = 3 - j3 = 4.24 \angle -45^\circ$$

$$\bar{I}_3 = \frac{\bar{V}_A}{-j5} = -\bar{I}_2 = -3 + j3 = 4.24 \angle 135^\circ$$

$$\begin{aligned} \bar{I}_4 &= \frac{\bar{V}_A - j10}{j100} = \frac{15 + j15 - j10}{j100} = \frac{15 + j5}{j100} \\ &= 0.05 - j0.15 = 0.158 \angle -71.57^\circ \end{aligned}$$

Quick check: Since \bar{I}_2 and \bar{I}_3 cancel at node A, then \bar{I}_4 must be the same as \bar{I}_1 . (good!)

Phasor diagram:

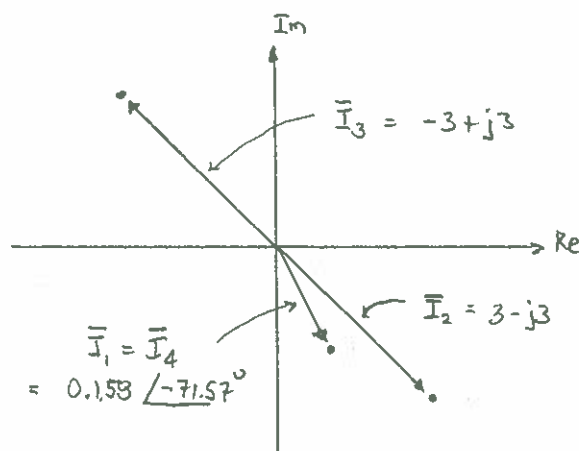

(b) We have $\theta_v = 0^\circ$ and $\theta_I = -71.57^\circ$, so power angle $\theta = \theta_v - \theta_I = 71.57^\circ$

$$\begin{aligned} \text{Apparent power} &= V_{1(\text{rms})} \times I_{1(\text{rms})} \\ &= \frac{20}{\sqrt{2}} \times \frac{0.158}{\sqrt{2}} = 1.58 \text{ VA} \end{aligned}$$

$$\begin{aligned} \text{Active (average) power} \quad P &= 1.58 \cos \theta \\ &= 0.5 \text{ W} \end{aligned}$$


$$\begin{aligned} \text{Reactive power} \quad Q &= 1.58 \sin \theta \\ &= 1.5 \text{ VAR} \end{aligned}$$

$$\text{Power factor} \quad \cos \theta = 0.316$$

Since $\theta_I < \theta_v$, the power factor is 0.316 lagging.

Question 3

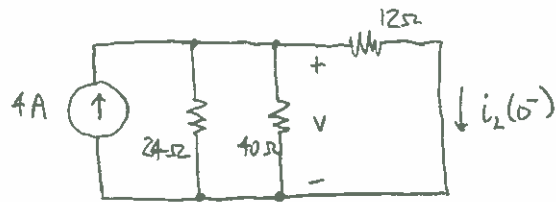(a) In steady-state at $t=0^-$, the equivalent circuit is




Three parallel resistors: $R_{eq} = \left[\frac{1}{24} + \frac{1}{40} + \frac{1}{12} \right]^{-1}$
 $= 6.667 \Omega$

Voltage $v = 4R_{eq} = 26.667 \text{ V}$

giving $i_L(0^-) = \frac{v}{12} = 2.222 \text{ A}$

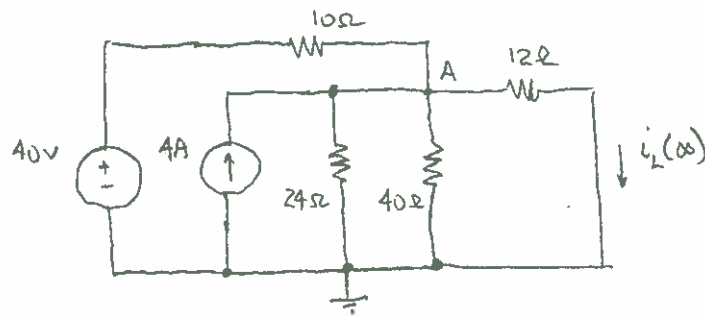In steady-state when $t \rightarrow \infty$, the equivalent circuit is




At node A: $-4 + \frac{V_A}{24} + \frac{V_A}{40} + \frac{V_A}{12} + \frac{V_A - 40}{10} = 0$
} this is $i_L(\infty)$

($\times 120$) $-480 + 5V_A + 3V_A + 10V_A + 12V_A - 480 = 0$
 $30V_A = 960$

$V_A = 32 \text{ V}$

Therefore, $i_L(\infty) = \frac{V_A}{12} = 2.667 \text{ A}$

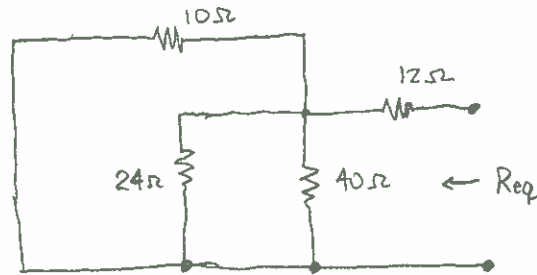We may zero the sources to determine the total resistance across the inductor, $t > 0$.



$$\begin{aligned} R_{eq} &= 10 // 24 // 40 + 12 \\ &= 6 + 12 \\ &= 18 \Omega \end{aligned}$$

$$\text{Time constant } \tau = L/R = \frac{0.09}{18} = 0.005 \text{ s } (5 \text{ ms})$$

The charging curve for $t \geq 0$ is given by

$$i_L(t) = K_1 + K_2 e^{-t/\tau}$$

$$\text{At } t=0^-, \quad i_L(0^-) = 2.222 = K_1 + K_2$$


$$\text{At } t \rightarrow \infty, \quad i_L(\infty) = 2.667 = K_1$$

$$\text{so } K_1 = 2.667, \quad K_2 = -0.4444$$

Finally,

$$i_L(t) = 2.667 - 0.4444 e^{-t/0.005}$$

Sketch:

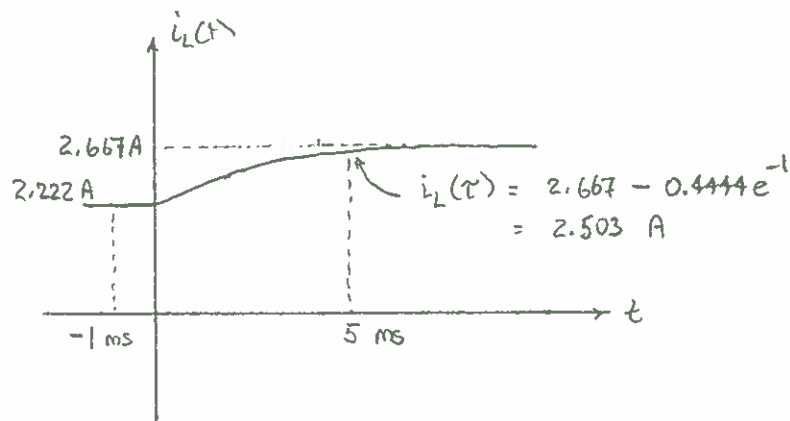


(b) For the inductor voltage, we may simply use

$$\begin{aligned} v_L(t) &= L \frac{di_L(t)}{dt} = 0.09 \frac{d}{dt} [2.667 - 0.4444 e^{-t/\tau}] \\ &= 0.09 \times \frac{0.4444}{\tau} e^{-t/\tau} \end{aligned}$$

$$V_L(t) = 88.889 e^{-t/0.005} \text{ V}, t \geq 0$$

Sketch:

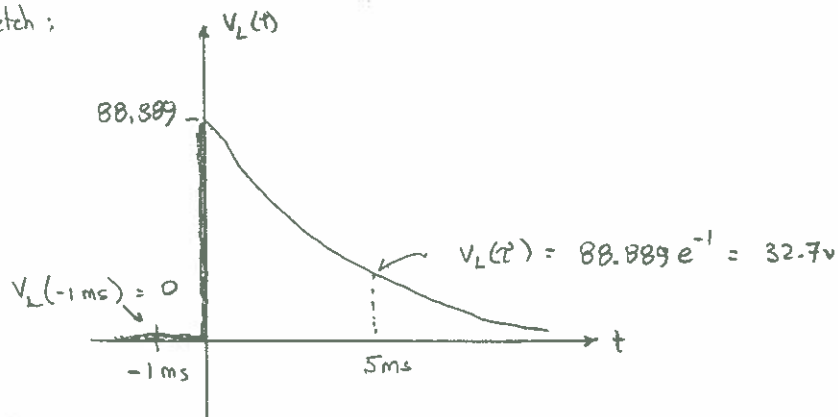

(c) When the switch is re-opened at 6 ms, we have

$$\begin{aligned} i_L(6 \text{ ms}) &= 2.667 - 0.4444 e^{-6/5} \\ &= 2.538 \text{ A} \end{aligned}$$

This will be the initial current at $t = 6 \text{ ms}$, which then decays as $t \rightarrow \infty$ to the value we determined for $i_L(0^-)$.

$$\begin{aligned} \text{At } t = 6 \text{ ms}, \quad i_L(t) &= 2.538 = K_1 + K_2 e^{-(t-0.006)/0.005} \\ &= K_1 + K_2 \end{aligned}$$

$$\text{At } t \rightarrow \infty \quad i_L(\infty) = 2.222 = K_1$$

$$\begin{aligned} \text{so } K_1 &= 2.222 \\ K_2 &= 0.316 \end{aligned}$$

$$\begin{aligned} \text{And } i_L(t) &= 2.222 + 0.316 e^{-(t-0.006)/0.005} \\ &= 2.222 + 0.316 e^{-6/5} e^{-t/\tau} \\ &= 2.229 + 0.0952 e^{-t/\tau}, \quad t \geq 6 \text{ ms} \end{aligned}$$


Time constant will also be different, $t \geq 6 \text{ ms}$

$$\begin{aligned} R_{eq} &= 24 // 40 + 12 \\ &= 15 + 12 = 27 \Omega \end{aligned}$$

$$\begin{aligned} \text{so } \tau &= L/R = 0.09/27 \\ &= 3.333 \text{ ms} \end{aligned}$$

Question 4

(a)

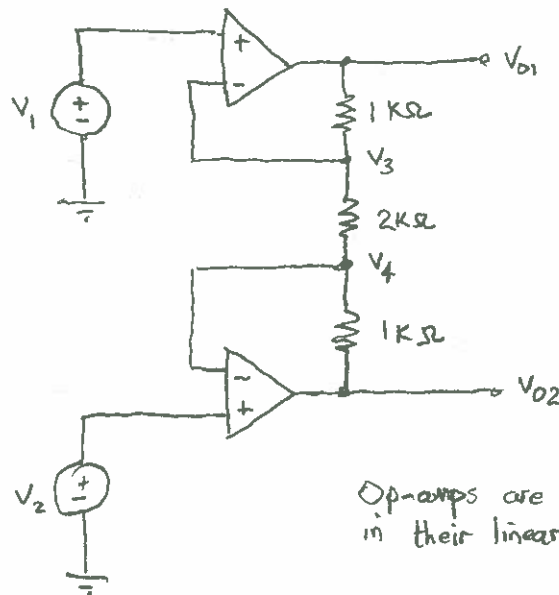

The summing-point constraints impose

$$V_3 = V_1 \quad \text{and} \quad V_4 = V_2$$

Using the node-voltage method,

$$\text{Node } V_3: \frac{V_3 - V_{01}}{1000} + \frac{V_3 - V_4}{2000} = 0$$

$$\text{so } 2(V_1 - V_{01}) + V_1 - V_2 = 0$$


$$\text{and } V_{01} = \frac{3V_1 - V_2}{2}$$

$$\text{Node } V_4: \frac{V_4 - V_{02}}{1000} + \frac{V_4 - V_3}{2000} = 0$$

$$\text{so } 2(V_2 - V_{02}) + V_2 - V_1 = 0$$

$$\text{and } V_{02} = \frac{3V_2 - V_1}{2}$$

(b)

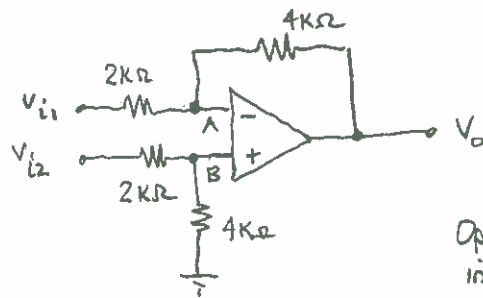Op-amp operating
in linear region

$$\text{Node A: } \frac{V_A - V_{i1}}{2000} + \frac{V_A - V_o}{4000} = 0$$

$$2V_A - 2V_{i1} + V_A - V_o = 0 \quad (1)$$

$$\text{Node B: } \frac{V_B - V_{i2}}{2000} + \frac{V_B}{4000} = 0$$

$$2V_B - 2V_{i2} + V_B = 0$$

$$3V_B = 2V_{i2}$$

$$\text{so } V_B = \frac{2}{3}V_{i2} \quad (2)$$

The summing-point constraints impose $V_A = V_B$, so

$$V_A = \frac{2}{3}V_{i2}$$

and from (1),

$$3\left(\frac{2}{3}V_{i2}\right) - 2V_{i1} = V_o$$


$$V_o = 2(V_{i2} - V_{i1})$$

$$\text{Using } V_{i1} = V_{o1} = \frac{3V_1 - V_2}{2} \text{ and } V_{i2} = V_{o2} = \frac{3V_2 - V_1}{2},$$

$$V_o = 2 \left[\frac{3V_2 - V_1}{2} - \frac{3V_1 - V_2}{2} \right]$$

Finally,

$$\boxed{V_o = 4(V_2 - V_1)}$$

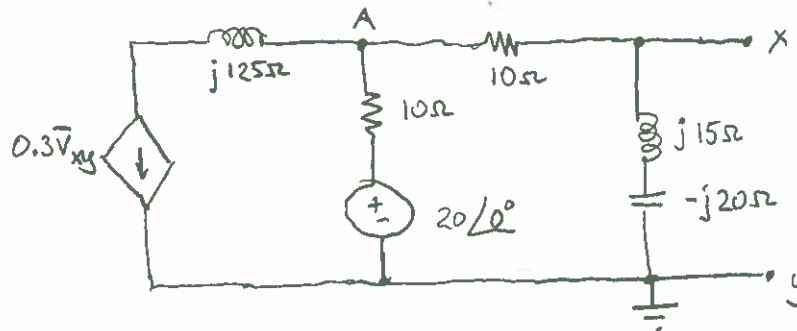Question 5(a) First find $V_T = V_{oc}$.

Node-voltage method:

$$\text{Node A: } 0.3\bar{V}_{xy} + \frac{\bar{V}_A - 20}{10} + \frac{\bar{V}_A - \bar{V}_x}{10} = 0$$

[Note: $\frac{10}{10}\bar{V}_{xy} = \bar{V}_x$]

$$3\bar{V}_x + \bar{V}_A - 20 + \bar{V}_A - \bar{V}_x = 0$$

$$2\bar{V}_A + 2\bar{V}_x = 20 \quad (1)$$

$$\text{Node X: } \frac{\bar{V}_x - \bar{V}_A}{10} + \frac{\bar{V}_x}{j15 - j20} = 0$$

$$\bar{V}_x - \bar{V}_A + \frac{2\bar{V}_x}{-j} = 0$$

$$\bar{V}_x(1 + 2j) = \bar{V}_A \quad (2)$$

Substitute \bar{V}_A from (2) into (1)

$$2\bar{V}_x(1 + 2j) + 2\bar{V}_x = 20$$


$$(4 + j4)\bar{V}_x = 20$$

$$\bar{V}_x = \frac{20}{4 + j4} = \frac{5}{1 + j} \cdot \frac{1 - j}{1 - j}$$

$$= \frac{5 - j5}{2} = 2.5 - j2.5$$

$$\text{Thus, } \bar{V}_T = \bar{V}_{oc} = \bar{V}_x = 2.5 - j2.5$$

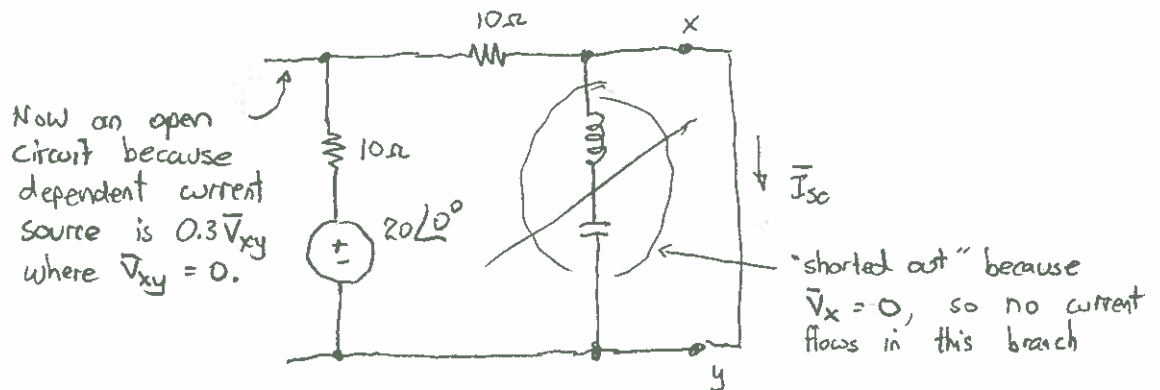
Since there is a dependent source, we must calculate \bar{I}_{sc} .
With x and y connected together, the circuit simplifies to:



By inspection,
$$\bar{I}_{sc} = \frac{20\angle 0^\circ}{10 + 10} = 1$$

Therefore,
$$\bar{Z}_T = \frac{\bar{V}_T}{\bar{I}_{sc}} = 2.5 - j2.5$$

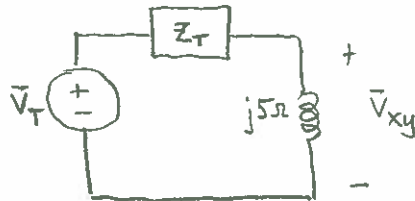(b) Using the newly found Thevenin equivalent



Voltage divider:
$$\begin{aligned} \bar{V}_{xy} &= \frac{j5}{Z_T + j5} \times (2.5 - j2.5) \\ &= \frac{j5}{2.5 - j2.5 + j5} \times (2.5 - j2.5) \\ &= \frac{j5}{2.5 + j2.5} \times (2.5 - j2.5) \\ &= \frac{5\angle 90^\circ}{2.5\sqrt{2}\angle 45^\circ} \times 2.5\sqrt{2}\angle -45^\circ \\ &= 5\angle 0^\circ \end{aligned}$$

In the time domain,
$$v_{xy}(t) = 5 \cos(2000t)$$

(c) We have $Z_T = 2.5 - j2.5 \Omega$

negative, so capacitive reactance




$$\frac{1}{j\omega C} = -j2.5$$

$$\text{so } C = \frac{1}{2.5 \omega} = \frac{1}{2.5 \times 2000} = 0.0002 \text{ F} \text{ (200 } \mu\text{F)}$$

Question 6

The motor's equivalent circuit:

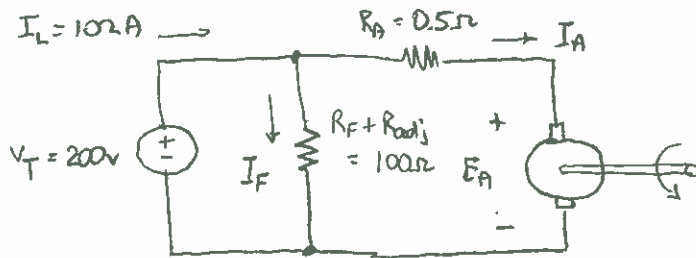

$$T_{\text{out}} = 40 \text{ Nm}$$

$$T_{\text{rot}} = 2 \text{ Nm}$$

(a) $I_F = \frac{200}{R_F + R_{\text{adj}}} = \frac{200}{100} = 2 \text{ A}$

$$I_A = I_L - I_F = 100 \text{ A}$$

(b) Total developed torque $T_{\text{dev}} = T_{\text{out}} + T_{\text{rot}} = 42 \text{ Nm}$

The machine constant can be determined

$$T_{\text{dev}} = K\phi I_A, \text{ so } K\phi = \frac{T_{\text{dev}}}{I_A} = \frac{42}{100} = 0.42$$

The speed may be determined using the other machine equation. First,

$$E_A = V_T - I_A R_A = 200 - 100(0.5) = 150 \text{ V}$$

$$E_A = K\phi\omega_m, \text{ so } \omega_m = \frac{E_A}{K\phi}$$

$$\omega_m = \frac{150}{0.42} = 357.14 \text{ r/s}$$

$$\text{so } n_m = \omega_m \times \frac{60}{2\pi} = 3410.5 \text{ rpm}$$

(c) Developed power $P_{dev} = T_{dev} \cdot \omega_m$

$$= 15,000 \text{ W}$$

$$= 20.1 \text{ HP}$$

Output power $P_{out} = T_{out} \cdot \omega_m$

$$= 14,286 \text{ W}$$

$$= 19.15 \text{ HP}$$

(d) Power losses

$$P_{\text{field-loss}} = I_F^2 (R_F + R_{adj})$$

$$= 400 \text{ W}$$

$$P_{\text{arm-loss}} = I_A^2 R_A$$

$$= 5000 \text{ W}$$

(e) Efficiency

$$P_{in} = V_T \cdot I_L = 20,400 \text{ W}$$

$$P_{out} = 14,286 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = 70\%$$