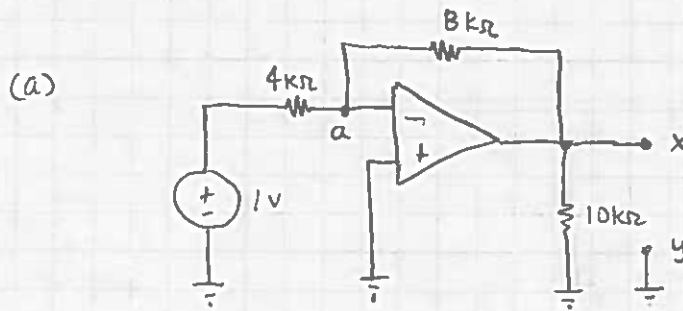



Question 1




By KCL at node a, $\frac{V_a - 1}{4k} + \frac{V_a - V_x}{8k} = 0$, where $V_a = 0$

Solving gives $V_x = V_{xy} = -2V$. Thus, the op-amp is producing -2v at its output. This is independent of the current being drawn at x (e.g., the 10kΩ resistor does not affect V_x in any way).


This is equivalent to

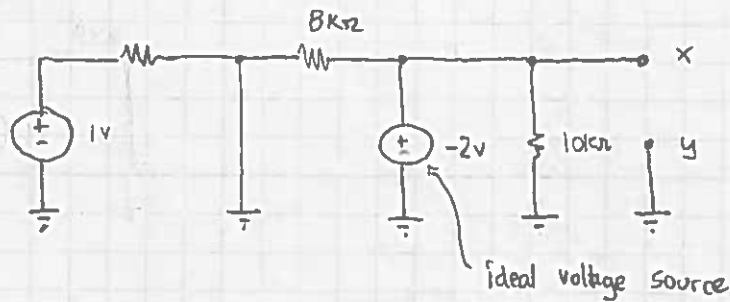

Zeroing the sources,

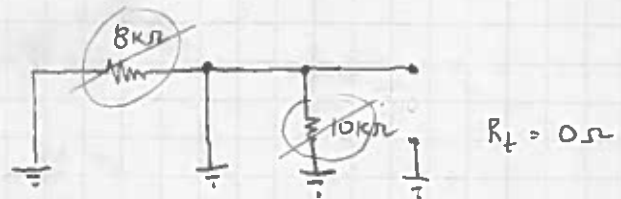

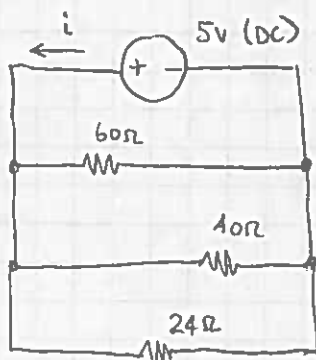(b) At DC, the impedance of the capacitor = ∞ (open circuit), and the impedance of the inductor = 0Ω (short circuit)




Three parallel resistors.

$$R_{eq} = \left[\frac{1}{60} + \frac{1}{40} + \frac{1}{24} \right]^{-1}$$

$$= [0.08333]^{-1} = 12\Omega$$

so $i = \frac{5V}{12\Omega} = 0.41667 A$

(c)

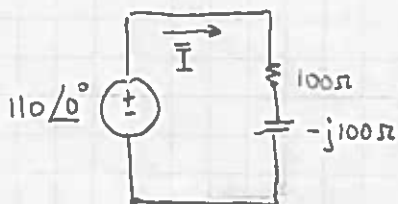

$$\bar{I} = \frac{\bar{V}}{100 - j100} = \frac{110 \angle 0^\circ}{100 - j100}$$

$$= \frac{110}{100\sqrt{2} \angle -45^\circ} = \frac{1.1}{\sqrt{2}} \angle 45^\circ$$

In the impedance, $\bar{S} = \frac{1}{2} \bar{V} \bar{I}^* = \frac{1}{2} \left[110 \times \frac{1.1}{\sqrt{2}} \angle -45^\circ \right]$

$$= \frac{121}{2\sqrt{2}} \angle -45^\circ = \boxed{42.78 \angle -45^\circ}$$

In rectangular form, $\bar{S} = \frac{121}{2\sqrt{2}} \cos(-45^\circ) + \frac{121}{2\sqrt{2}} \sin(-45^\circ)$


$$= \boxed{30.25 - j 30.25 \text{ VA}}$$

giving $P = 30.25 \text{ W}$
 $Q = -30.25 \text{ VAR}$

Alternatively, $P = I_{\text{rms}}^2 R = \left(\frac{1.1}{\sqrt{2}\sqrt{2}} \right)^2 \times 100 = 30.25 \text{ W}$


$$Q = I_{\text{rms}}^2 X = \left(\frac{1.1}{\sqrt{2}\sqrt{2}} \right)^2 \times -100 = -30.25 \text{ VAR}$$

(d)

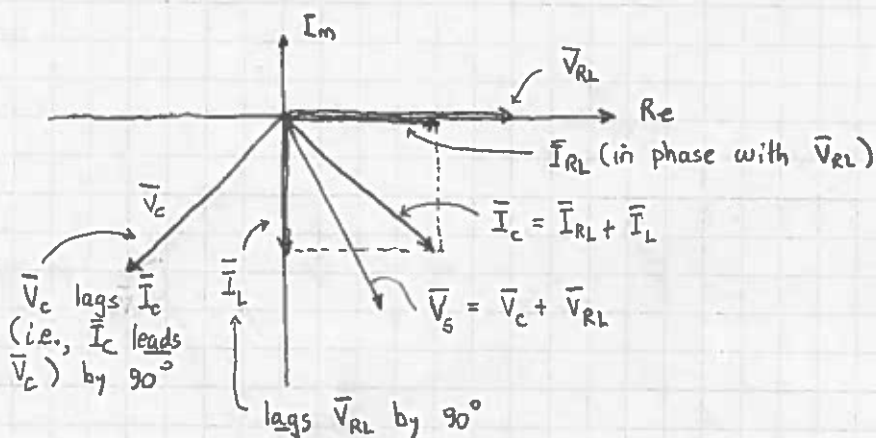

AMPAD

(c)

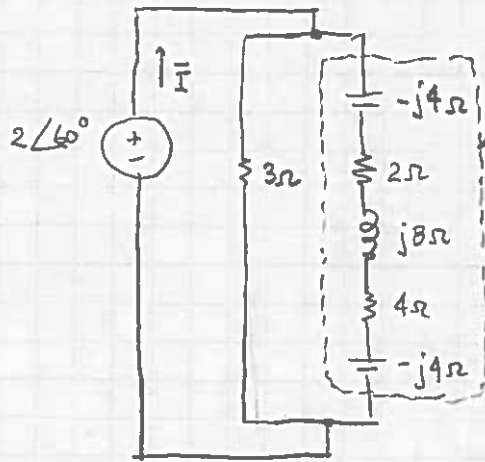

Impedance of series branch


$$Z_{eq} = -j4 + 2 + j8 + 4 - j4 = 6\Omega$$

Combined with 3Ω in parallel,

$$Z_{tot} = \frac{3 \times 6}{3 + 6} = 2\Omega$$

Therefore $\vec{I} = \frac{2\angle 60^\circ}{Z_{tot}} = \frac{2\angle 60^\circ}{2} = \boxed{1\angle 60^\circ}$

(f)

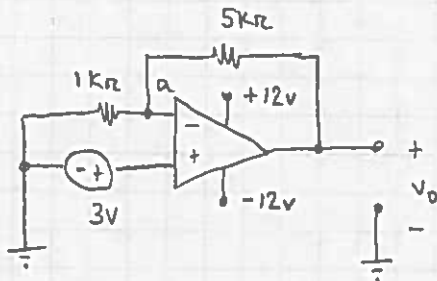

At node a,

$$\frac{V_a}{1k} + \frac{V_a - V_o}{5k} = 0$$

and $V_a = 3v$

$$\frac{3}{1k} + \frac{3 - V_o}{5k} = 0$$


$$15 + 3 - V_o = 0$$

$$V_o = 18$$

However, the op-amp will be saturated because the power supply voltages are only $\pm 12v$.

Therefore, $\boxed{V_o = 12v}$.

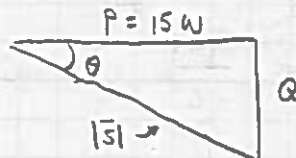(g) A leading PF tells us that $\theta_I > \theta_V$, so the power angle $\theta = \theta_V - \theta_I$ is negative



Power triangle


With a leading PF of 0.7, $\theta = -\cos^{-1}(0.7)$
 $= -45.57^\circ$

From the triangle, $Q = P \cdot \tan(\theta)$
 $= 15 \times \tan(-45.57^\circ)$
 $= -15.30 \text{ VAR}$


and apparent power $|S| = \sqrt{P^2 + Q^2}$

$$|S| = 21.43 \text{ VA}$$

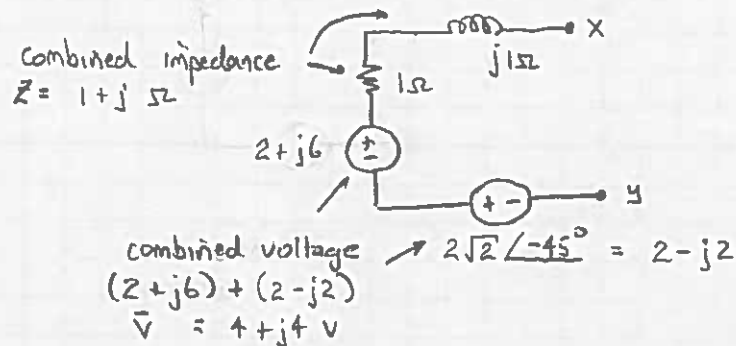(h) Rearranging the series sources and impedances




Source transformation

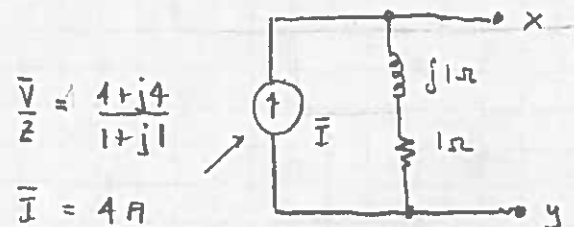


Question 2

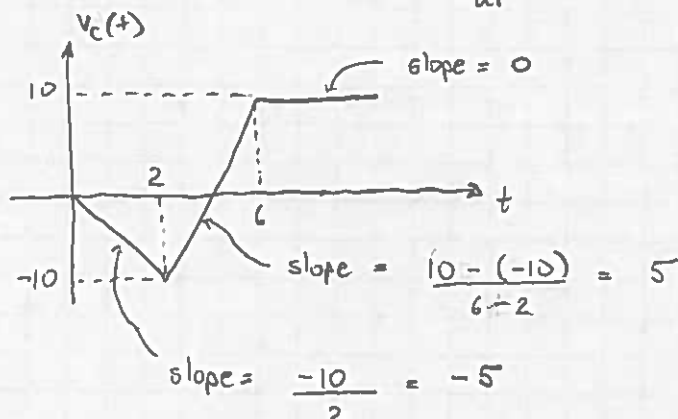
(a) For the capacitor, $i(t) = C \frac{dv(t)}{dt}$, where $C = 0.1 \text{ F}$



The current, power, and energy waveforms

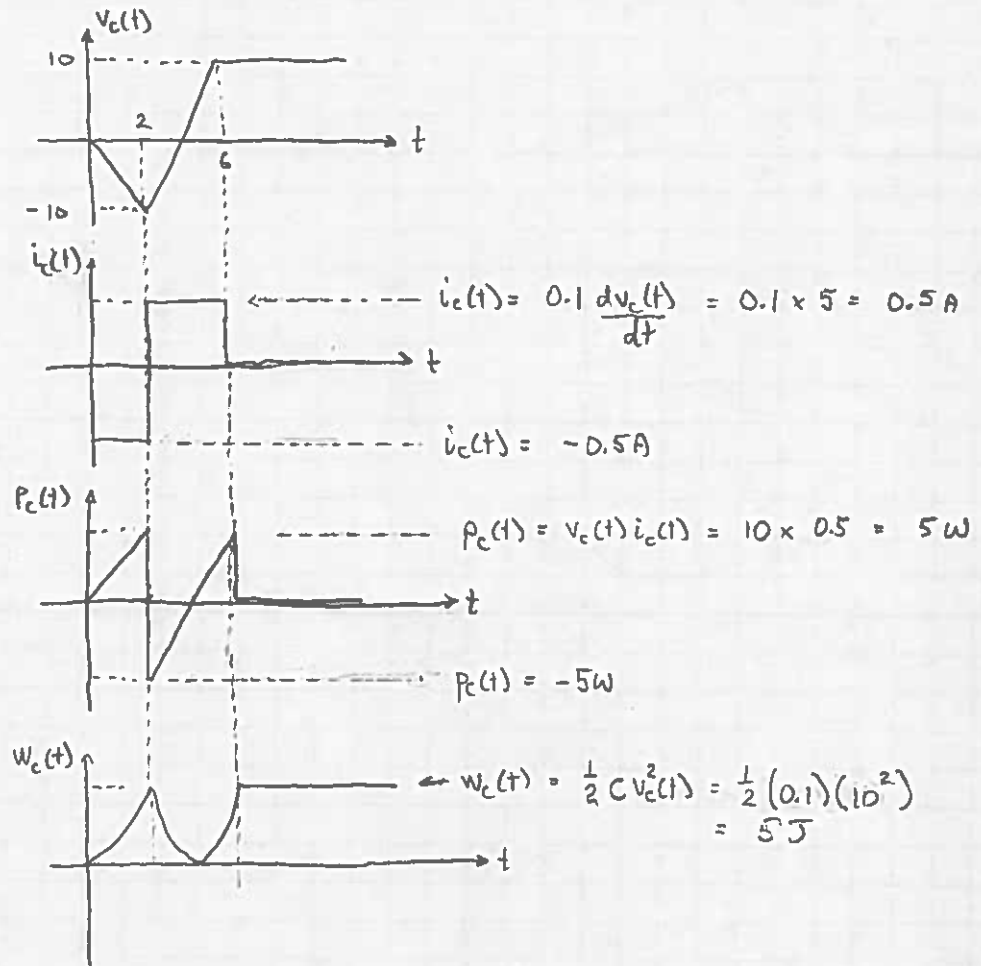

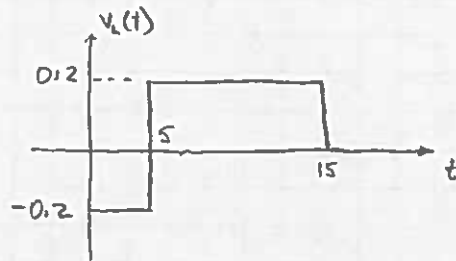(b) For the inductor, $i_L(t) = \frac{1}{L} \int_{t_1}^{t_2} v_L(t) dt + v_L(t_1)$, $L = 0.5 \text{ H}$



First interval: $0 \leq t \leq 5$, $i_L(t) = \frac{1}{0.5} \int_0^t (-0.2) dt + -1$

$\uparrow i_L(0)$

$$= 2 \left[-0.2t \right] \Big|_0^t - 1$$

$$= -0.4t - 1$$


Second interval: $5 \leq t \leq 15$,
$$i_L(t) = 2 \int_5^t 0.2 dt + i_L(5)$$

where $i_L(5) = -0.4(5) - 1 = -3 \text{ A}$


so
$$i_L(t) = 2 \left[0.2t \right]_5^t - 3 = 0.4t - 0.4(5) - 3 = 0.4t - 5$$

Finally, for $t \geq 15$,
$$i_L(t) = i_L(15) = 0.4(15) - 5 = 1 \text{ A}$$

The current and power waveforms

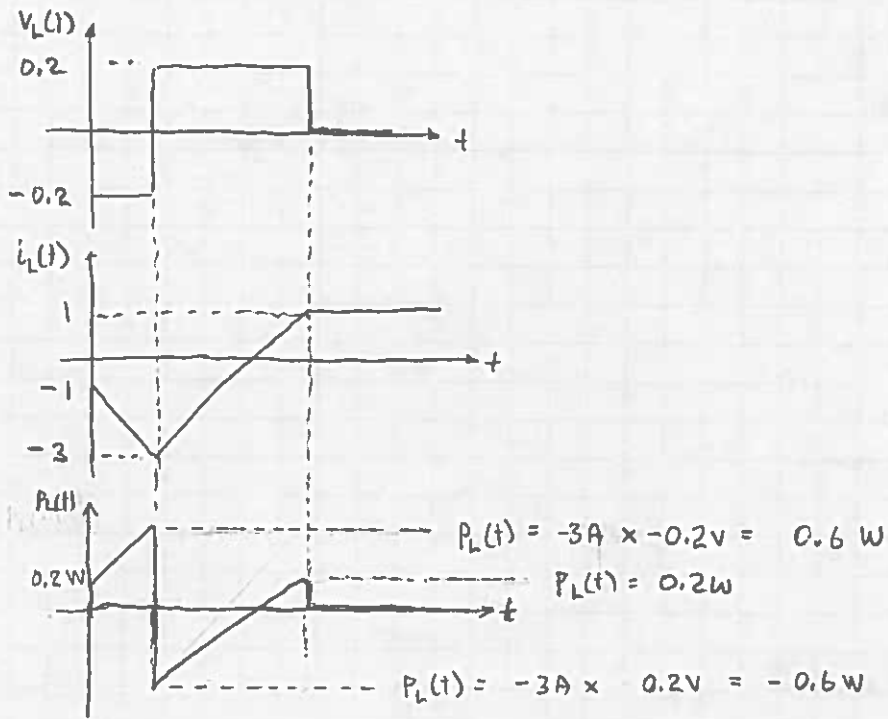

Question 3

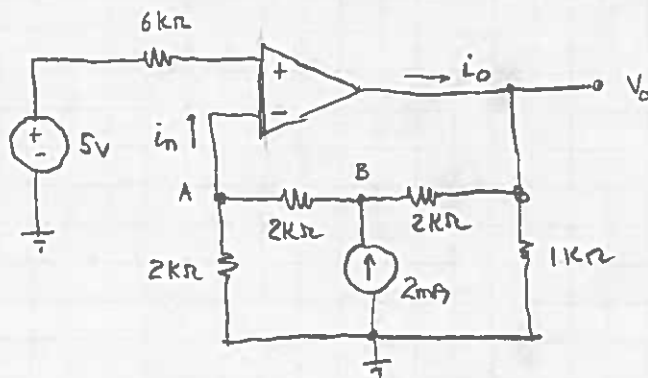

(a) Setting up for the node-voltage method

$$\text{node A: } \frac{V_A}{2K} + \frac{V_A - V_B}{2K} + i_n = 0$$

$$2V_A - V_B = 0$$

so $V_B = 2V_A$, and we know $V_A = 5V$

Then $V_B = 10V$.

$$\text{node B: } \frac{V_B - V_A}{2K} - 0.002 + \frac{V_B - V_D}{2K} = 0$$

$$V_B - V_A - 4 + V_B - V_D = 0$$

$$\text{so } V_D = 2V_B - V_A - 4$$

$$= 2(10) - 5 - 4 = \boxed{11V}$$


(b) At node V_D ,

$$\frac{V_D}{1K} + \frac{V_D - V_B}{2K} - i_o = 0$$

$$2V_D + V_D - V_B = (2K)i_o$$

$$i_o = \frac{3V_D - V_B}{2K} = \frac{33 - 10}{2K} = \boxed{11.5mA}$$

(c)

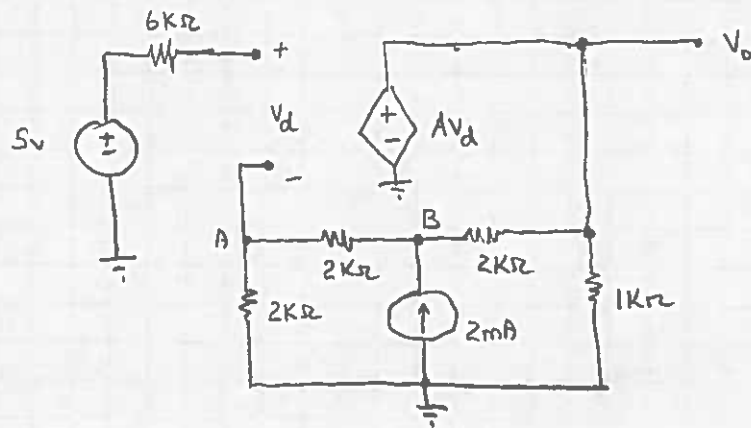

node A:

$$\frac{V_A}{2K} + \frac{V_A - V_B}{2K} = 0$$

$$2V_A - V_B = 0$$

so $V_B = 2V_A$, only this time, we don't know V_A . (1)

node B : unchanged from above $V_o = 2V_B - V_A - 4$

and from (1) $V_o = 2(2V_A) - V_A - 4$
 $= 3V_A - 4$ (2)

At the op-amp input terminals, $V_d = 5 - V_A$

and $V_o = AV_d = 100(5 - V_A)$ (3)

so $V_o = 500 - 100V_A$

$V_A = \frac{V_o - 500}{-100} = \frac{500 - V_o}{100}$ (4)

Substitute (4) into (3)

$$V_o = 3V_A - 4 = 3\left(\frac{500 - V_o}{100}\right) - 4$$

$$V_o = 15 - 0.03V_o - 4$$

$$V_o(1.03) = 11$$

so $V_o = 10.68 \text{ V}$ ← for an ideal opamp, this should be 11v

and $V_d = 5 - V_A$, where, from (2),


$$V_o = 3V_A - 4, \text{ so } V_A = \frac{V_o + 4}{3}$$

$$= \frac{10.68 + 4}{3} = 4.89 \text{ v}$$

Finally $V_d = 5 - 4.89 = 0.11 \text{ v}$ ← for an ideal opamp, this should be zero.

Question 4 [revised solution]

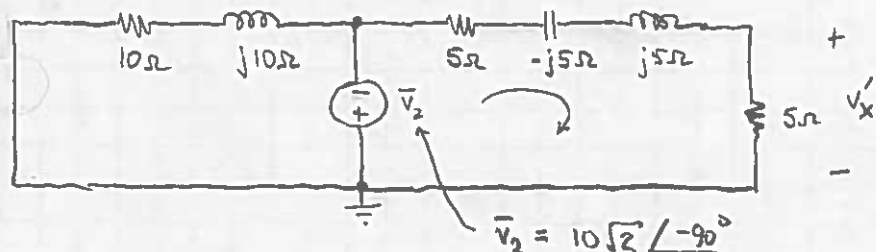(a) Let's zero \bar{V}_1 and \bar{I}_1 to start




In the right-hand portion of this circuit, we have a simple voltage divider

$$\bar{V}_x' = -\bar{V}_2 \times \frac{5}{5 - j5 + j5 + 5} = 0.5\bar{V}_2$$

$$\bar{V}_2 = 10\sqrt{2} \angle -90^\circ, \quad \text{so } \bar{V}_x' = \frac{-5\sqrt{2} \angle -90^\circ}{5\sqrt{2} \angle 90^\circ}$$

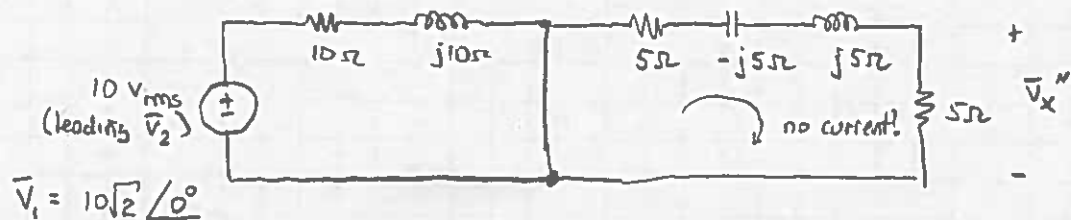
Next, let's zero \bar{V}_2 and \bar{I}_1 ,



There is no voltage or current in the right-hand portion of this circuit!

$$\bar{V}_x'' = 0.$$

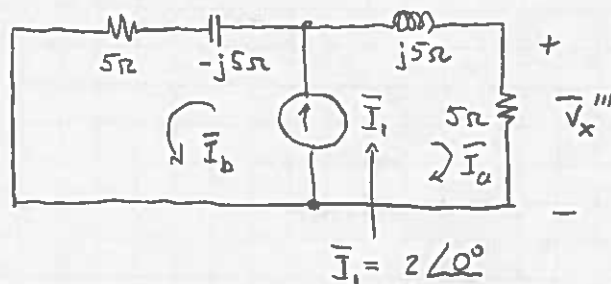Finally, the current source \bar{I}_1 , acting alone



Here, we have a current divider, and we need \bar{I}_a to find

$$\bar{V}_x''' = 5\bar{I}_a$$


By inspection,
$$\bar{I}_a = \frac{(5 - j5) \times 2}{5 - j5 + j5 + 5} = \frac{10 - j10}{10}$$

giving
$$\bar{V}_x''' = \frac{5(10 - j10)}{10} = 5 - j5 = 5\sqrt{2} \angle -45^\circ$$

By superposition, $\bar{V}_x = \bar{V}_x' + \bar{V}_x'' + \bar{V}_x'''$

$$\begin{aligned}\bar{V}_x &= 5\sqrt{2} \angle 90^\circ + 0 + 5 - j5 \\ &= -j5\sqrt{2} + 5 - j5 \\ &= 2.5 + j2.071 = 5.42 \angle -22.5^\circ\end{aligned}$$

(b) Phasor diagram

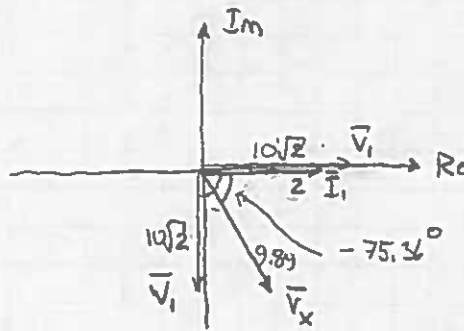

(c) $\bar{V}_2 = 10\sqrt{2} \angle -90^\circ$, and $\bar{I} = 5\sqrt{2} \angle -45^\circ$

$$\text{Complex power } \bar{S} = \frac{1}{2} \bar{V}_2 \bar{I}^* = \frac{1}{2} (10\sqrt{2} \angle -90^\circ) (5\sqrt{2} \angle 45^\circ)$$

$$\bar{S} = 50 \angle -45^\circ$$

or in rectangular representation

$$\bar{S} = P + jQ = 50 \cos(-45^\circ) + j50 \sin(-45^\circ)$$

$$P = 50/\sqrt{2} \text{ W}$$

$$Q = -50/\sqrt{2} \text{ VAR}$$

The power angle $\theta = -45^\circ$, so power factor is $1/\sqrt{2}$ leading

Question 5

(a) Under full load, the motor is providing $P_{out} = 15 \text{ HP}$ at 1200 rpm

$$\text{The torque } T_{out} = \frac{P_{out}}{\omega_m} = \frac{15 \times 746}{1200 \times 2\pi/60} = 89.047 \text{ Nm}$$

Since there are no rotational losses, $P_{dev} = P_{out}$

Losses in the armature and field

$$P_F = \frac{V_T^2}{R_F} = \frac{250^2}{50} = \boxed{1250 \text{ W}}$$

$$I_A = I_L - I_F = 54.5 - \frac{250}{50} = 49.5 \text{ A}$$

$$P_A = I_A^2 R_A = (49.5)^2 \times 0.484 = \boxed{1185.9 \text{ W}}$$

The induced voltage, by KVL,

$$E_A = V_T - I_A R_A = 250 - (49.5)(0.484) = \boxed{226.04 \text{ V}}$$

Efficiency: $P_{in} = V_T I_L = (250)(54.5) = 13,625 \text{ W}$

$$P_{out} = 15 \text{ HP} \times 746 = 11,190 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \boxed{82.1\%}$$

(b) With $n_m = 0$, $E_A = 0$ since $E_A = k\phi\omega_m$.

From part (a), we know the machine constant

$$\text{At } n_m = 1200 \text{ rpm, } E_A = 226.04 \text{ V}$$

$$k\phi = \frac{E_A}{\omega_m} = \frac{226.04}{1200 \times 2\pi/60} = 1.799$$

$$\text{Because } E_A = 0, \quad I_A = \frac{V_T - E_A}{R_A} = \frac{250}{0.484} = 516.53 \text{ A}$$

$$\text{so } T_{dev} = k\phi I_A = 1.799 \times 516.53 = 929.12 \text{ Nm}$$

$$T_{out} = T_{dev} = \boxed{929.12 \text{ Nm}}$$

$$P_{out} = \boxed{0 \text{ W}}$$

↑
since $n_m = 0$.
 $\omega_m = 0$.

(c) Assuming the same T_{out} , and adding T_{rot} to it:

$$T_{dev} = T_{out} + T_{rot} = 89.047 + 10 = 99.047 \text{ Nm}$$

This will cause an increase in armature current

$$I_A = \frac{T_{dev}}{k\phi} = \frac{99.047}{1.799} = 55.057 \text{ A}$$

And by KVL,
$$E_A = V_T - I_A R_A = 250 - (55.057)(0.484) = 223.35 \text{ V}$$

And
$$\omega_m = \frac{E_A}{k\phi} = \frac{223.35}{1.799} = 124.15 \text{ rad/sec}$$

$$n_m = \omega_m \times \frac{60}{2\pi} = \boxed{1185.58 \text{ rpm}}$$