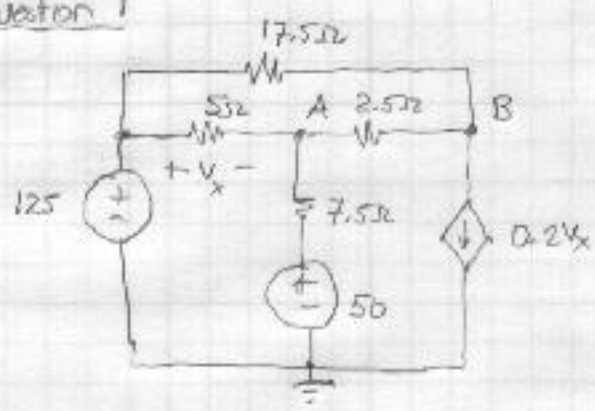


22-141 80 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS



Question 1



Node-voltage equations

$$A: \frac{V_A - 125}{5} + \frac{V_A - 50}{7.5} + \frac{V_A - V_B}{2.5} = 0$$

$$B: \frac{V_B - V_A}{2.5} + \frac{V_B - 125}{17.5} + 0.2V_x = 0$$


We also have $V_x = 125 - V_A$

Solve to find $V_A = 77.02$, $V_B = 62.02$

$$\text{Current in the dependent source: } i = 0.2V_x = 0.2(125 - 77.02) = 9.6 \text{ A}$$

$$\text{so } P = +9.6V_B = 595 \text{ W (absorbed)}$$

Question 2

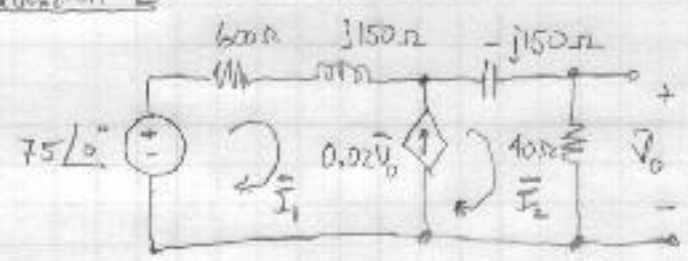

Try mesh-current method to find $\bar{V}_2 = \bar{V}_0$.

$$\bar{I}_1 / \bar{I}_2: -75 + (600 + j150)\bar{I}_1 + (40 - j150)\bar{I}_2 = 0$$

$$\text{Between meshes } \bar{I}_2 - \bar{I}_1 = 0.02\bar{V}_0$$


$$\text{and we also have } \bar{V}_0 = 40\bar{I}_2$$

$$\text{Solve to get } \bar{I}_1 = 0.06 + j0.045, \bar{I}_2 = 0.3 + j0.225$$



So $\bar{V}_o = 40 \bar{I}_2 = 12 + j9 = 15 \angle 25.35^\circ$

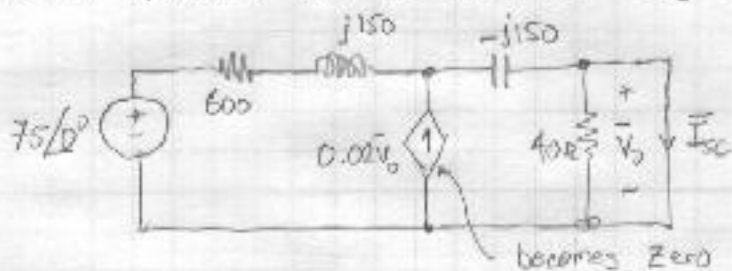Thevenin impedance must be determined using short-circuit current



Have $\bar{V}_o = 0$

We have $\bar{I}_{sc} = \frac{75}{600 + j150 - j150} = 0.125 \text{ A}$

Hence $Z_t = \frac{\bar{V}_o}{\bar{I}_{sc}} = \frac{12 + j9}{0.125} = 96 + j72$

(b) Z_t : $\frac{96\Omega}{R=96} + j72\Omega \leftarrow j\omega L = j72, \text{ so } L = \frac{72}{2\pi \times 1000} = 11.46 \text{ mH}$

3. When $t = 0^-$,



Try mesh-current method.


$i_1 = 500\mu\text{A}$, and for i_2

$-10 + 20k(i_2 + i_1) + (5k + 10k + 5k)i_2 = 0$

Solve to find $i_2 = 0$, so $V_c = 0$. Hence $V_c(0^-) = 0$.
After switch is closed,



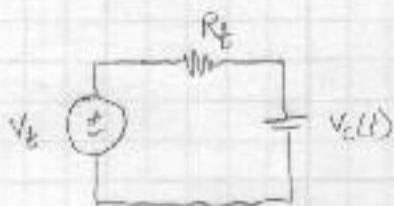We may reduce this to a Thevenin equivalent at the capacitor terminals



$$R_t = 10k \parallel (5k + 5k) = 5k$$

$$V_t = \frac{10k}{10k + 5k + 5k} \times 10 = 5v$$


$$\begin{aligned} \text{We have } V_c(t) &= V_t + (V_0 - V_t)e^{-t/R_t C} \\ &= 5 - 5e^{-t/(5000 \times 0.4 \times 10^{-6})} \\ &= 5 - 5e^{-500t} \end{aligned}$$

(b) Power in the capacitor $p = v_i = VC \frac{dv}{dt}$

$$\begin{aligned} &= (5 - 5e^{-500t})(2500e^{-500t}) \\ &= 12500(e^{-500t} - e^{-1000t}) \end{aligned}$$

(c) $w = \frac{1}{2} CV^2$ At $t=0, w=0$
 $t \rightarrow \infty, w = 5 \mu J$

Question 4

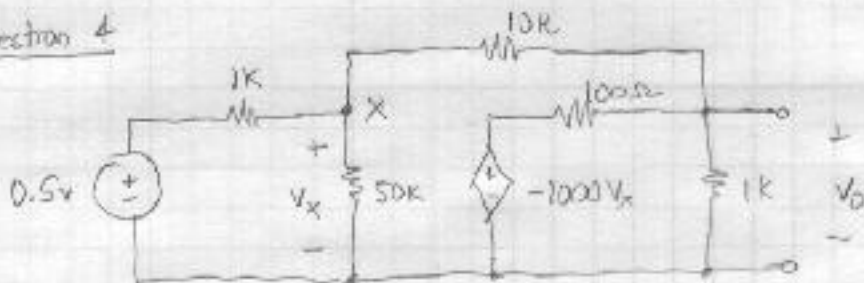

Node-voltage method:


$$\text{At } X: \frac{V_x - 0.5}{1k} + \frac{V_x - V_0}{10k} + \frac{V_x}{50k} = 0$$

$$\text{At } V_0: \frac{V_0 - V_x}{10k} + \frac{V_0 + 1000 V_x}{100} + \frac{V_0}{1k} = 0$$

Solving for V_0 gives $V_0 = -4.99 v$

Question 5

(a) Assuming D_1 off

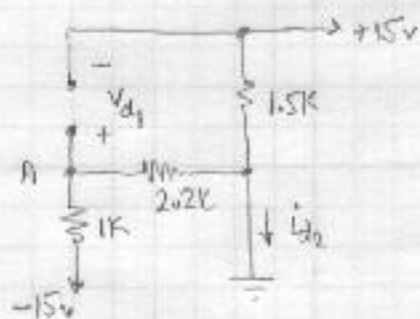


Have simple voltage divider at A

$$V_A = \frac{(0 - (-15)) \cdot 1000}{1000 + 2200}$$

$$\text{so } V_A = -4.69$$

$$\text{therefore, } V_{d1} = V_A - 15 = -19.69$$

(confirms reverse biased)

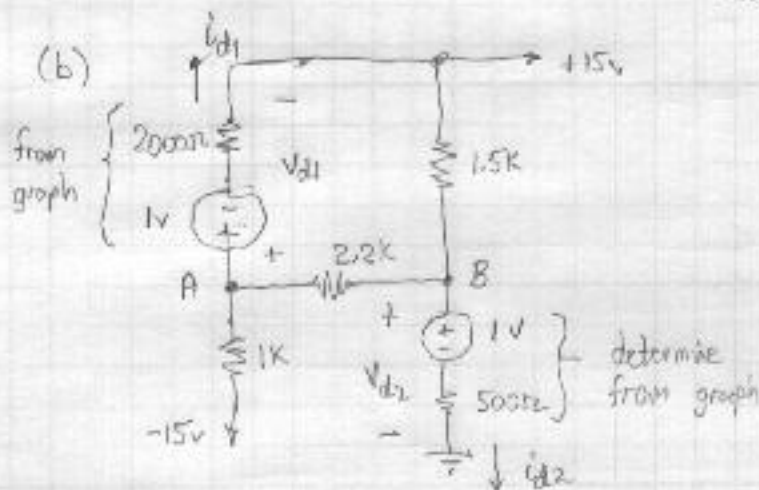

Node-voltage method: two voltage sources in series

$$A: \frac{V_A - (15 + 1)}{2000} + \frac{V_A - V_B}{2.2K} + \frac{V_A - (-15)}{1K} = 0$$

$$B: \frac{V_B - 1}{500} + \frac{V_B - V_A}{2.2K} + \frac{V_B - 15}{1.5K} = 0$$

Solve to find $V_A = -2.79$, $V_B = 3.44$

$$\text{We have } i_{D1} = \frac{V_A - (15 + 1)}{2000} = -9.4 \text{ mA}$$


$$i_{D2} = \frac{V_B - 1}{500} = 4.9 \text{ mA}$$

$$V_{D1} = V_A - 15 = -17.79 \text{ V}$$

$$V_{D2} = V_B = 3.44 \text{ V}$$

Question 6

(a)

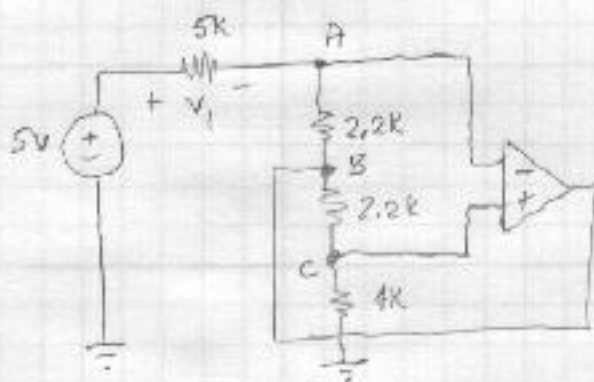

Node-voltage equations at inputs to op amp.


$$A: \frac{V_A - 5}{5k} + \frac{V_A - V_B}{2.2k} = 0$$

$$C: \frac{V_C - V_B}{2.2k} + \frac{V_C}{4k} = 0$$

And we know $V_C = V_A$

Solve to find $V_A = -20V$, so $V_1 = 5 - V_A = 25V$

(b)

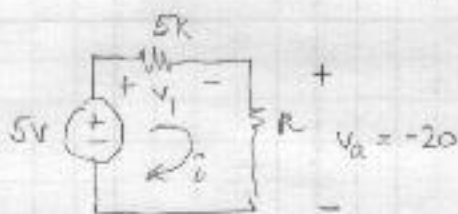

We have $i = \frac{V_1}{5000} = 5mA$, so $R = \frac{V_A}{i} = \frac{-20}{0.005} = -4000\Omega$

(negative resistor?)