

Question 1

(a) By quick inspection of the circuit,

$$V_A = 12 \text{ v}$$

$$V_C = 8 \text{ v}$$

$$V_F = -6 \text{ v}$$

We'll need node-voltage equations (this is the easiest method)

$$\text{Node B: } -2 + \frac{V_B - V_A}{4} + \frac{V_B - V_C}{2} = 0$$

$$-8 + V_B - V_A + 2V_B - 2V_C = 0$$

$$\text{so } -8 + V_B - 12 + 2V_B - 16 = 0$$

$$3V_B = 36$$

$$\boxed{V_B = 12 \text{ v}}$$

$$\text{Node D: } -8 + \frac{V_D - V_C}{11} + \frac{V_D}{1} = 0$$

$$-88 + V_D - V_C + 11V_D = 0$$

$$\text{so } -88 + V_D - 8 + 11V_D = 0$$

$$12V_D = 96$$

$$\boxed{V_D = 8 \text{ v}}$$

$$\text{Node E: } 3 + \frac{V_E - V_F}{10} + \frac{V_E}{5} = 0$$

$$30 + V_E - V_F + 2V_E = 0$$

$$\text{so } 30 + V_E + 6 + 2V_E = 0$$

$$3V_E = -36$$

$$\boxed{V_E = -12 \text{ v}}$$

$$\text{Node G: } 4 + \frac{V_G - V_A}{3} + \frac{V_G - V_F}{6} = 0$$


$$24 + 2V_G - 2V_A + V_G - V_F = 0$$

$$\text{so } 24 + 2V_G - 24 + V_G + 6 = 0$$

$$3V_G = -6$$

$$\boxed{V_G = -2}$$

(b) Power in the sources

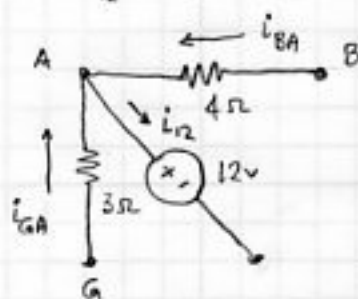At A: $V_{12} = 12V$ 

$$i_{BA} = \frac{V_B - V_A}{4} = 0$$

$$i_{GA} = \frac{V_G - V_A}{3} = \frac{-2 - 12}{3} = -14/3 \text{ A}$$

$$\begin{aligned} \text{Power } P_{12} &= V_{12} i_{12} \\ &= 12 \times \frac{-14}{3} \\ &= -56 \text{ W} \end{aligned}$$

$$\text{At B: } P_{2A} = -2 \times 12 = -24 \text{ W}$$

$$\text{At C: } i_{BC} = \frac{V_B - V_C}{2} = \frac{12 - 8}{2} = 2 \text{ A}$$

$$i_{DC} = \frac{V_D - V_C}{11} = \frac{8 - 8}{11} = 0$$

$$\text{so } i_{BV} = i_{BC} + i_{DC} = 2 \text{ A}$$

$$P_{BV} = 8 \times 2 = 16 \text{ W}$$

$$\text{At D: } P_{DA} = -8 \times 8 = -64 \text{ W}$$

$$\text{At E: } P_{EA} = 3 \times -12 = -36 \text{ W}$$


$$\text{At F: } i_{GF} = \frac{V_G - V_F}{6} = \frac{-2 + 6}{6} = 2/3 \text{ A}$$

$$i_{EF} = \frac{V_E - V_F}{10} = \frac{-12 + 6}{10} = -3/5 \text{ A}$$

$$\text{so } i_{6V} = \frac{2}{3} - \frac{3}{5} = \frac{1}{15} \text{ A}$$

$$P_{6V} = -6 \times \frac{1}{15} = -2/5 \text{ W}$$

$$\text{At G: } P_{GA} = 4 \times -2 = -8 \text{ W}$$

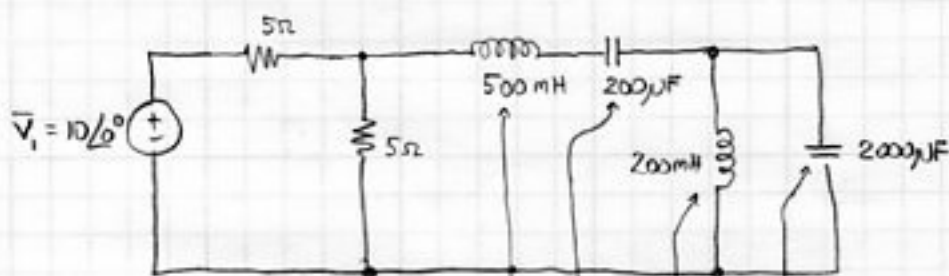Question 2Consider $V_1(t)$ acting alone

$$Z_L = j\omega L$$

$$= j(100) \times 0.5$$

$$= j50\Omega$$

$$Z_C = 1/j\omega C$$

$$= -j/(100 \times 200 \times 10^{-6})$$

$$= -j50\Omega$$

$$Z_C = 1/j\omega C$$

$$= -j/(100 \times 2000 \times 10^{-6})$$


$$= -j5\Omega$$

$$Z_L = j\omega L$$

$$= j(100) \times 0.2$$

$$= j20\Omega$$

Circuit simplifies to

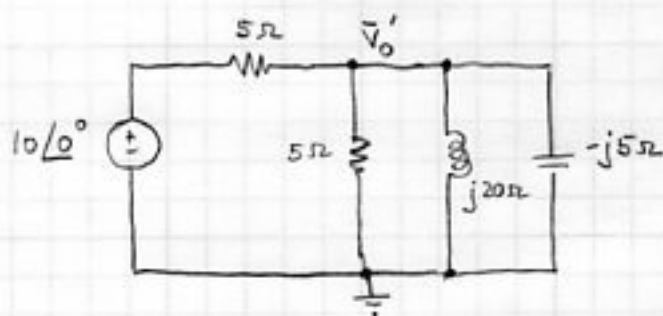

$$\text{At } \bar{V}'_o, \quad \frac{\bar{V}'_o - 10}{5} + \frac{\bar{V}'_o}{j20} + \frac{\bar{V}'_o}{-j5} + \frac{\bar{V}'_o}{5} = 0$$

$$\frac{\bar{V}'_o - 10}{5} - j\frac{\bar{V}'_o}{20} + j\frac{\bar{V}'_o}{5} + \frac{\bar{V}'_o}{5} = 0$$

$$4\bar{V}'_o - 40 - j\bar{V}'_o + 4j\bar{V}'_o + 4\bar{V}'_o = 0$$


$$(8 + j3)\bar{V}'_o = 40$$

$$\bar{V}'_o = \frac{40}{8 + j3}$$

$$\text{so } \bar{V}'_o = \frac{40(8 - j3)}{8^2 + 3^2} = \frac{320 - j120}{73}$$

$$\text{and } \bar{V}_o' = 4.3836 - j1.6438 \\ = 4.6816 \angle -20.556^\circ$$

Now consider $V_2(t)$ acting alone

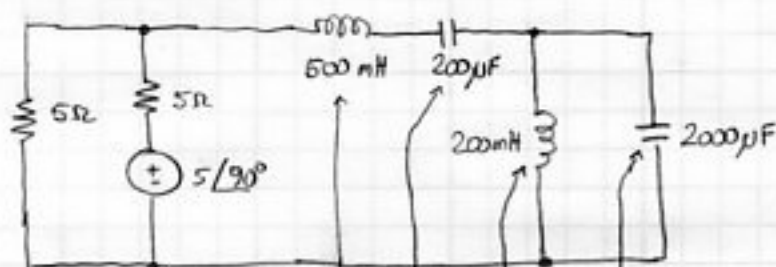

$$Z_L = j\omega L \\ = j(50)(0.5) \\ = j25\Omega$$

$$Z_C = 1/j\omega C \\ = -j/(50 \times 200 \times 10^{-6}) \\ = -j100\Omega$$

$$Z_C = 1/j\omega C \\ = -j/(50 \times 2000 \times 10^{-6}) \\ = -j10\Omega$$


$$Z_L = j\omega L \\ = j(50)(0.2) \\ = j10\Omega$$

The parallel LC connection gives

$$Z_{eq} = j10\Omega \parallel -j10\Omega = \frac{(j10)(-j10)}{j10 - j10} = \infty$$

This is an open circuit!

Circuit simplifies to

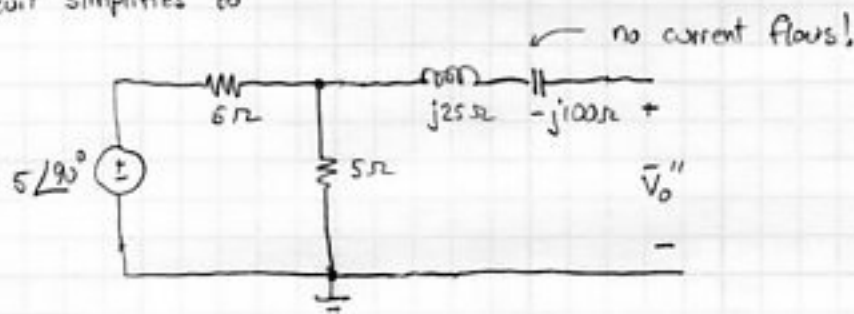

$$\text{by inspection; } \bar{V}_o'' = \frac{5}{5+5} \times 5\angle 90^\circ \\ = 2.5\angle 90^\circ$$

Therefore, $V_0'(t) = 4.6816 \cos(100t - 20.566^\circ)$


$$V_0''(t) = 2.5 \cos(50t + 90^\circ)$$

Finally, $V_0(t) = V_0'(t) + V_0''(t)$

$$= 4.6816 \cos(100t - 20.566^\circ) + 2.5 \cos(50t + 90^\circ)$$


[cannot simplify more]

(b) Phasor diagrams

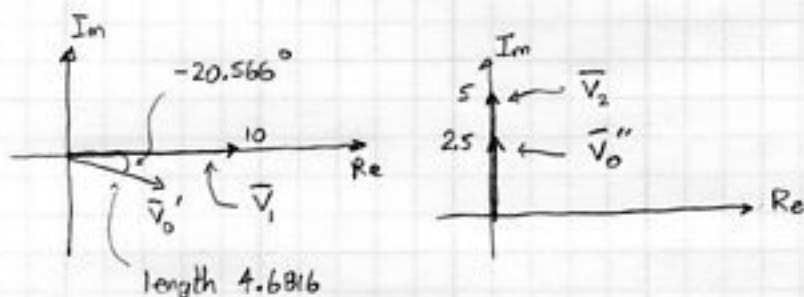

Question 3

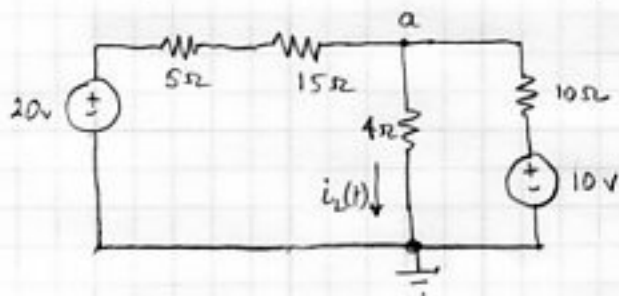(a) For $t < 0$, the circuit in DC steady-state is



$$\text{At node } a, \quad \frac{V_a - 20}{5 + 15} + \frac{V_a}{4} + \frac{V_a - 10}{10} = 0$$


$$V_a - 20 + 5V_a + 2V_a - 20 = 0$$

$$8V_a = 40$$

$$V_a = 5 \text{ V}$$

$$\text{Therefore } I_0 = i_L(t) \Big|_{t=0^-} = \frac{5 \text{ V}}{4 \Omega} = 1.25 \text{ A}$$

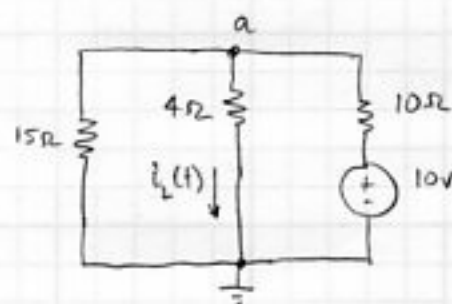Switch S_1 closes. At DC steady-state, $t \rightarrow \infty$,



$$\text{At node } a, \quad \frac{V_a - 10}{10} + \frac{V_a}{4} + \frac{V_a}{15} = 0$$

$$6V_a - 60 + 15V_a + 4V_a = 0$$

$$25V_a = 60, \quad \text{so } V_a = \frac{60}{25} = 2.4$$

$$\text{Therefore } i_L(t) \Big|_{t \rightarrow \infty} = \frac{2.4}{4} = 0.6 \text{ A}$$

Using the assumed solution,

$$i_L(t) = K_1 + K_2 e^{-t/\tau}$$


$$\text{At } t = 0^-: \quad i_L(0^-) = 1.25 = K_1 + K_2$$

$$\text{At } t \rightarrow \infty: \quad i_L(\infty) = 0.6 = K_1$$

$$\text{so } K_1 = 0.6$$

$$K_2 = 0.65$$

And the time constant

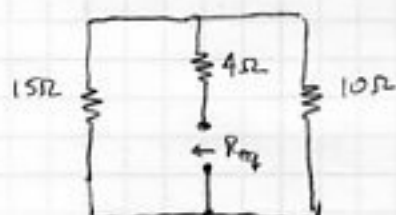


$$R_{eq} = 10 \parallel 15 + 4$$

$$= 6 + 4$$

$$= 10 \Omega$$

$$\text{so } \tau = \frac{L}{R} = \frac{10 \text{ H}}{10 \Omega} = 1 \text{ second}$$
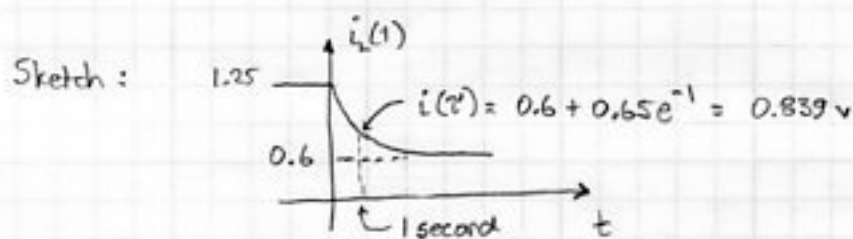
$$\text{Finally, } i_L(t) = 0.6 + 0.65e^{-t}$$




(b) Need $V_L(t)$, so we may use $V_L(t) = L \frac{di_L(t)}{dt}$

$$\begin{aligned} V_L(t) &= L \frac{d}{dt} [0.6 + 0.65e^{-t}] \\ &= 10 [-0.65e^{-t}] \\ &= -6.5e^{-t} \end{aligned}$$



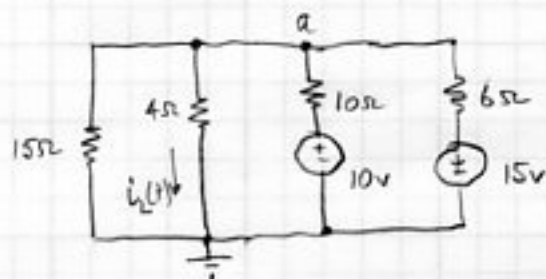(c) At $t=10\text{s}$, $i_L(10) = 0.6 + 0.65e^{-10}$
 $= 0.60003 \approx 0.6$

At $t \rightarrow \infty$, circuit becomes



At node a ,

$$\begin{aligned} \frac{V_a}{15} + \frac{V_a}{4} + \frac{V_a - 10}{10} + \frac{V_a - 15}{6} &= 0 \\ 4V_a + 15V_a + 6V_a - 60 + 10V_a - 150 &= 0 \\ 35V_a &= 210 \\ V_a &= 6 \text{ V} \end{aligned}$$

so $i_L(t) \Big|_{t \rightarrow \infty} = \frac{6}{4} = 1.50 \text{ A}$


Equivalent resistance when $t > 10s$.



$$\begin{aligned} R_{eq} &= (15 // 10) // 6 + 4 \\ &= 6 // 6 + 4 \\ &= 3 + 4 \\ &= 7 \Omega \end{aligned}$$

New time constant for $t > 10s$, $\tau = \frac{L}{R} = \frac{10}{7}$ seconds

Question 4

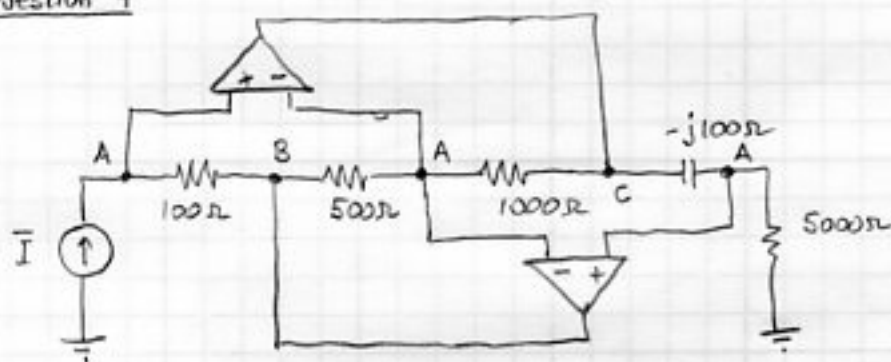

Note that the summing point constraints force three nodes to have the same voltage V_A .

At left-most node A: $-\bar{I} + i_p + \frac{\bar{V}_A - \bar{V}_B}{100} = 0$

so $\bar{V}_A - \bar{V}_B = 100 \bar{I}$ (1)

At middle node A: $\frac{\bar{V}_A - \bar{V}_B}{500} + \frac{\bar{V}_A - \bar{V}_C}{1000} + i_n + i_n = 0$

$$\begin{aligned} 2\bar{V}_A - 2\bar{V}_B + \bar{V}_A - \bar{V}_C &= 0 \\ 3\bar{V}_A - 2\bar{V}_B - \bar{V}_C &= 0 \end{aligned} \quad (2)$$

At right-most node A: $\frac{\bar{V}_A}{5000} + i_p + \frac{\bar{V}_A - \bar{V}_C}{-j100} = 0$

$$\begin{aligned} \bar{V}_A + j50\bar{V}_A - j50\bar{V}_C &= 0 \\ \bar{V}_A (1 + j50) &= j50\bar{V}_C \end{aligned} \quad (3)$$

From (1), $\bar{V}_B = \bar{V}_A - 100\bar{I}$

Substitute into (2),

$$3\bar{V}_a - 2(\bar{V}_a - 100\bar{I}) - \bar{V}_c = 0$$

$$\bar{V}_a + 200\bar{I} = \bar{V}_c$$

Substitute into (3),

$$\bar{V}_A (1 + j50) = j50(\bar{V}_a + 200\bar{I})$$

$$\bar{V}_c + j50\bar{V}_a = j50\bar{V}_a + j10000\bar{I}$$

$$\text{so } \bar{V}_a = j10000\bar{I}$$


(b) Total impedance $Z_{eq} = \frac{\bar{V}_a}{\bar{I}} = \frac{j10000\bar{I}}{\bar{I}}$
 $= j10000\Omega$

Equivalent circuit



Question 5

(a)

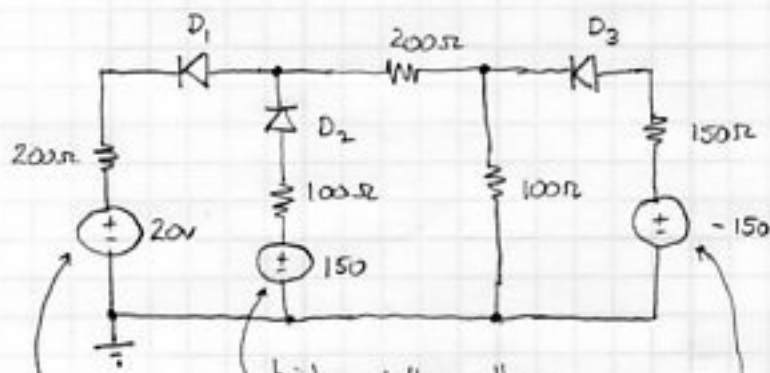


relatively low voltage - looks like D_1 is on. The 150V source looks like it will drive current downward in this branch.

higher voltage than anywhere else in circuit, suggesting that D_2 is on.

large negative voltage, suggesting current downward through the source. Looks like D_3 is off.

D_1 on
 D_2 on
 D_3 off

Ideal analysis:

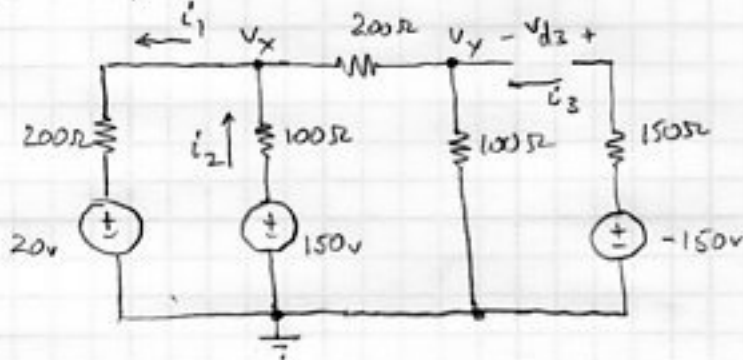

At node v_x : $\frac{v_x - 150}{100} + \frac{v_x - 20}{200} + \frac{v_x - v_y}{200} = 0$

$2v_x - 300 + v_x - 20 + v_x - v_y = 0$

$4v_x - v_y = 320$ (1)

At node V_y : $\frac{V_y - V_x}{200} + \frac{V_y}{100} = 0$

$$V_y - V_x + 2V_y = 0$$

$$V_x = 3V_y \quad (2)$$

Substitute into (1)

$$4(3V_y) - V_y = 320$$

$$12V_y - V_y = 320$$

$$11V_y = 320, \text{ so } V_y = \frac{320}{11} = \boxed{29.09 \text{ V}}$$

and $V_x = 3V_y = \frac{960}{11} = \boxed{87.27 \text{ V}}$

We have $i_1 = \frac{V_x - 20}{200} = 0.336 \text{ A}$ (POSITIVE - good!)

$$i_2 = -\frac{(V_x - 150)}{100} = 0.626 \text{ A}$$
 (POSITIVE - good!)

$$i_3 = 0$$


→ check D_3 voltage $-150 - V_y = -179.09 \text{ V}$
(NEGATIVE - good!)

(b) Need diode models

Segment A: slope = $10 \text{ mA} / (2.7 - 0.7) = 0.005$
so $R_A = 1 / 0.005 = 200 \Omega$

intercept precisely at 0.7 V , so

$$V = 200I + 0.7$$

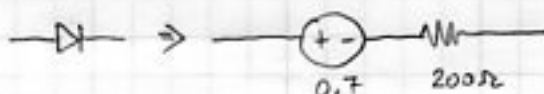


Segment B: $i_B = 0$, so B is an open circuit


Segment C: slope = $20\text{mA} / (-100 + 105) = 0.004$
 so $R_c = 250\Omega$

intercept at -100V , so

$$V = 250i - 100$$

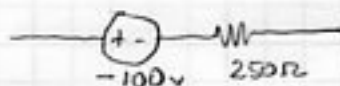


Analyze circuit

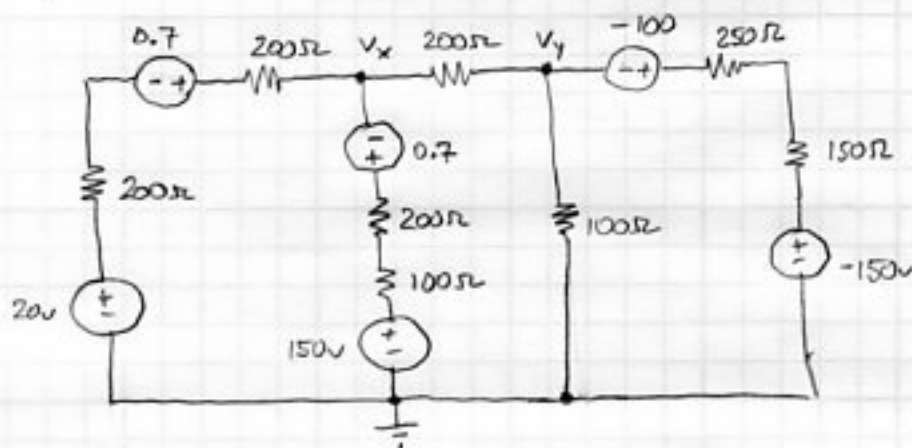

$D_1, D_2 \rightarrow$ segment A
 $D_3 \rightarrow$ operating in breakdown, segment C.

Redraw circuit

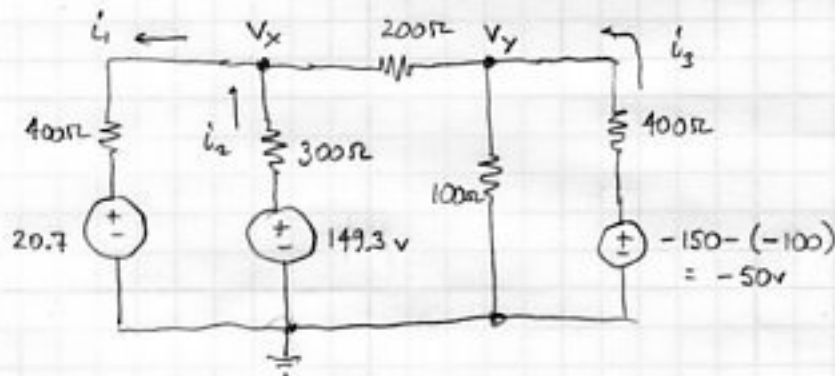

$$\text{At } V_x: \frac{V_x - 20.7}{400} + \frac{V_x - 149.3}{300} + \frac{V_x - V_y}{200} = 0$$

$$3V_x - 62.1 + 4V_x - 597.2 + 6V_x - 6V_y = 0$$

$$13V_x - 6V_y = 659.3 \quad (1)$$

$$\text{At } V_y: \frac{V_y - V_x}{200} + \frac{V_y}{100} + \frac{V_y + 50}{400} = 0$$

$$2V_y - 2V_x + 4V_y + V_y + 50 = 0$$

$$-2V_x + 7V_y = -50 \quad (2)$$

From (2), $-2V_x = -50 - 7V_y$, so $V_x = 25 + \frac{7}{2}V_y$
Substitute into (1)

$$13\left(25 + \frac{7}{2}V_y\right) - 6V_y = 659.3$$

$$325 + \frac{91}{2}V_y = 659.3$$

$$40.5V_y = 334.3$$

$$\text{so } V_y = \boxed{8.254 \text{ v}}$$

$$\text{And } V_x = 25 + \frac{7}{2}V_y = \boxed{53.89 \text{ v}}$$

$$\text{And } i_1 = \frac{V_x - 20.7}{400} = 0.06812 \text{ A}$$

$$\rightarrow V = (0.06812) \times 200 + 0.7 = 14.32 \text{ v}$$

[confirmed on segment A]

$$i_2 = -\frac{(V_x - 149.3)}{300} = 0.318 \text{ A}$$

$$\rightarrow V = (0.318) \times 200 + 0.7 = 64.307 \text{ v}$$

[confirmed on segment A]


$$i_3 = \frac{-50 - V_y}{400} = -0.1456 \text{ A}$$

$$\rightarrow V = (-0.1456) \times 250 - 100 = -136.41 \text{ v}$$

[confirmed on segment C]

Question 6

(a) The circuit model ...

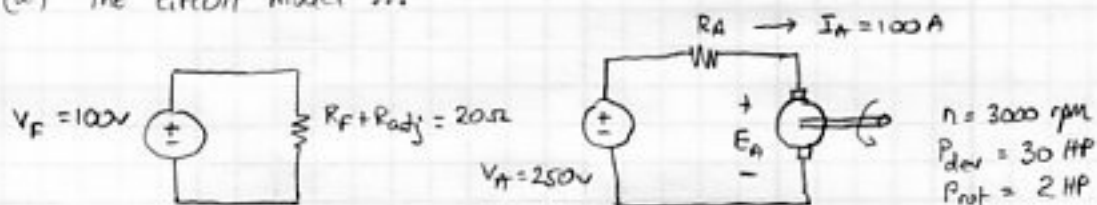

- The armature EMF E_A

We have $P_{dev} = I_A E_A$, so $E_A = \frac{P_{dev}}{I_A}$

$$E_A = \frac{30 \times 746 \text{ W}}{100} = 223.8 \text{ V}$$

- Armature resistance R_A

$$V_A = E_A + I_A R_A, \text{ so } R_A = \frac{V_A - E_A}{I_A}$$

$$R_A = \frac{250 - 223.8}{100} = 0.262 \Omega$$

- Machine constant $k\phi$

Can use $E_A = k\phi \omega_m$, so $k\phi = \frac{E_A}{\omega_m}$

$$k\phi = \frac{223.8}{3000 \times 2\pi/60} = 0.71238$$

- Efficiency η .

$$\begin{aligned} \text{Total output power } P_{out} &= P_{dev} - P_{rot} \\ &= 28 \text{ HP} \\ &= 20888 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{Total electrical input power } P_{in} &= V_A I_A + \frac{V_F^2}{(R_F + R_{adj})} \\ P_{in} &= 250 \times 100 + \frac{100^2}{20} \\ &= 25500 \text{ W} \end{aligned}$$

$$\begin{aligned} \eta &= \frac{P_{out}}{P_{in}} \times 100\% = \frac{20888}{25500} \times 100\% \\ &= 81.91\% \end{aligned}$$

(b) Motor is run with 0 developed power. This means that developed torque $T_{dev} = 0$, and

$$T_{dev} = k\phi I_A, \quad \text{so } I_A = 0.$$

Therefore, $E_A = V_A = 250\text{V}$.

$$\text{And } E_A = k\phi\omega_m, \quad \text{so } \omega_m = \frac{E_A}{k\phi}$$

$$\omega_m = \frac{250}{0.71233} = 350.936 \text{ r/s}$$

$$\text{so } n = 350.936 \times 60 / 2\pi$$

$$n = 3351.19 \text{ rpm (speeds up!)}$$

Wow! 15 pages.