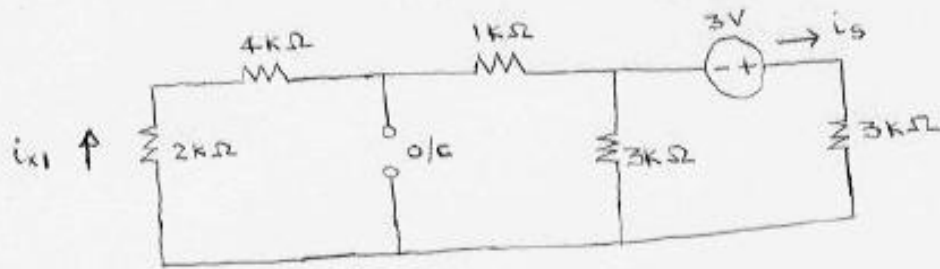


Q1. step #1: consider 3V source only.





Req seen by 3V source = $(7k \parallel 3k) + 3k = \frac{51}{10} k\Omega$

Total current supplied by the source $i_s = \frac{3V}{R_{eq}} = \frac{3V}{\frac{51}{10} k\Omega} = \frac{30}{51} mA$

Current Divider gives $i_{x1} = i_s * \frac{3k}{3k + 7k} = \frac{30}{51} * \frac{3}{10} = \frac{3}{17} mA$

step #2: Consider 1mA source only.

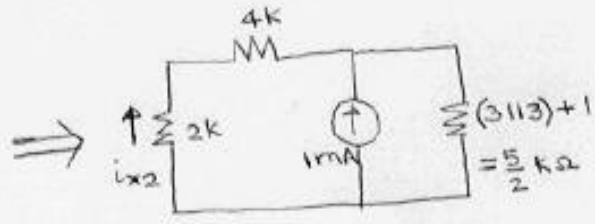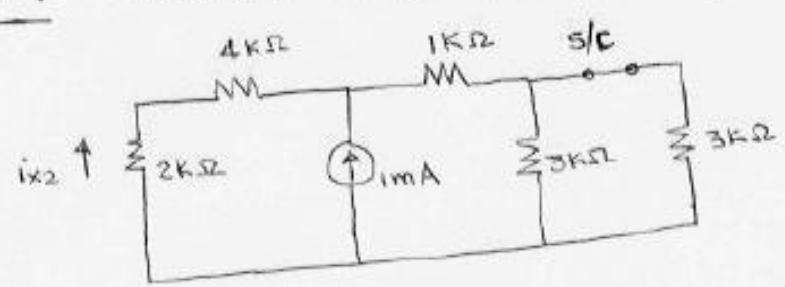

$i_{x2} = -1mA * \frac{5/2 k\Omega}{5/2 k\Omega + 6k\Omega} = -\frac{5}{17} mA$

using current division.

step #3: Apply principle of superposition.


$$i_x = i_{x1} + i_{x2}$$

$$= \frac{3}{17} mA + \left(-\frac{5}{17} mA\right)$$

$$= -\frac{2}{17} mA$$

In decimals, $i_x = -0.1176 mA$

Q2.

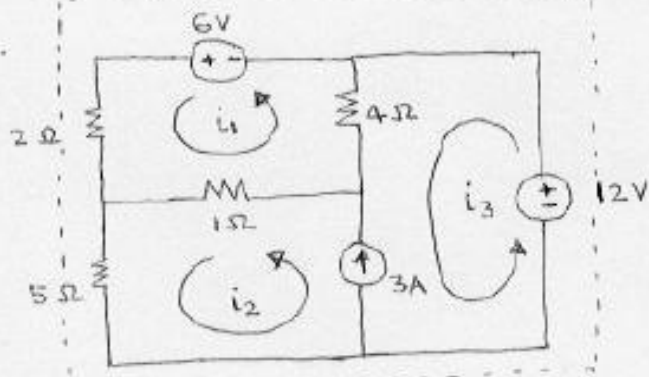

KVL in loop 1:

$$-6 + 2i_1 + 1(i_1 - i_2) + 4(i_1 - i_3) = 0$$

$$\text{i.e., } 7i_1 - i_2 - 4i_3 = 6 \rightarrow \textcircled{1}$$

Observation:

$$i_2 - i_3 = 3 \rightarrow \textcircled{2}$$

KVL for outer loop shown by dotted line:

$$-12 - 6 + 2i_1 + 5i_2 = 0$$

$$\text{i.e., } 2i_1 + 5i_2 = 18 \rightarrow \textcircled{3}$$

Solve $\textcircled{1}$, $\textcircled{2}$ and $\textcircled{3}$ to find i_3 supplied by 12-V source.

$$7i_1 - (i_3 + 3) - 4i_3 = 6$$

$$7i_1 - 5i_3 = 9 \rightarrow \textcircled{4}$$

$$2i_1 + 5(i_3 + 3) = 18$$

$$2i_1 + 5i_3 = 3 \rightarrow \textcircled{5}$$

$$\textcircled{4} \times 2 \quad 14i_1 - 10i_3 = 18$$

$$\textcircled{5} \times 7 \quad 14i_1 + 35i_3 = 21$$

$$\text{subtract} \quad 0 - 45i_3 = -3$$


$$i_3 = \frac{1}{15} \text{ A}$$

Power absorbed or delivered = ? Consider 12-V source.

 \therefore By convention, power is delivered.

$$P_{12V} = 12 * \frac{1}{15} = \frac{4}{5} \text{ W}$$
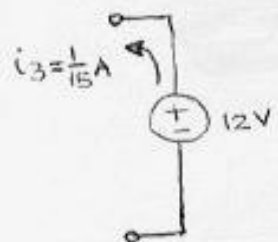
$$\text{In decimals, } P_{12V} = 0.8 \text{ W}$$




Q3.

step #1: Find open-circuit voltage V_{xy} .

Define node y as reference node.

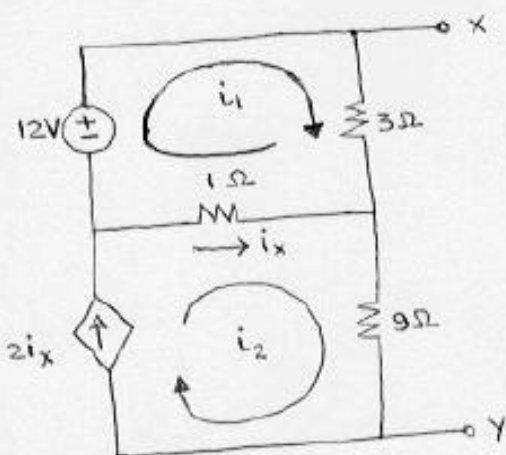$\therefore V_{xy} = V_x - V_y = V_x - 0 = V_x$. V_x needs to be calculated.



observation: $i_2 = 2i_x \rightarrow \textcircled{1}$

observation: $i_2 - i_1 = i_x \rightarrow \textcircled{2}$

substituting $\textcircled{1}$ in $\textcircled{2}$ gives

$$i_2 - i_1 = \frac{i_2}{2}$$

$$-2i_1 + i_2 = 0 \rightarrow \textcircled{3}$$

KVL in loop 1 gives:

$$-12 + 3i_1 + 1(i_1 - i_2) = 0$$


$$\text{i.e., } 4i_1 - i_2 = 12 \rightarrow \textcircled{4}$$

solving $\textcircled{3}$ and $\textcircled{4}$ gives $i_1 = 6\text{A}$ and $i_2 = 12\text{A}$.

$$\therefore V_{xy} = V_x = 3i_1 + 9i_2 = 3 \times 6 + 9 \times 12 = 126\text{V}$$

step #2: Find short-circuit current I_{sc} . Consider node y as

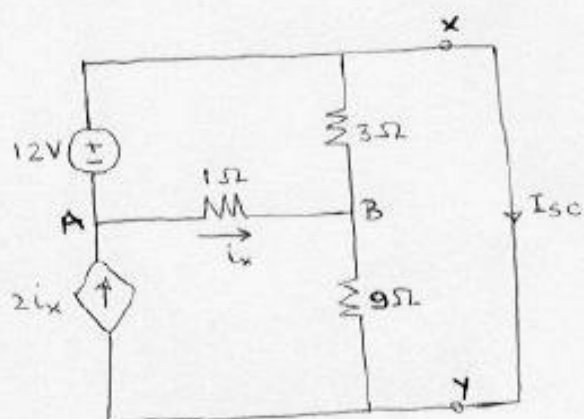reference node i.e. $V_y = 0\text{V}$. Also, $V_x = 0\text{V}$.



From observation,

$$V_x - V_A = 12\text{V}$$

$$\therefore 0 - V_A = 12$$

$$V_A = -12\text{V}$$

V_B needs to be calculated.

KCL at node B gives :

$$\frac{V_B - (-12)}{1} + \frac{V_B - 0}{3} + \frac{V_B - 0}{9} = 0$$

$$V_B = -\frac{108}{13} \text{ V}$$

$$\therefore i_x = \frac{V_A - V_B}{1} = \frac{-12 - \left(-\frac{108}{13}\right)}{1} = -\frac{48}{13} \text{ A}$$

KCL at node Y gives :

$$I_{sc} = 2i_x + \frac{0 - V_B}{9} = -\frac{96}{13} + \frac{12}{13} = -\frac{84}{13} \text{ A}$$


Step #3:

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{V_{xy}}{I_{sc}} = \frac{126}{-84/13} = -\frac{39}{2} \Omega$$


Too bad R_{TH} works out negative.

Step #4:


Thevenin Equivalent Circuit

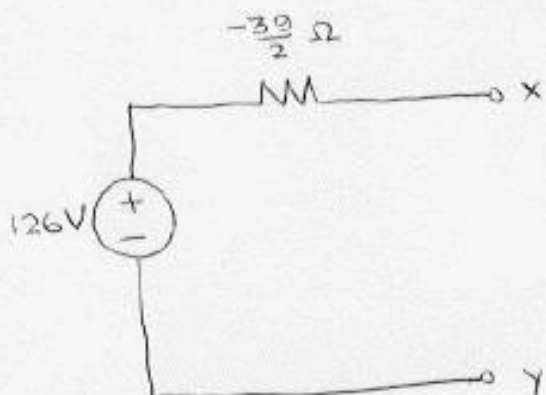

Norton Equivalent Circuit

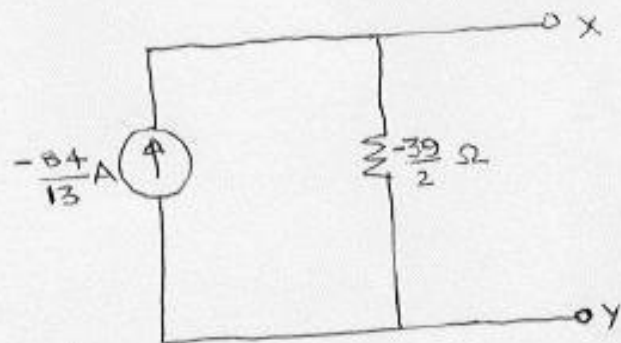

Q4.

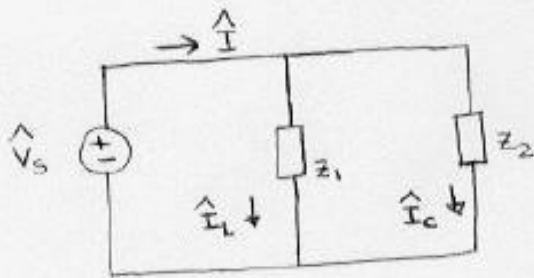

$$Z_1 = Z_L = j\omega L = j * 377 * 10 * 10^{-3} = j 3.77 \Omega = 3.77 \angle 90^\circ \Omega$$

$$Z_2 = Z_R + Z_C = R - \frac{j}{\omega C} = 30 - j * \frac{1}{(377 * 30 * 10^{-6})} = 30 - j 92.417 = 93.368 \angle -71.258^\circ$$

$$\hat{I}_L = \frac{\hat{V}_S}{Z_1} = \frac{120 \angle -45^\circ}{3.77 \angle 90^\circ} = 31.83 \angle -135^\circ \text{ A}$$

$$= -22.507 - j 22.507 \text{ A}$$

$$\hat{I}_C = \frac{\hat{V}_S}{Z_2} = \frac{120 \angle -45^\circ}{93.368 \angle -71.258^\circ} = 1.285 \angle 26.258^\circ \text{ A}$$

$$= 1.1524 + j 0.5685 \text{ A}$$

$$\therefore \text{Applying KCL } \hat{I} = \hat{I}_L + \hat{I}_C$$

$$= -22.507 - j 22.507 + 1.1524 + j 0.5685$$

$$= -21.3546 - j 21.9385 \text{ A}$$

$$= 30.6156 \angle -134.2273^\circ \text{ A}$$

$$\approx 30.62 \angle -134.23^\circ \text{ A}$$

$$i(t) = 30.62 \cos(377t - 134.23^\circ) \text{ A}$$

Note: Either 1- or 2-digit precision is good in phasor analysis questions.