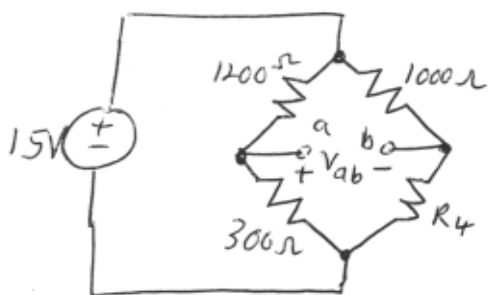


Question 1



(a) V_{ab} measured = $-2V$
Find R_4

(b) Now $R_5 = 200\Omega$ connected from a to b.
Find power in R_5


Soln: (a) with no element between a and b, we can use voltage division:

Call the bottom node 0V, then

$$V_a = \frac{300}{1500} \times 15V = 3V$$

$$V_{ab} = V_a - V_b \Rightarrow V_b = V_a - V_{ab} = 3V - (-2V) = 5V$$
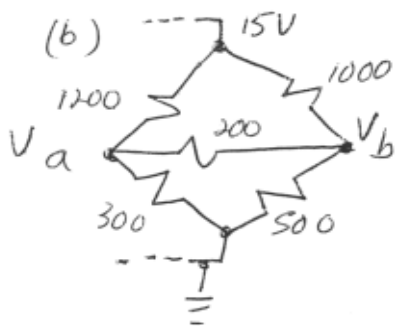
$$\therefore V_b = \frac{R_4}{1000 + R_4} \times 15V = 5V \Rightarrow \boxed{R_4 = 500\Omega}$$



Say we use the node method:

Node a: $\frac{V_a}{300} + \frac{V_a - V_b}{200} + \frac{V_a - 15}{1200} = 0$

$\times 1200$: $4V_a + 6(V_a - V_b) + V_a - 15 = 0$
 $\Rightarrow 11V_a - 6V_b = 15$ (1)

Node b: $\frac{V_b}{500} + \frac{V_b - V_a}{200} + \frac{V_b - 15}{1000} = 0$

$\times 1000$: $2V_b + 5(V_b - V_a) + V_b - 15 = 0$
 $-5V_a + 8V_b = 15$ (2)

$\frac{4}{3} \times (1)$: $\frac{44}{3}V_a - 8V_b = 20$ (3)

(2) + (3): $\frac{29}{3}V_a = 35 \Rightarrow V_a = 3.62V$


From (1) or (2) or (3) $V_b = 4.14V$

or could use $(V_{ab})^2$ ie $(-0.52V)^2$

$P = \frac{V_{ba}^2}{R} = \frac{(0.52V)^2}{200} = 1.35 \times 10^{-3} = \boxed{1.35mW}$

check $I^2 R = \left(\frac{0.52}{200}\right)^2 \times 200 = 1.35mW$

Question 2

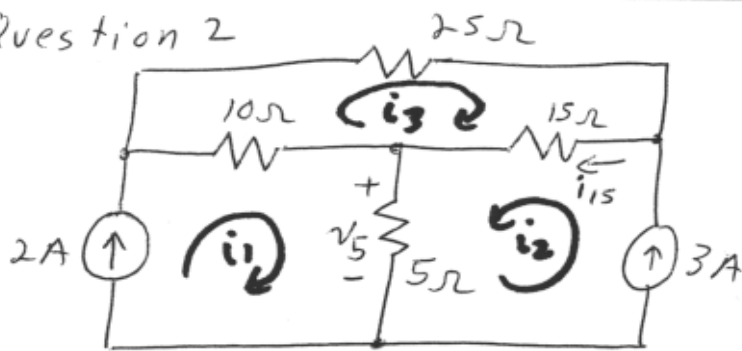

Find v_5
and i_{15}

Soln: Lots of current sources, so Mesh method is a good choice

$$\begin{aligned} \text{Loop 1: } & i_1 = 2A \\ \text{Loop 2: } & i_2 = 3A \end{aligned} \left. \vphantom{\begin{aligned} \text{Loop 1: } \\ \text{Loop 2: } \end{aligned}} \right\} \begin{aligned} \therefore v_5 &= iR \\ &= (i_1 + i_2)R \\ &= 5A \times 5\Omega = \boxed{25V} \end{aligned}$$

$$\text{Loop 3: } 25i_3 + 15(i_2 + i_3) + 10(i_3 - i_1) = 0$$

$$25i_3 + 15(3 + i_3) + 10(i_3 - 2) = 0$$


$$50i_3 = -25$$

$$i_3 = \underline{\underline{-\frac{1}{2}A}}$$

$$\therefore i_{15} = i_2 + i_3 = \boxed{2.5A}$$



Question 3

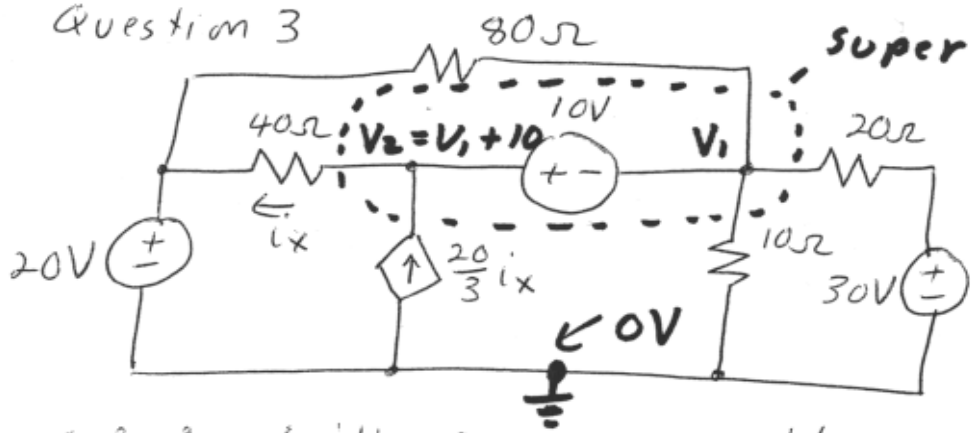

Find power in the dependent source

Soln: With so many voltage sources, there is just one node equation, i.e., for the super node:

$$\frac{V_2 - 20}{40} - \frac{20}{3} i_x + \frac{V_1 - 20}{80} + \frac{V_1}{10} + \frac{V_1 - 30}{20} = 0 \quad (1)$$

But $V_2 = V_1 + 10$ and $i_x = \frac{(V_1 + 10) - 20}{40}$

Substituting both expressions into (1) gives:


$$\frac{V_1 - 10}{40} + \frac{1}{6} (10 - V_1) + \frac{V_1 - 20}{80} + \frac{V_1}{10} + \frac{V_1 - 30}{20} = 0 \quad (2)$$

$$240 \times (1) : 6V_1 - 60 + 400 - 40V_1 + 3V_1 - 60 + 24V_1 + 12V_1 - 360 = 0$$

or $5V_1 = 80 \Rightarrow \underline{V_1 = 16V}$

$\therefore \underline{V_2 = 26V}$
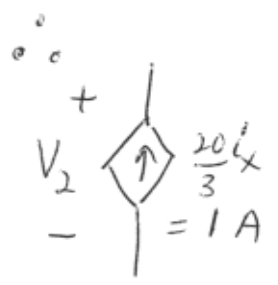
$$i_x = \frac{26 - 20}{40} = \underline{\underline{\frac{6}{40} A}}$$




← This is not passive notation

$\therefore P = -vi$
 $= -26 \times 1 = -26W$ ← supplying power

$\therefore 26W$ is being generated by the dependent source



Question 4

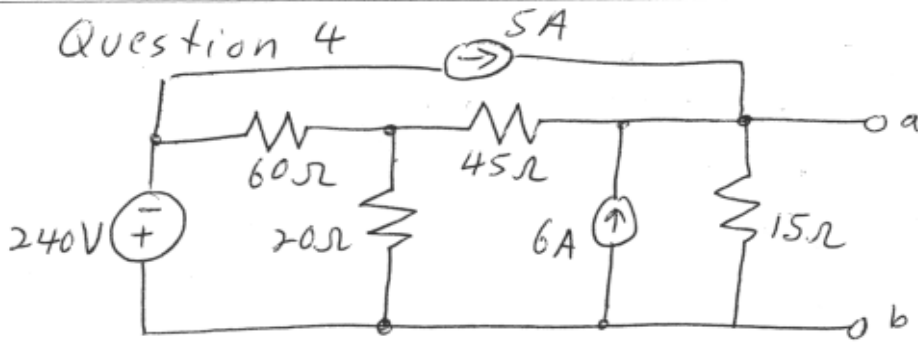




(a) Find V_{ab} by superposition

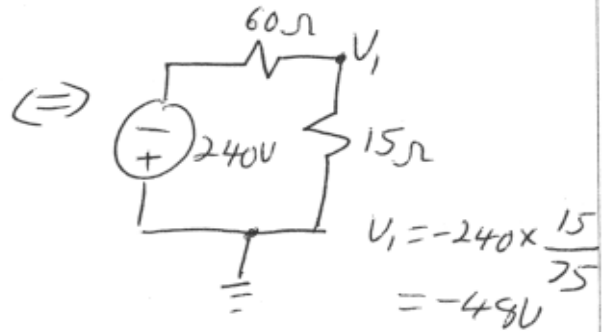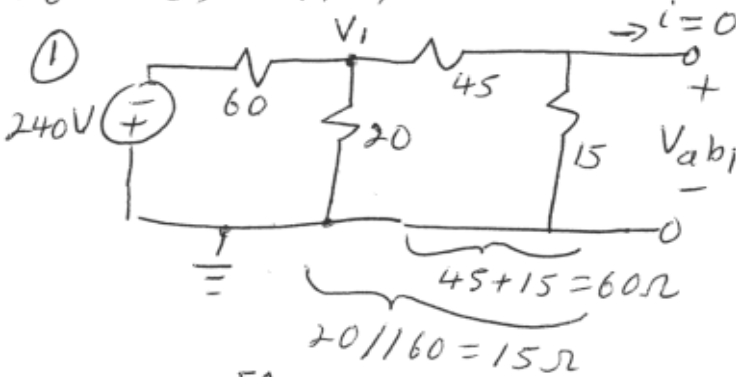(b) Short a to b and Find I_{ab}

Soln (a) Apply one independent source at a time:



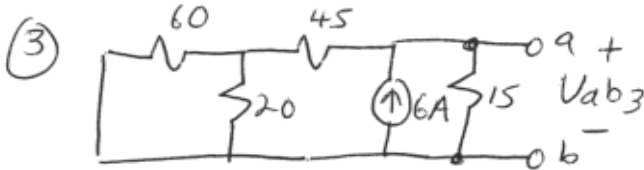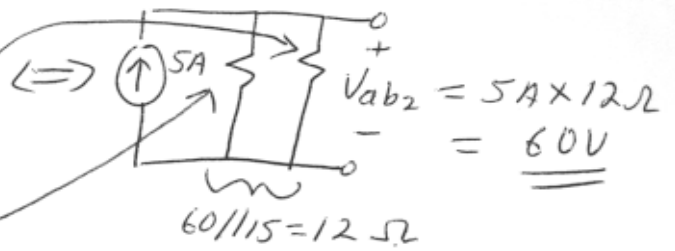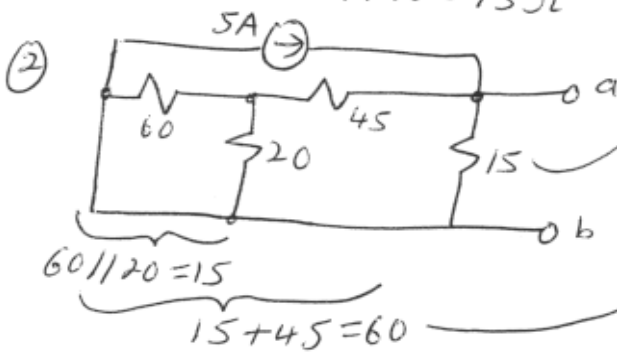$\therefore V_{ab1} = V_1 \times \frac{15}{45+15} = -12V$



Resistors combine same way as in step ②
 $\therefore V_{ab3} = 6A \times 12\Omega = 72V$

④ $V_{ab} = V_{ab1} + V_{ab2} + V_{ab3} = 120V$

(b) Realizing that we have just found V_{oc} in part (a), to find I_{sc} , use $I_{sc} = \frac{V_{oc}}{R_t}$.

sc = short circuit
oc = open circuit

Since no dependent sources, let all sources go to zero:

