
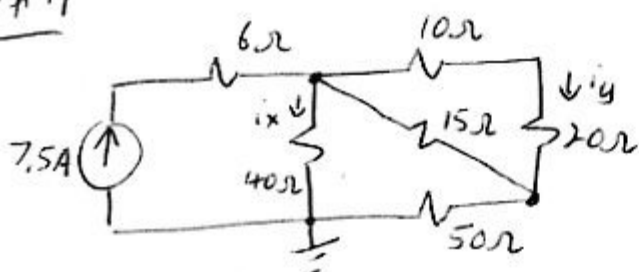


#11

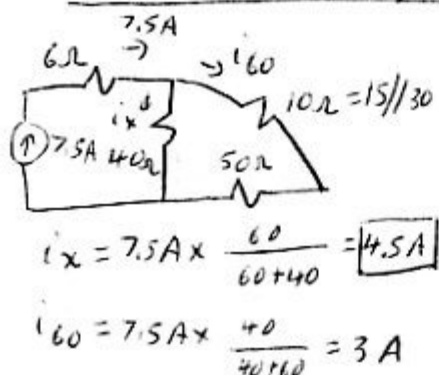


- Find i_x & i_y by the method of your choice.
- Find i_x & i_y by another method.
- What is the resistance "seen" by the 7.5A source (Hint: More than one way to do this)?

Soln: R combination Inspection Method with current division



$$i_x = 7.5A \times \frac{60}{60+40} = 4.5A$$

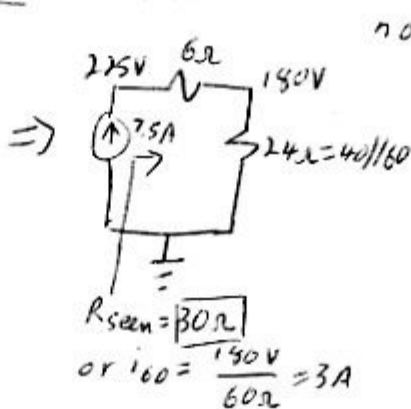
$$i_{60} = 7.5A \times \frac{40}{40+60} = 3A$$



$$R_{seen} = 30\Omega$$

$$\text{or } i_{60} = \frac{150V}{60\Omega} = 3A$$

now work backward:

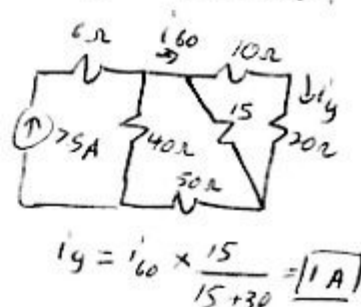

$$i_y = i_{60} \times \frac{15}{15+30} = 1A$$

Note: Other KVL, KCL, Ohm's Law inspection methods possible

Mesh Method



$$i_1 = 7.5A \text{ (given) (1)}$$

$$\text{loop 2: } 40(i_2 - i_1) + 15(i_2 - i_3) + 50i_2 = 0 \text{ (2)}$$

$$\text{loop 3: } 15(i_3 - i_2) + 30i_3 = 0 \text{ (3)}$$

Now solve (1), (2), (3):

$$(2) \rightarrow -40i_1 + 105i_2 - 15i_3 = 0$$

$$-40 \times 7.5 + 105i_2 - 15i_3 = 0$$

$$105i_2 - 15i_3 = 300 \text{ (4)}$$


$$(3) \rightarrow -15i_2 + 45i_3 = 0 \text{ (5)}$$

$$3 \times (4) + (5): 300i_2 = 900 \Rightarrow i_2 = 3A \text{ (6)}$$

$$(6) \rightarrow (5): -15 \times 3 + 45i_3 = 0 \Rightarrow i_3 = 1A \text{ (7)}$$

$$\therefore i_x = i_1 - i_2 = 4.5A \quad i_y = i_3 = 1A$$

Node Method

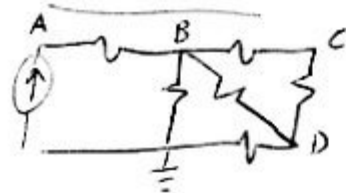

$$\text{Node B: } -7.5 + \frac{V_B}{40} + \frac{V_B - V_D}{15} + \frac{V_B - V_D}{30} = 0 \text{ (1)}$$


$$\text{Node D: } \frac{V_D - V_B}{15} + \frac{V_D - V_B}{30} + \frac{V_D}{50} = 0 \text{ (2)}$$

$$\left. \begin{array}{l} V_B = 150V \\ V_D = 150V \end{array} \right\}$$

$$\therefore i_x = \frac{150}{40\Omega} = 4.5A \quad i_y = \frac{150V - 150V}{30\Omega} = 1A$$

Note: By several ways you can find $V_p = 225V \therefore R_{seen} = 225V / 7.5A = 30\Omega$

#2

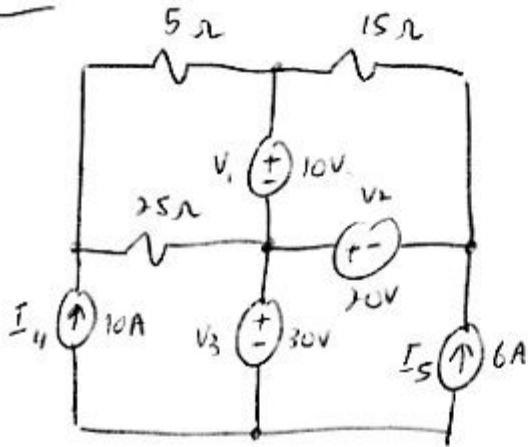


a) Find all node voltages

b) Find power for ~~each~~ the ^{10A} source, specifying if supplied or absorbed. Hint: ans is under 1000W. ϵ ?

c) Find power for the 30V source, specifying if supplied or absorbed. Hint: ans is under 500W.

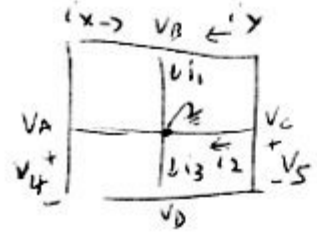d) Find Power ... 10V source... Hint ans < 100W.

Soln: lots of reasonable nodes for ground reference, let's choose the centre node as ground.



Given: $V_B = 10V, V_C = -20V, V_D = -30V$

Node A: $-10 + \frac{V_A}{25} + \frac{V_A - 10}{5} = 0$

$25 \times -250 + V_A + 5V_A - 50 = 0$

$6V_A = 300 \Rightarrow V_A = 50V$

(b) 10A source: $P = -vi$ (active) $= -V_4 \times 10A = -(V_A - V_D) \times 10$
 $= -80 \times 10$
 $= -800W$

6A source: $P = -vi = -V_5 \times 6 = -(V_C - V_D) \times 6$ supplied
 $= -(10) \times 6$
 $= -60W$ supplied


10V source: $P = vi = 10V \times i_1$
 $= 10 \times 6 \therefore i_1 = \frac{50V - 10V}{5\Omega} + \frac{-20V - 10V}{15\Omega} = 8 - 2 = 6A$
 $= 60W$ absorbed
 $i_x = 8A, i_y = -2A$ KCL to find i_1

20V source: $P = -vi = -20i_2$
 $= -20(2A + 6A) = -160W$ supplied

30V source: $P = +vi = 30V(I_4 + I_5) = 30(16A) = 480W$ absorbed

check $\sum P_{sources} = 480W$ supplied

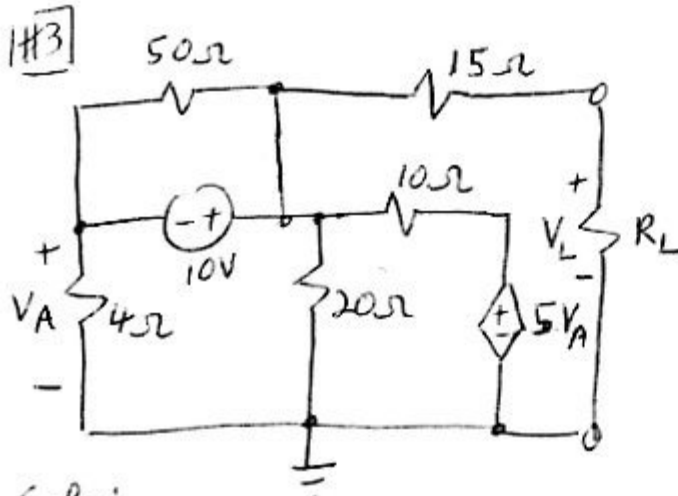
$\sum i^2 R = 320W + 60W + 100W = 480W$ absorbed \checkmark



- a) Find the Thevenin equivalent circuit to the left of the load resistor R_L .
- b) Find V_L if
- i) $R_L = 1.25\Omega$ ii) $R_L = 7.5\Omega$ iii) $R_L = 20\Omega$

Soln:

Step 1 Find V_{oc}

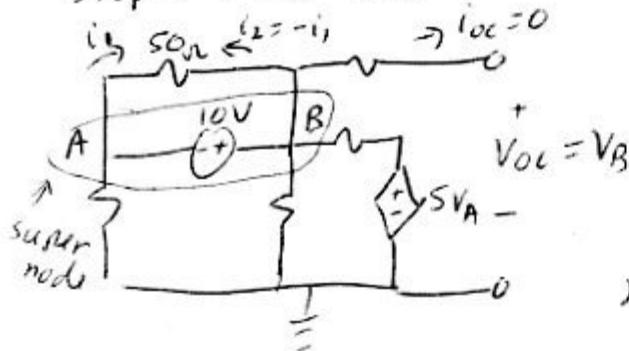

Node Method

Super node: V_B


$$\frac{V_A}{4} + \frac{V_A + 10}{20} + \frac{V_A + 10 - 5V_A}{10} = 0$$

$$20x: 5V_A + V_A + 10 - 5V_A + 20 = 0$$

$$-2V_A = -30V \Rightarrow V_A = 15V$$

$$\therefore V_t = V_{oc} = V_B = 15 + 10 = \boxed{25V}$$

Step 2 Find I_{sc}

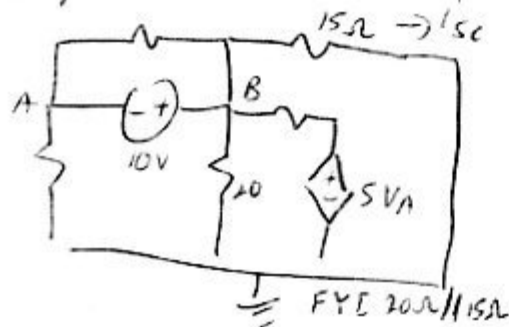

Super node:

$$\frac{V_A}{4} + \frac{V_A + 10}{20} + \frac{V_A + 10 - 5V_A}{10} + \frac{V_A + 10}{15} = 0$$


$$60x: 15V_A + 3V_A + 30 - 24V_A + 60 + 4V_A + 40 = 0$$

$$-2V_A = -130 \Rightarrow V_A = 65V$$

$$\therefore V_B = V_A + 10 = 75V \therefore I_{sc} = \frac{V_B}{15} = \boxed{5A}$$

Step 3 $R_t = \frac{V_{oc}}{I_{sc}} = 5\Omega$


(b)

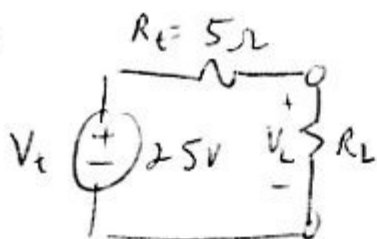

$$V_L = 25 \times \frac{R_L}{5 + R_L}$$


R_L	V_L
1.25Ω	5V
7.5Ω	15V
20Ω	20V

#4

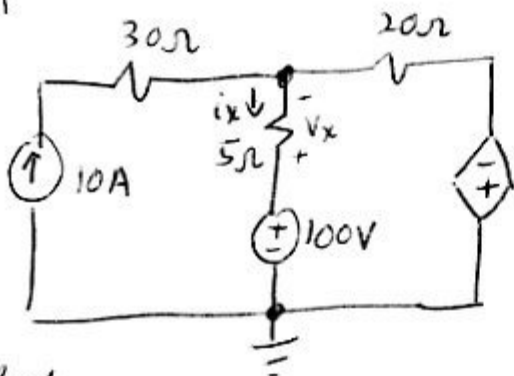

- a) Find i_x and V_x by superposition.
 (simpler prob: just find i_x)
 b) Find power ^{for the} 5Ω resistor and $100V$ source; specify if absorbed or supplied.


Soln:

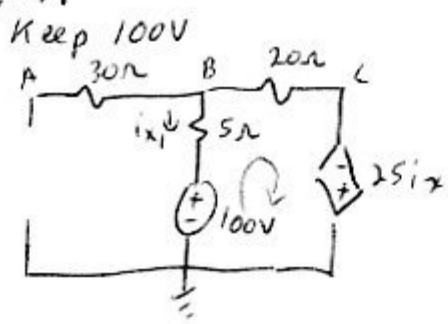

Inspection Method: \swarrow Ohm's Law
 KVL: $-100 - 5i_{x1} - 20i_{x1} - 25i_{x1} = 0$
 $i_{x1} = \frac{100}{-50} = -2A \Rightarrow V_{x1} = -i_x \times 5$ (Active notation)
 $= +10V$

or Node Method:
 $\frac{V_B - 100}{5} + \frac{V_B - (-25i_x)}{20} = 0$ (1) $i_{x1} = \frac{V_B - 100}{5}$ (2)
 Solve: $V_B = 90V, i_{x1} = -2A$

Keep 10A

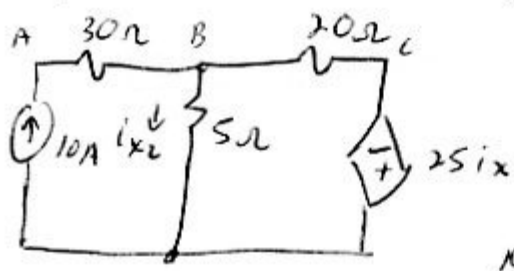

Inspection Method: $V_B = 5i_{x2}$
 KCL at B: $-10A + i_{x2} + \frac{5i_{x2} - (-25i_{x2})}{20} = 0$
 $i_{x2} = \frac{10}{2.5} = 4A \Rightarrow V_{x2} = -i_x \times 5 = -20V$

Node Method:
 Node B: $-10A + \frac{V_B}{5} + \frac{V_B - (-25i_x)}{20} = 0$ (1)
 $i_{x2} = V_B/5$ (2) solve: $V_B = 20V, i_{x2} = 4A$

Step 3 Add responses: $i_x = i_{x1} + i_{x2} = -2 + 4 = 2A$
 $V_x = V_{x1} + V_{x2} = 10 - 20 = -10V$

$P_5 = -V_x i_x$ (Active, not passive notation) \leftarrow or $i^2 R$ or V^2/R
 $= -(-10) \times 2 = +20W \therefore$ absorbed (as expected for R)

$P_{100} = 100V \times i_x$ (passive notation)
 $= 100V \times 2A = +200W \therefore$ absorbed
 (ie the 100V source is receiving energy \rightarrow "being charged")