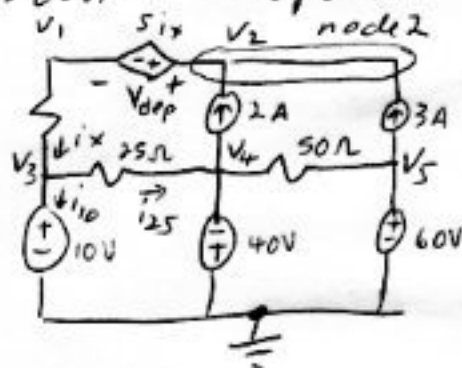


(a) Find all node voltages.

(b) Find power for the dependent source and for the 10V source, specifying if power is supplied or absorbed.

Soln 1 Inspection:



$$i_x = 2A + 3A \text{ (KCL at Node 2)}$$

$$\Rightarrow V_1 = 10V + i_x \times 15\Omega = 85V$$

$$V_2 = V_1 + 5i_x = 85 + 25 = 110V$$

$$V_3 = 10V \quad V_4 = -40V \quad V_5 = 60V \text{ (all given)}$$

$$P_{dep} = (V_{dep})(i_x) \text{ (passive notation)}$$


$$= (5i_x)(i_x) = 25V \times 5A = +125W \text{ absorb.}$$

$$P_{10} = 10V(i_{10}) \text{ (passive notation)}$$

$$= 10V(i_x - i_{25}) = 10V(5A - \frac{10V + 40V}{25\Omega})$$

$$= 10V(5A - 2A) = 30W \text{ absorb}$$

Soln 2 Node Method:

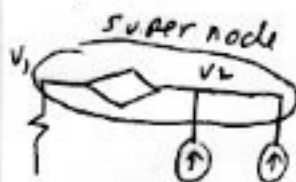

controller: $i_x = \frac{V_1 - 10V}{15} \quad (1)$

super node KCL: $\frac{V_1 - 10}{15} - 2 - 3 = 0 \quad (2)$

constraint: $5i_x = V_2 - V_1 \quad (3)$

solving (2) $\Rightarrow V_1 = 85V$

(1) $\Rightarrow i_x = \frac{85 - 10}{15} = 5A$

(3) $\Rightarrow 5 \times 5 = V_2 - V_1 \Rightarrow V_2 = 85 + 25 = 110V$

Check:

First use KCL & Ohm's Law to find branch currents	40V: -80W supplied
	60V: -300W "
	2A: -300W "
	1A: -150W "
	10V: +30W absorb
	$5i_x$: +125W
	<u>675W supplied</u>


$$\sum i^2 R = 5^2 \times 15$$

$$+ 2^2 \times 25$$


$$+ 2^2 \times 50$$

$$\underline{\underline{675W \text{ absorbed}}}$$

Energy is conserved ☺

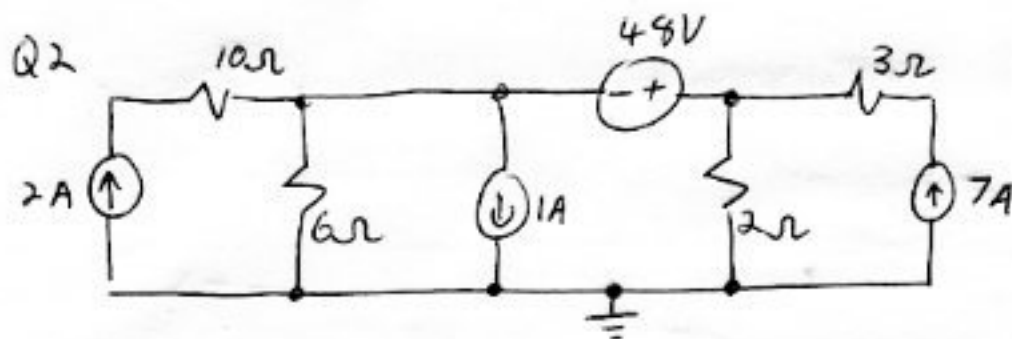

- (a) Find all mesh currents.
 (b) Using the results of part (a) find all node voltages.
 (c) Find power for each source, specify absorbed/supplied.
 (d) Calculate total power absorbed by the resistors.

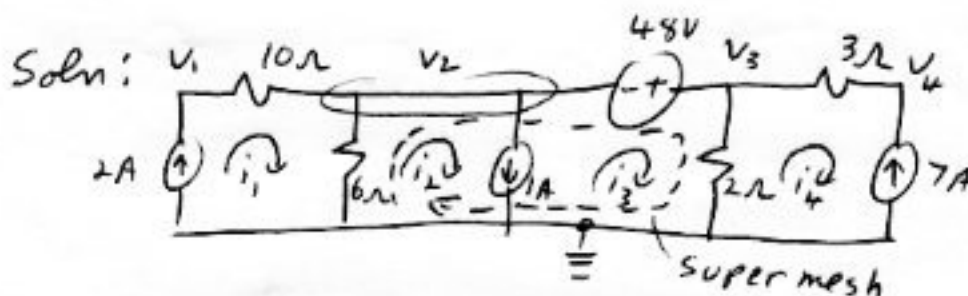

loop 1: $i_1 = 2A$ (given) (1) loop 4: $i_4 = -7A$ (given) (2)

super loop KVL: $6(i_2 - 2) - 48V + 2(i_3 + 7) = 0$ (3)

constraint: $1A = i_2 - i_3$ or $i_2 - i_3 = 1$ (4)

Solving these eqns: from (3): $6i_2 + 2i_3 = 46$ (5)

$2 \times (4) + (5)$: $8i_2 = 48 \Rightarrow i_2 = \underline{\underline{6A}}$

From (4): $i_3 = \underline{\underline{5A}}$

(b) $V_3 = iR = (i_3 - i_4) \times 2\Omega = 12 \times 2 = 24V$

$V_4 = V_3 - i_4 \times 3\Omega = 24 - (-7 \times 3) = 45V$

$V_2 = (i_1 - i_2) \times 6\Omega = -24V$ or $V_2 = V_3 - 48V = -24V$

$V_1 = V_2 + i_1 \times 10\Omega = -24 + 2 \times 10 = -4V$

(c) 2A: $P = -V_1 i_1 = -(-4)(2) = +8W$ absorb

1A: $P = V_2 \times 1A = -24 \times 1 = -24W$ supplied


48V: $P = -48 \times i_3 = -48 \times 5 = -240W$ supplied

7A: $P = -V_4 \times 7A = -(45) \times 7 = -315W$ supplied

$P_{\text{source total}} = 571W$ supplied


(d)
 $\sum i^2 R = 571W$
 By conserv. of Energy.

Q3

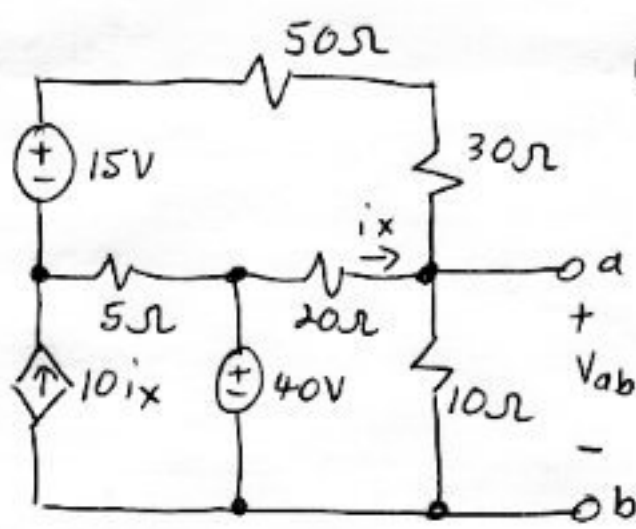

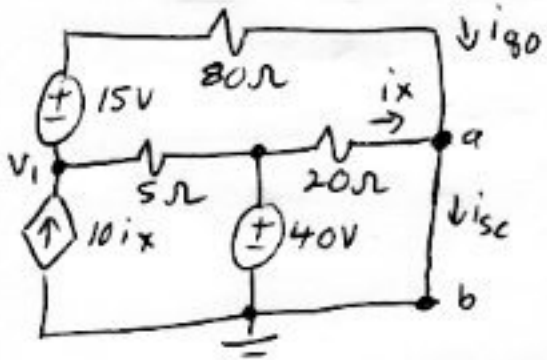(a) A voltmeter is connected to terminals a and b (acting like a resistor of infinite Ohms) and V_{ab} is measured to be $V_{ab} = +20V$. Determine the Thevenin Equivalent circuit for terminals a and b of the given circuit.

Soln $V_{oc} = 20V$
So just need I_{sc} :



(b) Predict V_{ab} if a resistor is now placed across terminals a & b for (i) $R_{ab} = 2.25\Omega$
(ii) $R_{ab} = 7.85\Omega$
(iii) $R_{ab} = 47\Omega$

$$i_x = \frac{40V}{20\Omega} = 2A$$

$$10i_x = 20A$$

Node 1: $-20A + \frac{V_1 - 40V}{5\Omega} + \frac{V_1 + 15V}{80\Omega} = 0$



$$\Rightarrow -1600 + 16V_1 - 640 + V_1 + 15 = 0$$


$$\text{or } 17V_1 = 2225V$$

$$V_1 = 130.89V$$


$$\therefore i_{80} = \frac{V_1 + 15V}{80\Omega} = \frac{130.89 + 15}{80} = 1.8235A$$
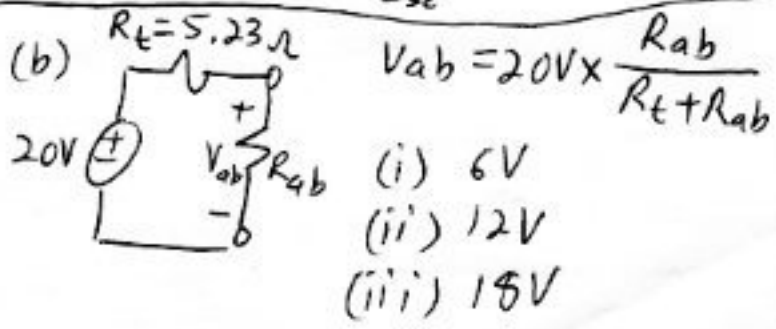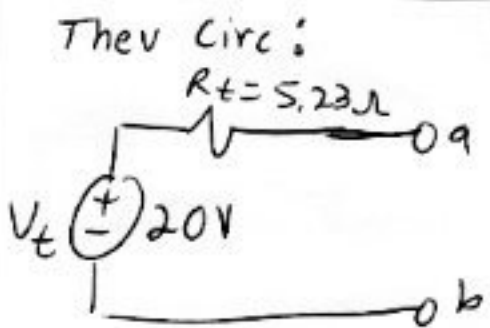
$$\therefore I_{sc} = i_x + i_{80} = 2 + 1.8235 = 3.8235A \Rightarrow R_t = \frac{V_{oc}}{I_{sc}} = 5.23\Omega$$



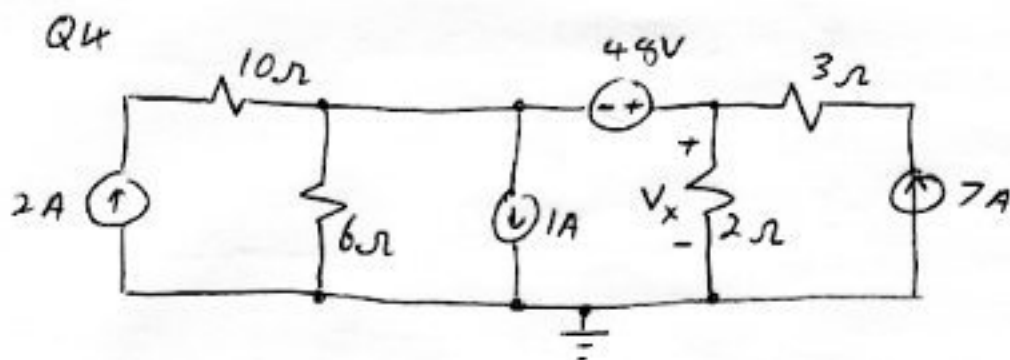

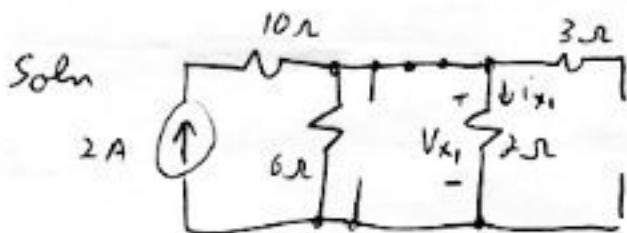
For this circuit (it is exactly the same circuit as in problem Q2), calculate V_x using the principle of superposition.



By current division

$$i_{x1} = 2A \times \frac{6}{6+2} = 1.5A$$

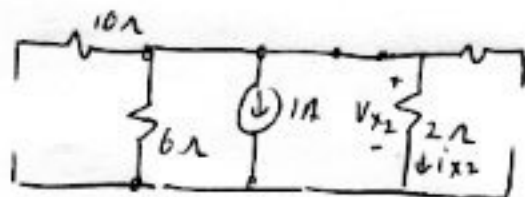
$$\therefore V_{x1} = 1.5 \times 2\Omega = \underline{3V}$$



By current division

$$i_{x2} = -1A \times \frac{6}{6+2} = -0.75A$$

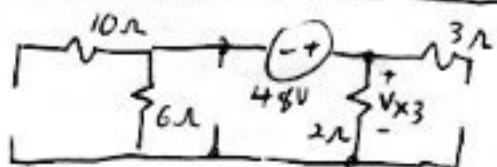
$$\therefore V_{x2} = -0.75 \times 2 = \underline{-1.5V}$$



Note the 2Ω R is in series with the 6Ω R.

By voltage division
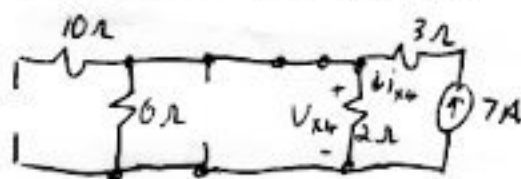
$$V_{x3} = 48 \times \frac{2}{2+6} = \underline{12V}$$



By current division

$$i_{x4} = 7A \times \frac{6}{6+2} = 5.25A$$

$$\therefore V_{x4} = 5.25A \times 2\Omega = \underline{10.5V}$$

$$\text{Total voltage: } V_x = V_{x1} + V_{x2} + V_{x3} + V_{x4} = \underline{24V}$$

This agrees with ans in Q2: $V_3 = V_x = 24V$.