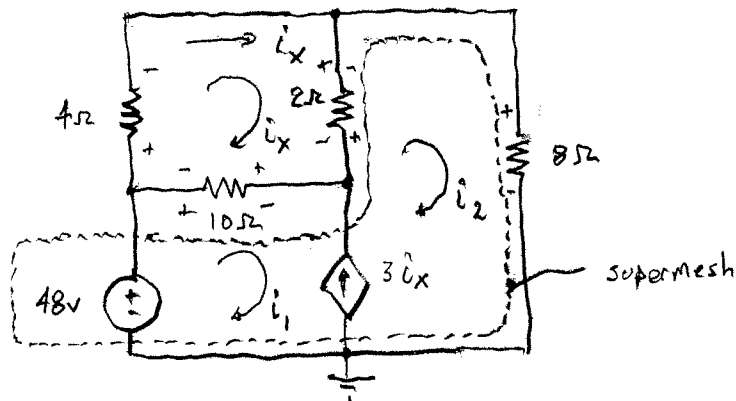


Question 1

(a)



$$\begin{aligned} \text{Mesh } i_x: \quad & 4i_x + 2(i_x - i_2) + 10(i_x - i_1) = 0 \\ & 4i_x + 2i_x - 2i_2 + 10i_x - 10i_1 = 0 \\ & 16i_x - 10i_1 - 2i_2 = 0 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{Supermesh:} \quad & -48 + 10(i_1 - i_x) + 2(i_2 - i_x) + 8i_2 = 0 \\ & -48 + 10i_1 - 10i_x + 2i_2 - 2i_x + 8i_2 = 0 \\ & 10i_1 + 10i_2 - 12i_x = 48 \end{aligned} \quad (2)$$

$$\begin{aligned} \text{And inside the supermesh,} \quad & i_2 - i_1 = 3i_x \\ \text{so} \quad & i_2 = i_1 + 3i_x \end{aligned} \quad (3)$$

Substitute (3) into (1) and (2)

$$\begin{aligned} (1) \quad & 16i_x - 10i_1 - 2(i_1 + 3i_x) = 0 \\ & 10i_x - 12i_1 = 0 \\ \text{so} \quad & i_x = \frac{6}{5}i_1 \end{aligned} \quad (4)$$

$$\begin{aligned} (2) \quad & 10i_1 + 10(i_1 + 3i_x) - 12i_x = 48 \\ & 20i_1 + 18i_x = 48 \end{aligned} \quad (5)$$

Substitute (4) into (5)


$$20i_1 + \frac{108}{5}i_1 = 48$$

$$\frac{208}{5} i_1 = 48 \quad \therefore i_1 = 1.1538 \text{ A}$$

And $i_x = \frac{6}{5} i_1 = 1.3846$

And, from (3), $i_2 = i_1 + 3i_x = 5.3077 \text{ A}$

(b)

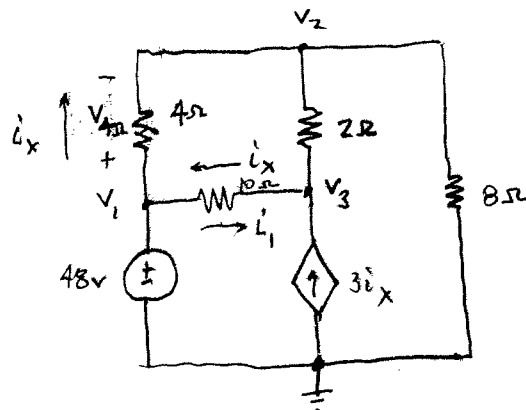

V_1 already known

$$V_1 = 48 \text{ V}$$


We have $V_{4\Omega} = 4i_x = 5.5385 \text{ V}$. By inspection, we may write

$$V_1 - V_2 = 5.5385 \text{ V},$$

$$\text{so } V_2 = V_1 - 5.5385 = 48 - 5.5385$$

$$V_2 = 42.4615 \text{ V}$$

Between V_1 and V_3 , we have

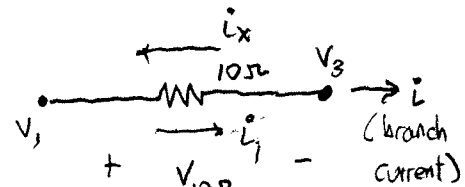


$$\text{we have } i = i_1 - i_x = -0.23077 \text{ A}$$

$$\text{so } V_{10\Omega} = 10i = -2.3077 \text{ V}$$

And, by inspection,

$$V_1 - V_3 = V_{10\Omega} \quad \text{so } V_3 = V_1 - V_{10} = 48 + 2.3077$$

$$V_3 = 50.3077$$

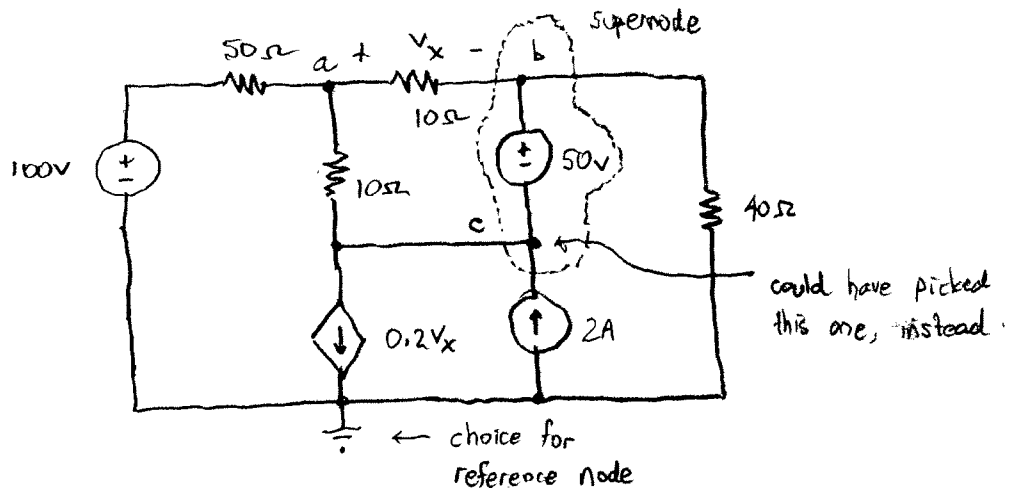Question 2

(a) Node voltages:

$$\text{Node a: } \frac{V_a - 100}{50} + \frac{V_a - V_c}{10} + \frac{V_a - V_b}{10} = 0$$

$$V_a - 100 + 5V_a - 5V_c + 5V_a - 5V_b = 0$$

$$11V_a - 5V_b - 5V_c = 100 \quad (1)$$

$$\text{Supernode: } \frac{V_b - V_a}{10} + \frac{V_b}{40} + \frac{V_c - V_a}{10} - 2 + 0.2V_x = 0$$

$$4V_b - 4V_a + V_b + 4V_c - 4V_a - 80 + 8V_x = 0$$

$$5V_b - 8V_a + 4V_c + 8V_x = 80 \quad (2)$$

We have the dependency $V_x = V_a - V_b$, so equation (2) becomes

$$5V_b - 8V_a + 4V_c + 8(V_a - V_b) = 80$$

$$5V_b - 8V_a + 4V_c + 8V_a - 8V_b = 80$$

$$-3V_b + 4V_c = 80 \quad (3)$$

Within the supernode, $V_b - V_c = 50\text{V}$

$$\text{so } V_b = V_c + 50 \quad (4)$$

Substitute (4) into (3)

$$\begin{aligned} -3(V_c + 50) + 4V_c &= 80 \\ -3V_c - 150 + 4V_c &= 80 \end{aligned}$$

$$\therefore V_c = 80 + 150 = 230\text{V}$$

And, from (4), $V_b = V_c + 50 = 280\text{V}$


Finally, from (1),

$$11V_a - 5(280) - 5(230) = 100$$

$$11V_a = 2650$$

$$\therefore V_a = 240.91\text{V}$$

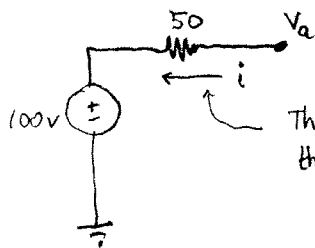(b) Consider node a; we need the current in the 100V source.



This is the first term in the node equation (i) for node a.

$$i = \frac{V_a - 100}{50} = 2.818\text{ A}$$


Observing the passive reference convention,

$$P_{100} = +Vi = 100 \times 2.818$$

$$\text{so } P_{100} = 281.8\text{ W}$$

POSITIVE IN VALUE, SO POWER IS ABSORBED.

Question 3

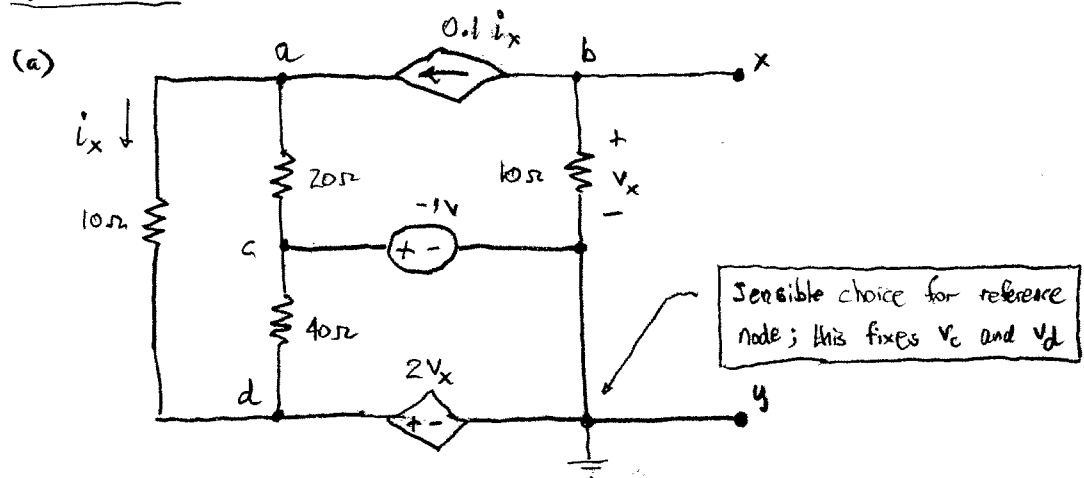

Set up node voltage method to find Thevenin voltage V_t .

By inspection, $V_c = -1V$
 $V_d = 2V_x$

and we note that $V_x = 2V_b$.

Node a: $-0.1 i_x + \frac{V_a - V_c}{20} + \frac{V_a - V_d}{10} = 0$

We observe that $i_x = \frac{V_a - V_d}{10}$, so

$$-0.1 \left(\frac{V_a - V_d}{10} \right) + \frac{V_a - V_c}{20} + \frac{V_a - V_d}{10} = 0$$

(x 100) $V_d - V_a + 5V_a - 5V_c + 10V_a - 10V_d = 0$

$$-14V_a - 5V_c - 9V_d = 0$$

or $14V_a - 5(-1) - 9(2V_b) = 0$

$$14V_a - 18V_b = -5 \quad (1)$$

Node b: $0.1 i_x + \frac{V_b}{10} = 0$

so $0.1 \left(\frac{V_a - V_d}{10} \right) + \frac{V_b}{10} = 0$

or $\frac{V_a - 2V_b}{100} + \frac{V_b}{10} = 0$

$$V_a - 2V_b + 10V_b = 0$$

$$\text{so } V_a = -8V_b \quad (2)$$


We need V_b , which is V_t . Substitute (2) into (1)

$$14(-8V_b) - 18V_b = -5$$

$$-130V_b = -5$$

$$\therefore V_t = V_b = \frac{5}{130} = \frac{1}{26} \text{ V} = 38.462 \text{ mV}$$

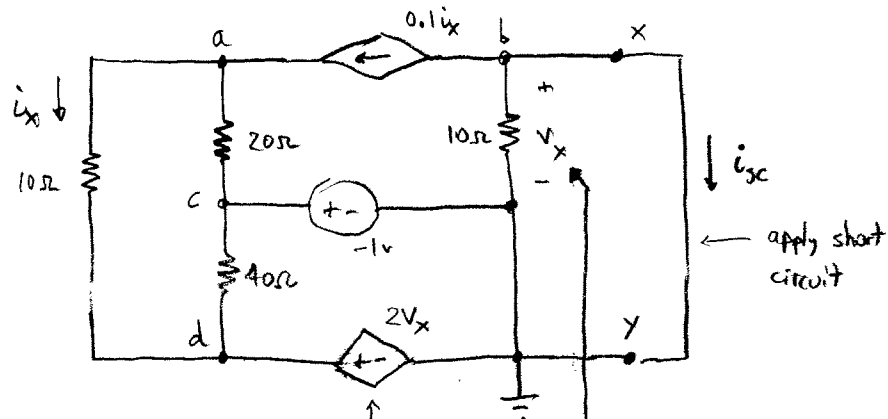Now, the Thevenin resistance R_t . Unfortunately, we can't take any short-cuts, and must determine short-circuit current i_{sc} .



Note that $V_x = 0$ thanks to short circuit ($V_b = V_x = 0$, same as reference node)

• Means that dependent source is a short circuit!

$$\text{Node a: } \frac{V_a}{10} + \frac{V_a + 1}{20} - 0.1 i_x = 0$$

$$\text{where } i_x = \frac{V_a}{10}, \text{ so } \frac{V_a}{10} + \frac{V_a + 1}{20} - \frac{V_a}{100} = 0$$

$$10V_a + 5(V_a + 1) - V_a = 0$$


$$14V_a = -5 \quad \therefore V_a = \frac{-5}{14}$$

Node b: $\frac{V_b}{10} + 0.1 i_x + i_{sc} = 0$

$$0.1 \left(\frac{V_a}{10} \right) + i_{sc} = 0$$


$$\text{so } i_{sc} = -\frac{V_a}{100} = \frac{5}{1400} \text{ A} = 3.5714 \text{ mA}$$

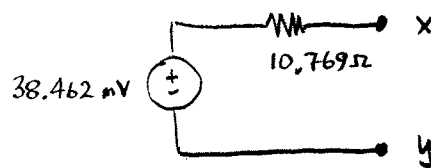Finally, $R_L = \frac{V_E}{i_{sc}} = \frac{1/26}{5/1400} = \frac{280}{26} \Omega = 10.769 \Omega$



THEVENIN
EQUIVALENT CIRCUIT

(b) Use the above Thevenin equivalent!

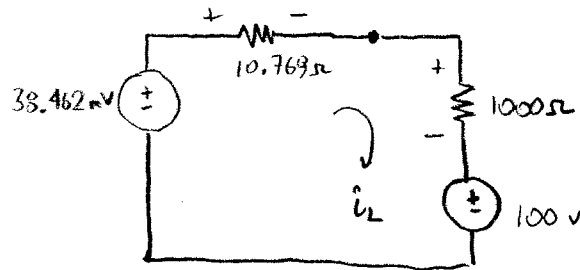


By KVL, $-0.038462 + (10.769 + 1000) i_L + 100 = 0$

$$\therefore i_L = -98.897 \text{ mA}$$

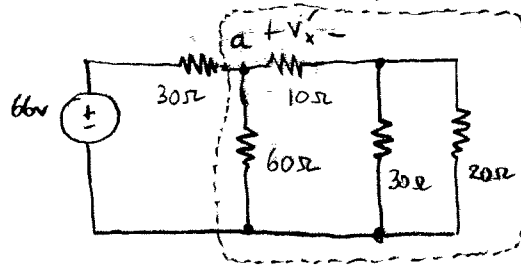Question 4

Consider the 66V source alone; zero the others. Find V_x' .



$$\begin{aligned} R_{eq} &= [(20 // 30) + 10] // 60 \\ &= (12 + 10) // 60 \\ &= \frac{22 \times 60}{22 + 60} = 16.0976 \Omega \end{aligned}$$

Based on the above grouping of series-parallel resistors, we can treat it as a simple voltage divider to find V_a


$$V_a = \frac{16.0976}{16.0976 + 30} \times 66 = 23.0476 \text{ V}$$

Voltage divider again to find V_x'

$$V_x' = \frac{10}{10 + (30 // 20)} V_a = \frac{10}{22} \times 23.0476$$

$$\text{so } \boxed{V_x' = 10.476 \text{ V}}$$

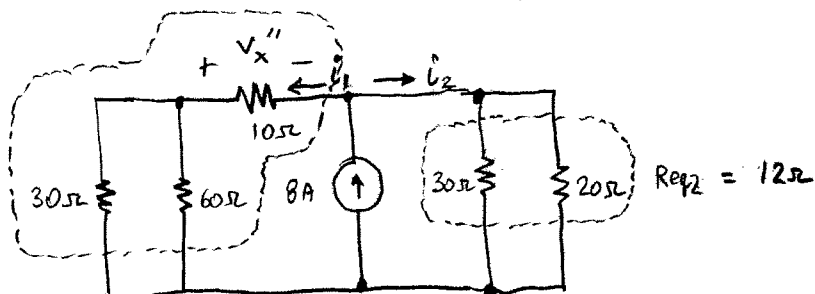Next, consider the 8A source alone; zero all others. Find V_x''



$$\begin{aligned} R_{eq1} &= 30 // 60 + 10 \\ &= 30 \Omega \end{aligned}$$


We have a current divider with R_{eq1} and R_{eq2} in parallel. Need i_1 ,

$$i_1 = \frac{R_{eq2}}{R_{eq1} + R_{eq2}} \times 8 \text{ A}$$

$$= \frac{12}{12 + 30} \times 8 = 2.2851 \text{ A}$$

Giving

$$V_x'' = -10i_1 = -22.851 \text{ V}$$

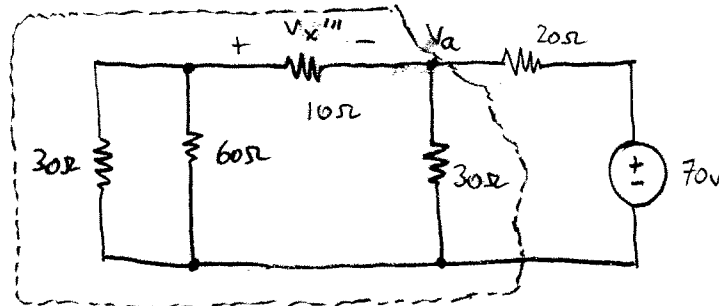Finally, the 70 V source alone. Find V_x''' 

$$R_{eq} = [(30 // 60) + 10] // 30 \\ = 15 \Omega$$

Following the same analysis as for the 66V source,

$$V_a = \frac{15}{15 + 20} \times 70 \text{ V} = 30 \text{ V}$$

Voltage divider again to find V_x''' (note polarity).

$$V_x''' = \frac{-10}{(60 // 30) + 10} \times V_a = \frac{10}{30} \times 30$$

$$V_x''' = -10 \text{ V}$$

Finally, by superposition

$$V_x = V_x' + V_x'' + V_x''' \\ = 10.476 - 22.851 - 10$$

$$V_x = -22.375 \text{ V}$$