

a) Find node voltages

b) Find power in all voltage sources

a) Reference node: 5

Note: $V_3 = 20V$

$V_4 = -40V$

Use supernode 1+2:

$$V_2 = V_1 + 100 \quad (1) \quad (\text{supernode constraint})$$

$$\text{KCL}_{1+2}: 2 + 4 - \frac{V_2}{10} - \frac{V_2 - 20}{10} = 0$$

$$60 - V_2 - V_2 + 20 = 0$$

$$V_2 = 40V$$

$$(1) \Rightarrow V_1 = V_2 - 100 = -60V$$

b) 100V source:

$$\text{KCL}_1: \hat{i}_{100} + 2 + 4 = 0, \hat{i}_{100} = -6 \text{ A}$$

$$P_{100} = 100 \cdot \hat{i}_{100} = 100 \cdot (-6) = \underline{-600 \text{ W}} \quad (600 \text{ W supplied})$$

20V source:

$$\text{KCL}_2: \frac{v_2 - v_3}{10} - 4 - \frac{v_3 - v_4}{40} - \hat{i}_{20} = 0$$

$$\hat{i}_{20} = \frac{40 - 20}{10} - 4 - \frac{20 - (-40)}{40} = -3.5 \text{ A}$$


$$P_{20} = 20 \cdot \hat{i}_{20} = 20 \cdot (-3.5) = -70 \text{ W} \quad (70 \text{ W supplied})$$

40V source:

$$\text{KCL}_5: \frac{v_2}{10} + \hat{i}_{20} - \hat{i}_{40} = 0$$

$$\hat{i}_{40} = \frac{40}{10} - 3.5 = 0.5 \text{ A}$$
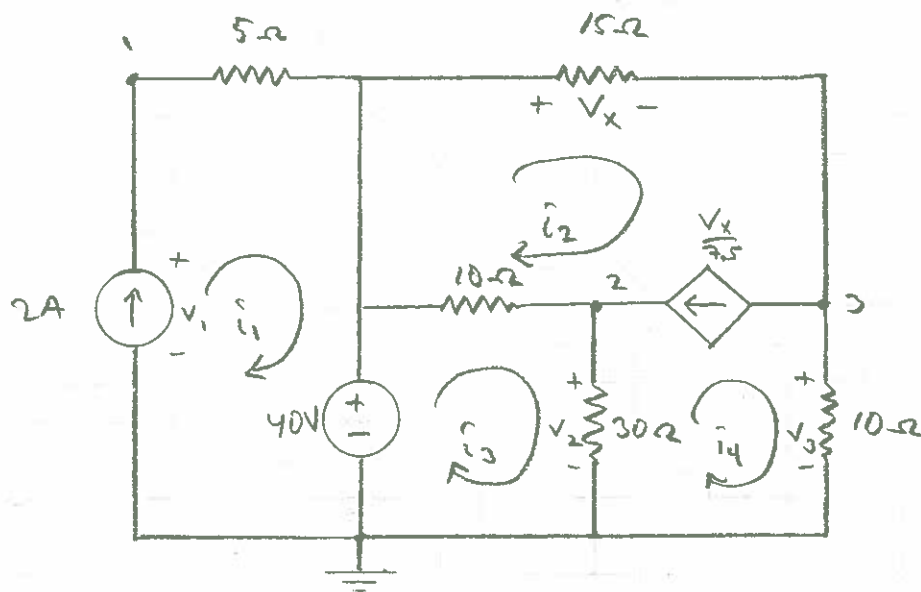
$$P_{40} = 40 \cdot \hat{i}_{40} = 40 \cdot 0.5 = 20 \text{ W} \quad (20 \text{ W absorbed})$$



a) Find mesh currents

b) Find node voltages

V_1, V_2, V_3

a) Mesh-current method:

Notes: $i_1 = 2A$

$$V_x = 15 \cdot i_2 \Rightarrow \frac{V_x}{2.5} = 2i_2$$

Use supermesh 2+4:

$$i_2 - i_4 = \frac{V_x}{2.5} = 2i_2 \Rightarrow i_2 = -i_4 \quad (1) \quad (\text{supermesh constraint})$$

$$\text{KVL}_{2+4}: 15i_2 + 10i_4 + 30(i_4 - i_3) + 10(i_2 - i_3) = 0$$

$$(1) \Rightarrow 15i_2 - 10i_2 - 30i_2 - 30i_3 + 10i_2 - 10i_3 = 0$$

$$-15i_2 - 40i_3 = 0 \quad (2)$$

$$\text{KVL}_3: -40 + 10(i_3 - i_2) + 30(i_3 - i_4) = 0$$

$$(1) \Rightarrow -40 + 10i_3 - 10i_2 + 30i_3 + 30i_2 = 0$$

$$20i_2 + 40i_3 = 40 \quad (3)$$

$$(2) + (3) \Rightarrow 5i_2 = 40$$

$$i_2 = \underline{8A}$$

$$(1) \Rightarrow i_4 = \underline{-8A}$$

$$(2) \Rightarrow -15 \cdot 8 - 40i_3 = 0$$

$$i_3 = \underline{-3A}$$


b) KVL: $-V_1 + 5i_1 + 40 = 0$

$$V_1 = 5 \cdot 2 + 40 = \underline{50V}$$

$$V_2 = 30(i_3 - i_4) = 30 \cdot (-3 + 8) = \underline{150V}$$

$$V_3 = 10 \cdot i_4 = 10 \cdot (-8) = \underline{-80V}$$

3)

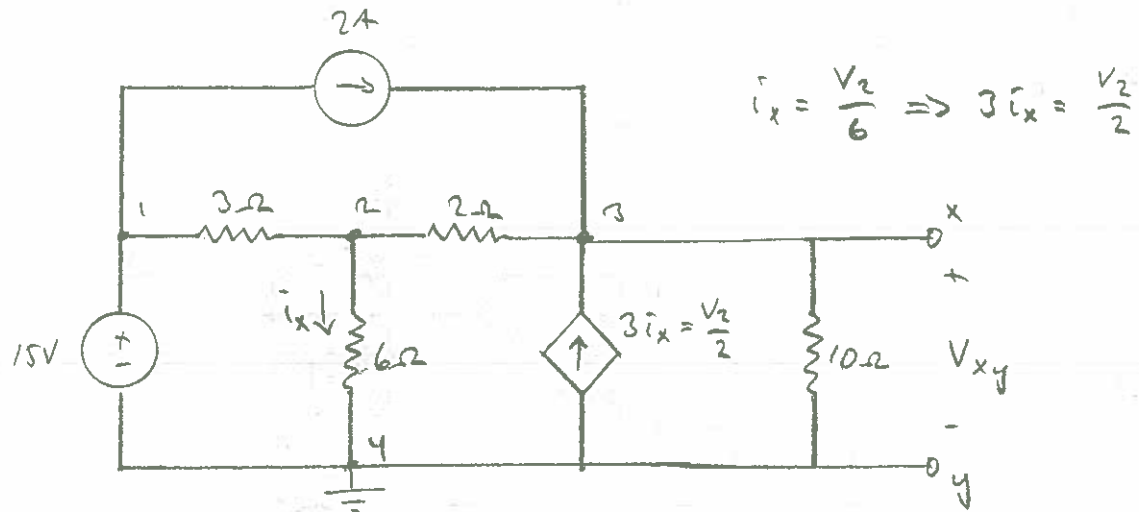

- a) Thévenin equivalent?
 b) V_{xy} for load consisting of $R = 10\Omega$ in series with 2A source?

a) 1) Find no-load voltage V_{xy}

Use node-voltage method with node 4 as reference

$V_1 = 15V$, solve for V_2 and $V_3 = V_{xy}$

$$\text{KCL}_2: \frac{15 - V_2}{3} - \frac{V_2}{6} - \frac{V_2 - V_3}{2} = 0$$

$$30 - 2V_2 - V_2 - 3V_2 + 3V_3 = 0$$

$$-6V_2 + 3V_3 = -30 \quad (1)$$

$$\text{KCL}_3: 2 + \frac{V_2 - V_3}{2} + \frac{V_2}{2} - \frac{V_3}{10} = 0$$

$$20 + 5V_2 - 5V_3 + 5V_2 - V_3 = 0$$

$$10V_2 - 6V_3 = -20 \quad (2)$$


$$2 \times (1) + (2) \Rightarrow -2V_2 = -80$$

$$V_2 = 40V$$

$$(1) \Rightarrow -6 \cdot 40 + 3V_0 = -30$$

$$V_0 = \underline{70V} = V_{Th}$$

2) Find short-circuit current i_{sc}

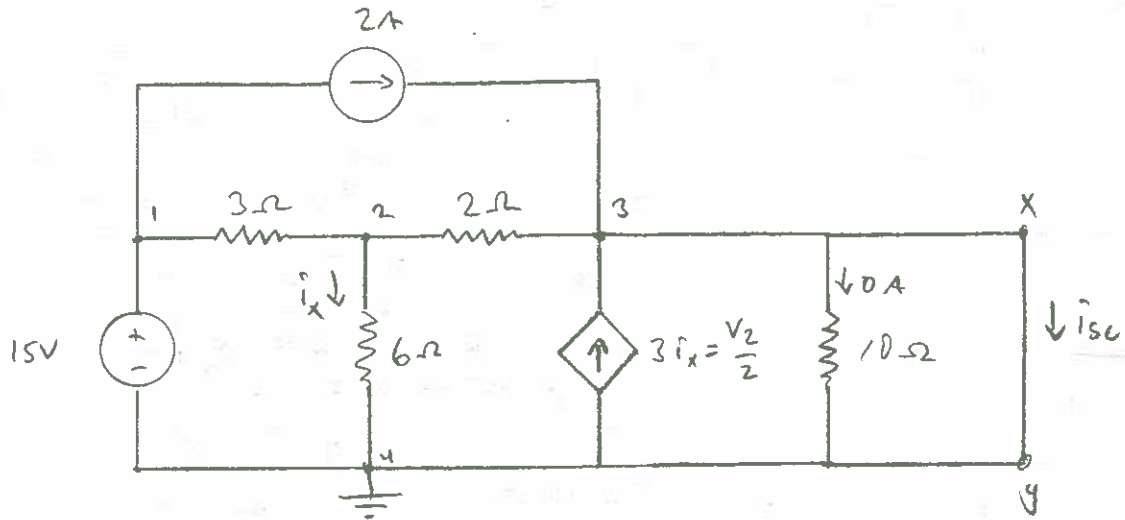

Note $V_1 = 15V$

$V_3 = 0V$ (due to short-circuit)

$$KCL_2: \frac{15 - V_2}{3} - \frac{V_2}{6} - \frac{V_2}{2} = 0$$

$$30 - 2V_2 - V_2 - 3V_2 = 0$$


$$V_2 = 5V$$

$$KCL_3: 2 + \frac{V_2 - 0}{2} + \frac{V_2}{2} - i_{sc} = 0$$


$$i_{sc} = 2 + \frac{5}{2} + \frac{5}{2} = 7A$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{70}{7} = \underline{10\Omega}$$

Thevenin equivalent:

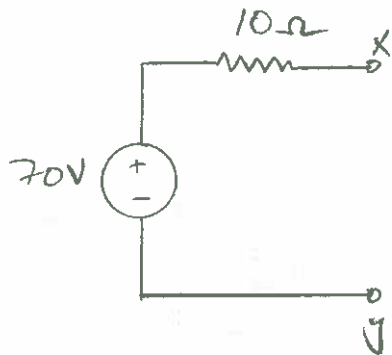



b)

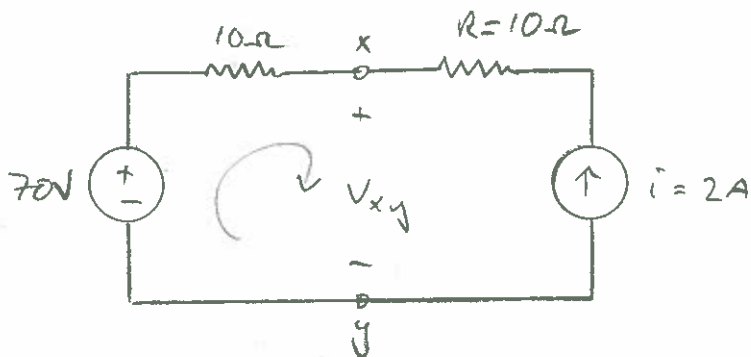

$$\text{KVL: } -70 - 10 \cdot 2 + V_{xy} = 0$$

$$V_{xy} = \underline{90V}$$

4.

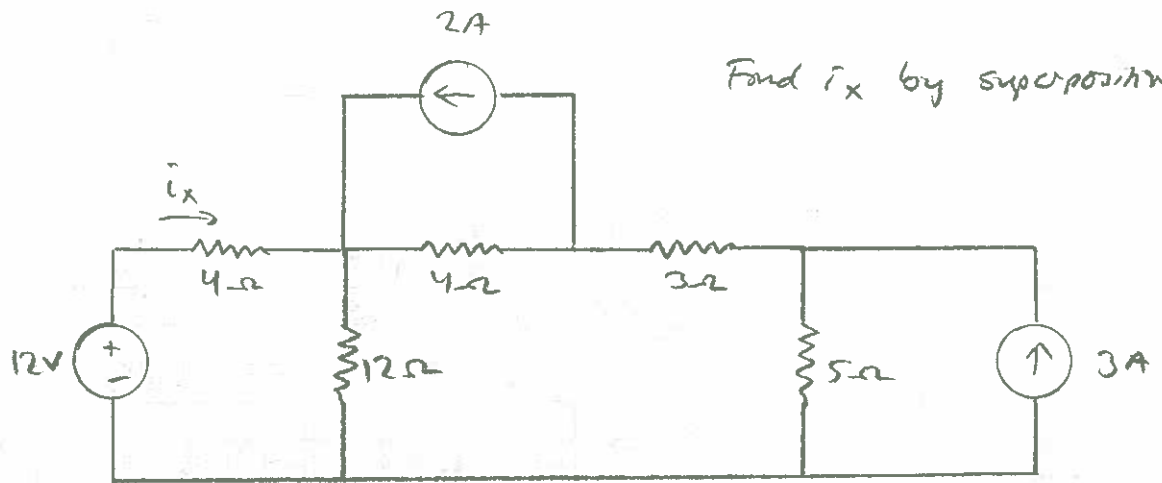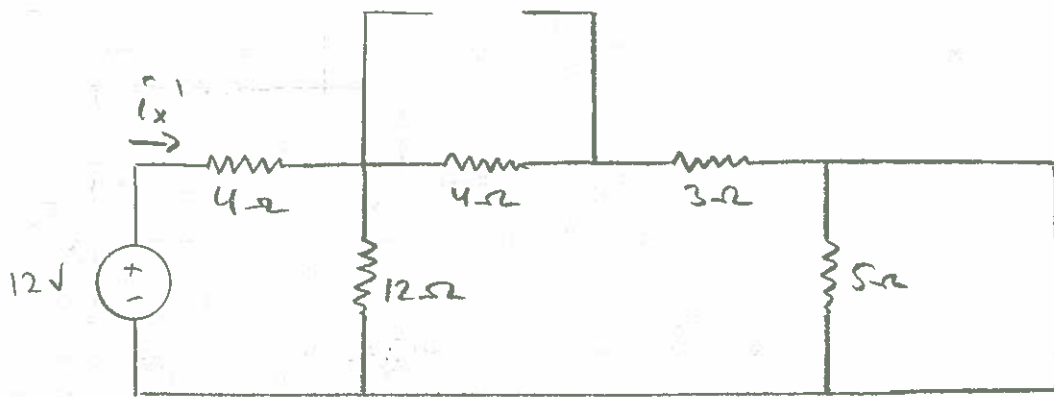
Find i_x by superpositiona) i_x due to 12V source, i_x' 

$$4 + 3 + 5 = 12 \Omega \text{ (in series)}$$

$$12 // 12 = 6 \Omega$$

$$i_x' = \frac{12}{4+6} = \underline{1.2 A}$$

b) i_x due to 2A source, i_x''

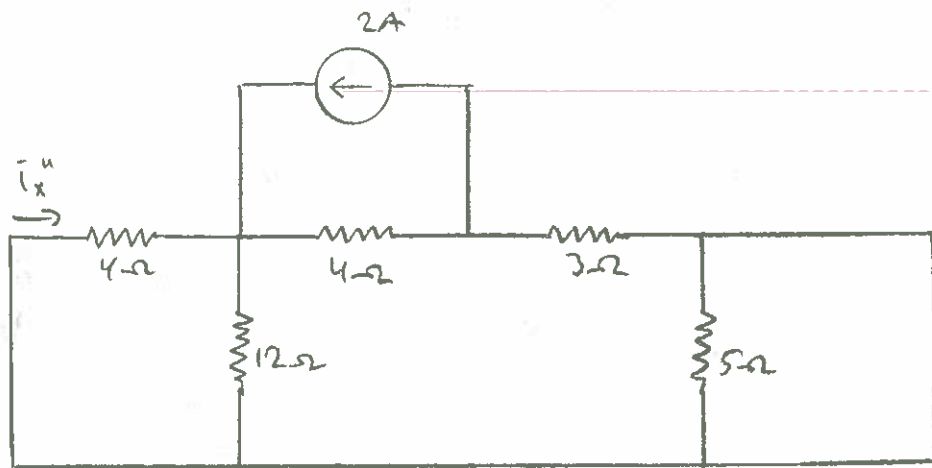


$$4 // 12 = \frac{4 \cdot 12}{4 + 12} = 3 \Omega \quad \rightarrow i_1$$

$$3 + 5 + 3 = 11 \Omega$$

$$i_1 = 2 \cdot \frac{4}{4 + 11} = 0.533 \text{ A} \quad (\text{current division})$$

$$i_x'' = -i_1 \cdot \frac{12}{12 + 4} = -0.4 \text{ A}$$

c) i_x due to 3A source, i_x'''

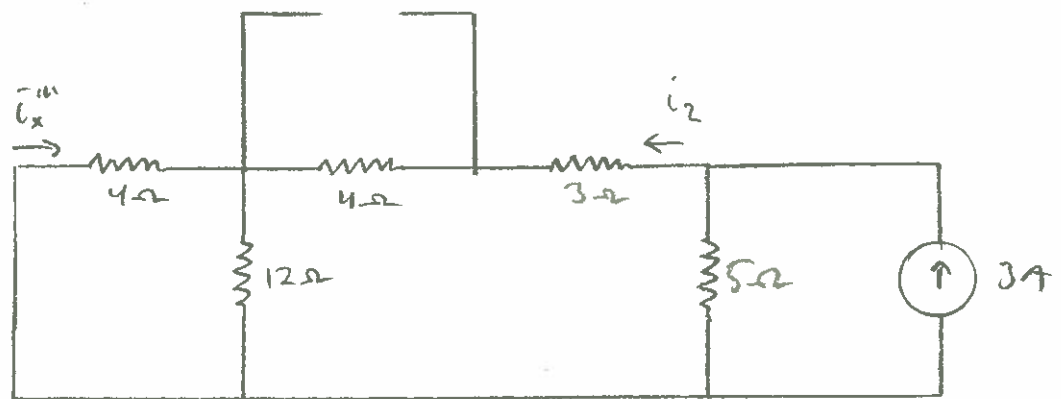

$$4 // 12 = 3 \Omega$$

$$3 + 4 + 3 = 10 \Omega$$

$$i_2 = 3 \cdot \frac{5}{5 + 10} = 1 \text{ A}$$

$$i_x^{(3)} = -i_2 \cdot \frac{12}{12+4} = -0.75A$$

d) Add contributions

$$i_x = i_x^{(1)} + i_x^{(2)} + i_x^{(3)} = 1.2 - 0.4 - 0.75 = \underline{0.05A}$$