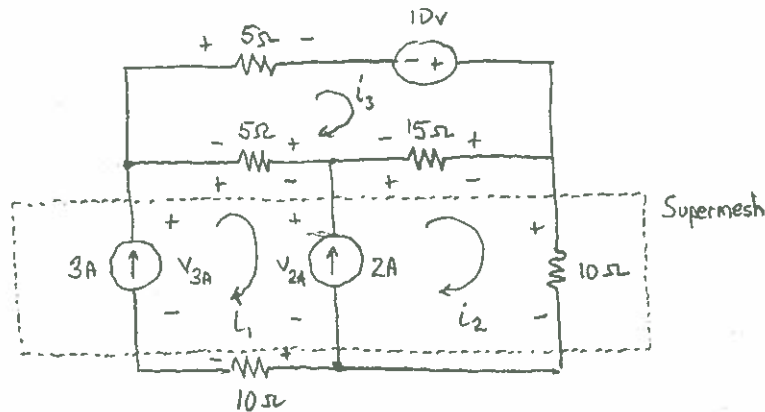


Question 1



- (a) We have a supermesh in which i_1 is already known. $i_1 = 3A$.
From the supermesh dependence equation

$$i_2 - i_1 = 2A, \quad \text{so} \quad i_2 = i_1 + 2A = 5A$$

Mesh 3: $5i_3 - 10 + 15(i_3 - i_2) + 5(i_3 - i_1) = 0$

$$5i_3 + 15i_3 - 75 + 5i_3 - 15 = 10$$

$$25i_3 = 100$$

$$\text{so } i_3 = 4A$$

$i_1 = 3A$
$i_2 = 5A$
$i_3 = 4A$

- (b) KVL in mesh 2 gives: $-V_{2A} + 15(i_2 - i_3) + 10i_2 = 0$

$$-V_{2A} + 15 \times 1 + 10 \times 5 = 0$$

$$V_{2A} = 65V$$

Power in the 2-amp source: $P_{2A} = -V_{2A}(i_2 - i_1)$

$$= -65 \times 2$$

$$= -130 \text{ W (130 W supplied)}$$

KVL in mesh 1 gives: $-V_{3A} + 5(i_1 - i_3) + V_{2A} + 10i_1 = 0$

$$-V_{3A} + 5 \times -1 + 65 + 10 \times 3 = 0$$

$$V_{3A} = 90V$$

Power in the 3-amp source $P_{3A} = -V_{3A}i_1$


$$= -90 \times 3$$

$$= -270 \text{ W (270 W supplied)}$$

Power in the 10-volt source:

$$\begin{aligned} P_{10v} &= -10 i_3 \\ &= -10 \times 4 \\ &= -40 \text{ W (40 W supplied)} \end{aligned}$$

Question 2

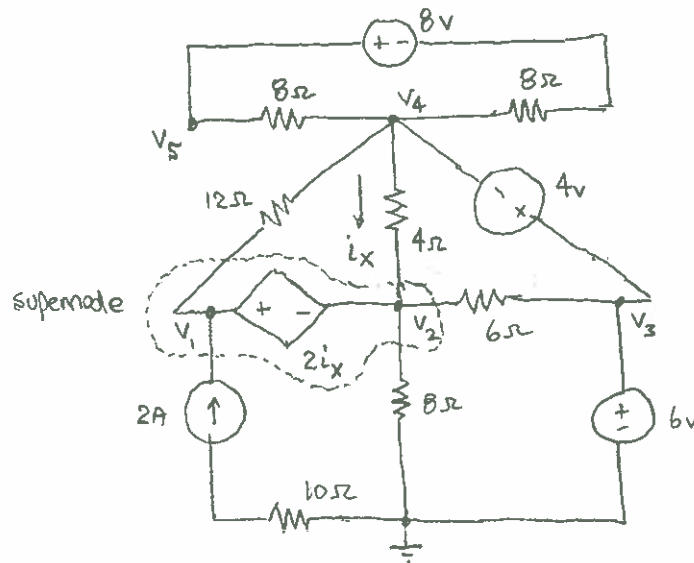

(a) By inspection, $V_3 = 6$ and $V_4 = 6 - 4 = 2\text{V}$.

$$\text{Supernode equation: } -2 + \frac{V_1 - V_4}{12} + \frac{V_2}{8} + \frac{V_2 - V_4}{4} + \frac{V_2 - V_3}{6} = 0$$

$$\begin{aligned} (\times 24) \quad -48 + 2(V_1 - 2) + 3V_2 + 6(V_2 - 2) + 4(V_2 - 6) &= 0 \\ -48 + 2V_1 - 4 + 3V_2 + 6V_2 - 12 + 4V_2 - 24 &= 0 \end{aligned}$$

$$2V_1 + 13V_2 = 88 \quad (1)$$

$$\text{Supernode dependence: } V_1 - V_2 = 2i_x \quad (2)$$

$$\text{Dependent source: } i_x = \frac{V_4 - V_2}{4} = \frac{2 - V_2}{4}$$

Combining this with equation (2),

$$V_1 - V_2 = \frac{2 - V_2}{2}$$

$$2V_1 - 2V_2 = 2 - V_2$$

$$2V_1 - V_2 = 2 \quad (3)$$

Subtract equation (3) from (1):

$$\begin{aligned} 2V_1 + 13V_2 &= 88 \\ - (2V_1 - V_2 &= 2) \end{aligned}$$


$$14V_2 = 86$$

$$\therefore V_2 = \frac{86}{14} = \frac{43}{7} = 6.143 \text{ v.}$$

From equation (3), $2V_1 = 2 + V_2$
 $2V_1 = 2 + \frac{43}{7} = \frac{57}{7}$

$$\therefore V_1 = \frac{57}{14} = 4.071 \text{ v}$$

(b) In the top part of the circuit

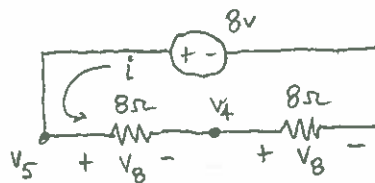


This is a simple voltage divider
 with $V_8 = \frac{1}{2} \times 8 \text{ v.}$

$$V_8 = 4 \text{ v.}$$

We also have $V_5 - V_4 = V_8 = 4 \text{ v.}$

From part (a), $V_4 = 2 \text{ v,}$ so $V_5 = 2 + 4 = 6 \text{ v}$

Question 3

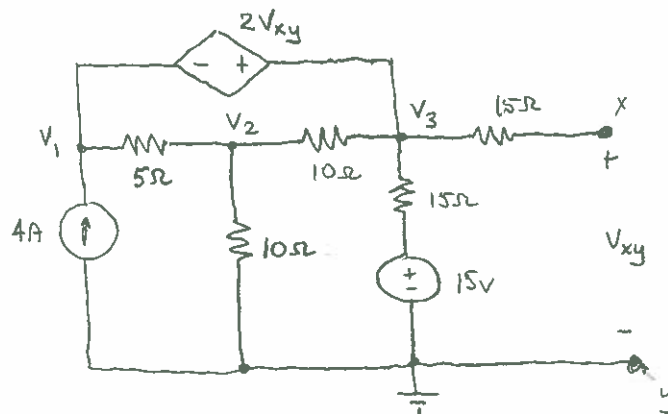

(a) Thevenin voltage.

Supernode equation: $-4 + \frac{V_1 - V_2}{5} + \frac{V_3 - V_2}{10} + \frac{V_2 - 15}{15} = 0$

$$(\times 30) \quad -120 + 6(V_1 - V_2) + 3(V_3 - V_2) + 2(V_2 - 15) = 0$$

$$6V_1 - 6V_2 + 3V_3 - 3V_2 + 2V_3 - 30 = 120$$

$$6V_1 - 9V_2 + 5V_3 = 150 \quad (1)$$

Supernode dependence: $V_3 - V_1 = 2V_{xy}$

With terminals x and y open-circuited, $V_{xy} = V_3$, so

$$V_3 - V_1 = 2V_3$$

$$V_1 = -V_3 \quad (2)$$

Node v_2 : $\frac{V_2 - V_1}{5} + \frac{V_2}{10} + \frac{V_2 - V_3}{10} = 0$

$$\begin{aligned} (\times 10) \quad 2(V_2 - V_1) + V_2 + V_2 - V_3 &= 0 \\ 2V_2 - 2V_1 + V_2 + V_2 - V_3 &= 0 \end{aligned}$$

$$-2V_1 + 4V_2 - V_3 = 0 \quad (3)$$

Substitute equation (2) into (1) and (3)

$$\begin{aligned} -6V_3 - 9V_2 + 5V_3 &= 150 \\ -9V_2 - V_3 &= 150 \end{aligned} \quad (4)$$

$$\begin{aligned} 2V_3 + 4V_2 - V_3 &= 0 \\ 4V_2 + V_3 &= 0 \end{aligned} \quad (5)$$

Add (4) and (5):


$$\begin{aligned} 4V_2 + V_3 &= 0 \\ -9V_2 - V_3 &= 150 \end{aligned}$$

$$-5V_2 = 150, \text{ so } V_2 = -30\text{v.}$$

And, from (3), $V_3 = -4V_2 = 120\text{v}$

Therefore, $V_t = V_{oc} = V_3 = 120\text{v}$

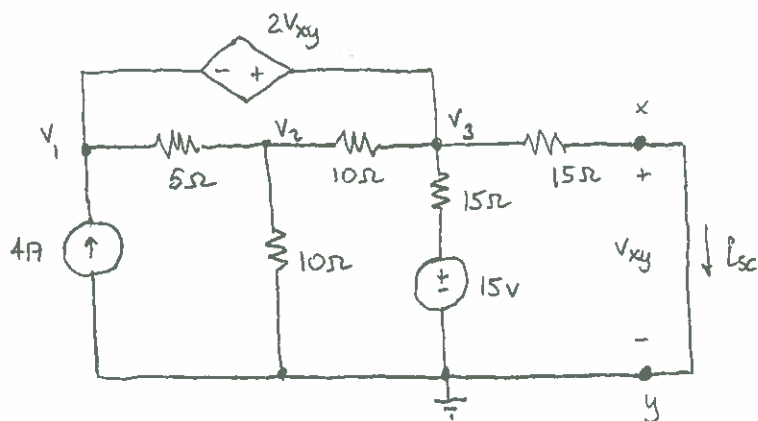Now Thevenin resistance. Unfortunately, there is a dependent source, so we must determine the short-circuit current i_s .



With the short circuit applied, $V_{xy} = 0$, so the dependent voltage source becomes a short circuit, so $V_3 = V_1$.

$$\text{Supernode equation: } -4 + \frac{V_1 - V_2}{5} + \frac{V_3 - V_2}{10} + \frac{V_3 - 15}{15} + \frac{V_3}{15} = 0$$

This is i_{sc}

$$(x30) \quad -120 + 6V_1 - 6V_2 + 3V_3 - 3V_2 + 2V_3 - 30 + 2V_3 = 0$$

$$6V_1 - 9V_2 + 7V_3 = 150$$

$$\text{With } V_1 = V_3, \quad 6V_3 - 9V_2 + 7V_3 = 150$$

$$-9V_2 + 13V_3 = 150 \quad (1)$$

$$\text{Node } V_2 \text{ (equation unchanged): } -2V_1 + 4V_2 - V_3 = 0$$

$$\text{so } -2V_3 + 4V_2 - V_3 = 0$$

$$4V_2 - 3V_3 = 0 \quad (2)$$

From (2), $V_2 = \frac{3}{4}V_3$, so (1) becomes

$$-9\left(\frac{3}{4}V_3\right) + 13V_3 = 150$$

$$(x4) \quad -27V_3 + 52V_3 = 600$$

$$25V_3 = 600$$

$$\text{so } V_3 = 24\text{V}$$


Therefore

$$i_{sc} = \frac{V_3}{15} = \frac{24}{15} = \frac{8}{5} = 1.6 \text{ A}$$

Finally,

$$R_L = \frac{V_L}{i_{sc}} = \frac{120}{8/5} = 75\Omega$$

(b) Using the Thevenin equivalent,

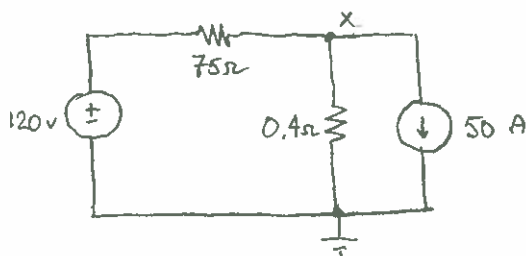

$$\text{At node } x: \frac{V_x - 120}{75} + 50 + \frac{V_x}{0.4} = 0$$


$$(x \cdot 75) \quad V_x - 120 + 3750 + 187.5V_x = 0$$

$$188.5V_x = 3630$$

$$V_x = 19.26 \text{ v.}$$


Question 4

(a) With only V_1 active:

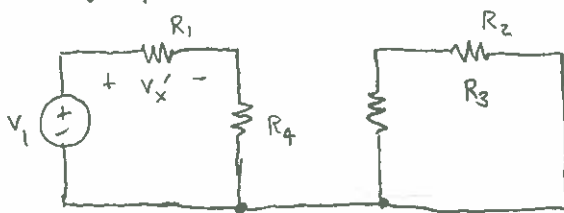

This is a simple voltage divider: $V'_x = \frac{R_1}{R_1 + R_4} \cdot V_1$


(b) With only I active,

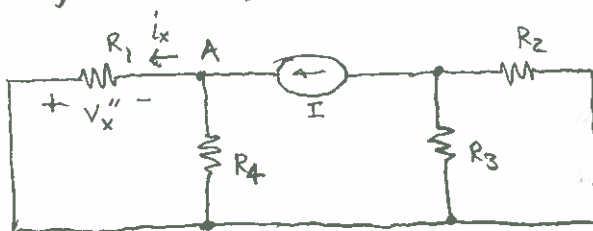

At node A, we have current division: $I_x = \frac{R_4}{R_1 + R_4} \cdot I$

$$\text{and } V''_x = -I_x R_1 = \frac{-R_1 R_4}{R_1 + R_4} \cdot I$$

(c) With only V_2 active

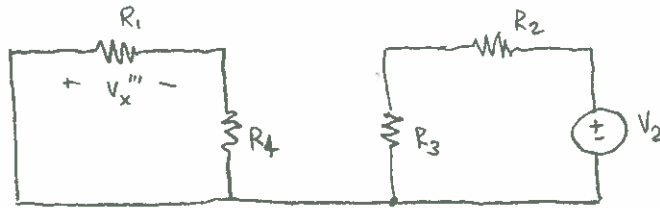

No current flow is possible in R_1 , so

$$V_x''' = 0$$

Therefore, by superposition:

$$\begin{aligned} V_x &= V_x' + V_x'' + V_x''' \\ &= V_1 \left(\frac{R_1}{R_1 + R_4} \right) - I \left(\frac{R_1 R_4}{R_1 + R_4} \right) \\ &= \frac{R_1}{R_1 + R_4} (V - IR_4) \end{aligned}$$