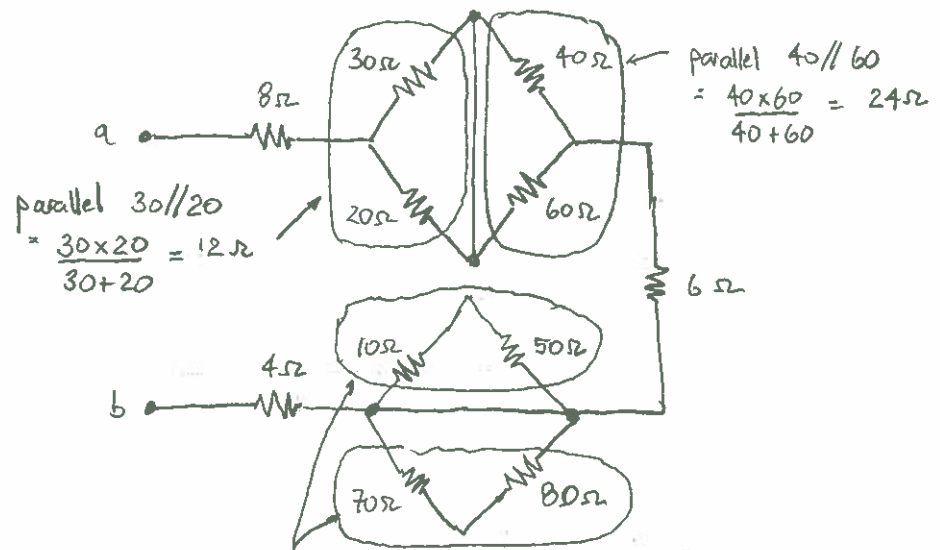


Question 1

(a)




Series resistors in parallel with a short-circuit.

$$\text{Total equivalent resistance } R_{ab} = 8 + 12 + 24 + 6 + 4$$

$$R_{ab} = 54\Omega$$

(b)

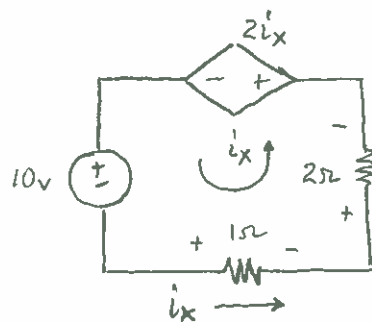

Defining a loop current i_x as shown, we may write a KVL equation

$$10 + 1 \cdot i_x + 2 - i_x + 2i_x = 0$$

$$10 + 5i_x = 0$$

$$\text{so } i_x = -2\text{ A}$$

Using the passive reference convention for the dependent source,


$$P_{2i_x} = + (2i_x)(i_x)$$

\uparrow voltage \uparrow current

$$= (-4)(-2) = 8\text{ W}$$

$$P_{2i_x} = 8\text{ W (absorbing)}$$

(c)

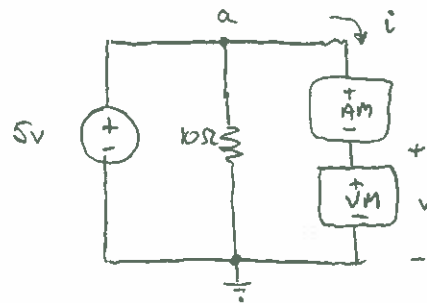


Since the voltmeter behaves like an open circuit, no current flows

$$i = 0$$

Since the ammeter behaves like a short circuit, the voltage across the voltmeter will be $V = V_a$

$$V = 5V$$

(d)

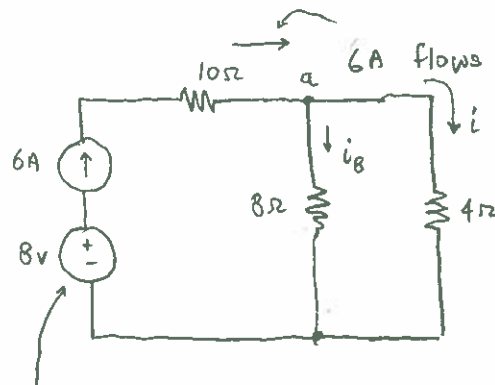

6A flows into node A irrespective of the voltage source and 10Ω resistor.


Voltage source does not influence the calculation.

We have a simple current divider

$$i = \frac{8\Omega}{8+4} \times 6A = 4A$$

$$i = 4A$$

(e)

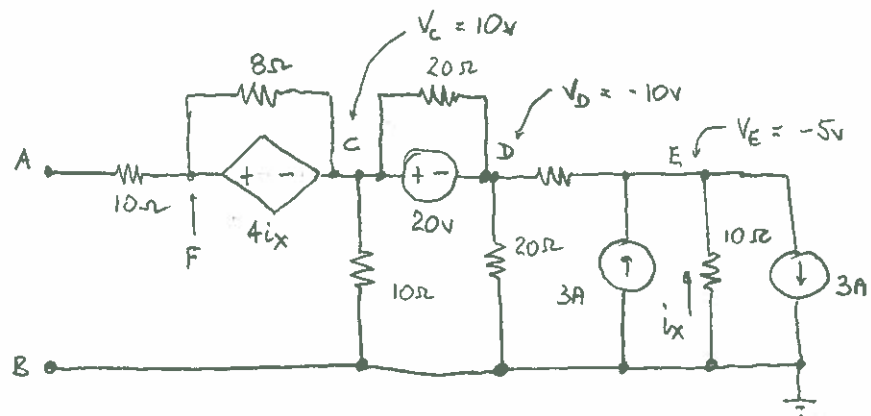


A complete analysis of this circuit is unnecessary. The key steps involve simply calculating i_x and the voltage at F.

Since we know $V_E = -5\text{V}$, then i_x , as drawn, will be

$$i_x = \frac{0 - V_E}{10} = \frac{0 - (-5)}{10} = 0.5\text{A}$$

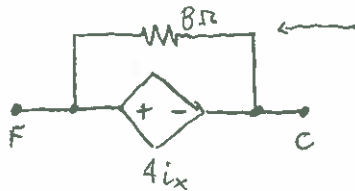Then at node F, we see that $V_F - V_C = 4i_x$



A resistor in parallel with a voltage source has no effect on the voltage of the source. Ignore this resistor.


$$\begin{aligned} \text{With } V_C = 10\text{V}, \text{ then } V_F &= V_C + 4i_x \\ &= 10 + 4(0.5) \\ &= 12\text{V} \end{aligned}$$

Finally, since the terminal A is open-circuited, $V_A = V_F$

$$\boxed{V_A = 12\text{V}}$$

Question 2

(a) Node-voltage method

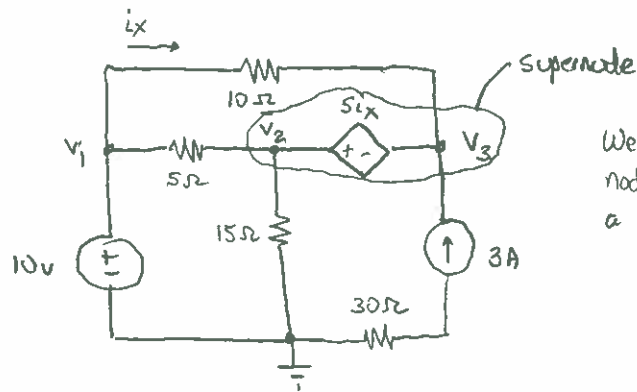

We know $V_1 = 10$, and nodes 2 and 3 form a supernode

$$\boxed{V_1 = 10\text{V}}$$

Supernode equation: $\frac{V_2 - V_1}{5} + \frac{V_2}{15} + \frac{V_3 - V_1}{10} - 3 = 0$

$$\begin{aligned} (\times 30) \quad 6V_2 - 60 + 2V_2 + 3V_3 - 30 - 90 &= 0 \\ 8V_2 + 3V_3 &= 180 \quad \leftarrow (1) \end{aligned}$$

Supernode dependence: $V_2 - V_3 = 5i_x$

$$\text{where } i_x = \frac{V_1 - V_3}{10} = \frac{10 - V_3}{10}$$

$$\text{so } V_2 - V_3 = 5 \left(\frac{10 - V_3}{10} \right)$$

$$V_2 - V_3 = 5 - \frac{V_3}{2}$$

$$\text{so } V_2 - 5 = \frac{V_3}{2}$$

$$\text{or } V_3 = 2V_2 - 10 \quad \leftarrow (2)$$

Combining (1) and (2)


$$\begin{aligned} 8V_2 + 3(2V_2 - 10) &= 180 \\ 14V_2 &= 210 \end{aligned}$$

$$\boxed{V_2 = 15\text{V}}$$

$$\text{and } V_3 = 2(15) - 10 = 20\text{V}$$

$$\boxed{V_3 = 20\text{V}}$$

(b) Mesh-current method

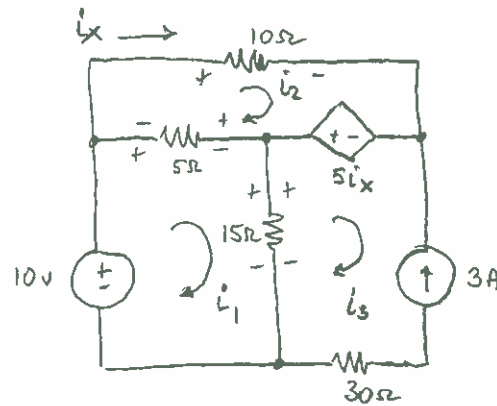

We know immediately that

$$i_3 = -3A$$

and that $i_x = i_2$.

Two mesh equations needed.

$$\begin{aligned} \text{Mesh 1: } & -10 + 5(i_1 - i_2) + 15(i_1 - i_3) = 0 \\ & -10 + 20i_1 - 5i_2 + 45 = 0 \\ & 20i_1 - 5i_2 = -35 \end{aligned} \quad \leftarrow (1)$$

$$\begin{aligned} \text{Mesh 2: } & 5(i_2 - i_1) + 10i_2 - 5i_x = 0 \\ & 10i_2 - 5i_1 = 0 \\ & i_1 = 2i_2 \end{aligned} \quad \leftarrow (2)$$

Substitute (2) into (1)

$$\begin{aligned} 20(2i_2) - 5i_2 &= -35 \\ 35i_2 &= -35 \end{aligned}$$

$$\text{so } i_2 = -1A$$


and from (2),

$$i_1 = -2A$$

Question (3)

(a) Thevenin voltage by superposition.

(i) Zero the voltage source

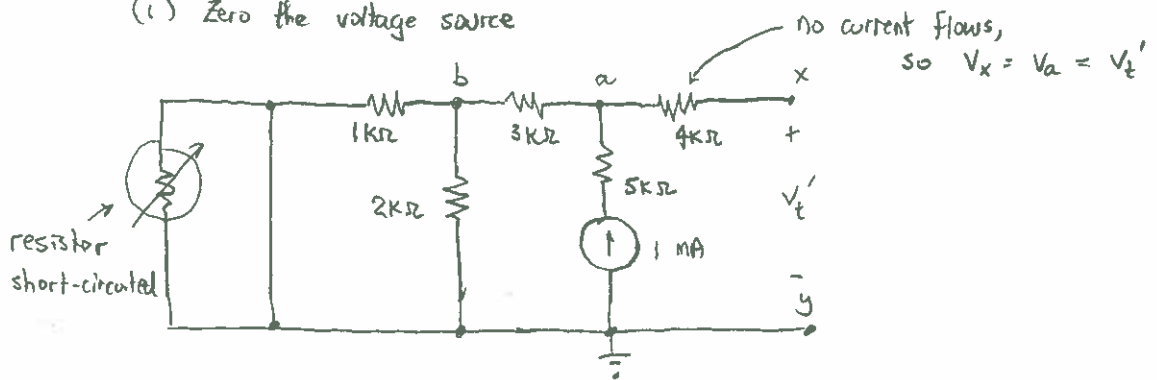Node-voltage method, where $V_t' = V_a$.


$$\begin{aligned} \text{Node a: } & -0.001 + \frac{V_a - V_b}{3000} = 0 \\ (\times 3000) & -3 + V_a - V_b = 0 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{Node b: } & \frac{V_b}{1000} + \frac{V_b}{2000} + \frac{V_b - V_a}{3000} = 0 \\ (\times 6000) & 6V_b + 3V_b + 2V_b - 2V_a = 0 \\ & 11V_b = 2V_a \end{aligned} \quad (2)$$

$$\begin{aligned} \text{From (1), } V_b = V_a - 3, \text{ so } & 11(V_a - 3) = 2V_a \\ & 11V_a - 2V_a = 33 \\ & V_a = 3.667 \text{ V} \end{aligned}$$

$$\text{Thus, } V_t' = 3.667 \text{ V}$$

(ii) Zero the current source

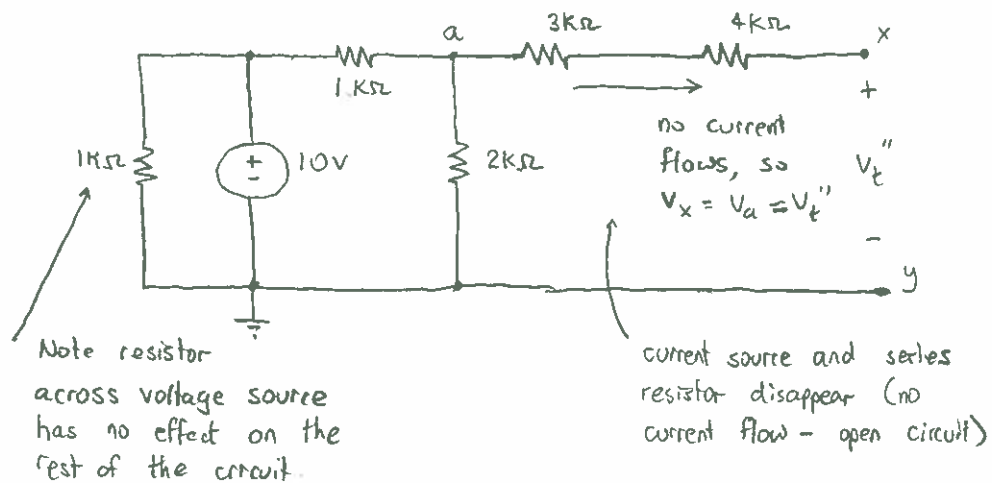

Here we have a simple resistor voltage divider,


$$\text{so } V_t'' = \frac{2000}{2000 + 1000} \times 10 = 6.667 \text{ v}$$

Finally, by superposition

$$V_t = V_t' + V_t'' \\ = 3.667 + 6.667$$

$$V_t = 10.333 \text{ v}$$


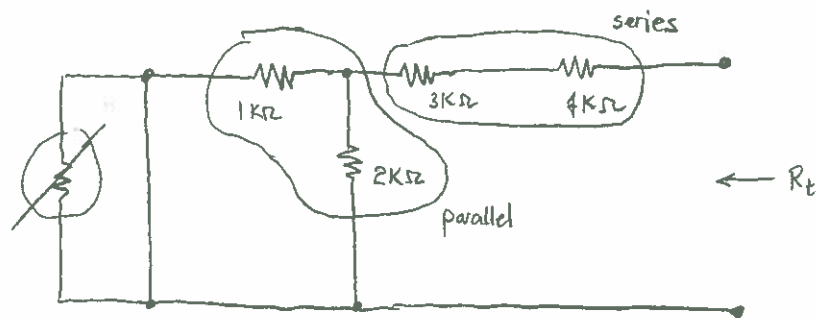
(b) Thevenin resistance. There are no dependent sources, so we may zero the sources.



By inspection: $R_t = (1\text{k}\Omega \parallel 2\text{k}\Omega) + 3\text{k}\Omega + 4\text{k}\Omega$

$$R_t = 7666.67\Omega$$

(c) The Norton equivalent circuit

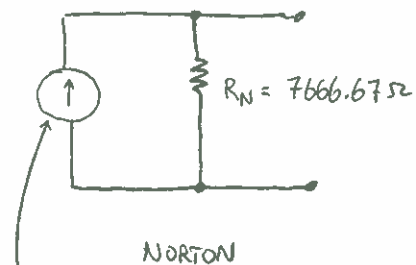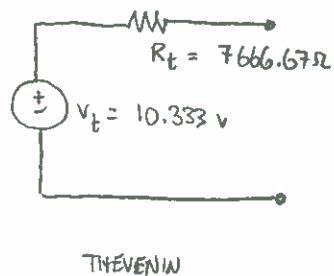

$$i_n = \frac{V_t}{R_t} = \frac{10.333}{7666.67}$$

$$= 1.348 \text{ mA}$$