
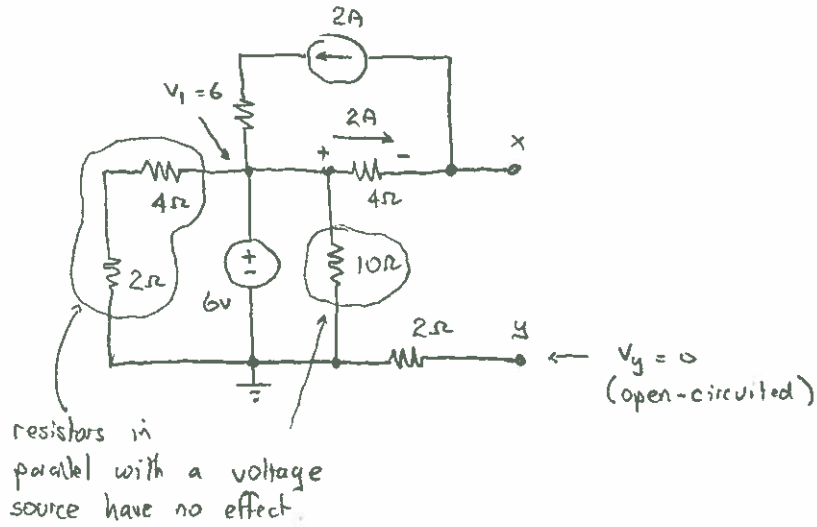


Question 1

(a)

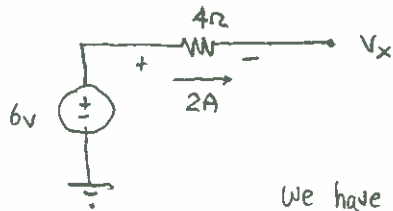


With terminals x and y open-circuited in this way, $V_y = 0$, and V_x is determined by the following key circuit elements.



We have $V_x = 6 - 2 \times 4 = -2$

so $V_{xy} = -2V$

(b)

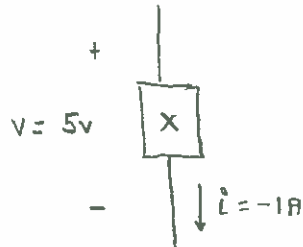


By the passive reference convention,

$P_x = Vi = 5(-1)$

$P_x = -5W$
(so delivering 5W of power)

(c)

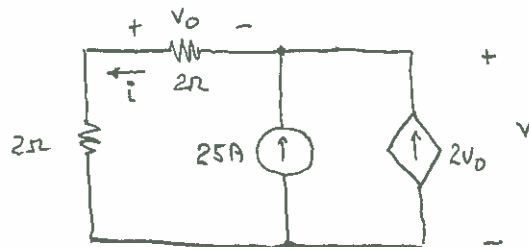

We have


$i = 25 + 2V_0$

and $V_0 = -2i$

Combining these two equations, $V_0 = -(25 + 2V_0)$
 $= -50 - 4V_0$

so $5V_0 = -50 \quad \therefore V_0 = -10V$

We now have

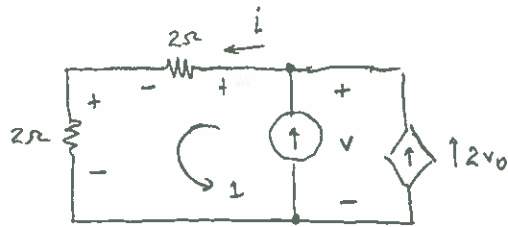

$$i = 25 + 2V_0$$

$$= 25 + 2(-10)$$

$$= 5A$$

KVL around loop 1 gives us $-V + 2i + 2i = 0$

$$V = 4i$$

$$V = 20W$$


Therefore, the power in the dependent source P_{2V_0} is

$$P_{2V_0} = -(2V_0)V \quad \text{by passive reference convention}$$


$$= -(-20)(20) = +400W$$

$P_{2V_0} = 400W \text{ (absorbing)}$

(d)

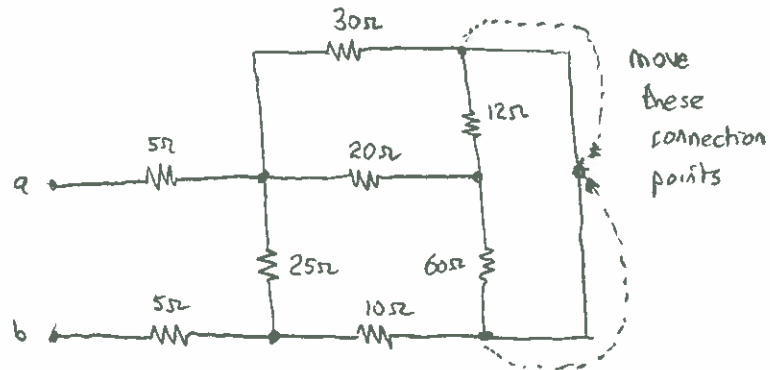


Redraw

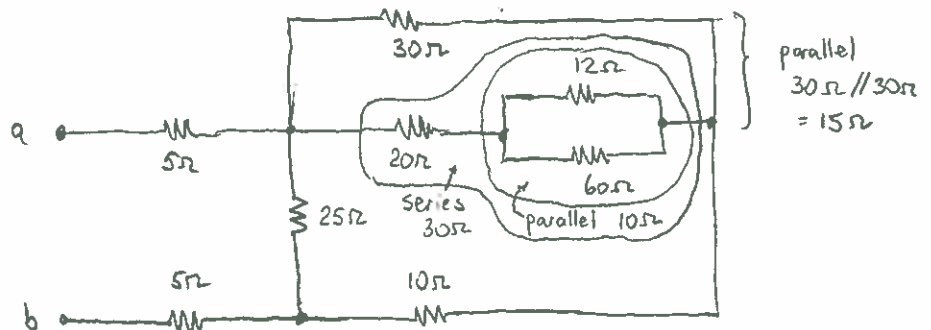

parallel
 $30\Omega // 30\Omega$
 $= 15\Omega$

Simplify

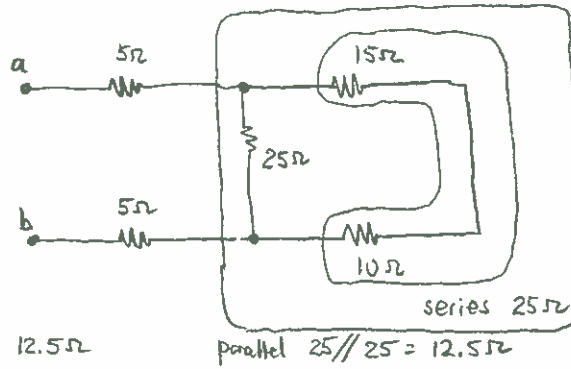

Finally,




$$R_{eq} = 5\Omega + 5\Omega + 12.5\Omega$$

$$\text{parallel } 25 // 25 = 12.5\Omega$$


$$R_{eq} = 22.5\Omega$$

AMPAD

(e)

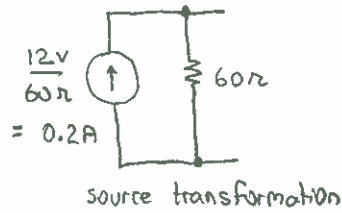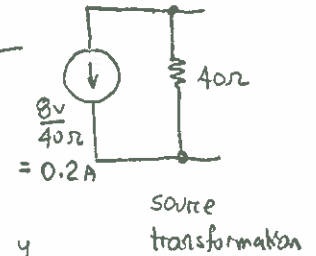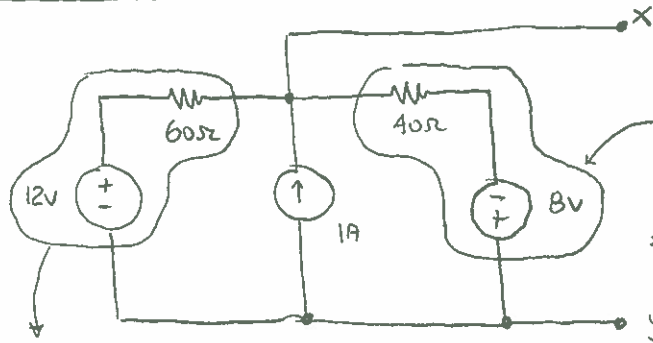


Redrawing

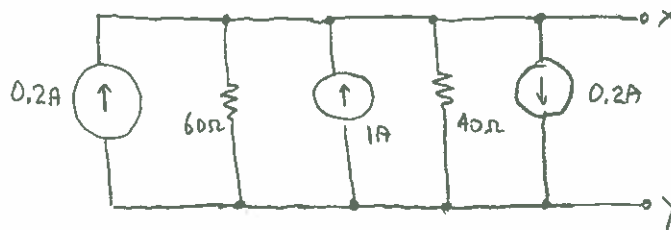

Current sources in parallel add:


$$0.2 + 1 - 0.2 = 1A$$

Resistors in parallel: $\frac{60 \times 40}{60 + 40} = 24\Omega$

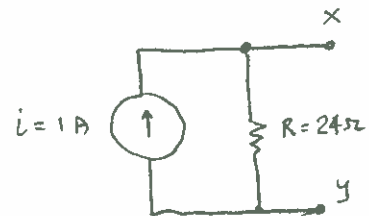

Question 2

(a) Setting up for node-voltage method

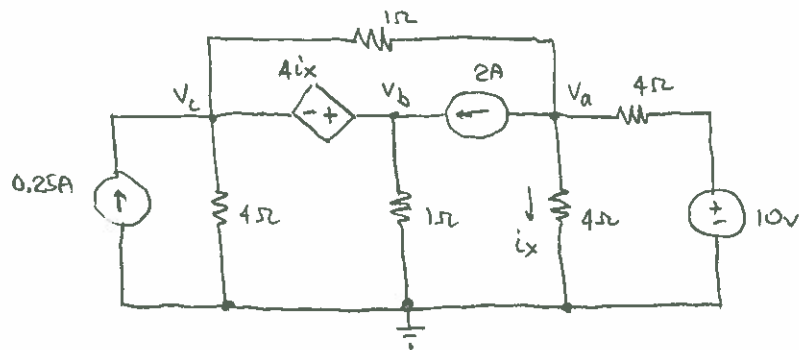

$$\begin{aligned} \text{Node a: } \frac{V_a - 10}{4} + \frac{V_a}{4} + \frac{V_a - V_c}{1} + 2 &= 0 \\ V_a - 10 + V_a + 4V_a - 4V_c + 8 &= 0 \\ 6V_a - 4V_c &= 2 \quad (1) \end{aligned}$$

$$\begin{aligned} \text{Supernode bc: } \frac{V_c}{4} - 0.25 + \frac{V_c - V_a}{1} + \frac{V_b}{1} - 2 &= 0 \\ V_c - 1 + 4V_c - 4V_a + 4V_b - 8 &= 0 \\ -4V_a + 4V_b + 5V_c &= 9 \quad (2) \end{aligned}$$

$$\begin{aligned} \text{Supernode dependence: } V_b - V_c &= 4i_x \quad \text{and } i_x = \frac{V_a}{4} \\ \text{so } V_b - V_c &= 4 \frac{V_a}{4} = V_a \\ -V_a + V_b - V_c &= 0 \quad (3) \end{aligned}$$

Solve for 3 unknowns, 3 equations

Subtract 4 times equation (3) from (2)

$$\begin{aligned} (2) \quad -4V_a + 4V_b + 5V_c &= 9 \\ - 4 \times (3) \quad -4V_a + 4V_b - 4V_c &= 0 \\ \hline &= 9V_c = 9, \quad \text{so } \boxed{V_c = 1.} \end{aligned}$$


$$\begin{aligned} \text{From (1), } 6V_a - 4(1) &= 2 \\ 6V_a &= 6 \end{aligned}$$

$$\text{so } \boxed{V_a = 1}$$

and from (3), $-1 + V_b - 1 = 0$


$$\text{so } \boxed{V_b = 2}$$

(b) Any method will do.

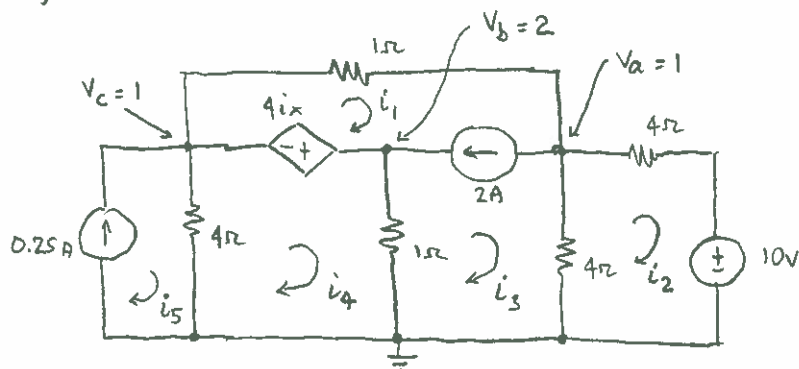

Clearly, $i_5 = 0.25 \text{ A}$. By far the easiest method is to relate branch currents and mesh currents

E.g.,

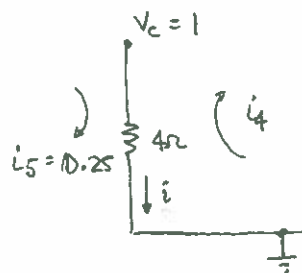

$$\text{branch current } i = \frac{V_c}{4} = 0.25 \text{ A}$$

$$\text{mesh currents } i_5 - i_4 = i$$

$$\text{so } \boxed{i_4 = 0 \text{ A}}$$

$$\text{Similarly, } i_4 - i_3 = \frac{V_b}{1\Omega}, \text{ so } \boxed{i_3 = -\frac{V_b}{1} = -2 \text{ A}}$$

$$\text{And, } i_3 - i_2 = \frac{V_a}{4}, \text{ so } i_2 = i_3 - \frac{V_a}{4} = -2 - \frac{1}{4}$$

$$\boxed{i_2 = -2.25 \text{ A}}$$

$$\text{Finally, using the supermesh dependence: } \begin{aligned} i_1 - i_3 &= 2 \\ i_1 &= 2 + i_3 \end{aligned}$$

$$\boxed{\begin{aligned} i_1 &= 2 + -2 \\ &= 0 \end{aligned}}$$

Alternate (labour-intensive) solution to part (b)!

As before, by inspection $i_5 = 0.25$

$$\text{Mesh } i_4: \quad 4(i_4 - i_5) - 4i_x + 1(i_4 - i_3) = 0$$

$$4i_4 - 4i_5 - 4i_x + i_4 - i_3 = 0$$

$$4i_4 - 4(0.25) - 4i_x + i_4 - i_3 = 0$$

$$4i_4 - 1 - 4i_x + i_4 - i_3 = 0$$

$$5i_4 - i_3 - 4i_x = 1$$

$$\text{And: } i_x = i_3 - i_2$$

$$5i_4 - i_3 - 4(i_3 - i_2) = 1$$

$$5i_4 - i_3 - 4i_3 + 4i_2 = 1$$

$$4i_2 - 5i_3 + 5i_4 = 1 \quad (1)$$

$$\text{Supermesh } i_1, i_3: \quad 1 \times i_1 + 4(i_3 - i_2) + 1 \times (i_3 - i_4) + 4i_x = 0$$

$$i_1 + 4i_3 - 4i_2 + i_3 - i_4 + 4i_x = 0$$

$$i_1 - 4i_2 + 5i_3 - i_4 + 4i_x = 0$$

$$\text{And: } i_x = i_3 - i_2$$

$$i_1 - 4i_2 + 5i_3 - i_4 + 4(i_3 - i_2) = 0$$

$$i_1 - 4i_2 + 6i_3 - i_4 + 4i_3 - 4i_2 = 0$$

$$i_1 - 8i_2 + 9i_3 - i_4 = 0 \quad (2)$$

$$\text{Supermesh dependence: } i_1 - i_3 = 2 \quad (3)$$

$$\text{Mesh } i_2: \quad 4(i_2 - i_3) + 4i_2 + 10 = 0$$

$$8i_2 - 4i_3 = -10 \quad (4)$$

Solve for 4 unknowns and 4 equations:

$$4i_2 - 5i_3 + 5i_4 = 1 \quad (1)$$

$$i_1 - 8i_2 + 9i_3 - i_4 = 0 \quad (2)$$

$$i_1 - i_3 = 2 \quad (3)$$

$$8i_2 - 4i_3 = -10 \quad (4)$$

Add (2) and (4)

$$\begin{array}{r}
 i_1 - 8i_2 + 9i_3 - i_4 = 0 \\
 + \quad \quad \quad 8i_2 - 4i_3 = -10 \\
 \hline
 = i_1 + 5i_3 - i_4 = -10
 \end{array} \quad (5)$$

From (3), $i_1 = i_3 + 2$, so (5) becomes

$$\begin{array}{r}
 i_3 + 2 + 5i_3 - i_4 = -10 \\
 6i_3 - i_4 = -12
 \end{array} \quad (6)$$

From (4), $8i_2 = 4i_3 - 10$, so $i_2 = \frac{1}{8}(4i_3 - 10)$. Substitute into (1),

$$\begin{array}{r}
 \frac{1}{2}(4i_3 - 10) - 5i_3 + 5i_4 = 1 \\
 4i_3 - 10 - 10i_3 + 10i_4 = 2 \\
 -6i_3 + 10i_4 = 12
 \end{array} \quad (7)$$

From (6), $i_4 = 12 + 6i_3$, so using (7)

$$\begin{array}{r}
 -6i_3 + 10(12 + 6i_3) = 12 \\
 -6i_3 + 120 + 60i_3 = 12 \\
 54i_3 = -108
 \end{array}$$

$$i_3 = -2 \text{ A}$$

$$\text{Then, } \boxed{
 \begin{array}{l}
 i_4 = 12 + 6i_3 \\
 = 0 \text{ A}
 \end{array}
 }$$

$$\begin{array}{r}
 \text{From (4), } 8i_2 - 4i_3 = -10 \\
 8i_2 - 4(-2) = -10 \\
 8i_2 + 8 = -10 \\
 8i_2 = -18,
 \end{array}$$


$$\boxed{i_2 = -2.25 \text{ A}}$$

$$\begin{array}{r}
 \text{From (3), } i_1 - i_3 = 2 \\
 i_1 = i_3 + 2, \quad \boxed{i_1 = 0 \text{ A}}
 \end{array}$$

GAH!


Question 3

(a) With the load circuit attached

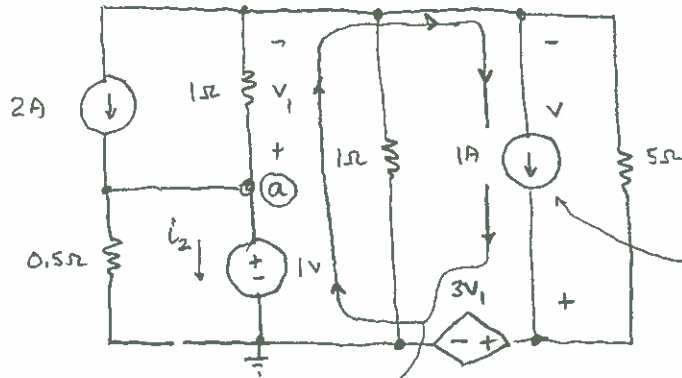

This is delivering 5W of power, so $p = -5w$

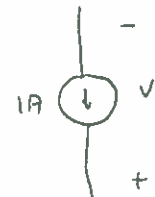This implies the voltage polarity indicated



$$V = \frac{-p}{i} = \frac{-(-5)}{1A} = 5V.$$

KVL around this loop gives

$$\begin{aligned} -V + 3V_1 - 1 + V_1 &= 0 \\ -5 + 3V_1 - 1 + V_1 &= 0 \\ 4V_1 &= 6 \end{aligned}$$


$$\therefore V_1 = 1.5V$$

Node equation at a: $\frac{V_a}{0.5} - 2 + i_2 + i_1 = 0$

With $V_a = 1, V_1 = 1.5,$ $\frac{1}{0.5} - 2 + i_2 + V_1 = 0$


$$2 - 2 + i_2 + 1.5 = 0$$

$$\therefore i_2 = -1.5A$$

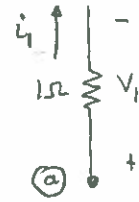

where $i_1 = \frac{V_1}{1\Omega} = 1.5$

(b) With the load disconnected,

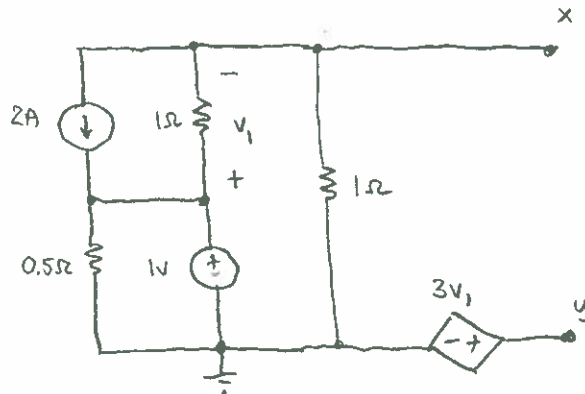

Thevenin voltage: Only one node equation required

$$\text{Node } x: \quad \frac{V_x}{1} + \frac{V_x - 1}{1} + 2 = 0$$

$$V_x + V_x - 1 + 2 = 0$$

$$2V_x = -1$$


$$V_x = -0.5$$

$$\text{We also know } V_1 = 1 - V_x = 1.5 \text{ v}$$

$$\text{Hence, } V_y = 3V_1 = 4.5 \text{ v}$$

$$\text{and } \boxed{V_t = V_{oc} = V_x - V_y = -5 \text{ v}}$$

Now, need i_{sc}

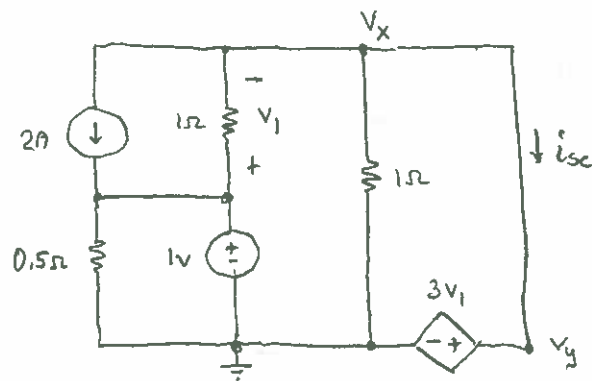

We now have
 $V_x = V_y = 3V_1$

$$\text{At node } x: \quad \frac{V_x}{1} + \frac{V_x - 1}{1} + 2 + i_{sc} = 0 \quad (1)$$

$$\text{where } V_x = 3V_1$$

$$\text{We know } V_1 = 1 - V_x, \text{ so}$$

$$V_x = 3(1 - V_x) = 3 - 3V_x$$

$$4V_x = 3, \text{ so } V_x = \frac{3}{4}$$

$$\text{Substitute into (1): } \frac{3}{4} + \left(\frac{3}{4} - 1\right) + 2 + i_{sc} = 0$$

$$\frac{1}{2} + 2 = -i_{sc}, \text{ so } i_{sc} = -2.5 \text{ A}$$

Finally,
$$R_t = \frac{V_t}{I_{sc}} = \frac{-5}{-2.5} = 2 \Omega$$

