

Name: _____


Lecture Section: _____

L01 - Norm Bartley

L02 - Brent Maundy

L03 - Pouyan (Yani) Jazayeri

L04 - Anis Haque

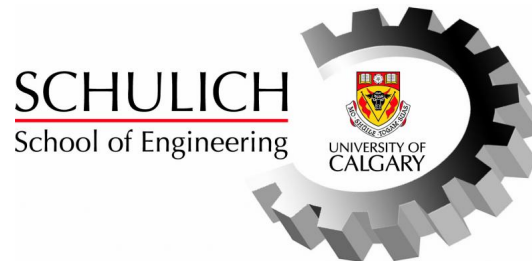

ENGG 225 - Fundamentals of Electrical Circuits and Machines

Midterm Examination

Thursday, February 26, 2015

Time: 7:00 - 8:30 PM


Instructions:

- Time allowed is 90 minutes.
 - The examination is closed-book.
 - Only calculators sanctioned by the Schulich School of Engineering are permitted in the examination.
 - The maximum number of marks is 50, as indicated; please attempt all questions. The midterm examination counts 25% toward the final grade.
 - Please use a pen or heavy pencil to ensure legibility.
 - Please answer questions in the spaces provided; if space is insufficient, please use the back of the pages.
 - Please show your work; where appropriate, marks will be awarded for proper and well-reasoned explanations.
-

UCID: _____


1. [18 marks.] Parts (a)-(f) below each have an identical weighting of three marks. Please answer the questions in the boxes provided.

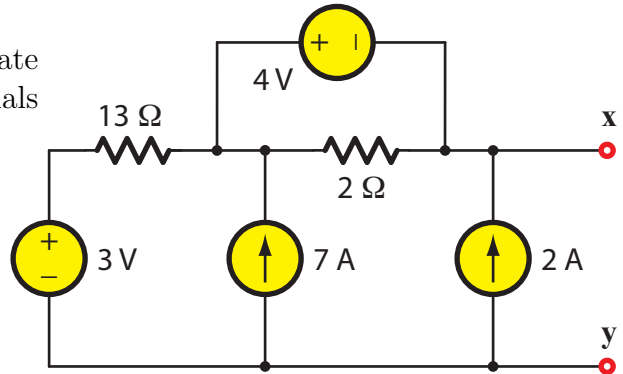- (a) [3] For the circuit given at right, calculate the Thévenin resistance R_t at the terminals **x** and **y**.




Answer: $R_t =$

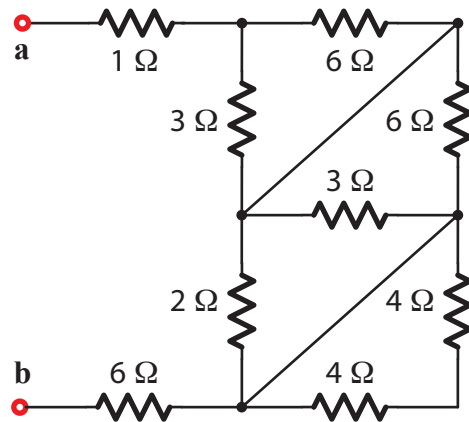- (b) [3] In the circuit at right, determine the equivalent resistance R_{eq} as seen at the terminals **a** and **b**.




Answer: $R_{eq} =$

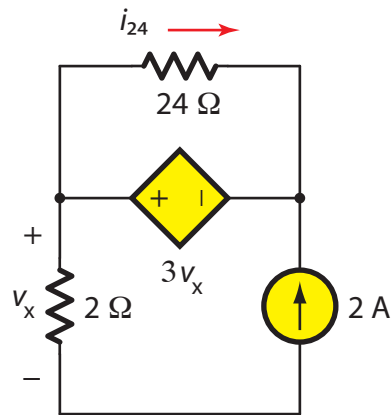- (c) [3] In the circuit at right, determine the current i_{24} through the $24\ \Omega$ resistor.



Answer: $i_{24} =$

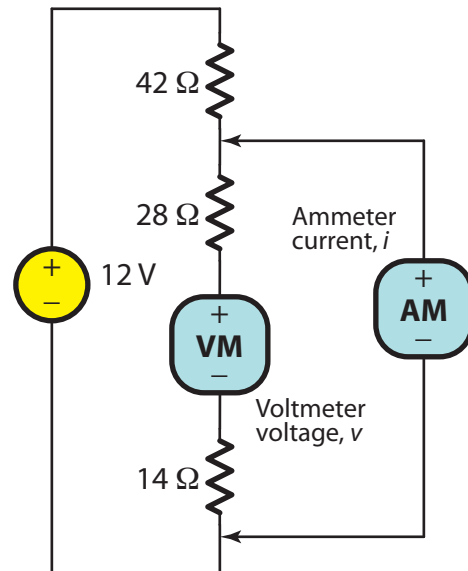
- (d) [3] Suppose that a student in ENGG 225 has designed the voltage divider circuit shown at right, and is about to test the circuit with a voltmeter and an ammeter. However, the student accidentally connects them both *incorrectly*. What will be the voltage reading v , and current reading i in the circuit as shown.



Answer: $v =$

Answer: $i =$

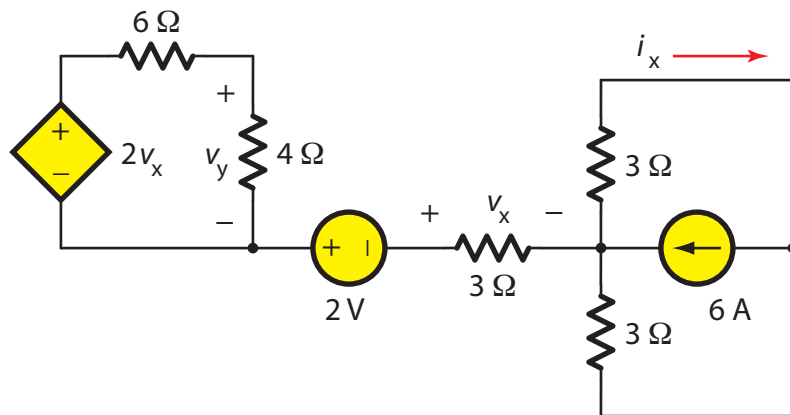
(e) [3] In the circuit at right, find v_y and i_x .



Answer: $v_y =$

Answer: $i_x =$

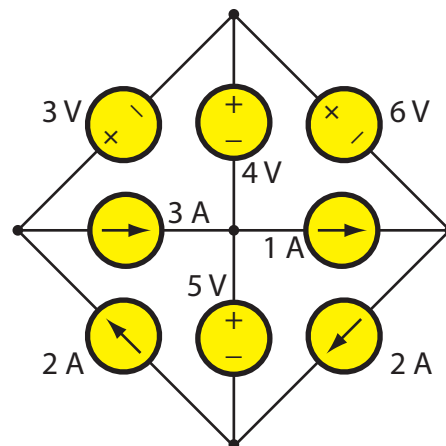
(f) [3] Determine the power p_{4v} in the 4 V source.



Answer: $p_{4v} =$

2. [16 marks.] Consider the circuit below.

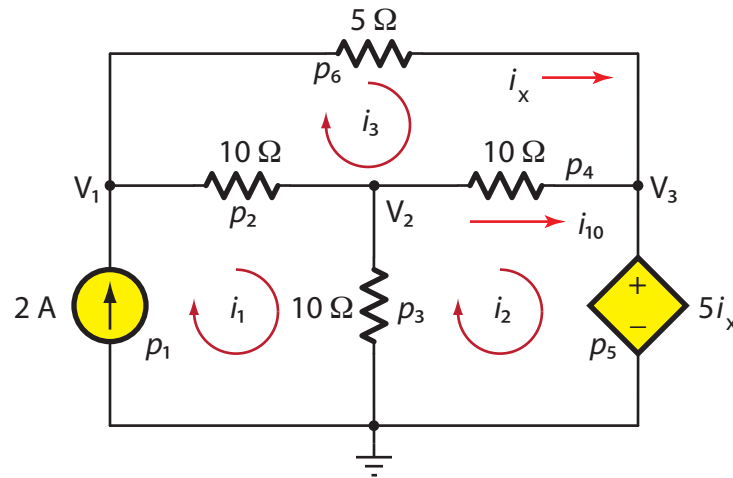
- (a) [6] Write down the mesh-current equations with the unknown mesh currents as the only variables.
- (b) [4] Solve for the mesh currents and find i_{10} .
- (c) [6] Using your mesh currents from part (b), calculate the power in all circuit elements ($p_1, p_2, p_3, p_4, p_5, p_6$). (If you have not solved part (b), you can assume non-zero values for the mesh currents. Clearly state your assumptions.)



(Question 2, additional workspace ...)

3. [16 marks.] Consider the circuit below.

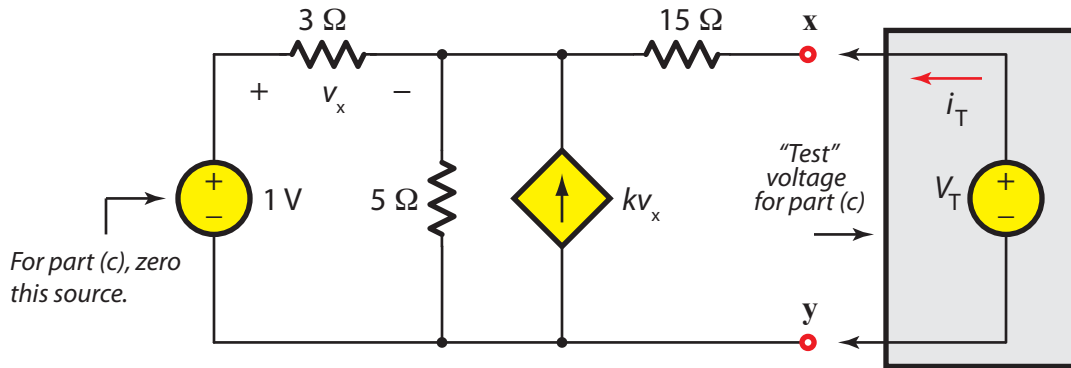- (a) [7] Assuming that $k = \frac{2}{3}$, determine the Thévenin equivalent circuit as seen to the left of the terminals **x** and **y**.
- (b) [4] Calculate the value of k such that the short-circuit current $i_{sc} = 0$ A.
- (c) [5] Now connect a “test” voltage source V_T to the circuit’s terminals as shown, and zero the 1-V source (i.e., replace the 1-V source with a short circuit). Using whatever value of k you calculated in part (b), determine the ratio of V_T to the test current i_T .



(Question 3, additional workspace ...)

(Please do not write in this space.)

#1 (18)	#2 (16)	#3 (16)	Total (50)