

Name: \_\_\_\_\_

Lecture Section: \_\_\_\_\_

**L01** - *Chris Macnab*

**L02** - *Norm Bartley*

**L03** - *Norm Bartley*

**L04** - *Anis Haque*



ENGG 225 - Fundamentals of Electrical Circuits and Machines

## Midterm Examination

Tuesday, February 23, 2016

Time: 7:00 - 8:30 PM

---


### Instructions:

- Time allowed is 90 minutes.
  - The examination is closed-book.
  - Only calculators sanctioned by the Schulich School of Engineering are permitted in the examination.
  - The maximum number of marks is 45, as indicated; please attempt all questions. The midterm examination counts 25% toward the final grade.
  - Please use a pen or heavy pencil to ensure legibility.
  - Please answer questions in the spaces provided; if space is insufficient, please use the back of the pages.
  - Please show your work; where appropriate, marks will be awarded for proper and well-reasoned explanations.
-

UCID: \_\_\_\_\_


1. [15 marks.] Parts (a)-(e) below each have an identical weighting of three marks. Please answer the questions in the boxes provided.

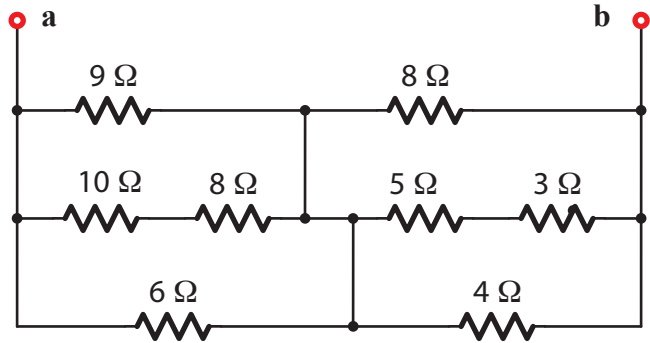- (a) [3] In the circuit at right, determine the equivalent resistance  $R_{eq}$  as seen at the terminals **a** and **b**.




Answer:  $R_{eq} =$

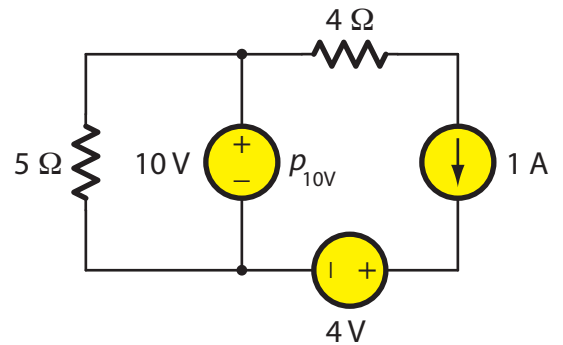- (b) [3] In the circuit at right, determine the power  $p_{10V}$  in the 10-Volt source.




Answer:  $p_{10V} =$

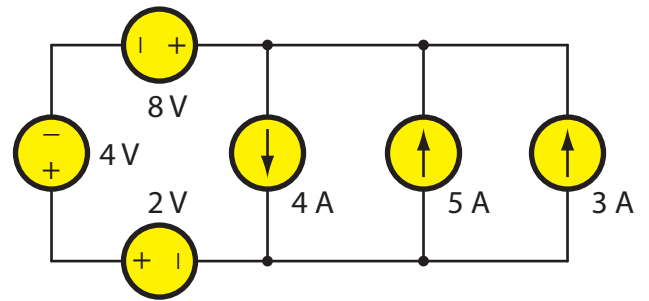- (c) [3] Simplify the circuit at right so that there is only one voltage source and one current source.




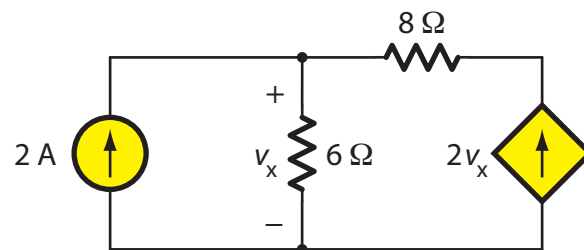- (d) [3] In the circuit at right, find  $v_x$ .




Answer:  $v_x =$

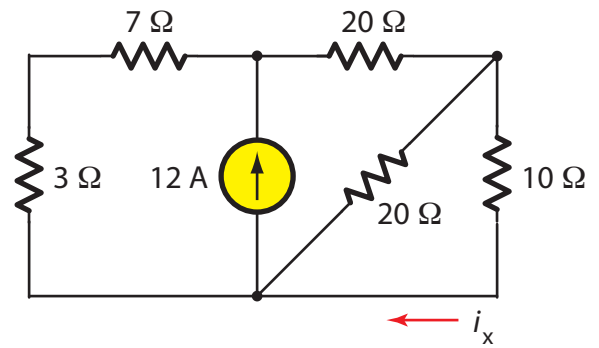(e) [3] In the circuit at right, find  $i_x$ .



Answer:  $i_x =$

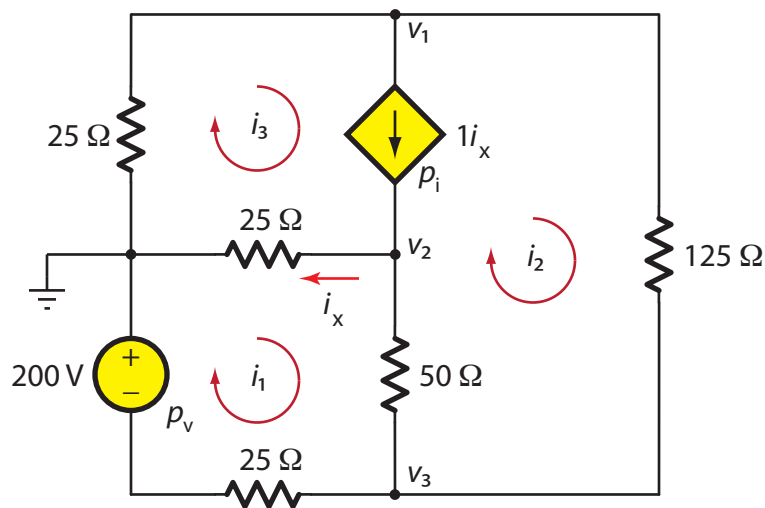
2. [18 marks.] Consider the circuit below.



- [9] Determine the mesh currents  $i_1$ ,  $i_2$ , and  $i_3$ .
- [4] Using your answers from part (a), determine the power in both sources,  $p_v$  and  $p_i$ , as indicated.
- [5] Write (*but do not solve*) the node-voltage equations. Express the equations using only the node voltages  $v_1$ ,  $v_2$ , and  $v_3$  as variables. It is not necessary to simplify your equations.

*(Question 2, additional workspace ...)*

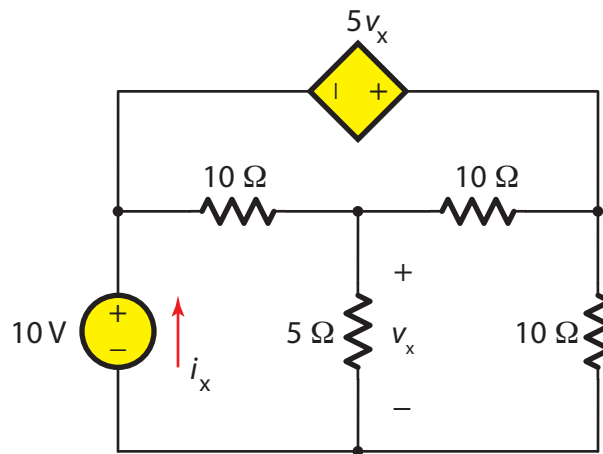3. [12 marks.] Consider the circuit below, which you may analyze using any method of your choosing.



- (a) [8] Determine the voltage  $v_x$ .
- (b) [4] Determine the current  $i_x$ .

*(Question 3, additional workspace ...)*

*(Please do not write in this space.)*

#1 (15)	#2 (18)	#3 (12)	Total (45)