
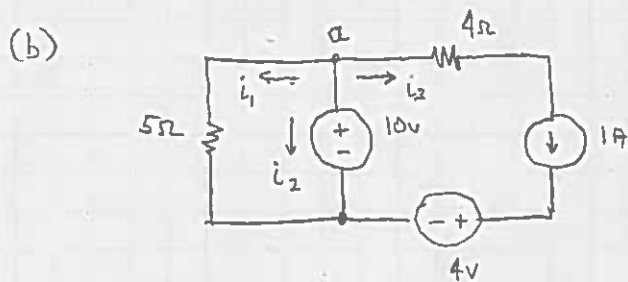
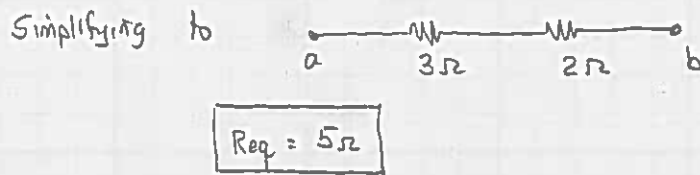


Question 1

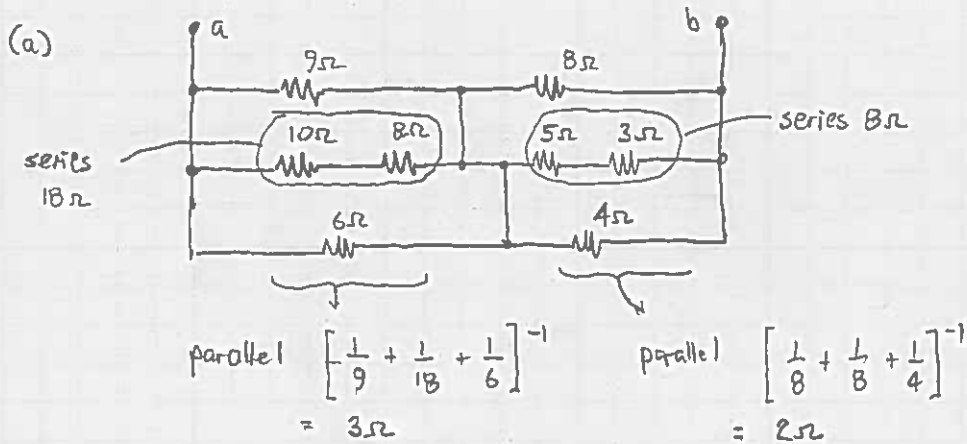


We have $i_3 = 1A$.
 Also, $i_1 = \frac{10V}{5\Omega} = 2A$


Then, KCL at node a gives $-i_1 - i_2 - i_3 = 0$
 so $i_2 = -i_1 - i_3 = -2 - 1 = -3A$

Power in the 10-volt source, using the passive reference convention

$$P_{10V} = Vi = 10 \times -3 = -30W$$

$P_{10V} = -30W$

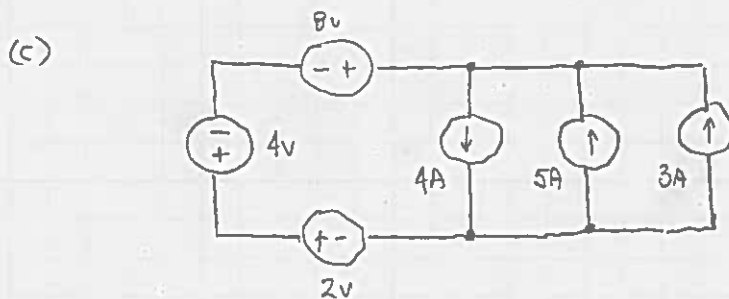

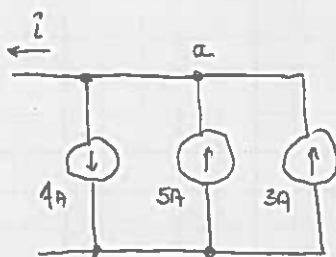


By KCL at node

$$-i - 4 + 5 + 3 = 0$$

$$\text{so } i = 4 \text{ A}$$

Simplifies to

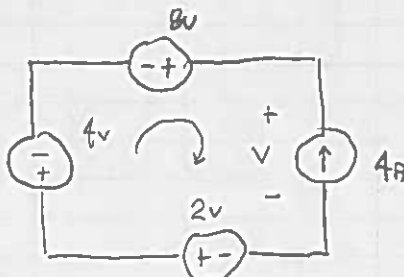


KVL gives


$$-2 + 4 - 6 + V = 0$$

$$\text{so } V = 6 \text{ V}$$

Equivalent circuit:

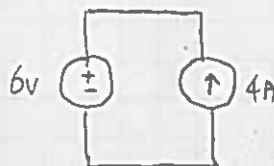

(d)

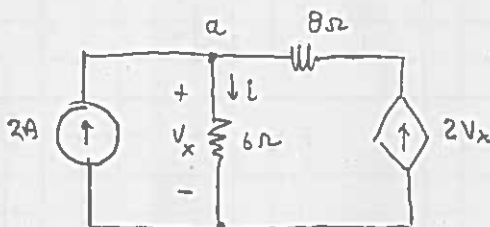

KCL at node a

$$2 + 2V_x - i = 0$$

$$i = 2 + 2V_x \quad (1)$$

$$\text{and } V_x = 6i \quad (2)$$

Substituting (2) into (1) gives

$$i = 2 + 2(6i)$$

$$= 2 + 12i$$


$$\text{so } -11i = 2, \text{ and } i = -\frac{2}{11} \text{ A}$$

$$= -0.18182 \text{ A}$$

Finally, $V_x = 6i$

$$V_x = -\frac{12}{11} \text{ V} = -1.09091 \text{ V}$$

(e)

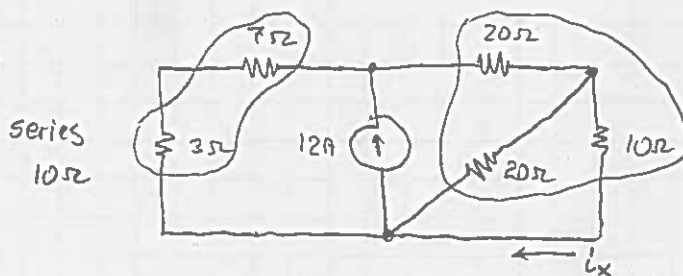


equivalent resistance

$$(10 \parallel 20) + 20$$

$$= 26.667 \Omega$$


This simplifies to:

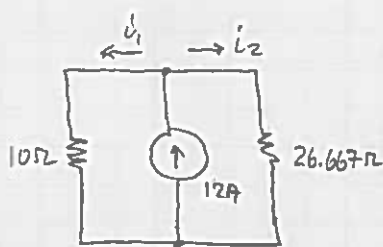

This is a current divider, and we need i_2

$$i_2 = \frac{10}{10 + 26.667} \times 12 = 3.27273 \text{ A}$$

$\Rightarrow i_2$ splits further

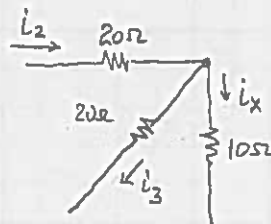


$$i_x = \frac{20}{20 + 10} \times i_2$$

$$i_x = 2.18182 \text{ A}$$

Question 2

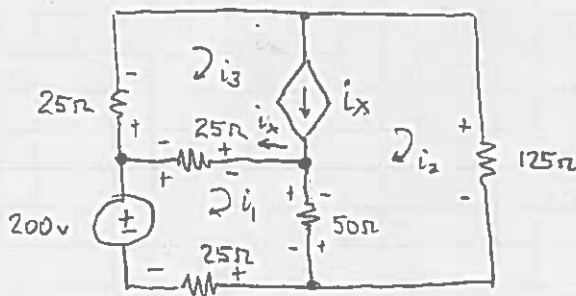(a) Intended method is to use mesh-current analysis



Mesh i_1 :

$$-200 + 25(i_1 - i_3) + 50(i_1 - i_2) + 25i_1 = 0$$

$$-200 + 25i_1 - 25i_3 + 50i_1 - 50i_2 + 25i_1 = 0$$

$$100i_1 - 50i_2 - 25i_3 = 200 \quad (1)$$

Supermesh i_2, i_3 :

$$25i_3 + 125i_2 + 50(i_2 - i_1) + 25(i_3 - i_1) = 0$$

$$25i_3 + 125i_2 + 50i_2 - 50i_1 + 25i_3 - 25i_1 = 0$$

$$-75i_1 + 175i_2 + 50i_3 = 0 \quad (2)$$

Supermesh dependence: $i_3 - i_2 = i_x \quad (3)$

where $i_x = i_3 - i_1$

Substitute into (3): $i_3 - i_2 = i_3 - i_1$

giving $i_1 = i_2$ (4)

Now substitute (4) into (1) and (2)

$$\begin{aligned} 100i_1 - 50i_1 - 25i_3 &= 200 \\ 50i_1 - 25i_3 &= 200 \end{aligned} \quad (5)$$

$$\begin{aligned} -75i_1 + 175i_1 + 50i_3 &= 0 \\ 100i_1 + 50i_3 &= 0 \end{aligned} \quad (6)$$

so $-50i_3 = 100i_1$
 $i_3 = -2i_1$


Substitute into (5): $50i_1 - 25(-2i_1) = 200$
 $100i_1 = 200$

so $i_1 = 2\text{ A}$

and $i_2 = 2\text{ A}$

finally, $i_3 = -2i_1$, giving $i_3 = -4\text{ A}$

Alternative method using node-voltage

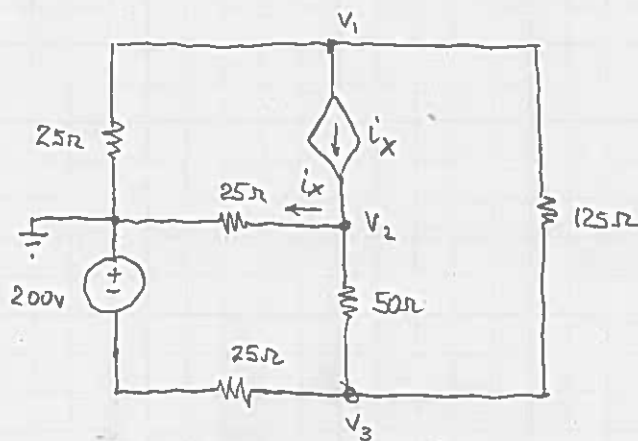

The node equations ...

$$\text{Node } V_1: \quad \frac{V_1}{25} + i_x + \frac{V_1 - V_3}{125} = 0$$

where the controlling current $i_x = \frac{V_2}{25}$.

$$\text{so } \frac{V_1}{25} + \frac{V_2}{25} + \frac{V_1 - V_3}{125} = 0$$

$$\begin{aligned} (\times 125) \quad 5V_1 + 5V_2 + V_1 - V_3 &= 0 \\ 6V_1 + 5V_2 - V_3 &= 0 \end{aligned} \quad (1)$$

$$\text{Node } V_2: \quad \frac{V_2}{25} + \frac{V_2 - V_3}{50} - i_x = 0$$

$$\text{or } \frac{V_2}{25} + \frac{V_2 - V_3}{50} - \frac{V_2}{25} = 0$$

$$\begin{aligned} (\times 50) \quad 2V_2 + V_2 - V_3 - 2V_2 &= 0 \\ V_2 &= V_3 \end{aligned} \quad (2)$$

$$\text{Node } V_3: \quad \frac{V_3 + 200}{25} + \frac{V_3 - V_2}{50} + \frac{V_3 - V_1}{125} = 0$$

$$\begin{aligned} (\times 250) \quad 10V_3 + 2000 + 5V_3 - 5V_2 + 2V_3 - 2V_1 &= 0 \\ 17V_3 - 5V_2 - 2V_1 &= -2000 \end{aligned} \quad (3)$$

Substitute (2) into (1) and (3)

$$\begin{aligned} 6V_1 + 5V_2 - V_2 &= 0 \\ 6V_1 + 4V_2 &= 0 \end{aligned} \quad (4)$$

$$\begin{aligned} 17V_2 - 5V_2 - 2V_1 &= -2000 \\ 12V_2 - 2V_1 &= -2000 \end{aligned} \quad (5)$$

From (5), $2V_1 = 12V_2 + 2000$, so $V_1 = 6V_2 + 1000$.
Substitute into (4)


$$\begin{aligned} 6(6V_2 + 1000) + 4V_2 &= 0 \\ 36V_2 + 6000 + 4V_2 &= 0 \\ 40V_2 &= -6000 \end{aligned}$$

$$\text{so } V_2 = -150 \text{ V}$$

Therefore, $V_1 = 6V_2 + 1000 = 6(-150) + 1000 = 100 \text{ V}$.

And $V_3 = V_2$, so $V_3 = -150 \text{ V}$.

Now the mesh currents:

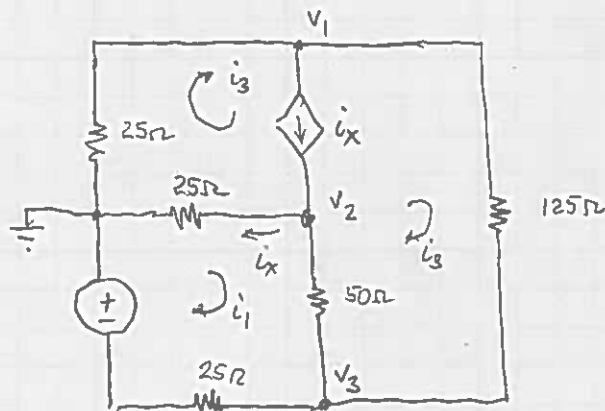

Looking at mesh 3:

$$i_3 = -\frac{V_1}{25} = -\frac{100}{25}$$

$$i_3 = -4 \text{ A}$$

In mesh 1:

$$i_1 = \frac{V_3 - (-200)}{25} = \frac{-150 + 200}{25}$$


$$i_1 = 2 \text{ A}$$

In mesh 2:

$$i_2 = \frac{V_1 - V_3}{125} = \frac{100 - (-150)}{125}$$

$$i_2 = 2 \text{ A}$$

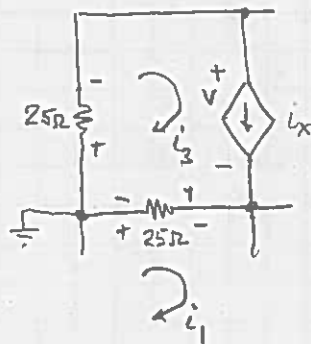(b) Intended method by mesh-current analysis



$$\text{Mesh } i_2: 25i_2 + V + 25(i_2 - i_1) = 0$$

$$\text{so } 25(-4) + V + 25(-4 - 2) = 0$$


$$-100 + V - 150 = 0$$

$$V = 250 \text{ V}$$

$$\text{Power: } P_i = vi_x = 250(i_2 - i_1)$$

$$= 250(-6)$$

$$P_i = -1500 \text{ W}$$

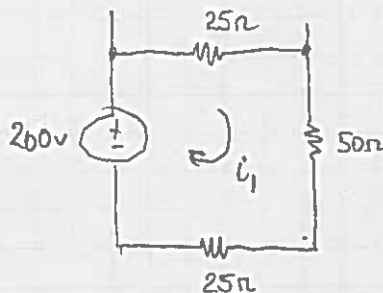

$$p_1 = -vi_1 = -200(2)$$

$$p_1 = -400 \text{ W}$$

(c) Node V_1 : $\frac{V_1}{25} + i_x + \frac{V_1 - V_3}{125} = 0$

where $i_x = V_2/25$

so $\frac{V_1}{25} + \frac{V_2}{25} + \frac{V_1 - V_3}{125} = 0$


Node V_2 : $\frac{V_2}{25} + \frac{V_2 - V_3}{50} - \frac{V_2}{25} = 0$

[simplifies to $V_2 = V_3$]

Node V_3 : $\frac{V_3 + 200}{25} + \frac{V_3 - V_2}{50} + \frac{V_3 - V_1}{125} = 0$

Question 3

(a) Using the node-voltage method

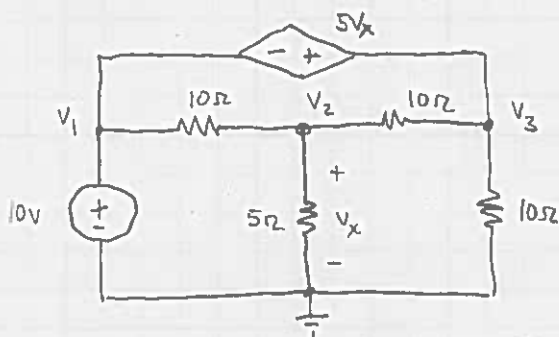

With the bottom of the circuit as reference, we see

$$V_1 = 10 \text{ V}$$

AND $V_3 = V_1 + 5V_x = 10 + 5V_x$

This leaves a single node V_2 unknown

$$\text{Node } V_2: \quad \frac{V_2 - 10}{10} + \frac{V_2 - V_3}{10} + \frac{V_2}{5} = 0$$

$$(\times 10) \quad V_2 - 10 + V_2 - V_3 + 2V_2 = 0$$

$$4V_2 - V_3 = 10$$

$$\text{Substituting for } V_3: \quad 4V_2 - (10 + 5V_x) = 10$$

where we note $V_x = V_2$.


$$4V_2 - 10 - 5V_2 = 10$$

$$-V_2 = 20$$

$$V_2 = -20$$

$$\text{Therefore, } \boxed{V_x = -20}$$

Using the mesh-current method,

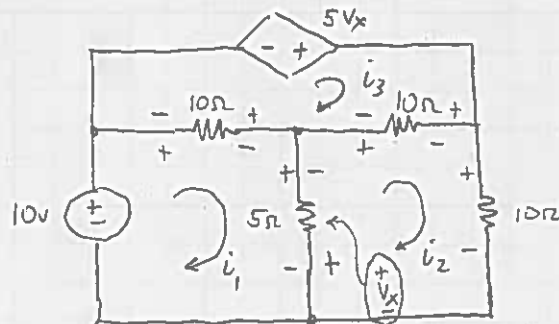

$$\text{Mesh } i_1: \quad -10 + 10(i_1 - i_3) + 5(i_1 - i_2) = 0$$

$$15i_1 - 5i_2 - 10i_3 = 10 \quad (1)$$

$$\text{Mesh } i_2: \quad 5(i_2 - i_1) + 10(i_2 - i_3) + 10i_2 = 0$$

$$-5i_1 + 25i_2 - 10i_3 = 0 \quad (2)$$

$$\text{Mesh } i_3: \quad 10(i_3 - i_1) - 5V_x + 10(i_3 - i_2) = 0$$

$$-10i_1 - 10i_2 + 20i_3 = 5V_x \quad (3)$$

We also know that $V_x = 5(i_1 - i_2)$, so equation (3) becomes

$$\begin{aligned} -10i_1 - 10i_2 + 20i_3 &= 25i_1 - 25i_2 \\ -35i_1 + 15i_2 + 20i_3 &= 0 \end{aligned} \quad (4)$$

Add equation (4) to $3 \times$ equation (1)

$$\begin{aligned} -35i_1 + 15i_2 + 20i_3 &= 0 & (4) \\ 45i_1 - 15i_2 - 30i_3 &= 30 & (1) \times 3 \end{aligned}$$

$$10i_1 - 10i_3 = 90$$

$$\text{so } i_1 = 3 + i_3 \text{ and } i_3 = i_1 - 3$$

Substitute into (2) and (4)

$$\begin{aligned} -5i_1 + 25i_2 - 10(i_1 - 3) &= 0 \\ -15i_1 + 25i_2 &= -30 \end{aligned} \quad (5)$$

$$\begin{aligned} -35i_1 + 15i_2 + 20(i_1 - 3) &= 0 \\ -15i_1 + 15i_2 &= 60 \end{aligned} \quad (6)$$

Add $-1 \times$ equation (5) to (6)

$$\begin{aligned} 15i_1 - 25i_2 &= 30 \\ -15i_1 + 15i_2 &= 60 \end{aligned}$$

$$-10i_2 = 90, \quad \text{so } i_2 = -9 \text{ A}$$

Substitute back into (6)


$$\begin{aligned} -15i_1 + 15(-9) &= 60 \\ -15i_1 &= 60 + 135 \end{aligned}$$

$$i_1 = -13 \text{ A}$$

We don't need i_3 , and then $V_x = 5(i_1 - i_2)$
 $= 5(-13 + 9)$

$$\boxed{V_x = -20 \text{ V}}$$

(b) From the node-voltage method

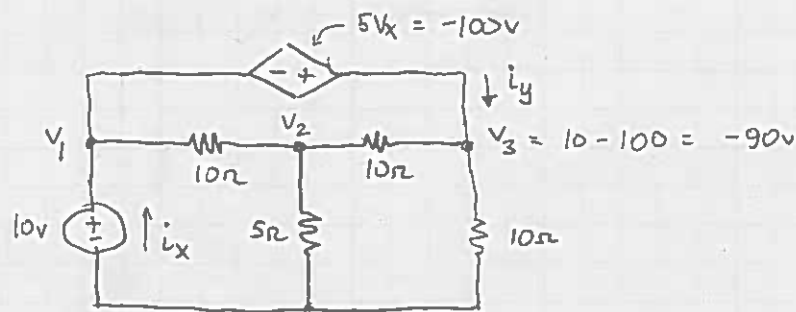

Need to KCL at V_1 , but first need i_y at node V_3

$$\frac{V_3 - V_2}{10} + \frac{V_3}{10} - i_y = 0$$

$$\frac{-90 - (-20)}{10} + \frac{-90}{10} = i_y$$

$$-7 - 9 = i_y, \quad \text{so } i_y = -16 \text{ A}$$

Then, at node V_1

$$-i_x + i_y + \frac{V_1 - V_2}{10} = 0$$

$$i_x = -16 + \frac{10 - (-20)}{10}$$

$$\boxed{i_x = -13 \text{ A}}$$

Using the mesh-current method, from our previous calculation,

$$\boxed{i_x = i_1 = -13 \text{ A}}$$