
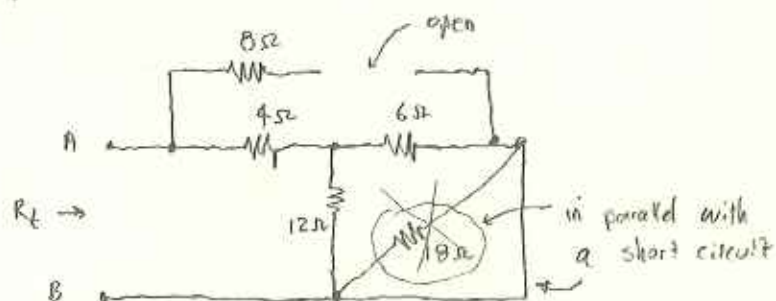


Question 1

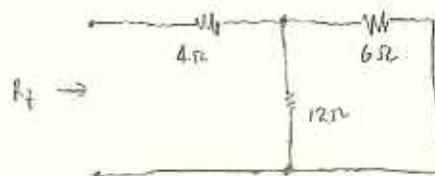- (a) Since there are no dependent sources, we may zero the independent ones.




or reducing



$$R_t = (12 // 6) + 4 = \boxed{8\Omega}$$

(b)

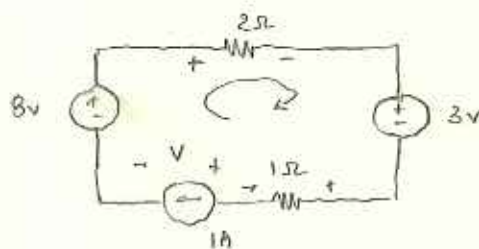

Need to find voltage V . Common loop current $i = 1A$.
KVL around the loop gives

$$-8 + 2i + 3 + 1i + V = 0$$


$$-8 + 2 + 3 + 1 + V = 0$$

$$V = 2V$$

$$\text{Power } p_{1\Omega} = iV = 1A \times 2V = \boxed{2W}$$

This is positive, so power is absorbed.


(c)

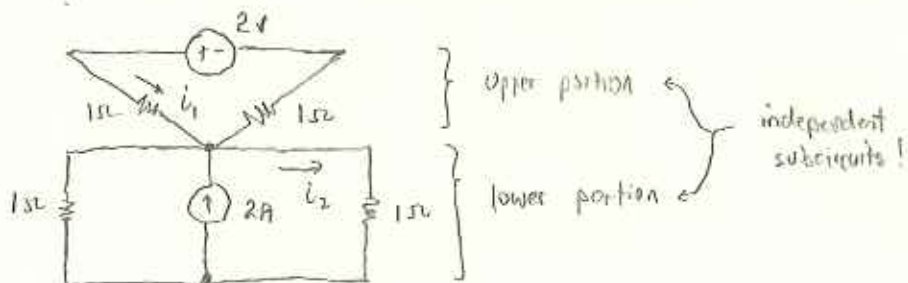

Note that the upper portion of the circuit is independent of the lower part, since there is no return path for current between the two portions.

The upper part redrawn

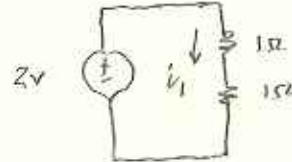
$$i_1 = \frac{V}{R} = \frac{2}{1+1} = \boxed{1 \text{ A}}$$



The lower part is a simple current divider


$$i_2 = \frac{1\Omega}{1\Omega + 1\Omega} \times 2 \text{ A} = \boxed{1 \text{ A}}$$

(d)

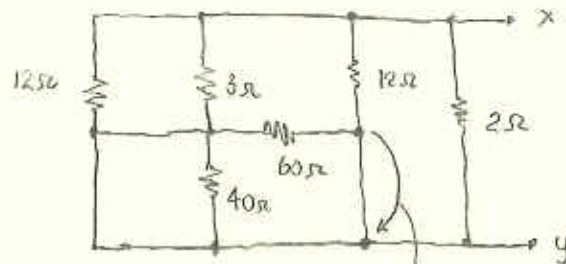


straightening resistor branches.

drag this node down to the bottom wire.

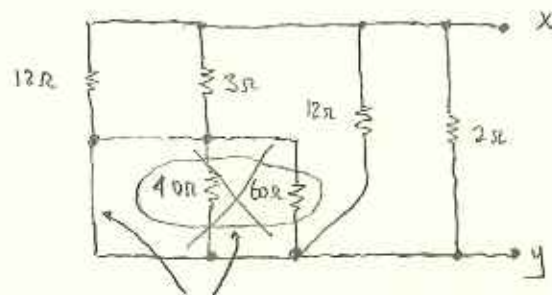


in parallel with a short circuit
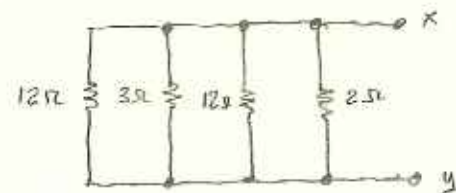
$$R_{eq} = \left(\frac{1}{12} + \frac{1}{3} + \frac{1}{12} + \frac{1}{2} \right)^{-1} = \boxed{1 \Omega}$$



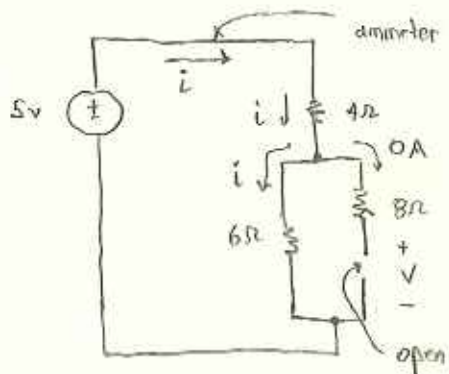(c) An equivalent circuit using the internal resistances of the voltmeter and ammeter




$$i = \frac{5V}{4\Omega + 6\Omega} = \boxed{0.5 A}$$

There is no current in the 8Ω resistor, so no voltage across it. Therefore,

$$v = i \times 6\Omega = \boxed{3V}$$

Question 2

(a)

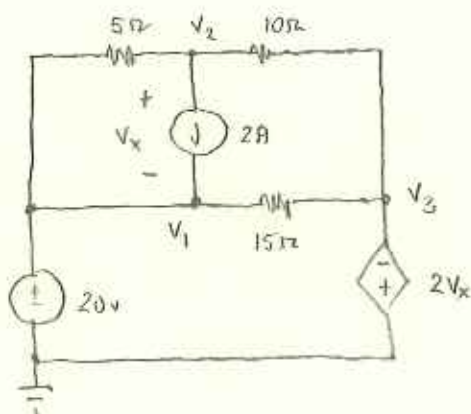

We see that $v_1 = 20V$, and also $v_3 = -2v_x$.

$$\text{Node } v_2: \frac{v_2 - 20}{5} + 2 + \frac{v_2 - v_3}{10} = 0$$

$$\begin{aligned} (\times 10) \quad 2v_2 - 40 + 20 + v_2 - v_3 &= 0 \\ 3v_2 - v_3 &= 20 \end{aligned}$$

Substituting for v_3

$$\begin{aligned} 3v_2 - (-2v_x) &= 20 \\ 3v_2 + 2v_x &= 20 \end{aligned}$$

We also know that $v_x = v_2 - v_1$, so

$$\begin{aligned} 3v_2 + 2(v_2 - v_1) &= 20 \\ 3v_2 + 2v_2 - 40 &= 20 \\ 5v_2 &= 60 \end{aligned}$$

$$\text{so } v_2 = 12$$

$$\text{Also, } V_x = V_2 - 20 = -8$$

$$\text{and } V_3 = -2V_x = 16$$

$$\boxed{\begin{array}{l} V_2 = 12 \\ V_3 = 16 \end{array}}$$

(b) Meshes i_1 and i_2 form a supermesh

$$\begin{aligned} \text{Supermesh } i_1, i_2: \quad 5i_1 + 10i_2 + 15(i_2 - i_3) &= 0 \\ 5i_1 + 10i_2 + 15i_2 - 15i_3 &= 0 \\ 5i_1 + 25i_2 - 15i_3 &= 0 \end{aligned} \quad (1)$$

$$\text{Supermesh dependence: } i_1 - i_2 = 2 \quad (2)$$

$$\begin{aligned} \text{Mesh } i_3: \quad -20 + 15(i_3 - i_2) - 2V_x &= 0 \\ 15i_3 - 15i_2 - 2V_x &= 20 \end{aligned} \quad (3)$$

We need to express V_x in terms of mesh currents.
In mesh i_1 , we have

$$5i_1 + V_x = 0, \quad \text{so } V_x = -5i_1$$

Substitute into (3)

$$15i_3 - 15i_2 + 10i_1 = 20 \quad (4)$$

If we add equations (1) and (4), we can eliminate i_3

$$\begin{array}{r} 5i_1 + 25i_2 - 15i_3 = 0 \\ 10i_1 - 15i_2 + 15i_3 = 20 \\ \hline 15i_1 + 10i_2 = 20 \end{array} \quad (5)$$

From (2), $i_1 = 2 + i_2$, so equation (5) becomes

$$\begin{aligned} 15(2 + i_2) + 10i_2 &= 20 \\ 30 + 15i_2 + 10i_2 &= 20 \\ 25i_2 &= -10 \end{aligned}$$

$$\text{so } i_2 = -0.4$$

From (3), $i_3 = 1.6 \text{ A}$, and from (1), $i_3 = -0.1333 \text{ A}$

$$\boxed{\begin{array}{l} i_1 = 1.6 \text{ A} \\ i_2 = -0.4 \text{ A} \\ i_3 = -0.1333 \text{ A} \end{array}}$$

(c) Using $i_2 = -0.1333 \text{ A}$ from part (b)

$$P_1 = -V_1 i_2 = -20 \times -0.1333 = \boxed{2.667 \text{ W (absorbed)}}$$

Using i_3 again from part (b), we also need V_x ,

$$\text{From part (a), } V_x = V_2 - V_1 = 12 - 20 = -8 \text{ V}$$

$$\text{From part (b), } V_x = -5i_3 = -5(1.6) = -8 \text{ V}$$


$$\text{so } P_2 = -(2V_x) i_3 = 16i_3 = \boxed{-2.333 \text{ W (delivered)}}$$

Using V_x from either part (a) or (b)

$$P_3 = i V_x = 2 \times -8 = \boxed{-16 \text{ W delivered}}$$

Question 3

(a) Thevenin voltage.

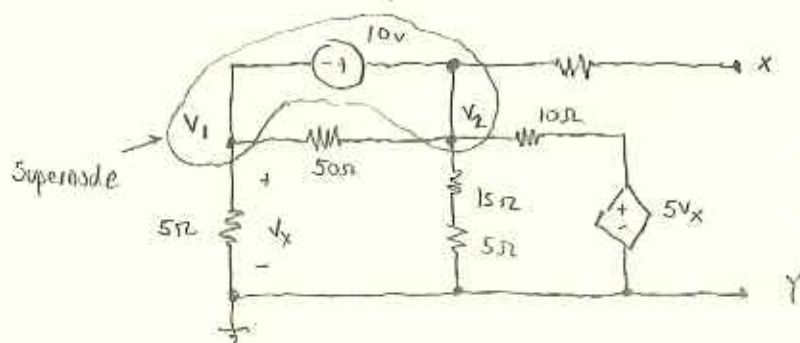

$$\text{Supernode } V_1, V_2: \quad \frac{V_1}{5} + \frac{V_1 - V_2}{50} + \frac{V_2 - V_1}{50} + \frac{V_2}{15+5} + \frac{V_2 - 5V_x}{10} = 0$$

$$\begin{aligned} (\times 20) \quad 4V_1 + V_2 + 2V_2 - 10V_x &= 0 \\ 4V_1 + 3V_2 - 10V_x &= 0 \end{aligned} \quad (1)$$

$$\text{Dependence: } V_2 - V_1 = 10 \quad (2)$$

We also see that $V_x = V_1$, so equation (1) becomes


$$\begin{aligned} 4V_1 + 3V_2 - 10V_1 &= 0 \\ -6V_1 &= -3V_2, \quad \text{so } V_2 = 2V_1 \quad \text{or } V_1 = \frac{1}{2}V_2 \end{aligned}$$

From (2), $V_2 - \frac{1}{2}V_2 = 10$
 so $V_2 = 20\text{ v}$

Since the terminal X is open-circuited, no current flows in the 10Ω resistor connecting V_2 and X, so

$$V_t = V_x = V_2 = 20\text{V}$$

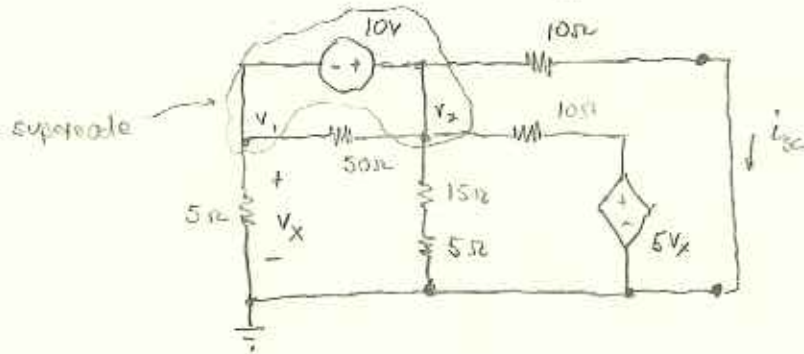Thevenin resistance: since there is a dependent source, we need to find i_{sc} .



Supernode v_1, v_2 : $\frac{v_1}{5} + \frac{v_1 - v_2}{50} + \frac{v_2 - v_1}{50} + \frac{v_2}{20} + \frac{v_2 - 5V_x}{10} + \frac{v_2}{10} = 0$

(x20) $4v_1 + v_2 + 2v_2 - 10V_x + 2v_2 = 0$
 $4v_1 + 5v_2 - 10V_x = 0$

This is i_{sc} .

As before, $V_x = v_1$, so $4v_1 + 5v_2 - 10v_1 = 0$
 $-6v_1 + 5v_2 = 0$ (1)

The dependence equation, also as before, $v_2 - v_1 = 10$ (2)

From (2), $v_1 = v_2 - 10$, so from (1)


$-6(v_2 - 10) + 5v_2 = 0$
 $-6v_2 + 60 + 5v_2 = 0$

$v_2 = 60\text{ v}$

The short-circuit current $i_{sc} = \frac{v_2}{10} = 6\text{ A}$

Therefore, $R_t = \frac{V_t}{i_{sc}} = \frac{20}{6} = 3.333\Omega$

(b) Using the Thevenin equivalent,

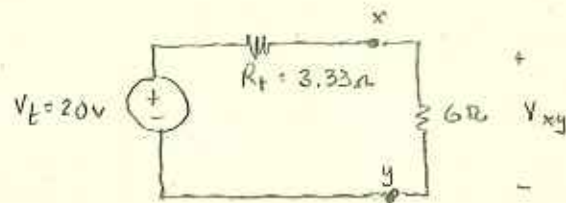

By voltage division,
$$V_{xy} = \frac{6\Omega}{6\Omega + 3.33\Omega} \times 20V = \boxed{12.86V}$$