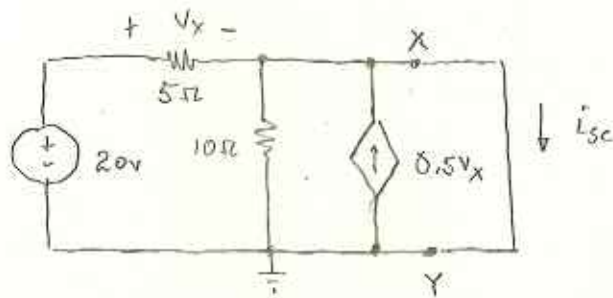


Question 1

(a)




Note that both V_x and $V_y = 0$. Therefore, $V_x = 20V$.
 Writing a node-voltage equation at X

$$\text{node X: } \frac{V_x - 20}{5} + \frac{V_x}{10} - 0.5(20) + I_{sc} = 0$$

$$-4 + 0 - 10 + I_{sc} = 0$$

$$I_{sc} = 14 \text{ A}$$

(b)

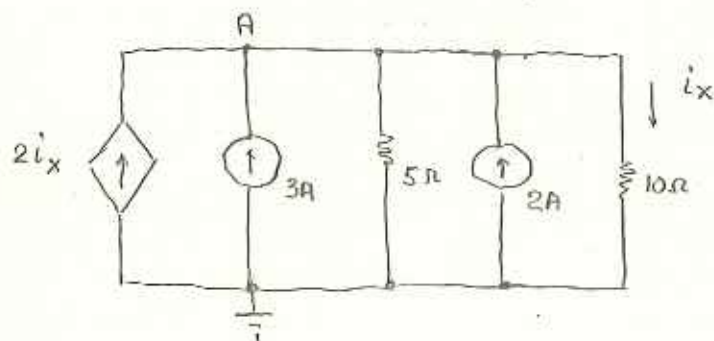

$$\text{At node A: } -2I_x - 3 + \frac{V_A}{5} - 2 + \frac{V_A}{10} = 0$$

$$\text{and } I_x = \frac{V_A}{10}$$


$$\text{so } -2\left(\frac{V_A}{10}\right) - 5 + \frac{3V_A}{10} = 0$$

$$\frac{V_A}{10} = 5, \text{ so } V_A = 50V$$

$$\text{Power in the 3A source } P_{3A} = -3A \times V_A = -150W$$


$$|P_{3A}| = 150W \text{ delivering}$$

(c)

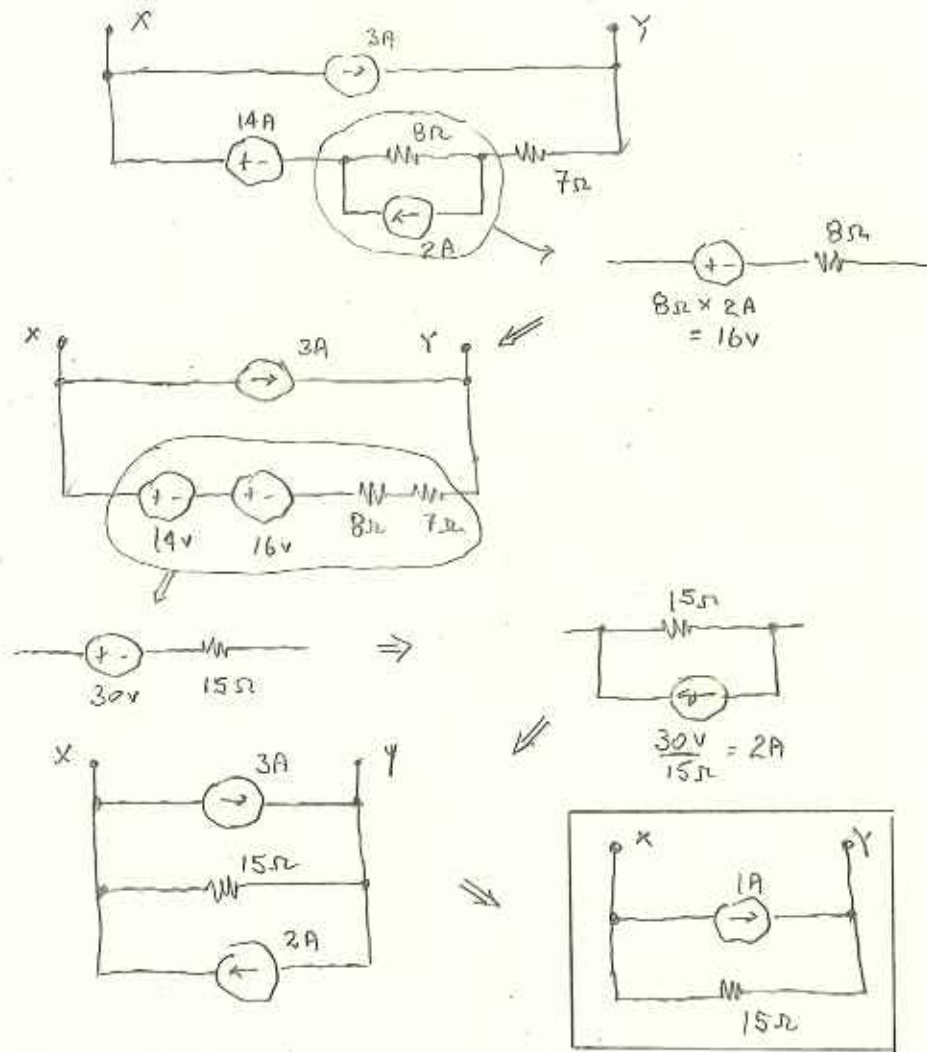

(d) The cross-connection actually places the 30Ω, 24Ω, and 20Ω resistors in parallel.


Undoing the cross-connection, ...

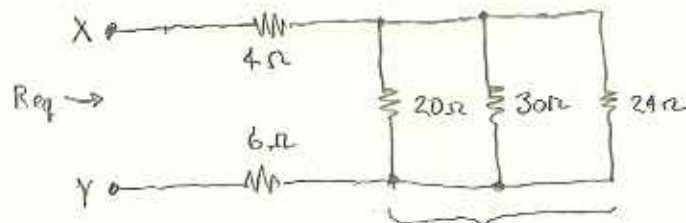

$$20 // 30 // 24 = 8\Omega$$

$$R_{eq} = 6\Omega + 8\Omega + 4\Omega = \boxed{18\Omega}$$

(e)

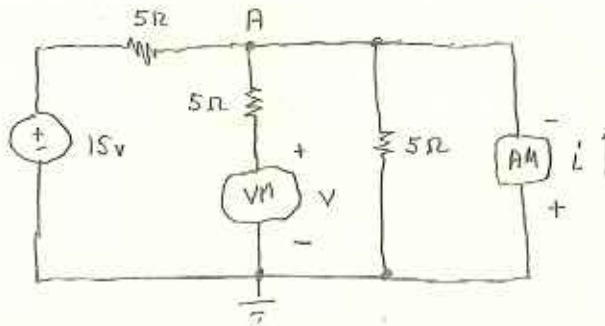


Since the ammeter behaves like a short circuit, $V_A = 0$

Therefore $V = 0$

No current flows in either of the middle two branches, so it all flows through the top 5Ω resistor and the ammeter

$$i = -\frac{15\text{V}}{5\Omega} = -3\text{A}$$

Question 2

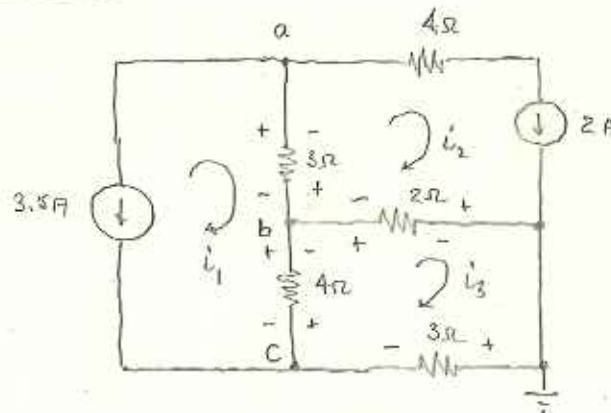

(a) Node-voltage equations (not simplified)

$$\text{Node a: } 3.5 + 2 + \frac{V_a - V_b}{3} = 0$$

$$\text{Node b: } \frac{V_b - V_a}{3} + \frac{V_b - V_c}{4} + \frac{V_b}{2} = 0$$

$$\text{Node c: } -3.5 + \frac{V_c - V_b}{4} + \frac{V_c}{3} = 0$$

(b) Mesh-current equations, using the directions indicated.

$$\text{mesh 1: } i_1 = -3.5 \text{ A}$$

$$\text{mesh 2: } i_2 = 2 \text{ A}$$

$$\text{mesh 3: } 3i_3 + 4(i_3 - i_1) + 2(i_3 - i_2) = 0$$

(c) Either set of equations can be used to solve for the node voltages. The simpler solution is to carry on with the mesh-current analysis.

Using $i_1 = -3.5$ and $i_2 = 2$, the equation for mesh 3 becomes

$$\begin{aligned} 3i_3 + 4(i_3 + 3.5) + 2(i_3 - 2) &= 0 \\ 3i_3 + 4i_3 + 14 + 2i_3 - 4 &= 0 \\ 9i_3 &= -10 \end{aligned}$$

$$\text{so } i_3 = -10/9$$

$$\text{At node c: } V_c = -3i_3 = -3(-10/9) = 10/3 \text{ V}$$


$$\begin{aligned} \text{At node b: } V_b &= 2(i_3 - i_2) = 2(-10/9 - 2) \\ &= -56/9 \\ &= -6.222 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{At node a: } V_a &= V_b + 3(i_1 - i_2) \\ &= -6.222 + 3(-3.5 - 2) \\ &= -22.722 \text{ V} \end{aligned}$$

$\begin{aligned} V_a &= 3.3333 \text{ V} \\ V_b &= -6.2222 \text{ V} \\ V_c &= -22.7222 \text{ V} \end{aligned}$
--

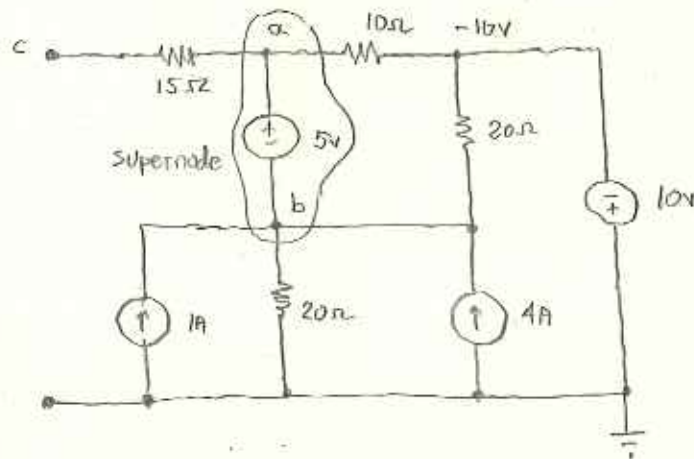Question 3

Finding the Thevenin equivalent for the part of the circuit in the box. First, V_t



Using the node-voltage method, there is one supernode

$$\begin{aligned} \text{supernode } a, b: \quad & \frac{V_a - (-10)}{10} + \frac{V_b}{20} + \frac{V_b - (-10)}{20} - 1 - 1 = 0 \\ (\times 20) \quad & 2V_a + 20 + V_b + V_b + 10 - 20 - 20 = 0 \\ & 2V_a + 2V_b = 70 \quad (1) \end{aligned}$$


$$\begin{aligned} \text{supernode dependence:} \quad & V_a - V_b = 5 \\ \text{so } & V_b = V_a - 5 \quad (2) \end{aligned}$$

$$\begin{aligned} \text{Substituting (2) into (1):} \quad & 2V_a + 2V_a - 10 = 70 \\ & 4V_a = 80 \\ & V_a = 20 \text{ V} \end{aligned}$$


With terminal c open, no current flows through the 15Ω resistor

$$\text{so } V_c = V_a = V_t = 20 \text{ V}$$

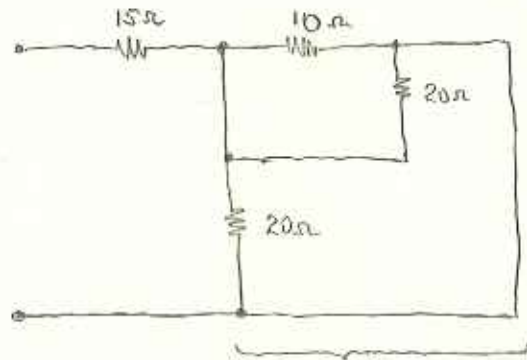Now find R_t . There are no dependent sources, so we may zero the independent ones.




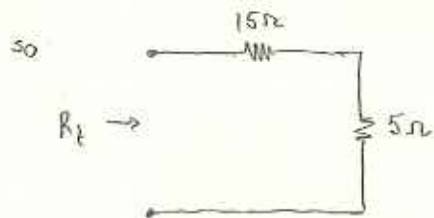all three resistors in parallel
 $10 // 20 // 20 = 5 \Omega$



so $R_t = 15 + 5 = 20 \Omega$

The over-all equivalent circuit is

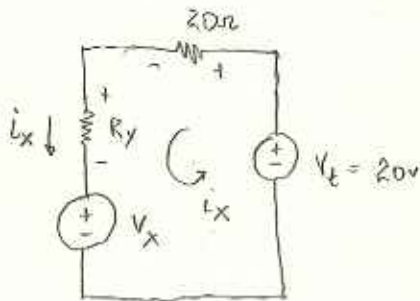

KVL around the loop gives

$$V_x - 20 + 20i_x + i_x R_x = 0$$

$$V_x - 20 + i_x(20 + R_x) = 0$$

so $i_x = \frac{-(V_x - 20)}{20 + R_x}$

$$i_x = \frac{20 - V_x}{20 + R_x}$$

Using this simple formula...

$$V_x = 5, R_x = 10 : \quad i_x = \frac{20 - 5}{20 + 10} = 0.5 \text{ A}$$

$$V_x = 10, R_x = 30 : \quad i_x = \frac{20 - 10}{20 + 30} = 0.2 \text{ A}$$

$$V_x = 0, R_x = 0 : \quad i_x = \frac{20}{20} = 1 \text{ A}$$