

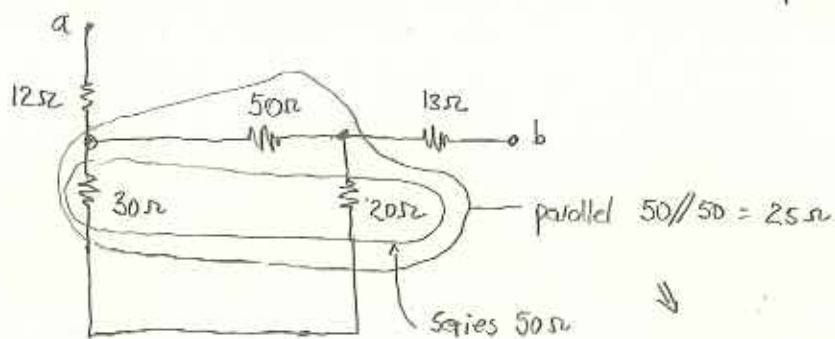


## Question 1

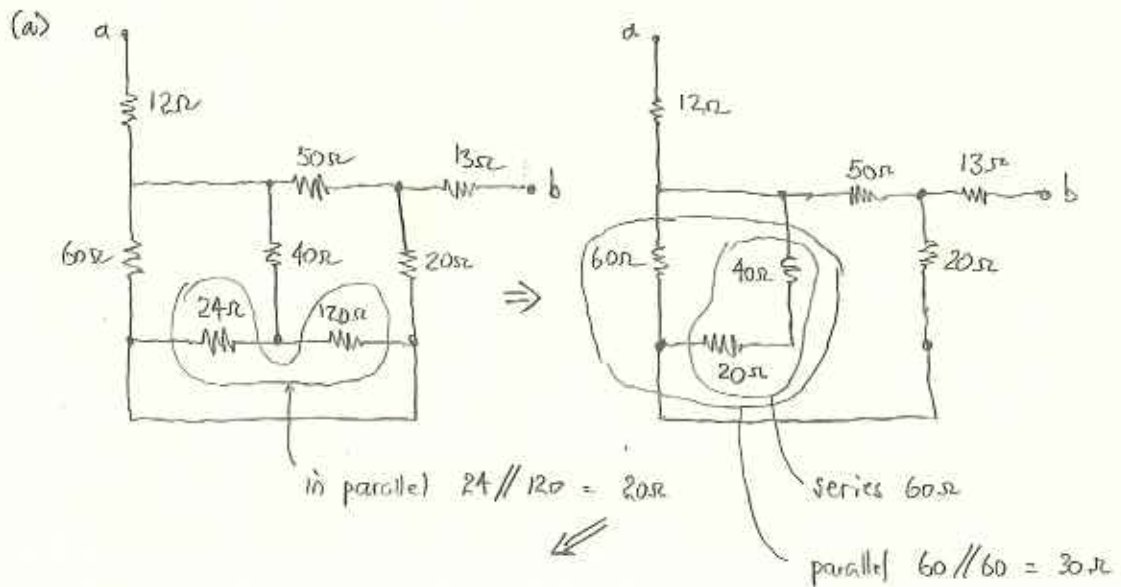

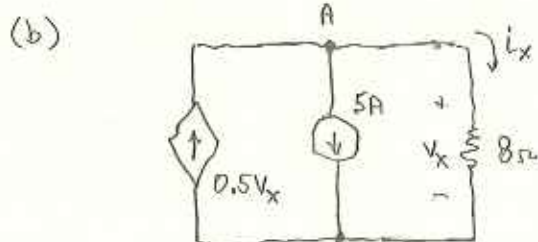Series:  $R_{ab} = 12 + 25 + 13$   
 $= \underline{\underline{50\Omega}}$



KCL at A gives

$$0.5V_x - 5 - i_x = 0$$

and  $V_x = 8i_x$ , or  $i_x = V_x/8$


Therefore,

$$0.5V_x - 5 - V_x/8 = 0$$

$$0.5V_x - 5 - 0.125V_x = 0$$

$$0.375V_x = 5, \quad \text{so} \quad V_x = \underline{\underline{13.333\text{ V}}}$$

(c)

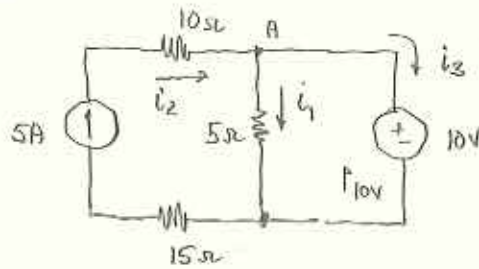

With the current directions defined as shown,  $i_2 = 5A$ , and

$$i_1 = \frac{10V}{5\Omega} = 2A.$$


KCL at node A gives  $i_2 - i_1 - i_3 = 0$ , so  $i_3 = i_2 - i_1$

$$i_3 = 5 - 2 = 3A$$

The power in the 10V source  $P_{10V} = +10V \times i_3$   
 $= +30W$

$|P_{10V}| = \underline{30W}$ , and this is absorbed.

(d)

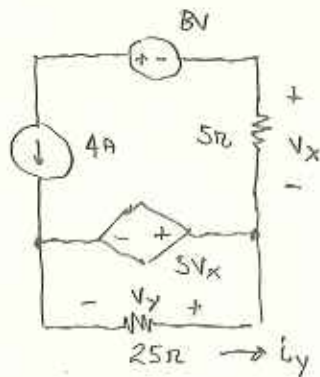

The voltage across the 25Ω resistor is indicated here as  $V_y$ .

$V_y$  must be  $V_y = 5V_x$  (parallel)

$$\text{so } i_y = -\frac{V_y}{25} = -\frac{5V_x}{25}$$


$$= -V_x/5$$

The current through the 5Ω resistor must be 4A in the direction of the current source (series).

$$\text{so } V_x = -4A \times 5\Omega \\ = -20V$$

$$\text{Therefore, } i_y = -V_x/5 \\ = -(-20)/5 \\ = \underline{4A}$$

(e)

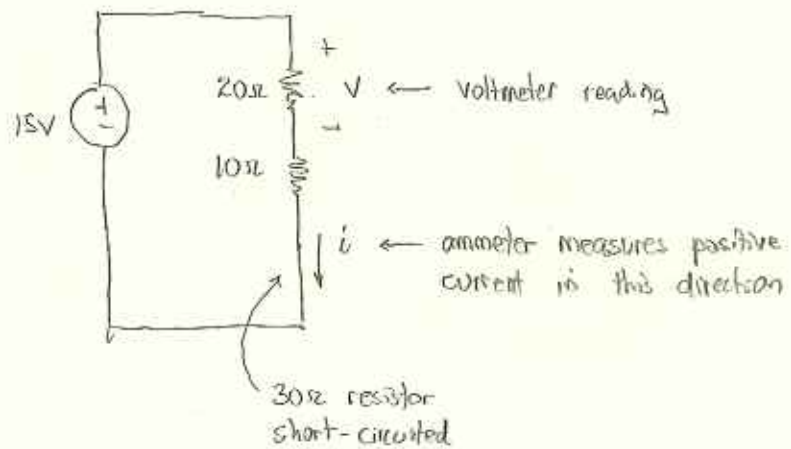


We have a simple voltage divider:  $V = \frac{20}{20+10} \times 15$

$$V = \underline{\underline{10\text{V}}}$$

And  $i = \frac{15}{20+10} = \underline{\underline{0.5\text{A}}}$

## Question 2

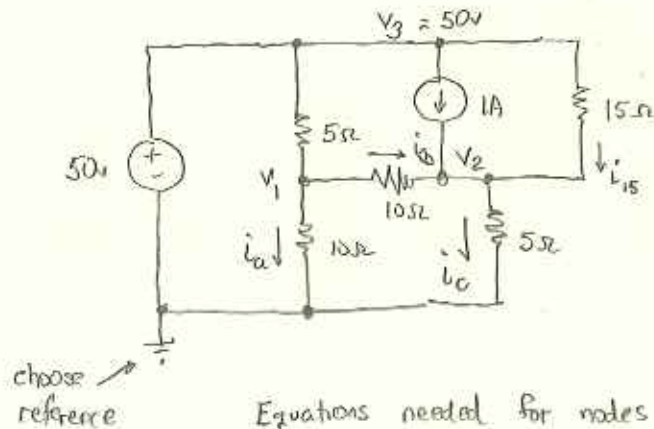Equations needed for nodes  $v_1$  and  $v_2$ 

$$\text{Node } v_1: \frac{v_1}{10} + \frac{v_1 - 50}{5} + \frac{v_1 - v_2}{10} = 0$$

$$\begin{aligned} (\times 10) \quad v_1 + 2v_1 - 100 + v_1 - v_2 &= 0 \\ 4v_1 - v_2 &= 100 \end{aligned} \quad (1)$$

$$\text{Node } v_2: \frac{v_2 - v_1}{10} - 1 + \frac{v_2}{5} + \frac{v_2 - 50}{15} = 0$$

$$\begin{aligned} (\times 30) \quad 3v_2 - 3v_1 - 30 + 6v_2 + 2v_2 - 100 &= 0 \\ 11v_2 - 3v_1 &= 130 \end{aligned} \quad (2)$$

From (1),  $v_2 = 4v_1 - 100$ . Substitute into (2)

$$\begin{aligned} 11(4v_1 - 100) - 3v_1 &= 130 \\ 44v_1 - 1100 - 3v_1 &= 130 \end{aligned}$$

$$41v_1 = 1230, \quad \text{so } \underline{v_1 = 30\text{V}}$$

From (2),  $v_2 = 4(30) - 100$ , so  $\underline{v_2 = 20\text{V}}$ .

$$\text{current } i_a: \quad i_a = \frac{v_1}{10\Omega} = \underline{\underline{3\text{A}}}$$

$$\text{current } i_b: \quad i_b = \frac{v_1 - v_2}{10\Omega} = \frac{30 - 20}{10} = \underline{\underline{1\text{A}}}$$

$$\text{current } i_c: \quad i_c = \frac{v_2}{5\Omega} = \frac{20}{5} = \underline{\underline{4\text{A}}}$$


With the current  $i_{15}$  in the  $15\Omega$  resistor as labeled,

$$i_{15} = \frac{50 - V_2}{15\Omega} = \frac{50 - 20}{15} = 2A$$

$$\begin{aligned} \text{The power } P_{15} &= i_{15}^2 \times 15\Omega \\ &= 2^2 \times 15 \end{aligned}$$

$$P_{15} = \underline{60W}$$

Question 3

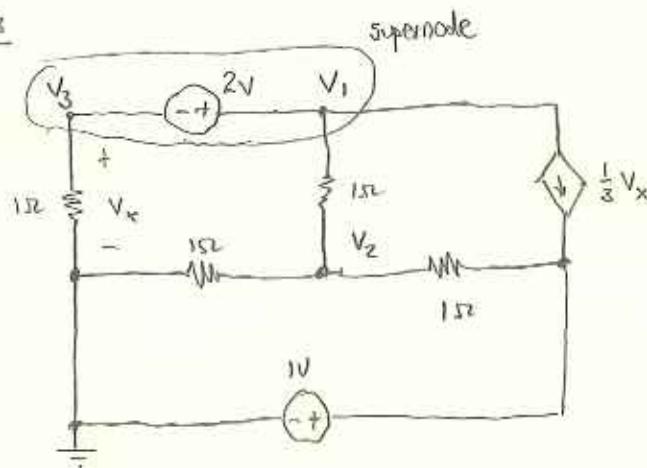

(a) Node-voltage method.

$$\begin{aligned} \text{Supernode: } \frac{V_3}{1} + \frac{V_1 - V_2}{1} + \frac{1}{3}V_x &= 0 \\ V_3 + V_1 - V_2 + \frac{1}{3}V_x &= 0 \end{aligned}$$

Note that  $V_x = V_3$  in the above circuit

$$\frac{4}{3}V_3 + V_1 - V_2 = 0 \quad (1)$$

$$\text{Supernode dependence: } V_1 - V_3 = 2V$$

$$\text{or } V_3 = V_1 - 2$$

$$\text{Substitute into (1) giving } \frac{4}{3}(V_1 - 2) + V_1 - V_2 = 0$$

$$\frac{7}{3}V_1 - V_2 = \frac{8}{3}$$

$$(x3) \quad 7V_1 - 3V_2 = 8 \quad (2)$$

$$\begin{aligned} \text{Node } v_2: \quad \frac{v_2}{1} + \frac{v_2 - 1}{1} + \frac{v_2 - v_1}{1} &= 0 \\ v_2 + v_2 - 1 + v_2 - v_1 &= 0 \\ 3v_2 - v_1 &= 1 \end{aligned} \quad (3)$$

From (3),  $v_1 = 3v_2 - 1$ . Substitute into (2)

$$\begin{aligned} 7(3v_2 - 1) - 3v_2 &= 8 \\ 21v_2 - 7 - 3v_2 &= 8 \\ 18v_2 &= 15 \end{aligned}$$

$$\text{so } v_2 = \frac{15}{18} = \underline{\underline{\frac{5}{6} \text{ V}}}$$

Substitute back into (3):  $3\left(\frac{5}{6}\right) - v_1 = 1$


$$v_1 = \frac{15}{6} - 1 = \frac{9}{6}$$

$$\underline{\underline{v_1 = \frac{3}{2} \text{ V}}}$$

Finally, from the supernode dependence  $v_3 = v_1 - 2$

$$v_3 = \frac{3}{2} - 2 = \underline{\underline{-\frac{1}{2} \text{ V}}}$$

(b) Mesh-current method

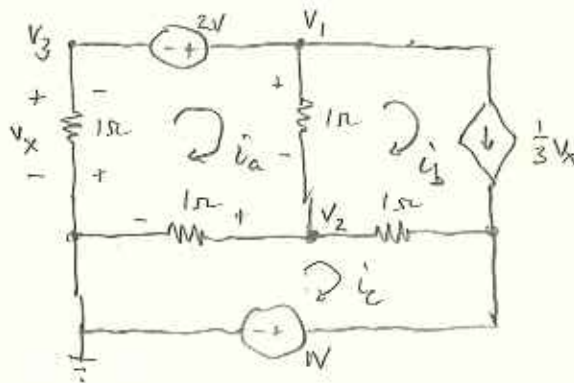

$$\begin{aligned} \text{mesh a: } -2 + 1 \times (i_a - i_b) + 1 \times (i_a - i_c) + i_a \times 1 &= 0 \\ -2 + i_a - i_b + i_a - i_c + i_a &= 0 \\ 3i_a - i_b - i_c &= 2 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{mesh c: } 1 + 1 \times (i_c - i_a) + 1 \times (i_c - i_b) &= 0 \\ 1 + i_c - i_a + i_c - i_b &= 0 \\ 2i_c - i_a - i_b &= -1 \quad (2) \end{aligned}$$

$$\begin{aligned} \text{mesh b: } i_b &= \frac{1}{3} V_x, \text{ where } V_x = -1 \times i_a \\ \text{Therefore, } i_b &= -\frac{1}{3} i_a \quad (3) \end{aligned}$$

Substitute (3) into (1) and (2)

$$\begin{aligned} (1) \rightarrow 3i_a + \frac{1}{3}i_a - i_c &= 2 \\ \frac{10}{3}i_a - i_c &= 2 \\ (\times 3) \quad 10i_a - 3i_c &= 6 \quad (4) \end{aligned}$$

$$\begin{aligned} (2) \rightarrow 2i_c - i_a + \frac{1}{3}i_a &= -1 \\ 2i_c - \frac{2}{3}i_a &= -1 \\ (\times 3) \quad 6i_c - 2i_a &= -3 \quad (5) \end{aligned}$$


From (4),  $i_c = \frac{10}{3}i_a - 2$ . Substitute into (5)

$$\begin{aligned} 6\left(\frac{10}{3}i_a - 2\right) - 2i_a &= -3 \\ 20i_a - 12 - 2i_a &= -3 \\ 18i_a &= 9 \\ i_a &= \underline{\underline{\frac{1}{2} \text{ A}}} \end{aligned}$$

And from (4),  $i_c = \left(\frac{10}{3}\right)\left(\frac{1}{2}\right) - 2 = \underline{\underline{-\frac{1}{3} \text{ A}}}$


And from (3),  $i_b = \left(-\frac{1}{3}\right)\left(\frac{1}{2}\right) = \underline{\underline{-\frac{1}{6} \text{ A}}}$

From the circuit, we see that

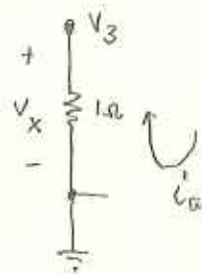


$$V_3 = V_x = -\frac{1}{2} \times 1 = \underline{\underline{-\frac{1}{2} \text{ V}}}$$

For node  $V_2$ ,

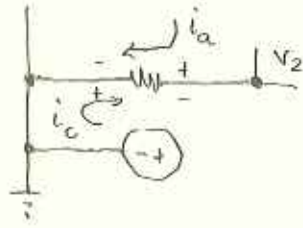

$$\begin{aligned} V_2 &= (i_a - i_c) \times 1\Omega \\ &= \frac{1}{2} - \left(-\frac{1}{3}\right) \\ &= \underline{\underline{\frac{5}{6} \text{ V}}} \end{aligned}$$

For node  $V_1$ ,

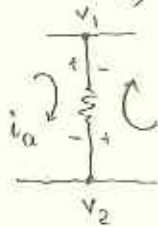

$$\begin{aligned} V_1 &= V_2 + (i_a - i_b) \times 1\Omega \\ &= \frac{5}{6} + \frac{1}{2} - \left(\frac{1}{6}\right) \\ &= \underline{\underline{\frac{3}{2} \text{ V}}} \end{aligned}$$