

Last Name: Solutions

Lecture Section: _____

First Name: _____

L01 - Pouyan (Yani) Jazayeri

L02 - Norm Bartley

L03 - Denis Onen

L04 - Anis Haque



ENGG 225 - Fundamentals of Electrical Circuits and Machines

Midterm Examination

Thursday, February 27, 2020

Time: 7:00 - 9:00 PM

Instructions:

- Time allowed is 2 hours.
 - The examination is closed-book.
 - Only calculators sanctioned by the Schulich School of Engineering (Casio FX-260, Casio FX-300MS, or TI-30XIIS) are permitted in the examination.
 - The maximum number of marks is 40, as indicated; please attempt all questions. The midterm examination counts 25% toward the final grade.
 - Please use a pen or heavy pencil to ensure legibility.
 - Please answer questions in the spaces provided; if space is insufficient, please use the back of the pages.
 - Please show your work; where appropriate, marks will be awarded for proper and well-reasoned explanations.
-



UCID: _____

1. [15 marks.] Parts (a)-(e) below each have an identical weighting of three marks. Please answer the questions in the boxes provided.

- (a) [3] In the circuit at right, find the total equivalent resistance R_{ab} between the terminals a and b.

Note 3Ω and 4Ω resistors in series, and then in parallel with a wire.

Circuit simplifies to:

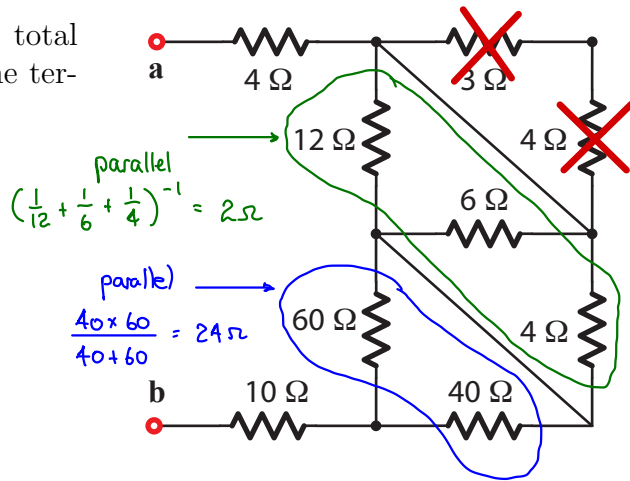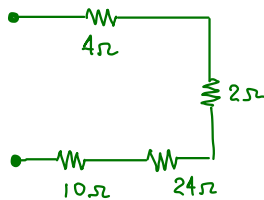


parallel $(\frac{1}{12} + \frac{1}{6} + \frac{1}{4})^{-1} = 2\Omega$

parallel $\frac{40 \times 60}{40 + 60} = 24\Omega$

$R_{ab} = 4 + 2 + 24 + 10 = 40\Omega$

Answer: $R_{ab} = 40\Omega$

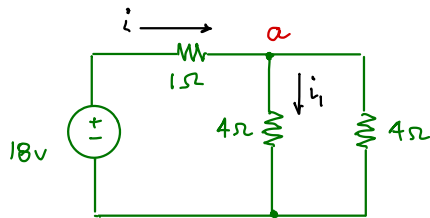- (b) [3] In the circuit at right, find the current i_x .




Total equivalent resistance across the source:

$R_{eq} = 4 // 4 + 1 = 3\Omega$

Therefore, $i = 18V / 3\Omega = 6A$


Current division at node a:

$i_1 = \frac{4}{4+4} \times i = 3A$

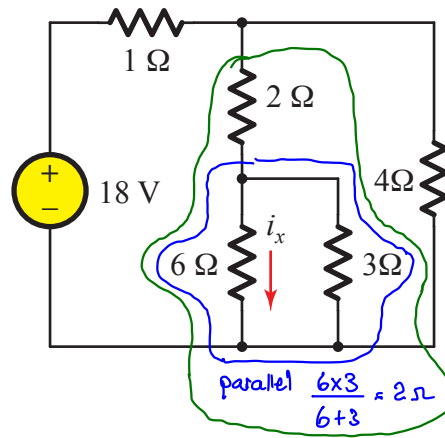


parallel $\frac{6 \times 3}{6 + 3} = 2\Omega$ Series $2 + 2 = 4\Omega$

Answer: $i_x = 1A$

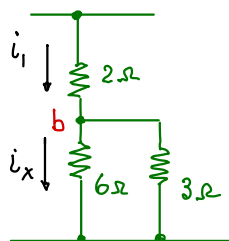

Current division at node b: $i_x = \frac{3}{6+3} \times i_1 = 1A$

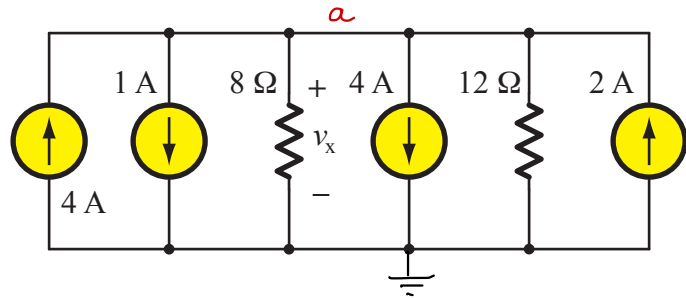(c) [3] Calculate the voltage v_x in the circuit at right.



Many ways to solve this.
Node a is the whole top wire.

Node equation:

$$\text{Node a: } -4 + 1 + \frac{v_a}{8} + 4 + \frac{v_a}{12} - 2 = 0$$

$$(\times 24) \quad -96 + 24 + 3v_a + 96 + 2v_a - 48 = 0$$


$$5v_a = 24$$

$$\text{so } v_a = 4.8.$$


And $v_a = v_x$.

Answer: $v_x = 4.8\text{V}$

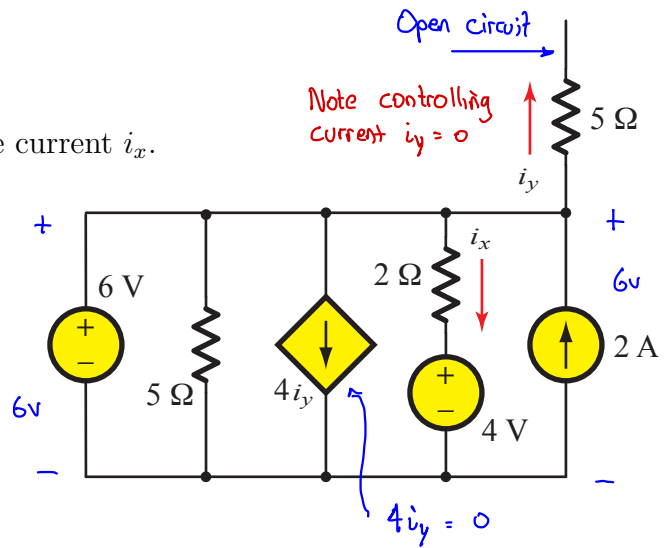(d) [3] In the circuit at right, calculate the current i_x .



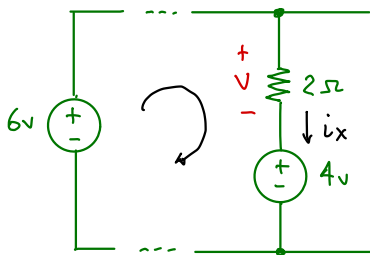Note 5 parallel branches with 6V across each.



KVL around this loop gives

$$-6 + v + 4 = 0$$

$$v = 2\text{V}$$

Therefore, $i_x = \frac{2\text{V}}{2\Omega} = 1\text{A}$

Answer: $i_x = 1\text{A}$

- (e) [3] In the circuit at right, assume that the voltmeter and ammeters are ideal. Give the voltmeter's reading v , and the two ammeter readings i_1 and i_2 .

Current i_1

$$i_1 = \frac{4\text{V}}{(1+3)\Omega} = 1\text{A}$$


Current i_2

There is no path for current through voltmeter, so $i = 0$ and $i_2 = 0$

Voltage v

Node b: $V_b = 0$ (ammeter is short-circuit to ground)

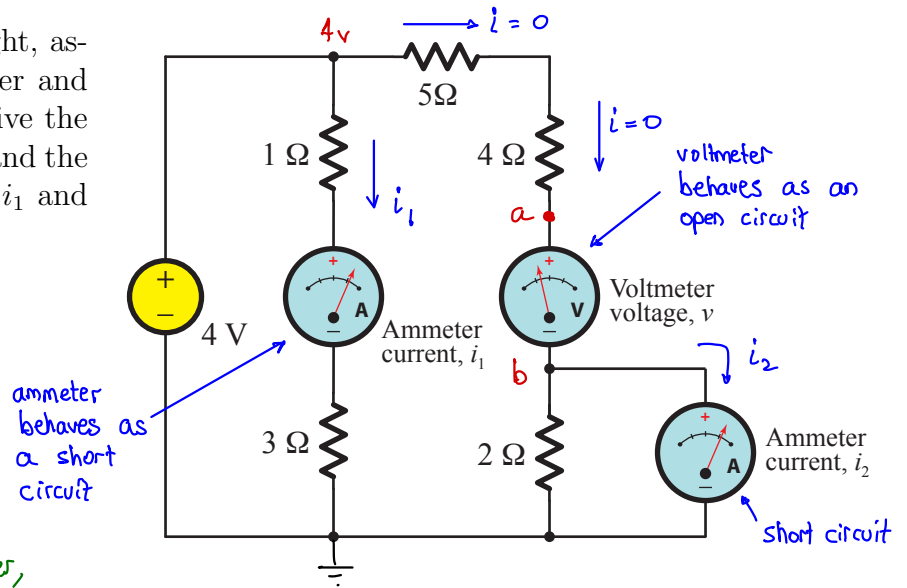Node a: $V_a = 4\text{V}$ (same as voltage across the source because $i = 0$ through 5Ω and 4Ω resistors)




Answer: $v = 4\text{V}$

Answer: $i_1 = 1\text{A}$

Answer: $i_2 = 0\text{A}$

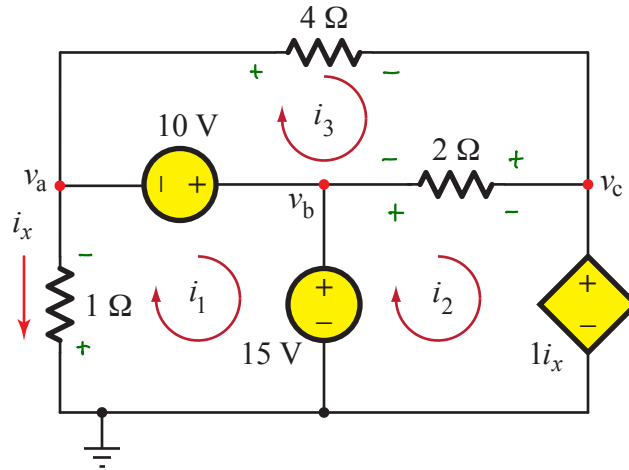2. [11 marks.] Consider the circuit below.



- (a) [8] Determine the mesh currents i_1, i_2, i_3 .
- (b) [3] Using your answers to part (a), calculate the node voltages v_a, v_b, v_c .

Mesh currents (Amperes)

Parameter	Value
i_1	-5A
i_2	5A
i_3	0A

Node voltages (Volts)

Parameter	Value
v_a	5v
v_b	15v
v_c	5v

Solve for i_2 and i_3 . Add equations (2) and (3):

$$\begin{array}{r} -2i_2 + 6i_3 = -10 \\ 2i_2 - 2i_3 = 10 \\ \hline 4i_3 = 0, \quad \text{so } \boxed{i_3 = 0} \end{array}$$

Then, from equation (3), $2i_2 - 0 = 10$, so $\boxed{i_2 = 5A}$

Mesh-current equations

Mesh i_1 : $15 + 1 \times i_1 - 10 = 0$
 so $\boxed{i_1 = -5A}$

Mesh i_2 : $-15 + 2(i_2 - i_3) + 1i_x = 0$
 $2i_2 - 2i_3 + i_x = 15$ — (1)

Mesh i_3 : $10 + 4i_3 + 2(i_3 - i_2) = 0$
 $-2i_2 + 6i_3 = -10$ — (2)

For the dependent source, we see that

$$i_x = -i_1 = 5A$$

Substitute into equation (1)

$$\begin{array}{r} 2i_2 - 2i_3 + 5 = 15 \\ 2i_2 - 2i_3 = 10 \end{array}$$
 — (3)

By inspection at nodes b and c:

Node b: $V_b = 15\text{V}$

Node c: $V_c = 1 \cdot i_x = -i_c$ $V_c = 5\text{V}$

(Question 2, additional workspace ...)

Two ways to solve for V_a .

1. KVL around mesh i_1


$$-V_a - 10 + 15 = 0$$

$$V_a = 5\text{V}$$


2. We know $i_1 = -5\text{A}$, so

$$V_a = -1 \times i_a$$

$$V_a = 5\text{V}$$

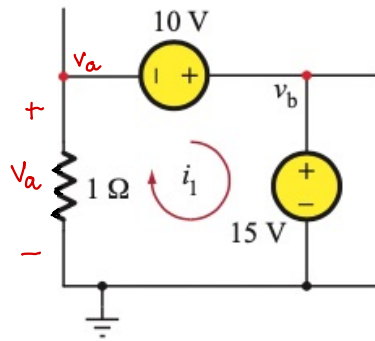

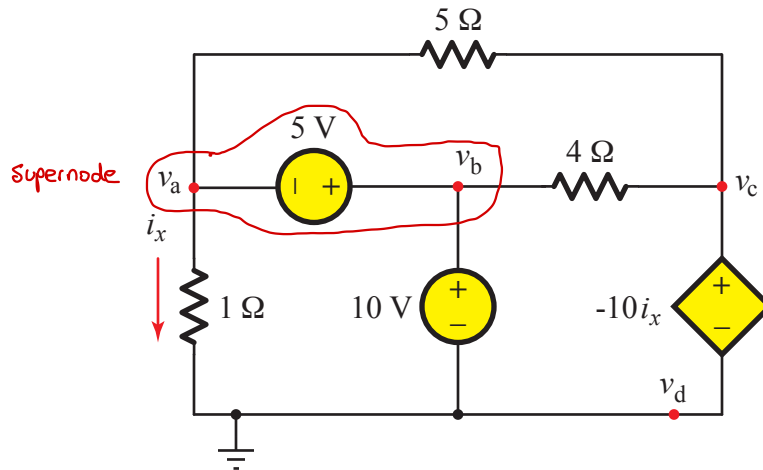3. [14 marks.] Consider the circuit below.



- (a) [8] Use the node-voltage method to solve for the node voltages v_a, v_b, v_c .
- (b) [6] Using your answers to part (a), calculate the power in all the circuit elements, and confirm energy balance.

Node voltages (Volts)

Parameter	Value
v_a	5v
v_b	10v
v_c	-50v
v_d	0v (reference)

Power (Watts)

Parameter	Value
$p_{1\Omega}$	25w
$p_{4\Omega}$	605w
$p_{5\Omega}$	900w
p_{10V}	-310w
p_{5V}	80w
p_{-10ix}	-1300w
Total	0w

We immediately know that

$$V_b = 10v$$

Nodes a and b form a supernode, for which the dependence equation is

$$V_b - V_a = 5v$$

With $V_b = 10v$, we will therefore know V_a immediately:

$$V_a = V_b - 5 = 10 - 5$$

$$V_a = 5v$$

Finally, for node c

$$V_c = -10i_x \quad \text{--- (1)}$$

where we see that

$$i_x = \frac{V_a}{1\Omega} = 5A$$

Therefore, from (1),

$$V_c = -10 \times 5 = -50v$$

$$V_c = -50v$$

Power calculations

(Question 3, additional workspace ...)

1Ω resistor

$$P_{1\Omega} = i_x^2 R = (5)^2 \times 1 = 25 \text{ W}$$

5Ω resistor

$$P_{5\Omega} = \frac{(V_a - V_c)^2}{5} = \frac{(V_c - V_a)^2}{5} = \frac{(-50 - 5)^2}{5} = 605 \text{ W}$$

4Ω resistor

$$P_{4\Omega} = \frac{(V_b - V_c)^2}{4} = \frac{(V_c - V_b)^2}{4} = \frac{(-50 - 10)^2}{4} = 900 \text{ W}$$

The 5-volt source

We will need a KCL calculation at node a to find i_a

$$\begin{aligned} \frac{V_a}{1} + \frac{V_a - V_c}{5} + i_a &= 0 \\ 5 + \frac{5 - (-50)}{5} + i_a &= 0 \\ i_a &= -16 \text{ A} \end{aligned}$$


Therefore, $P_{5V} = -(5)i_a = 80 \text{ W}$

The dependent source

Similarly, we need a KCL equation at node c to find i_c

$$\begin{aligned} \frac{V_c - V_b}{4} + \frac{V_c - V_a}{5} + i_c &= 0 \\ \frac{-50 - 60}{4} + \frac{-50 - 5}{5} + i_c &= 0 \\ i_c &= 26 \text{ A} \end{aligned}$$

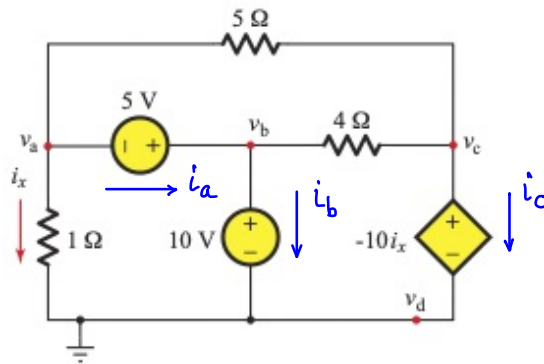Therefore, $P_{-10i_x} = (-10i_x)i_c = -50 \times 26 = -1300 \text{ W}$



The 10V source

Finally, a KCL equation at node b is needed

$$\begin{aligned} -i_a + i_b + \frac{V_b - V_c}{4} &= 0 \\ -(-16) + i_b + \frac{-60 - (-50)}{4} &= 0 \\ i_b &= -31 \text{ A} \end{aligned}$$

Therefore, $P_{10V} = 10 \times i_b = -310 \text{ W}$

(Please do not write in this space.)

#1 (15)	#2 (11)	#3 (14)	Total (40)