

Question 1

By KCL, we may write: $5.6 \text{ mA} = i_1 + i_2 + i_3$ (1)

We have $i_1 = 2i_2$ and $i_2 = 9i_3$, so $i_1 = 18i_3$

Substituting for i_1 and i_2 into equation (1),

$$5.6 \text{ mA} = 18i_3 + 9i_3 + i_3 = 28i_3$$

Therefore, $i_3 = 0.2 \text{ mA}$

The total voltage is given as 4V across all circuit elements.


$$R_3 = \frac{V}{i_3} = \frac{4}{0.2 \text{ mA}} = 20 \text{ k}\Omega$$

$$i_2 = 9i_3 = 1.8 \text{ mA}, \text{ so } R_2 = \frac{4}{1.8 \text{ mA}} = 2222.2 \Omega$$

$$i_1 = 2i_2 = 3.6 \text{ mA}, \text{ so } R_1 = \frac{4}{3.6 \text{ mA}} = 1111.1 \Omega$$


Question 2

Consider the 180V source alone

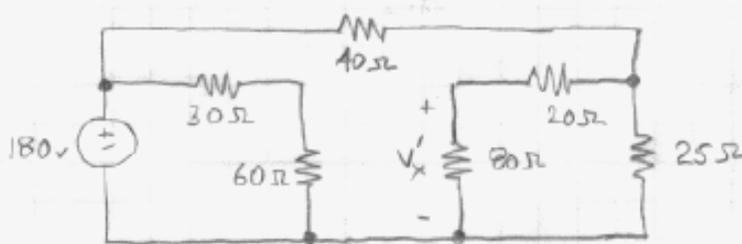


Note the 30Ω and 60Ω resistors do not influence V_x in any way

Redraw

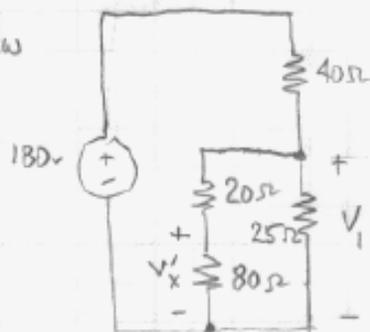

Equivalently, combining resistors,

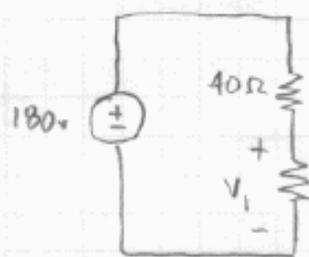


$$R_{eq} = (20 + 80) // 25 = 20\Omega$$

$$\text{Hence, } V_1 = \frac{20}{20+40} \times 180 = 60\text{V}$$


And after replacing R_{eq} with the original circuit,

$$V'_x = \frac{80}{80+20} \times V_1 = 48\text{V}$$

Now take the current source alone

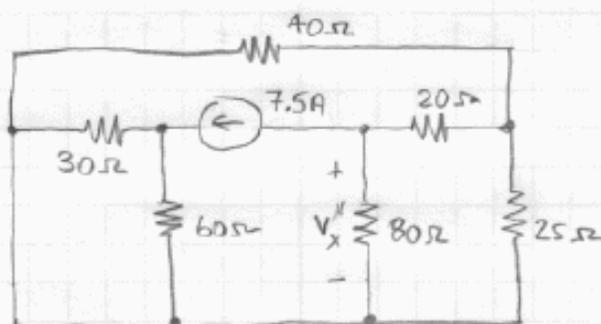

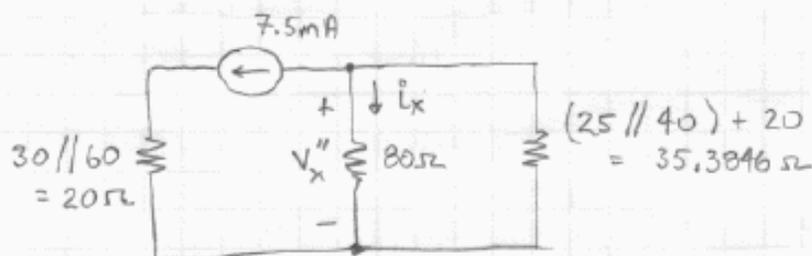After recognizing that we may combine several resistors,



Have a current divider:
$$i_x = \frac{-35.3846}{35.3846 + 80} \times 7.5\text{mA}$$

$$= -2.3\text{mA}$$


Therefore,
$$V_x'' = 80 i_x = -184\text{V}$$

Finally,
$$V_x = V_x' + V_x'' = -136\text{V}$$

Question 3

(a) The mesh-current method would be simplest to use. There are three meshes. One mesh current is fixed at 19.6 A. Thus, we will have two equations, two unknowns.

(b) Set up for mesh-current method

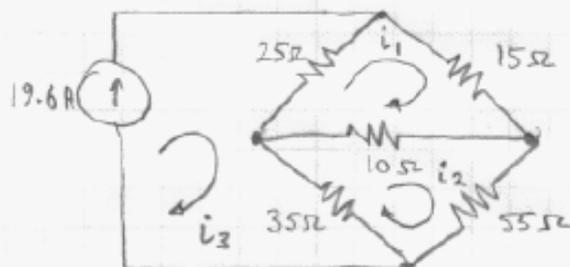

$$\text{Mesh 1: } 15i_1 + 10(i_1 - i_2) + 25(i_1 - i_3) = 0$$

$$\text{or } 50i_1 - 10i_2 - 25i_3 = 0$$

$$\text{But } i_3 = 19.6 \text{ A, so } 50i_1 - 10i_2 = 490 \quad (1)$$

$$\text{Mesh 2: } 55i_2 + 35(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$\text{or } 100i_2 - 10i_1 - 35i_3 = 0$$

$$\text{Again } i_3 = 19.6 \text{ A, so } -10i_1 + 100i_2 = 686 \quad (2)$$

Add equation (1) to 5 times equation (2)

$$\begin{array}{r} 50i_1 - 10i_2 = 490 \\ + \quad -50i_1 + 500i_2 = 3430 \\ \hline \end{array}$$

$$490i_2 = 3920 \quad \therefore i_2 = 8 \text{ A}$$


$$\text{From (1), } 50i_1 - 80 = 490 \quad \therefore i_1 = 11.4 \text{ A}$$

The power in the 10Ω resistor can be determined from the branch current, which is either $i_1 - i_2$ or $i_2 - i_1$

$$i_1 - i_2 = 3.4 \text{ A, so } P_{10} = (3.4)^2 10$$

$$P_{10} = 115.6 \text{ W}$$

Question 4.

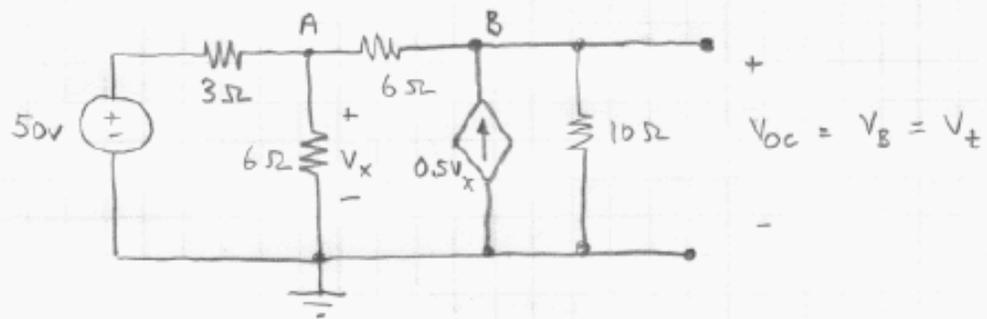First, find the Thevenin voltage V_t 

Node-voltage method looks easiest.

$$\begin{aligned} \text{Node A: } \quad & \frac{V_A - 50}{3} + \frac{V_A}{6} + \frac{V_A - V_B}{6} = 0 \\ \text{or } \quad & 2V_A - 100 + V_A + V_A - V_B = 0 \\ & 4V_A - V_B = 100 \quad (1) \end{aligned}$$

$$\begin{aligned} \text{Node B: } \quad & \frac{V_B - V_A}{6} - 0.5V_x + \frac{V_B}{10} = 0 \\ \text{or } \quad & 5V_B - 5V_A - 15V_x + 3V_B = 0 \end{aligned}$$

We may recognize that $V_x = V_A$ (this was a very popular mistake!)

$$\begin{aligned} \text{so } \quad & 5V_B - 5V_A - 15V_A + 3V_B = 0 \\ & 8V_B = 20V_A \quad (2) \end{aligned}$$


From (2), $V_A = (2/5)V_B$, so from (1)

$$(8/5)V_B - V_B = 100$$

$$\therefore V_B = 166.67 \text{ V}$$

$$V_t = V_{bc} = V_B = 166.67 \text{ V}$$

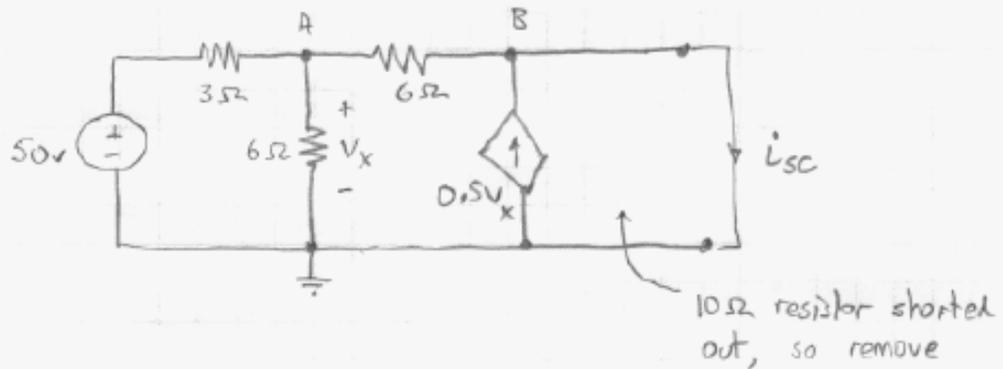Next, we need to find i_{sc} to get Thevenin resistance



Sticking with the node voltage method,

$$\text{Node A: Same as before: } 4V_A - V_B = 100 \quad (1)$$

$$\text{Node B: } \frac{V_B - V_A}{6} - 0.5V_x + i_{sc} = 0$$

$$\text{or } V_B - V_A - 3V_x + 6i_{sc} = 0$$

As before, $V_x = V_A$. We also have, because of the short circuit, $V_B = 0$

$$-V_A - 3V_A + 6i_{sc} = 0$$

$$V_A = (3/2)i_{sc} \quad (2)$$

Substitute (2) into (1) with $V_B = 0$,

$$6i_{sc} = 100 \quad \therefore i_{sc} = 16.667 \text{ A}$$

$$\text{Finally, } R_t = \frac{V_t}{i_{sc}} = \frac{166.667 \text{ V}}{16.667 \text{ A}}$$

$$= 10 \Omega$$

