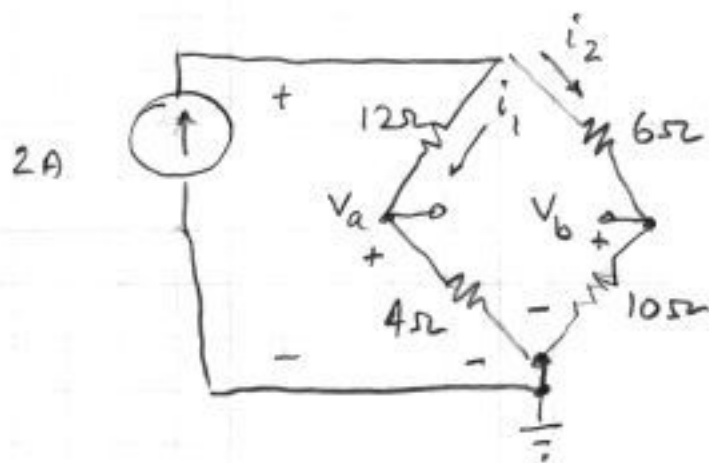


Question 1

(a) Many ways to solve this



We have two parallel branches with  $16\Omega$  in each.


Current will split evenly

$$i_1 = i_2 = 1A$$

Therefore,  $V_a = 1 \times 4 = 4V$   
 $V_b = 1 \times 10 = 10V$

And  $V_{ab} = V_a - V_b = -6V$

(b) Set up for mesh-current method

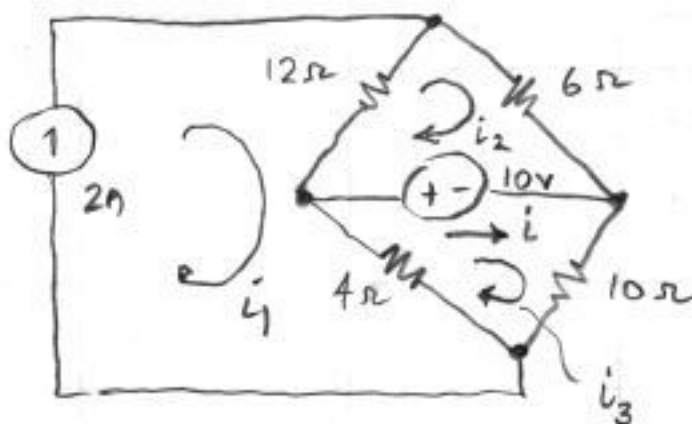

We will need

$$i = i_3 - i_2$$

Mesh 1:  $i_1 = 2A$

Mesh 2:  $6i_2 - 10 + 12(i_2 - i_1) = 0$   
 $-12i_1 + 18i_2 = 10$  (1)

Mesh 3:  $10i_3 + 4(i_3 - i_1) + 10 = 0$   
 $-4i_1 + 14i_3 = -10$  (2)

Substitute for  $i_1$

$$-24 + 18i_2 = 10$$

$$\text{so } 18i_2 = 34$$

$$\therefore i_2 = \frac{17}{9} = 1.889$$

22-141 50 SHEETS  
 22-142 100 SHEETS  
 22-144 200 SHEETS




$$\begin{aligned} -8 + 14i_3 &= -10 \\ 14i_3 &= -2 \end{aligned} \quad \therefore \boxed{i_3 = -\frac{1}{7}} = -0.1429$$

$$\text{Finally, } i = i_3 - i_2 = -\frac{1}{7} - \frac{17}{9} = -\frac{9}{63} - \frac{119}{63}$$

$$\boxed{i = -\frac{128}{63}} = -2.082 \text{ A}$$

### Question 2

Thevenin equivalent. Solve for  $V_t$

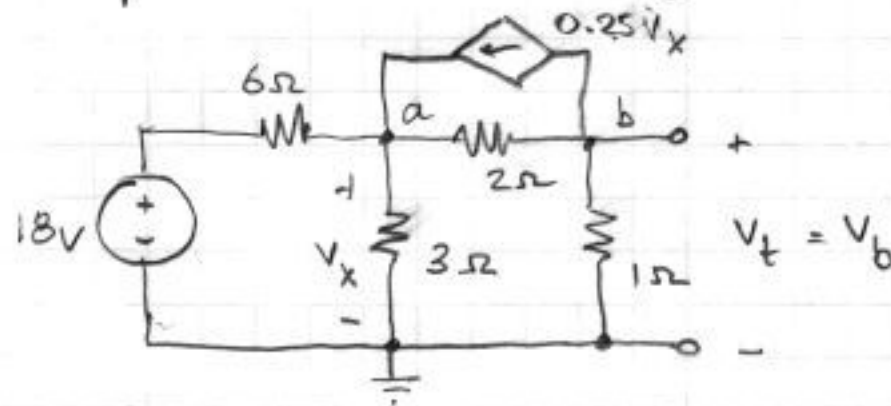

Node-voltage method a sensible way to proceed

$$\text{Node a: } \frac{V_a - 18}{6} + \frac{V_a - V_b}{2} - 0.25V_x + \frac{V_a}{3} = 0$$

We observe that  $V_x = V_a$ , so

$$\frac{V_a - 18}{6} + \frac{V_a - V_b}{2} - 0.25V_a + \frac{V_a}{3} = 0$$

$$2V_a - 36 + 6V_a - 6V_b - 3V_a + 4V_a = 0$$

$$9V_a - 6V_b = 36 \quad (1)$$

$$\text{Node b: } \frac{V_b - V_a}{2} + \frac{V_b}{1} + 0.25V_x = 0$$

$$2V_b - 2V_a + 4V_b + V_a = 0$$


$$-V_a + 6V_b = 0 \quad (2)$$

From (2),  $V_a = 6V_b$ , so from (1)

$$54V_b - 6V_b = 36$$

$$48V_b = 36 \quad \therefore \boxed{V_t = V_b = 0.75\text{V}}$$

Now solve for  $i_{sc}$  and  $R_t$

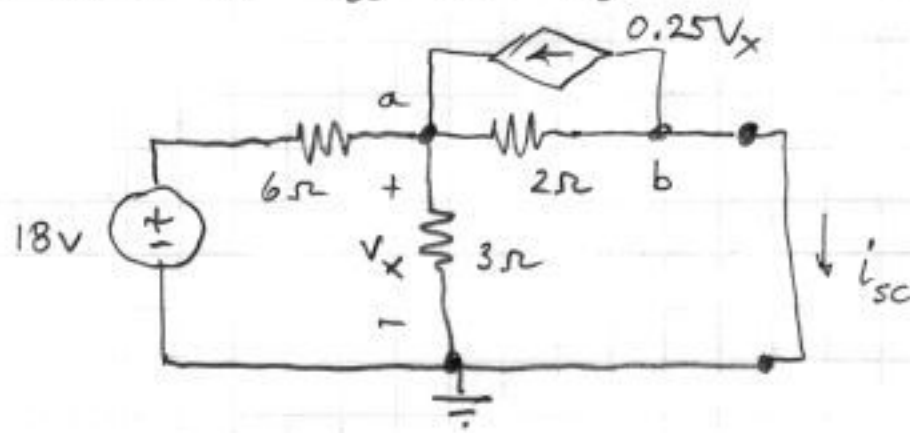

Let's stick with node-voltage in terms of unknown  $i_{sc}$ .  
 $V_b$  now known as  $V_b = 0$ .

$$\text{node a: } \frac{V_a - 18}{6} + \frac{V_a}{3} + \frac{V_a - V_b}{2} - 0.25V_x = 0$$

(unchanged from previous calculation)

$$9V_a - 6V_b = 36$$

$$V_a = 4$$

$$\text{node b: } \frac{V_b - V_a}{2} + 0.25V_x + i_{sc} = 0$$

$$2V_b - 2V_a + V_a + 4i_{sc} = 0$$

$$-V_a + 4i_{sc} = 0$$


$$i_{sc} = \frac{V_a}{4} = 1$$

Therefore,

$$\boxed{\begin{aligned} V_t &= 0.75 \text{ V} \\ R_t &= \frac{V_t}{i_{sc}} = 0.75 \Omega \end{aligned}}$$

Question 3

(a) Node-voltage method

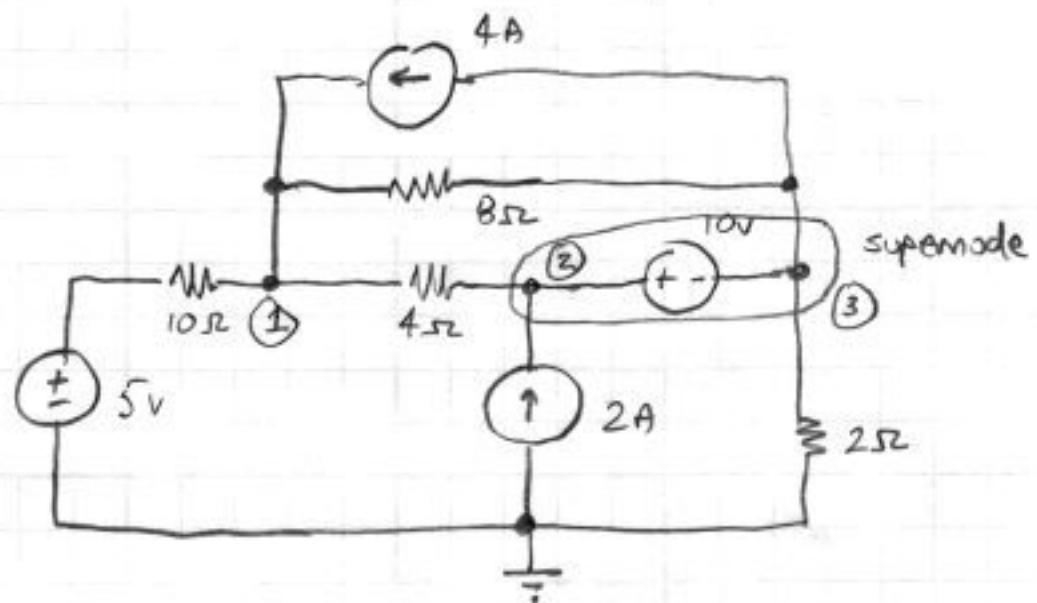

$$\text{Node 1: } \frac{V_1 - 5}{10} + \frac{V_1 - V_2}{4} + \frac{V_1 - V_3}{8} - 4 = 0$$

$$4V_1 - 20 + 10V_1 - 10V_2 + 5V_1 - 5V_3 - 160 = 0$$

$$19V_1 - 10V_2 - 5V_3 = 180 \quad (1)$$

$$\text{Supernode: } \frac{V_2 - V_1}{4} - 2 + \frac{V_3}{2} + \frac{V_3 - V_1}{8} + 4 = 0$$

$$2V_2 - 2V_1 - 16 + 4V_3 + V_3 - V_1 + 32 = 0$$

$$-3V_1 + 2V_2 + 5V_3 = -16 \quad (2)$$

$$\text{And within the supernode, } \begin{aligned} V_2 - V_3 &= 10 \\ \text{so } V_3 &= V_2 - 10 \end{aligned} \quad (3)$$

Substituting (3) into (1) and (2)

$$\begin{aligned} 19V_1 - 10V_2 - 5(V_2 - 10) &= 180 \\ 19V_1 - 15V_2 &= 130 \end{aligned} \quad (4)$$

$$\begin{aligned} -3V_1 + 2V_2 + 5(V_2 - 10) &= -16 \\ -3V_1 + 7V_2 &= 34 \end{aligned} \quad (5)$$

$$\text{From (5), } V_2 = \frac{34 + 3V_1}{7}, \text{ and substitute into (4)}$$

$$19V_1 - 15 \left( \frac{34 + 3V_1}{7} \right) = 130$$

$$133V_1 - 510 - 45V_1 = 910$$

$$88V_1 = 1420$$

$$\text{so } V_1 = 16.136 \text{ v}$$

and therefore

$$V_2 = \frac{34 + 3(16.136)}{7}$$

$$\text{so } V_2 = 11.773 \text{ v}$$


We don't need it, but  $V_3 = V_2 - 10 = 1.773$

Finally,

$$i_x = \frac{V_2 - V_1}{4}$$

$$i_x = 1.09091$$

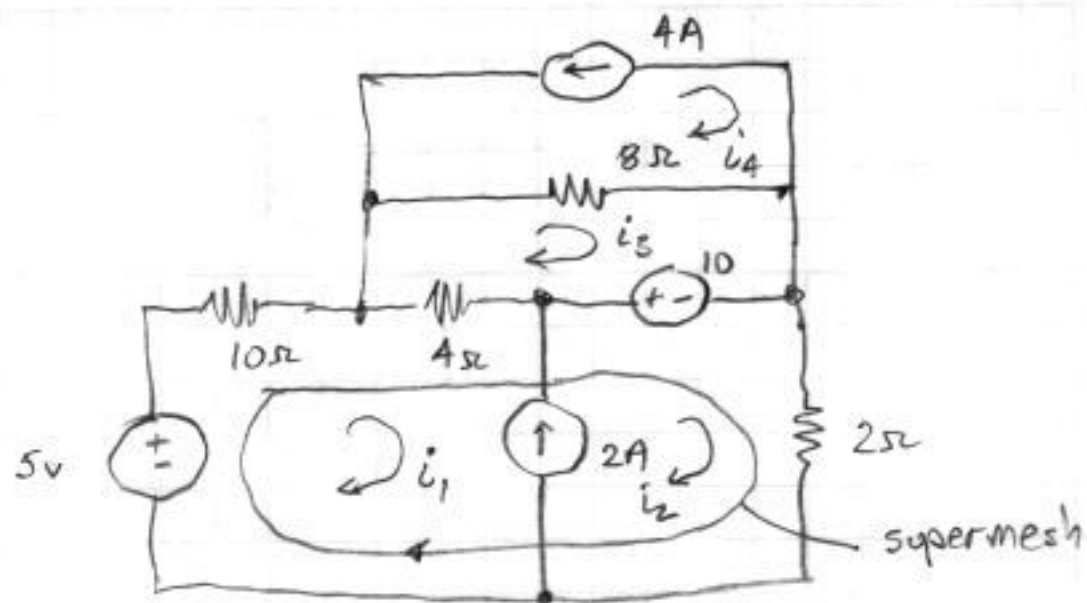Alternatively, by the mesh-current method



$$\text{Supermesh: } -5 + 10i_1 + 4(i_1 - i_3) + 10 + 2i_2 = 0$$

$$14i_1 + 2i_2 - 4i_3 = -5 \quad (1)$$

$$\begin{aligned} \text{Mesh 3: } 4(i_3 - i_1) + 8(i_3 - i_4) - 10 &= 0 \\ -4i_1 + 12i_3 - 8i_4 &= 10 \end{aligned} \quad (2)$$

$$\text{Mesh 4: } i_4 = -4A \quad (3)$$

$$\begin{aligned} \text{And within the supernode, } i_2 - i_1 &= 2 \\ \text{so } i_2 &= 2 + i_1 \end{aligned} \quad (4)$$

First, substitute (3) into (2)

$$\begin{aligned} -4i_1 + 12i_3 - 8(-4) &= 10 \\ -4i_1 + 12i_3 &= -22 \end{aligned} \quad (5)$$

Substitute (4) into (1)

$$\begin{aligned} 14i_1 + 2(2 + i_1) - 4i_3 &= -5 \\ 16i_1 - 4i_3 &= -9 \end{aligned} \quad (6)$$

Add  $4 \times (5)$  with (6)

$$\begin{aligned} -16i_1 + 48i_3 &= -88 \\ 16i_1 - 4i_3 &= -9 \\ \hline 44i_3 &= -97 \end{aligned}$$

$$\therefore i_3 = -2.2045$$

From (6),

$$\begin{aligned} i_1 &= \frac{4i_3 - 9}{16} \\ &= \frac{4(-2.2045) - 9}{16} \end{aligned}$$

$$\therefore i_1 = -1.1136$$


Don't need 'em but

$$\begin{aligned} i_2 &= 0.8864 \\ i_4 &= -4 \end{aligned}$$

And finally  $i_x = i_1 - i_3$

$$\boxed{i_x = 1.09091}$$

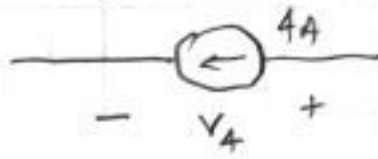(b) Using node voltages  $v_1, v_3$ , and assigning the polarity as follows




We have  $v_4 = v_3 - v_1 = -14.3634 \text{ v}$

and  $P = v_i = -57.4 \text{ W}$  GENERATING
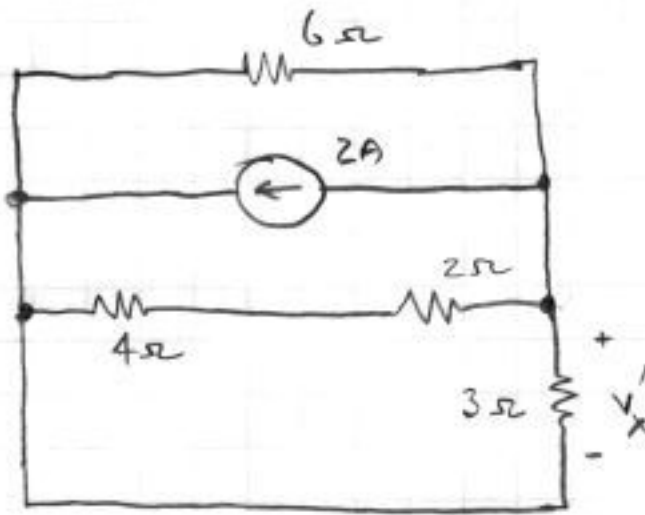
### Question 4

Solve by superposition. Let's start with the 2A source



It appears that the total resistance across the source is

$$R_{eq} = 6 \parallel (2+4) \parallel 3$$


and that  $v'_x$  is the total voltage across the source.

$$\begin{aligned} R_{eq} &= 6 \parallel 6 \parallel 3 \\ &= 3 \parallel 3 \\ &= 1.5 \Omega \end{aligned}$$


and therefore,

$$v'_x = -2 \text{ A} \times 1.5 \Omega = -3 \text{ V}$$

Next, the 1A source acting alone

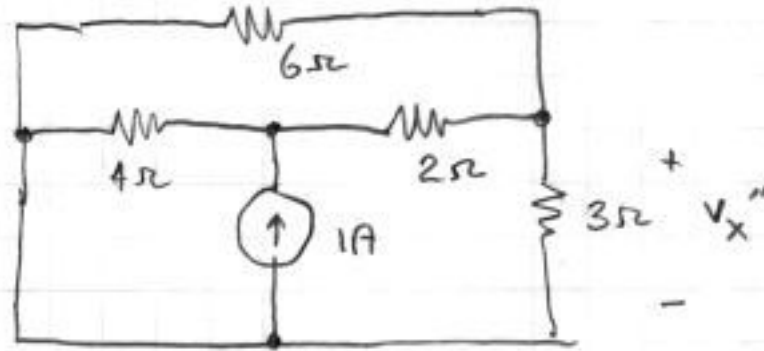

Redrawing,

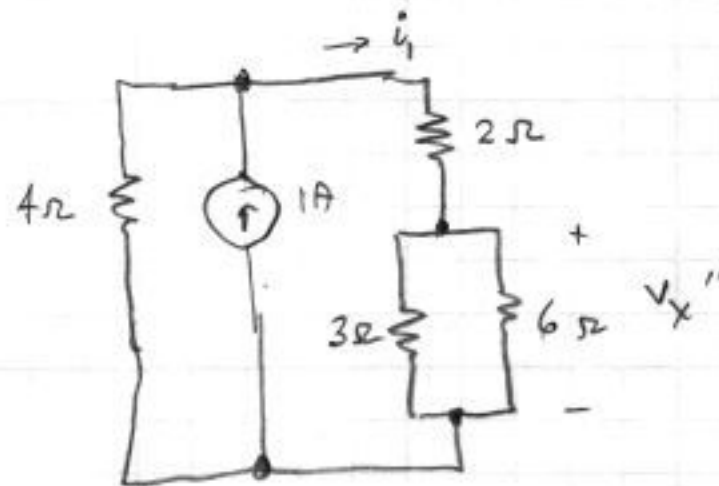


On the right side,  $R_{eq} = 2 + 6 // 3 = 4\Omega$

Current divider, so  $i_1 = \frac{4}{4+4} \times 1 = 0.5 \text{ A}$

Therefore,  $V_x'' = 0.5 \times 3 // 6 = 1 \text{ V.}$

Finally, the 20V source acting alone

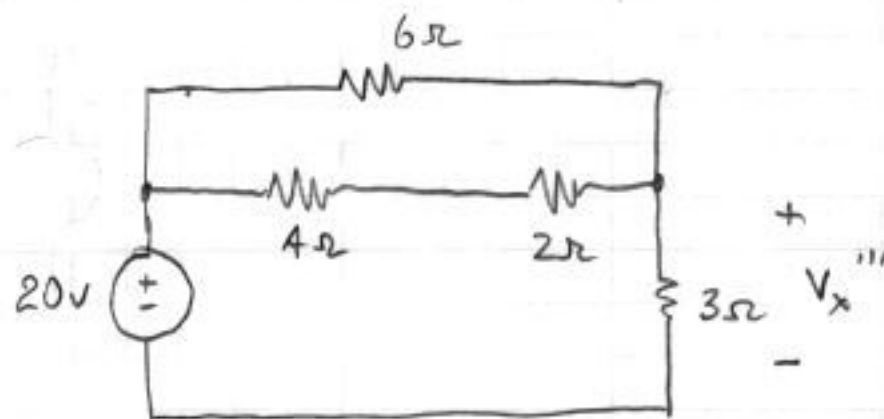



Voltage divider

$$V_x''' = \frac{3}{3 + (6 \parallel (2+4)) + 3} \times 20$$
$$= 10 \text{ V}$$

Combining all three results,

$$V_x = V_x' + V_x'' + V_x'''$$
$$= -3 + 1 + 10$$

$$\boxed{V_x = 8 \text{ V}}$$