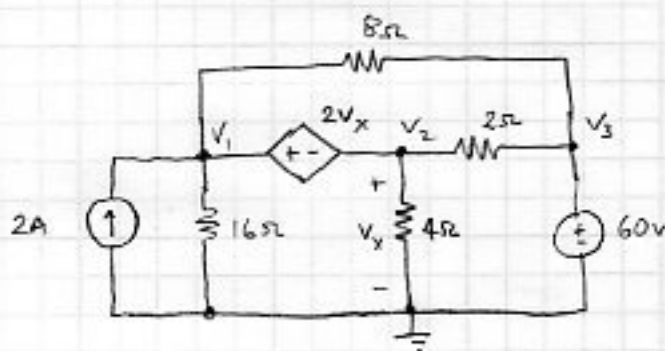


Question 1

(a)



Solving for node voltages, so set up the node-voltage method.

Node V_3 : $V_3 = 60$

$$\text{Supernode } V_1/V_2: \quad -2 + \frac{V_1}{16} + \frac{V_1 - V_3}{8} + \frac{V_2}{4} + \frac{V_2 - V_3}{2} = 0$$

$$\text{or } -32 + V_1 + 2V_1 - 2V_3 + 4V_2 + 8V_2 - 8V_3 = 0$$

$$\text{so } 3V_1 + 12V_2 - 10V_3 = 32$$

Substitute $V_3 = 60$ and this simplifies to

$$3V_1 + 12V_2 - 600 = 32$$

$$3V_1 + 12V_2 = 632 \quad (1)$$

Within the supernode:

$$V_1 - V_2 = 2V_x, \text{ where } V_x = V_2$$

$$V_1 - V_2 = 2V_2$$

$$V_1 = 3V_2 \quad (2)$$

Substitute (2) into (1)

$$9V_2 + 12V_2 = 632$$

$$21V_2 = 632$$

so $V_2 = 30.1 \text{ v}$


and from (2), $V_1 = 90.3 \text{ v}$

(b) Using the passive reference convention for power

$$p = -2V_1 = -180.6 \text{ W}$$

Question 2

(a)

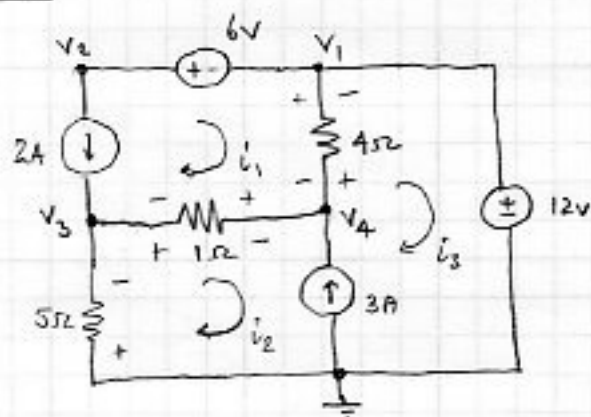

Solving for mesh currents, so set up for the mesh-current method

$$\text{Loop 1: } i_1 = -2A$$

$$\text{Supermesh } i_2/i_3: \quad 5i_2 + (i_2 - i_1) + 4(i_3 - i_1) + 12 = 0$$

$$6i_2 - 5i_1 + 4i_3 = -12$$

$$\text{Substitute } i_1 = -2$$

$$6i_2 + 10 + 4i_3 = -12$$

$$6i_2 + 4i_3 = -22 \quad (1)$$

And within the supermesh

$$i_3 - i_2 = 3$$

$$i_3 = 3 + i_2 \quad (2)$$

Substitute (2) into (1)

$$6i_2 + 4(3 + i_2) = -22$$

$$6i_2 + 12 + 4i_2 = -22$$

$$10i_2 = -34$$

$$i_2 = -3.4 \text{ A}$$

and substitute back into (2)


$$i_3 = 3 + (-3.4) = -0.4 \text{ A}$$

- (b) Note that $V_1 = 12\text{v}$.
 Note also that node V_2 is simply 6 volts higher than V_1 , since the two nodes are joined by a voltage source.

$$V_1 = 12$$

$$V_2 = 18$$

At node V_4 ,

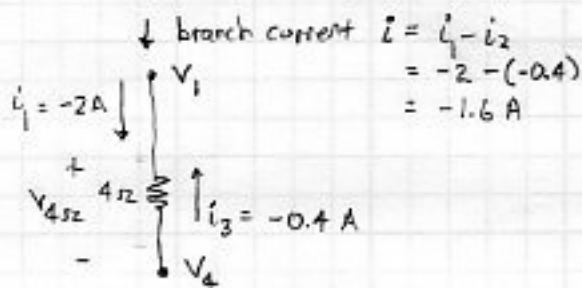

$$\text{so } V_{4r} \text{ as shown} = i \times 4\Omega = -6.4\text{v}$$

$$\text{Therefore, } V_1 - V_4 = V_{4r} = -6.4\text{v}$$

$$12 - V_4 = -6.4$$

$$V_4 = 12 + 6.4 = 18.4\text{v}$$

At node V_3 , use loop i_2 (easiest)


$$V_3 = -i_2 \times 5$$

$$= -(-3.4) \times 5$$

$$= 17\text{v}$$

Question 3

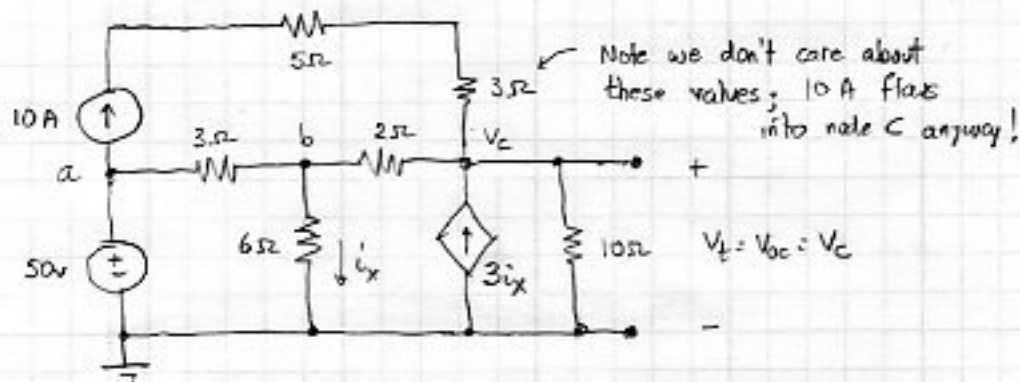(a) Let's begin with the Thevenin voltage $V_t = V_{oc}$.



Setting up for the node-voltage method.

$$\text{Node a: } V_a = 50\text{V}$$

$$\begin{aligned} \text{Node b: } \frac{V_b - V_a}{3} + \frac{V_b}{6} + \frac{V_b - V_c}{2} &= 0 \\ 2V_b - 2V_a + V_b + 3V_b - 3V_c &= 0 \\ -2a + 6V_b - 3V_c &= 0 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{Node c: } -10 - 3i_x + \frac{V_c - V_b}{2} + \frac{V_c}{10} &= 0 \\ \rightarrow \text{note that } i_x = \frac{V_b}{6}, \text{ so} \\ -10 - 0.5V_b + \frac{V_c - V_b}{2} + \frac{V_c}{10} &= 0 \\ -100 - 5V_b + 5V_c - 5V_b + V_c &= 0 \\ -10V_b + 6V_c &= 100 \end{aligned} \quad (2)$$

From (1) with $V_a = 50$,

$$\begin{aligned} -100 + 6V_b - 3V_c &= 0 \\ 6V_b - 3V_c &= 100 \end{aligned} \quad (3)$$

$$\text{From (2), } V_b = \frac{100 - 6V_c}{-10} = 0.6V_c - 10$$

Substitute into (3)


$$6(0.6V_c - 10) - 3V_c = 100$$

$$3.6V_c - 60 - 3V_c = 100$$

$$0.6V_c = 160$$

Hence, $V_c = \frac{160}{0.6} = \boxed{266.67}$ THEVENIN VOLTAGE V_t

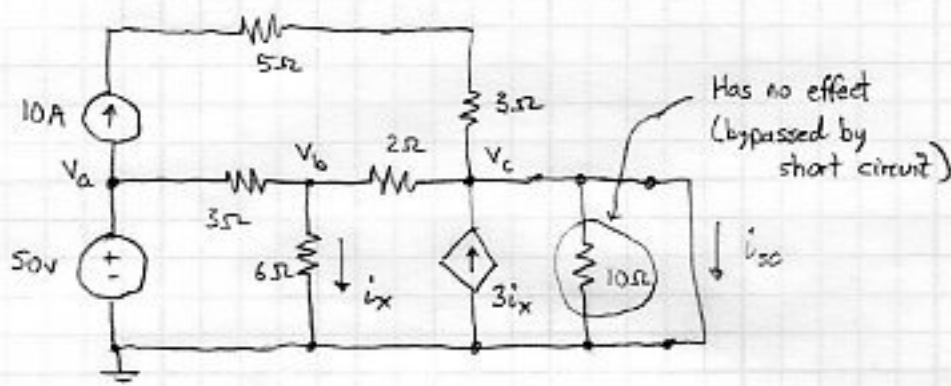Next find R_t . Unfortunately, no short-cuts thanks to the dependent source.



Node voltage method.

Node a: $V_a = 50$, as before

Node b: $\frac{V_b - V_a}{3} + \frac{V_b}{6} + \frac{V_b - V_c}{2} = 0$

→ We know $V_a = 50$ and $V_c = 0$ (thanks to short circuit)

$$\frac{V_b - 50}{3} + \frac{V_b}{6} + \frac{V_b}{2} = 0$$

$$2V_b - 100 + V_b + 3V_b = 0$$

$$6V_b = 100$$



$$\text{so } V_b = 16.67 \text{ v}$$

Node c: $-10 - 3i_x + \frac{V_c - V_b}{2} + \frac{V_c}{10} + i_{sc} = 0$

$$-10 - 0.5V_b - 0.5V_b + i_{sc} = 0$$

$$\begin{aligned} \text{so } I_{sc} &= 10 + V_b \\ &= \boxed{26.67 \text{ A}} \quad \text{SHORT-CIRCUIT CURRENT} \end{aligned}$$
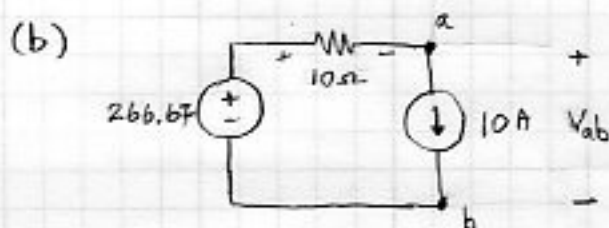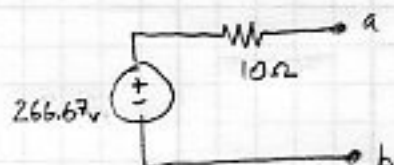
$$\text{Therefore, } R_t = \frac{V_t}{I_{sc}} = \frac{266.67}{26.67} = 10 \Omega$$




$$\text{KVL around this loop gives } -266.67 + 10(10) + V_{ab} = 0$$


$$V_{ab} = 166.67 \text{ V}$$

Question 4

(i) 12-volt source acting alone

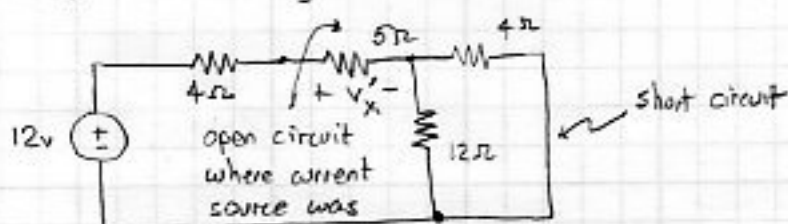


Redrawing

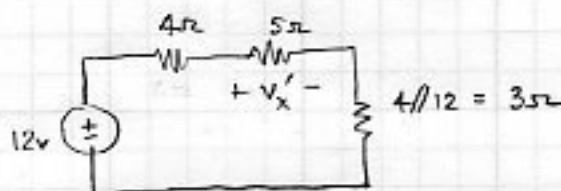


Voltage divider : $V_x' = \frac{5}{4+5+3} \times 12 = 5V$

(ii) 2-amp source acting alone

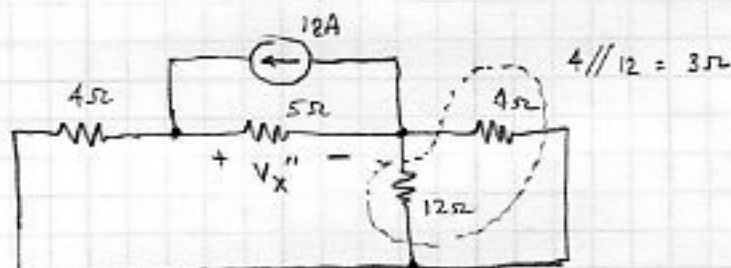

Redrawing

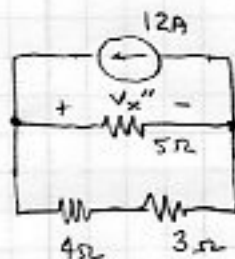


Total Req across current source


$$R_{eq} = 7 \parallel 5 = 2.9167 \Omega = \frac{35}{12} \Omega$$

Therefore, $V_x'' = 12 \times \frac{35}{12} = 35V$

(iii) 19-volt source acting alone

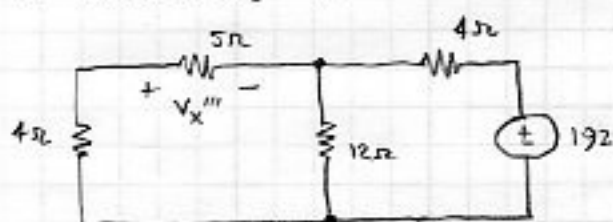

Redraw

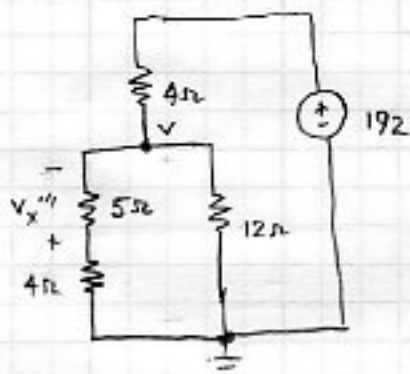

Voltage dividers again:
$$V = \frac{(4+5) \parallel 12}{(4+5) \parallel 12 + 4} \times 192$$

$$= 108 \text{ v}$$

And
$$V_x''' = \frac{-5}{5+4} \times V = -60 \text{ v}$$

Finally,

$$\begin{aligned} V_x &= V_x' + V_x'' + V_x''' \\ &= 5 + 35 - 60 \\ &= -20 \text{ v} \end{aligned}$$